



**KTH Informations- och
kommunikationsteknik**

IE1204 Digital Design


L9: State Machines

Masoumeh (Azin) Ebrahimi

KTH/ICT

mebr@kth.se


IE1204 Digital Design

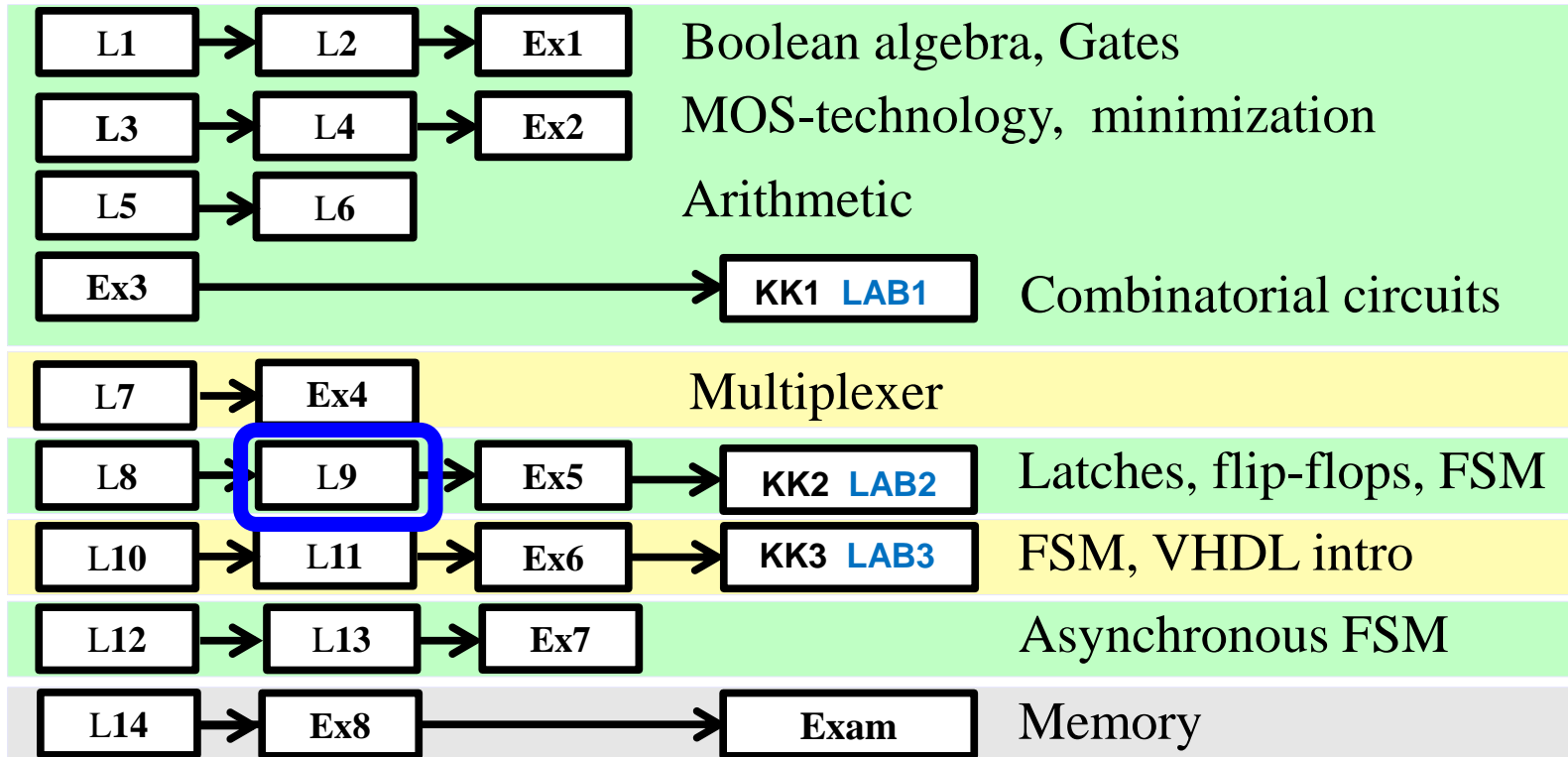

This lecture

- BV pp. 485-507


Sequential System

 

A sequential system has a built-in memory - the output depends therefore BOTH on the current and previous value(s) of the input signal

Lecture 8 - Lecture 13


Moore-type machine

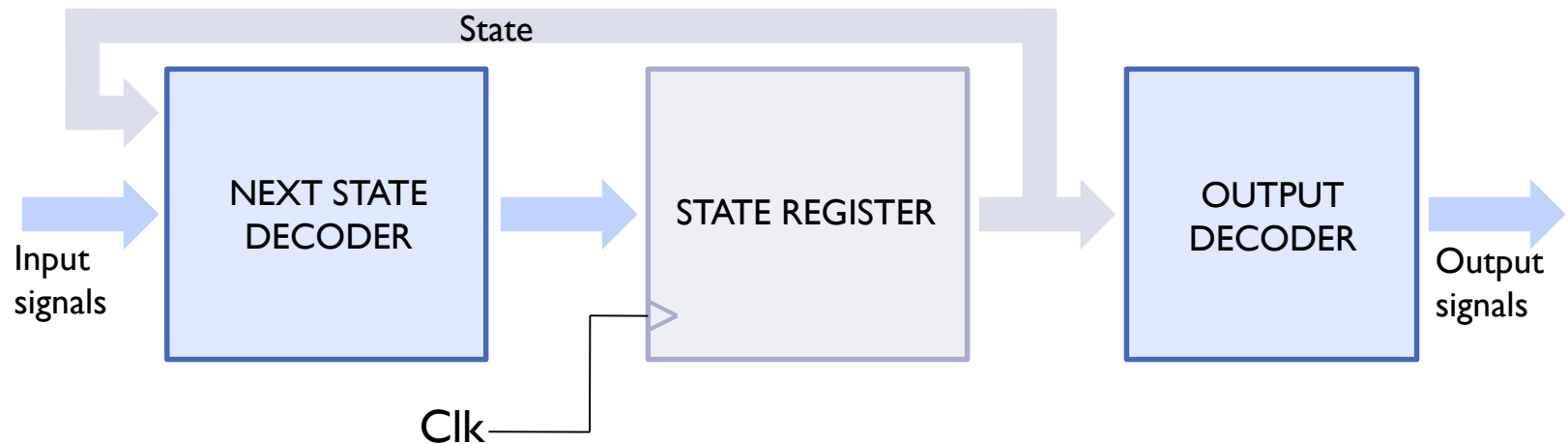

- In a Moore-type machine, output signals depend only on the current state


State register D-flip-flops

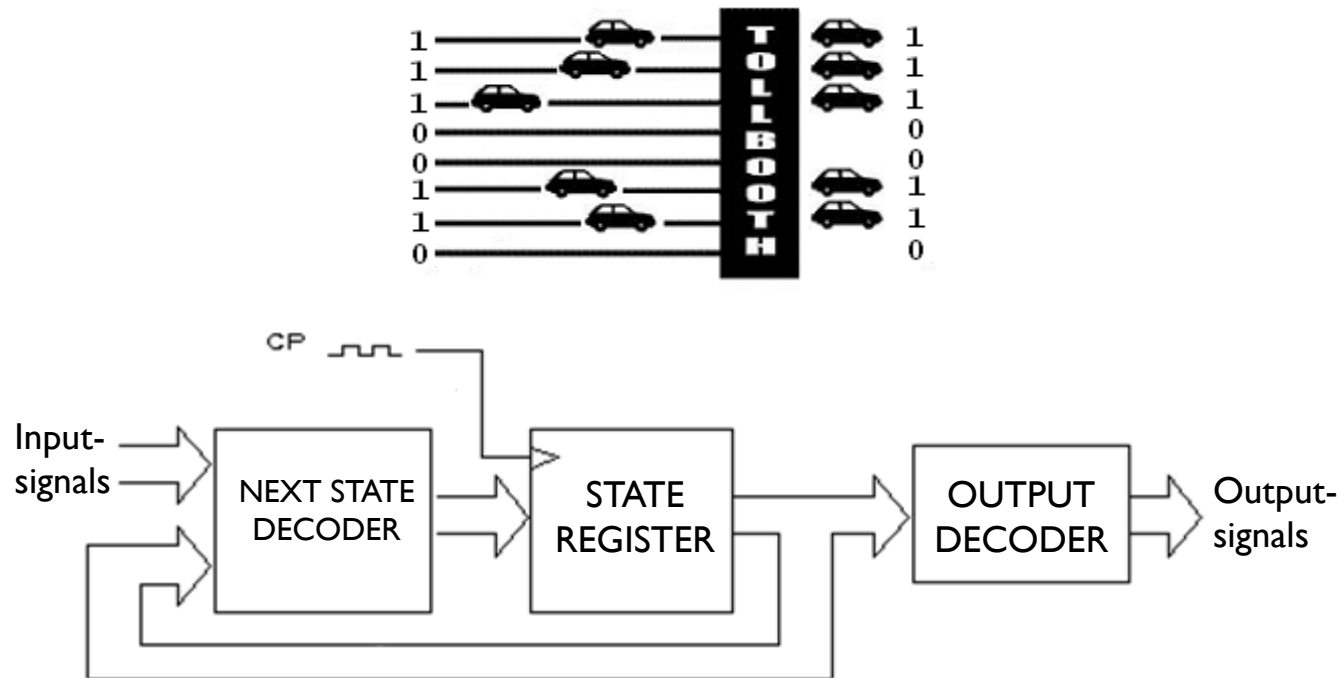State register D flip-flops slows down the race between signals until the value is stable. (Compare with the tollbooth).




State register D-flip-flops

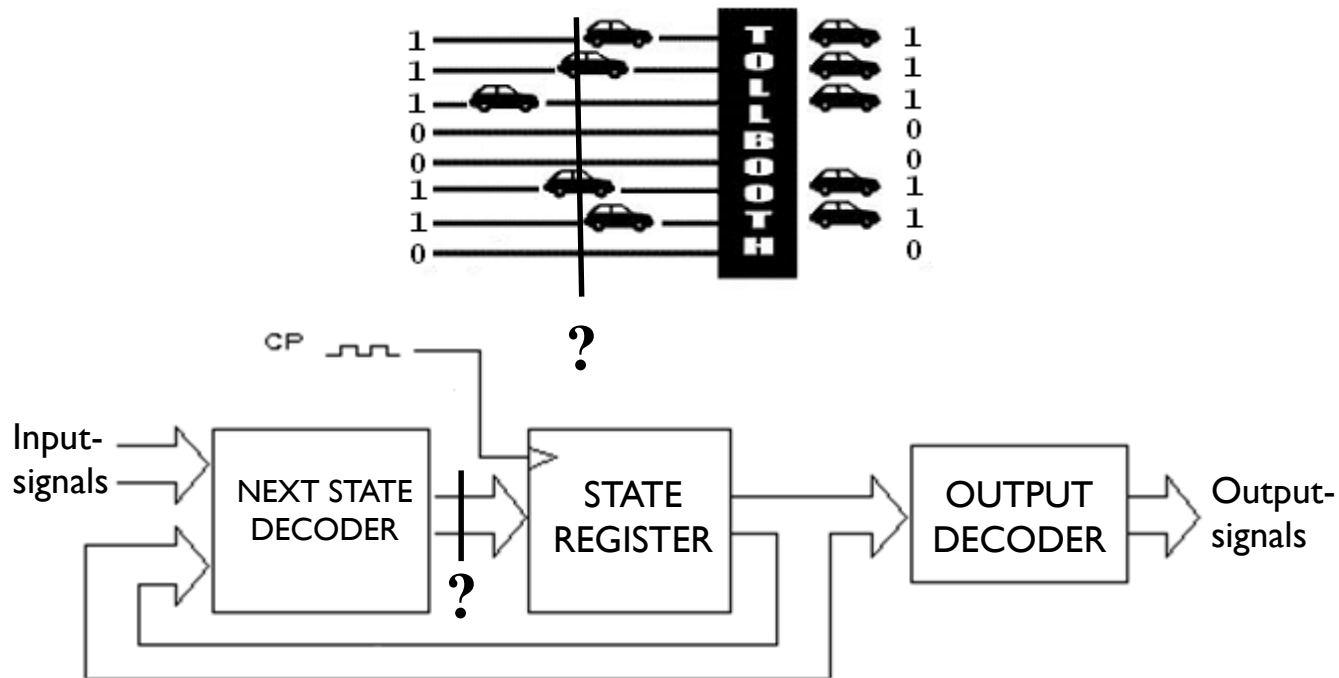State register D flip-flops slows down the race between signals until the value is stable. (Compare with the tollbooth).





State register D-flip-flops

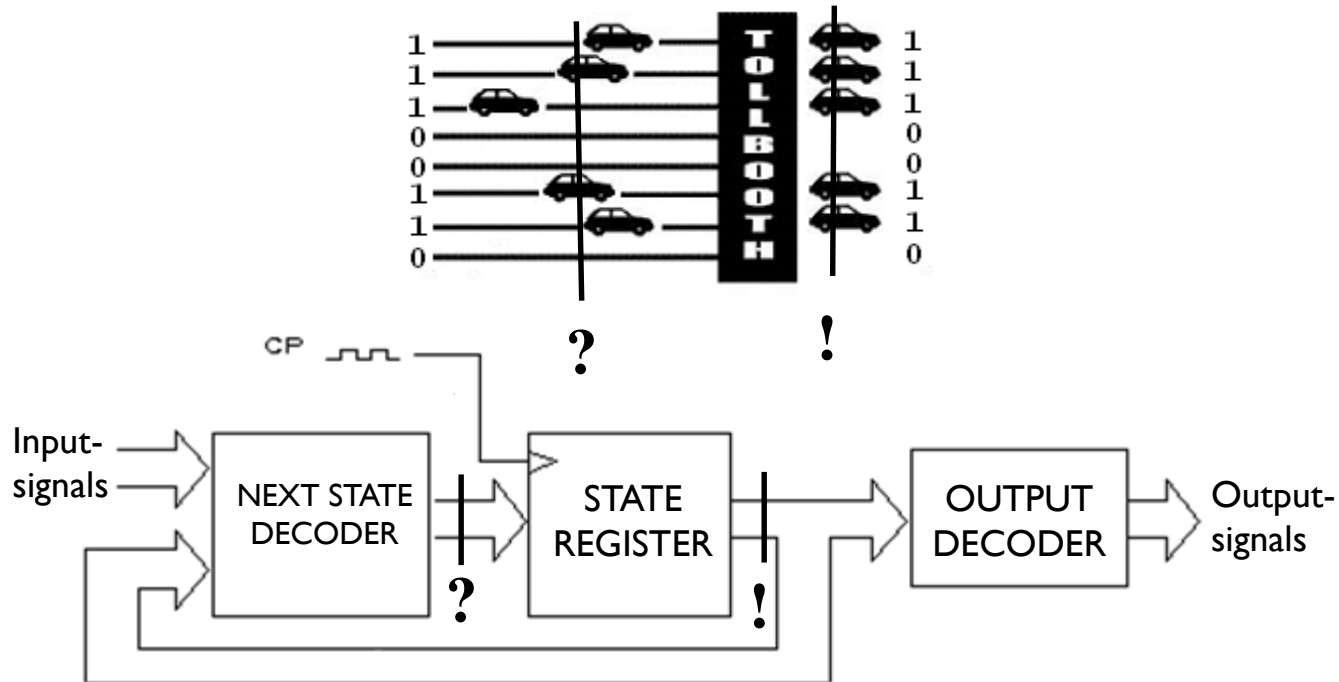State register D flip-flops slows down the race between signals until the value is stable. (Compare with the tollbooth).




Quickie Question ...

  
Which of the following timing diagram is valid for a **edge-triggered D flip-flop**?



Alt: A

 

Alt: B

 


Alt: C




Quickie Question ...

 
Which of the following timing diagram is valid for a **edge-triggered D flip-flop**?



Alt: A

 

Alt: B

 



Alt: C




*D is copied to output at the edge, when
Clock goes from 0 to 1*

Quickie Question ...

  
Which of the following timing diagram is valid for a **D Latch**?



Alt: A

 

Alt: B


 


Alt: C




Quickie Question ... Latch

  
Which of the following timing diagram is valid for a **D Latch**?



Alt: A

 

Alt: B

 

Alt: C

*D is connected to output when Enable is 1,
and is locked when Enable is 0*



Design task:


Bit sequence detector

- Specification
 - Circuit has an input w and an output z
 - If the input w is 1 in two consecutive clock pulses (or more), the output z should be set to 1 otherwise 0
 - Use a Moore machine with D flip-flops to implement the design

State Diagram

- There are many ways to draw a state diagram
- Here we follow the notation of the textbook (Brown/Vranesic)

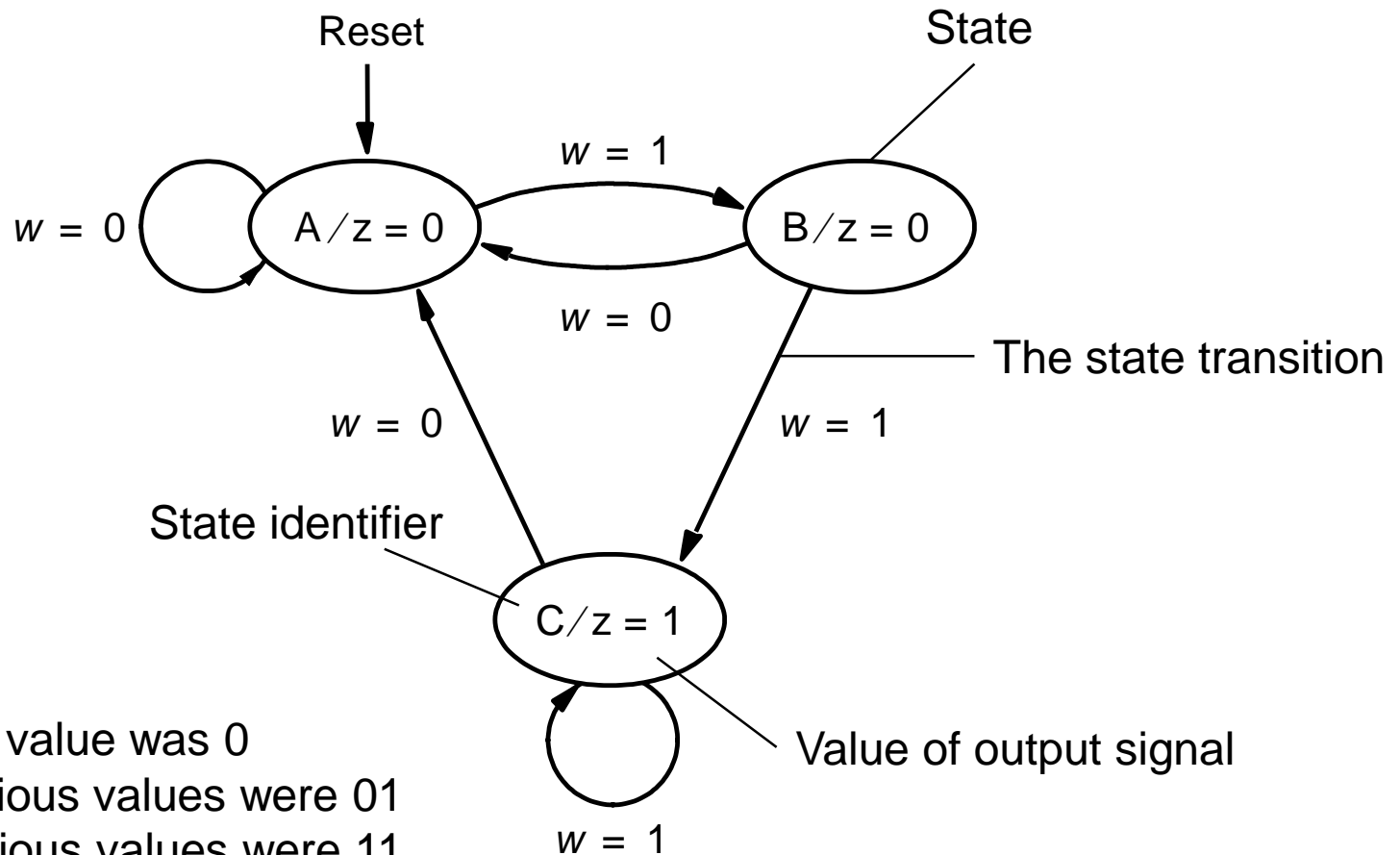State Diagram of the bit sequence detector




A = previous value was 0

B = two previous values were 01

C = two previous values were 11

State Table

State Diagram

 


State Table

Present state	Next state		Output z
	w = 0	w = 1	
A	A	B	0
B	A	C	0
C	A	C	1

Three states - two bits are needed!

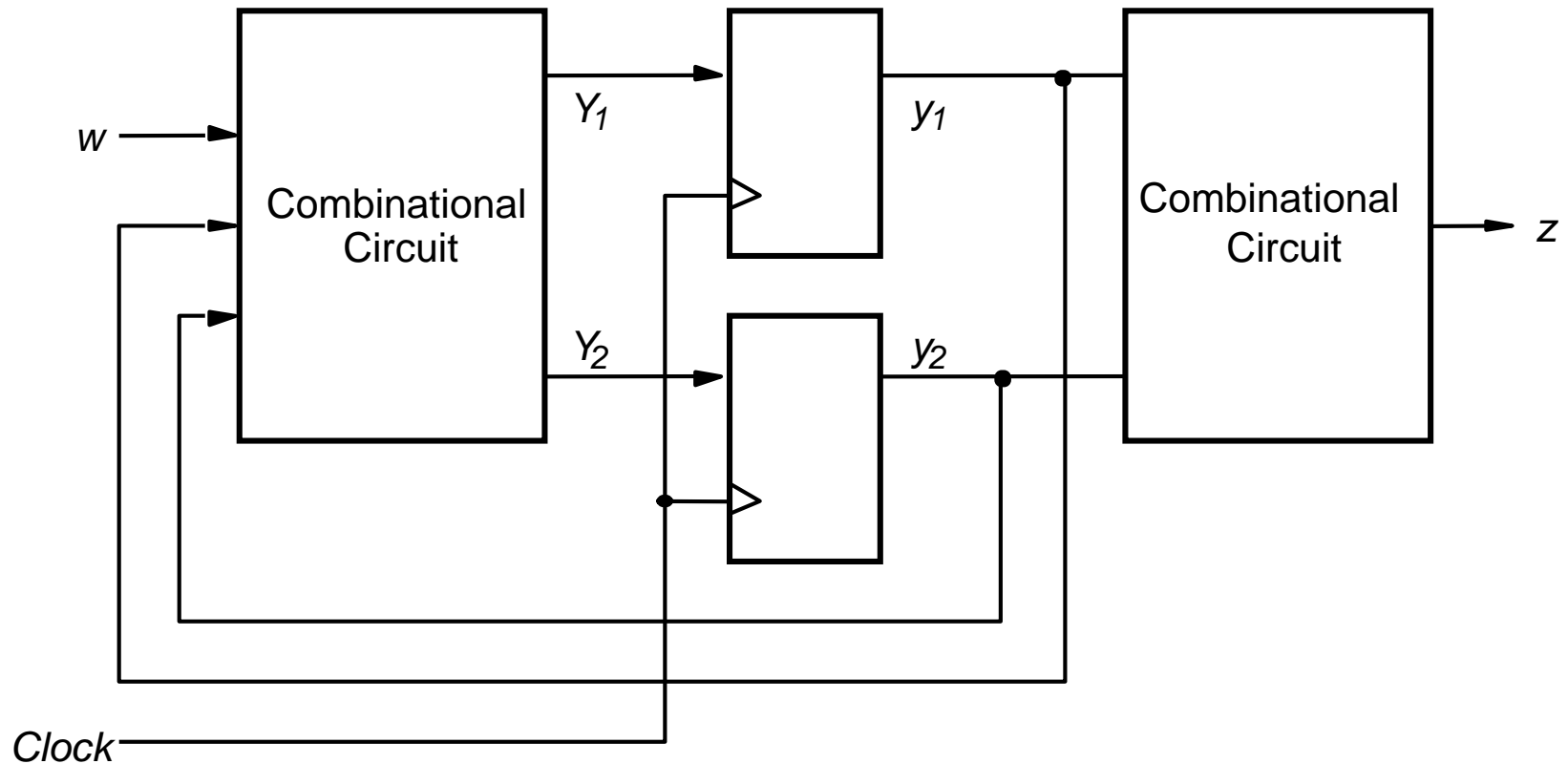Schematic of the implementation of the bit sequence detector



Design decisions: Choice of flip-flops and state assignment

- The designer must determine which flip-flop to use
 - D, T, or JK flip-flop
- The designer must choose the assignment for each state

State Assignment for the bit sequence detector

- In this example, we use
 - D flip-flops
 - State assignments $A = 00$, $B = 01$, $C = 10$
 - The assignment 11 is not present. We make it "don't care".

State Assignment bit sequence detector

State Table

Present state	Next state		Output z
	$w = 0$	$w = 1$	
A	A	B	0
B	A	C	0
C	A	C	1

A = 00

B = 01

C = 10




State-assigned Table

	Present state y_2y_1	Next state		Output z
		$w = 0$	$w = 1$	
		Y_2Y_1	Y_2Y_1	
A	00	00	01	0
B	01	00	10	0
C	10	00	10	1
	11	dd	dd	d

$$Y_2Y_1 = f(y_2y_1w) \quad z = f(y_2y_1)$$

Next-state expressions

 - We must now derive next-state expressions
 - Inputs to both flip-flops, Y_1 and Y_2
- To get minimized logic functions, we use Karnaugh diagrams



$$Y_2Y_1 = f(y_2y_1w) \quad Y_2 = f(y_2y_1w) \quad Y_1 = f(y_2y_1w) \quad z = f(y_2y_1)$$

From State-assigned Table to Karnaughmap

$$Y_2Y_1 = f(y_2y_1w) \quad Y_2 = f(y_2y_1w) \quad Y_1 = f(y_2y_1w)$$

Present state y_2y_1	Next state		Output z
	$w = 0$	$w = 1$	
	Y_2Y_1	Y_2Y_1	
00	00	01	0
01	00	10	0
10	00	10	1
11	dd	dd	d



		Y_1			
		$w=0$	$w=1$	$w=2$	$w=3$
y_2	y_1	00	01	11	10
		0	1	2	3
0		0	0	d	0
1		1	0	d	0

$$Y_1 = w\bar{y}_1\bar{y}_2$$

Present state y_2y_1	Next state		Output z
	$w = 0$	$w = 1$	
	Y_2Y_1	Y_2Y_1	
00	00	01	0
01	00	10	0
10	00	10	1
11	dd	dd	d



		Y_2			
		$w=0$	$w=1$	$w=2$	$w=3$
y_2	y_1	00	01	11	10
		0	1	2	3
0		0	0	d	0
1		0	1	d	1

$$Y_2 = wy_1 + wy_2 = w(y_1 + y_2)$$

Output expression

- Now we derive the expression for output

Present state y_2y_1	Next state		Output z
	$w = 0$	$w = 1$	
	Y_2Y_1	Y_2Y_1	
00	00	01	0
01	00	10	0
10	00	10	1
11	<i>dd</i>	<i>dd</i>	<i>d</i>



		z	
y_2	y_1	0	1
0		0	0
1		1	d

$$z = y_2$$


Implementation

$$Y_2 = wy_1 + wy_2 =$$

$$= w(y_1 + y_2)$$


$$Y_1 = w\bar{y}_1\bar{y}_2$$

$$z = y_2$$

 


Timing diagram

 State transitions occur only on the positive clock edge!





$y_2 y_1$
A = 00
B = 01
C = 10

 

Timing diagram

  State transitions occur only on the positive clock edge!



$$z = y_2$$

In other terms

Present state

y

Next state

y^+

Exercises and Hemert-book:

$$y_2^+ y_1^+ = f(y_2 y_1 w) \quad y_2^+ = f(y_2 y_1 w) \quad y_1^+ = f(y_2 y_1 w)$$


With another lineup

$$y_2^+ y_1^+ = f(y_2 y_1 w) \quad y_2^+ = f(y_2 y_1 w) \quad y_1^+ = f(y_2 y_1 w)$$

		$y_2^+ y_1^+$	
		w 0	w 1
$y_2 y_1$	A 00	00	01
	B 01	00	10
	11	<i>dd</i>	<i>dd</i>
C 10	00	10	

		y_2^+	
		w 0	w 1
$y_2 y_1$	00	0	0
	01	0	1
	11	<i>d</i>	<i>d</i>
10	0	1	


		y_1^+	
		w 0	w 1
$y_2 y_1$	00	0	1
	01	0	0
	11	<i>d</i>	<i>d</i>
10	0	0	

 

*In exercises
we use this
method*


You could directly write down the codet state table as a "Karnaugh map".

Mealy-type machine

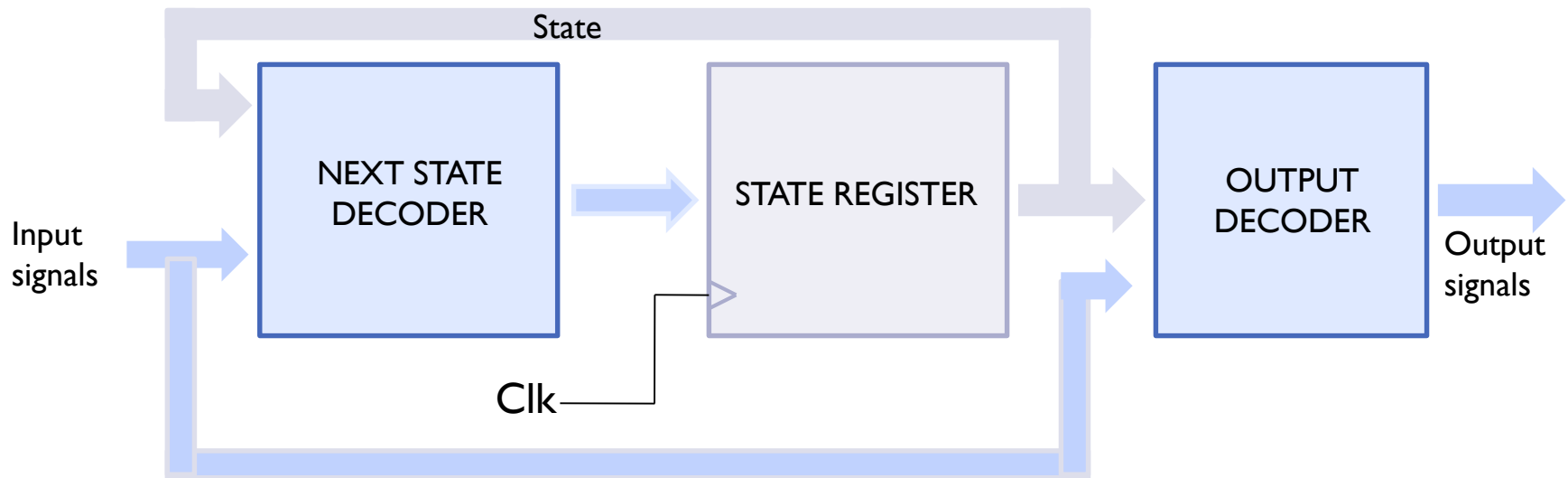


- In a Mealy machine, output signals depend on both the current state and inputs

Bit sequences detector Mealy machine

 

 - The state diagram for the Mealy machine requires only two states
- The output depends on both the state and the input




A = previous value was 0

B = previous value was 1

State table

State Diagram

 

State Table

Present state	Next state		Output z	
	$w = 0$	$w = 1$	$w = 0$	$w = 1$
A	A	B	0	0
B	A	B	0	1

Two states - just one flip-flop is needed!

State Assignment

State Table

Present state	Next state		Output z	
	$w = 0$	$w = 1$	$w = 0$	$w = 1$
A	A	B	0	0
B	A	B	0	1

State-assigned Table

Present state	Next state		Output	
	$w = 0$	$w = 1$	$w = 0$	$w = 1$
y	Y	Y	z	z
0	0	1	0	0
1	0	1	0	1

$$\mathbf{A} = 0$$

$$\mathbf{B} = 1$$





A
B

$$Y = w$$

$$z = yw$$



Implementation

$$Y = w$$
$$z = yw$$

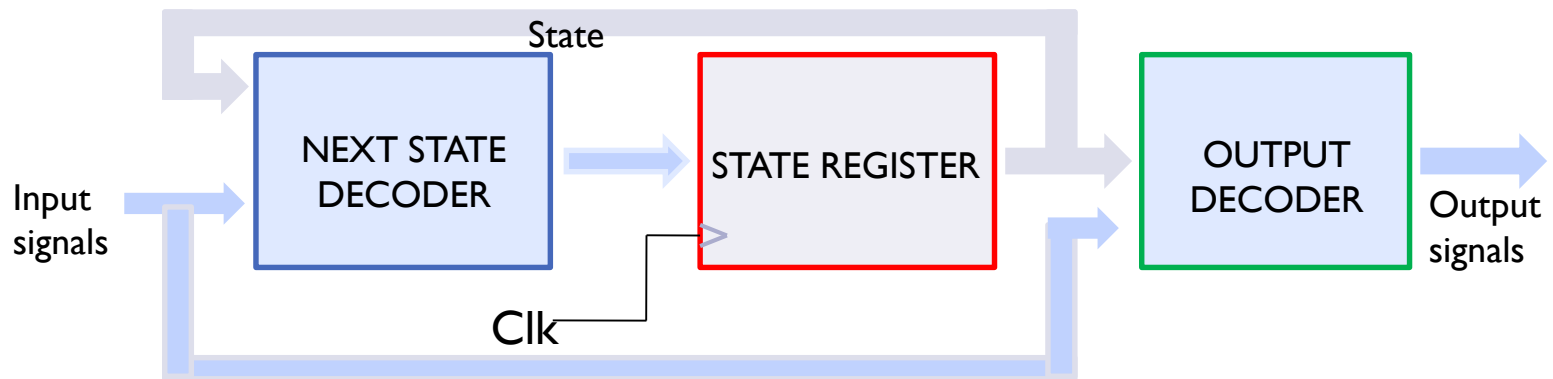 


Timing diagram

  - The output may change during the clock period because it is a function of the input signal
- Compared to Moore machine, Mealy machine “reacts” earlier (bit sequence is detected in t_4 compared to the t_5 in Moore-machine)




Mealy machine with output register

 - In the Mealy machine the output can change during the entire clock period
- We can add a register (flip-flop) at the end in order to synchronize the output with the clock edge



Timing diagram

 - Mealy machine with output registers has the same timing diagram as Moore machine



Discussion


Moore vs Mealy

- Moore machine output values depend only on the current state
- Mealy machine output values depend on the current state and the values of the input signals
- Mealy machine often needs fewer state
- Mealy machine outputs are not synchronized with the clock, which is why an output register is often added

Alternative state assignments

- The choice of state assignment may play a major role in implementation as it affects the logic for
 - next-state decoder
 - output decoder

State diagram bit sequences detector

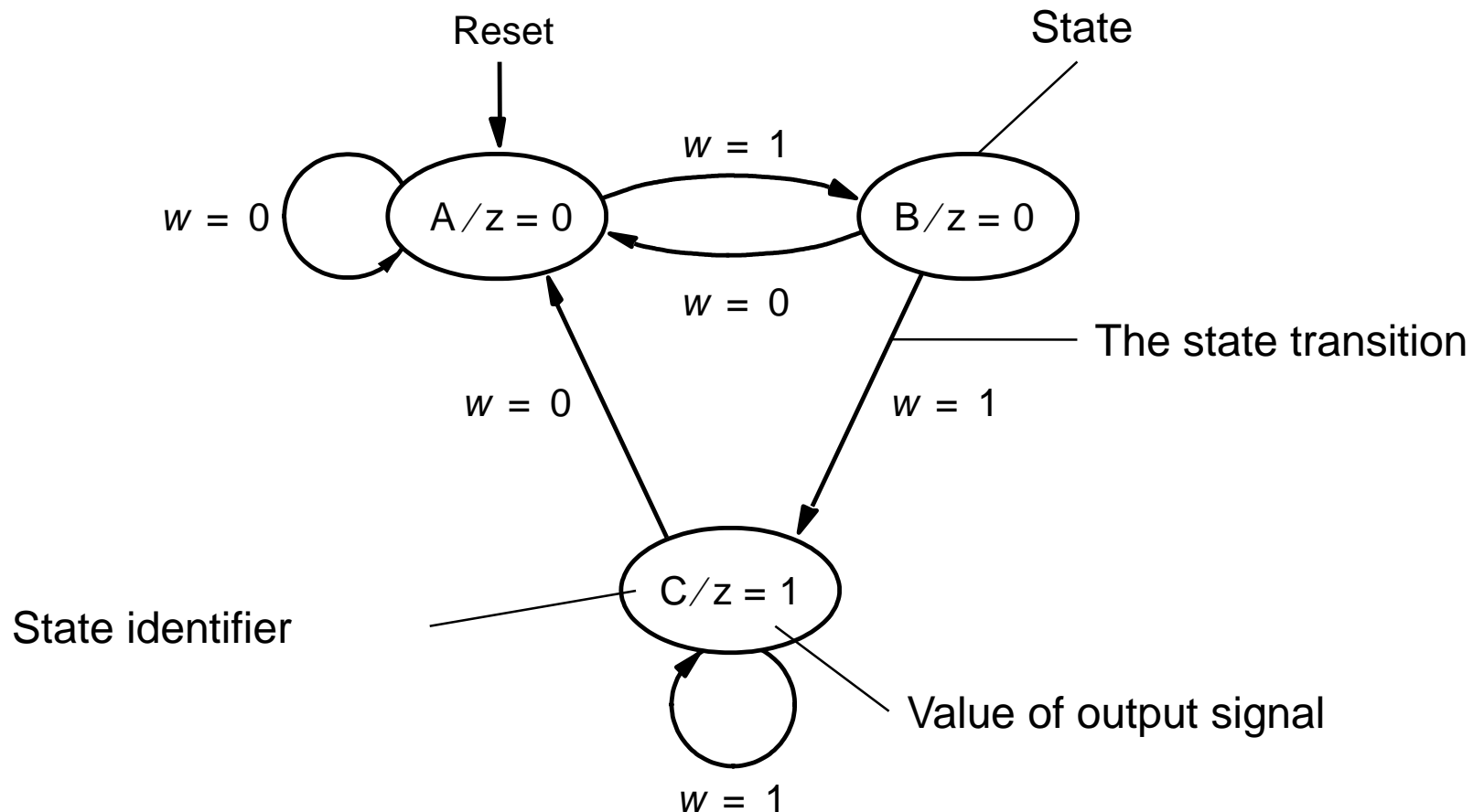

Binary encoding

- Binary code follows the representation of a binary number, that is, the order is 00, 01, 10, 11

A = 00
B = 01
C = 10
 11


A
 B
 C



Present state y_2y_1	Next state		Output z
	$w = 0$	$w = 1$	
	Y_2Y_1	Y_2Y_1	
00	00	01	0
01	00	10	0
10	00	10	1
11	<i>dd</i>	<i>dd</i>	<i>d</i>

Implementation of bit sequence detector for binary code

2 D-flip-flops
2 AND-gates
1 OR-gate

 

Gray code

- In Gray code, one bit is changed at a time, i.e, 00, 01, 11, 10
- Gray code is good for counters

A = 00

B = 01

C = 11

10




A
B
C

Present state y_2y_1	Next state		Output z
	$w = 0$	$w = 1$	
	Y_2Y_1	Y_2Y_1	
00			
01			
11			
10			



State Table

State Diagram

 


State Table

Present state	Next state		Output z
	$w = 0$	$w = 1$	
A			
B			
C			

Three states - two bits are needed!

State Table

State Diagram

 


State Table

Present state	Next state		Output z
	w = 0	w = 1	
A	A	B	0
B	A	C	0
C	A	C	1

Three states - two bits are needed!

Gray code

 - In Gray code, one bit is changed at a time, i.e, 00, 01, 11, 10
- Gray code is good for counters



A = 00

B = 01

C = 11

10



A
B
C

Present state y_2y_1	Next state		Output z
	$w = 0$	$w = 1$	
	Y_2Y_1	Y_2Y_1	
00			
01			
11			
10			

Gray code

- In Gray code, one bit is changed at a time, i.e, 00, 01, 11, 10
- Gray code is good for counters

A = 00
B = 01
C = 11
 10



A
 B
 C


Present state y_2y_1	Next state		Output z
	$w = 0$	$w = 1$	
	Y_2Y_1	Y_2Y_1	
00	00	01	0
01	00	11	0
11	00	11	1
10	dd	dd	d

$$Y_1 = w$$

$$Y_2 = wy_1$$


$$z = y_2$$

 Implementation of bit sequence detector for Gray code



Implementation of bit sequence detector for Gray code

2 D-flip-flops
1 AND-gate

 

One-hot encoding

- One-hot encoding uses one flip-flop per state
- For each state, only one bit is 'hot' (1), all other bits are 0, i.e. 0001, 0010, 0100, 1000
- One-hot encoding typically minimizes the combinatorial logic, but increases the number of flip-flops

Which encoding is best?

- There is no code which is the best in every situation, but it all depends on the state diagram
- One can also use 'own codes' suitable for implementation, for example 00, 11, 10, 01

Summary

- There are two types of state machines
 - Moore machine
 - Mealy machine
- Different state assignments give us different circuit implementations
- Next lecture: BV pp. 528-566