



**KTH Informations- och
kommunikationsteknik**


L4: Karnaugh diagrams, two-, and multi-level minimization

Masoumeh (Azin) Ebrahimi


KTH/ICT

mebr@kth.se

IE1204 Digital Design

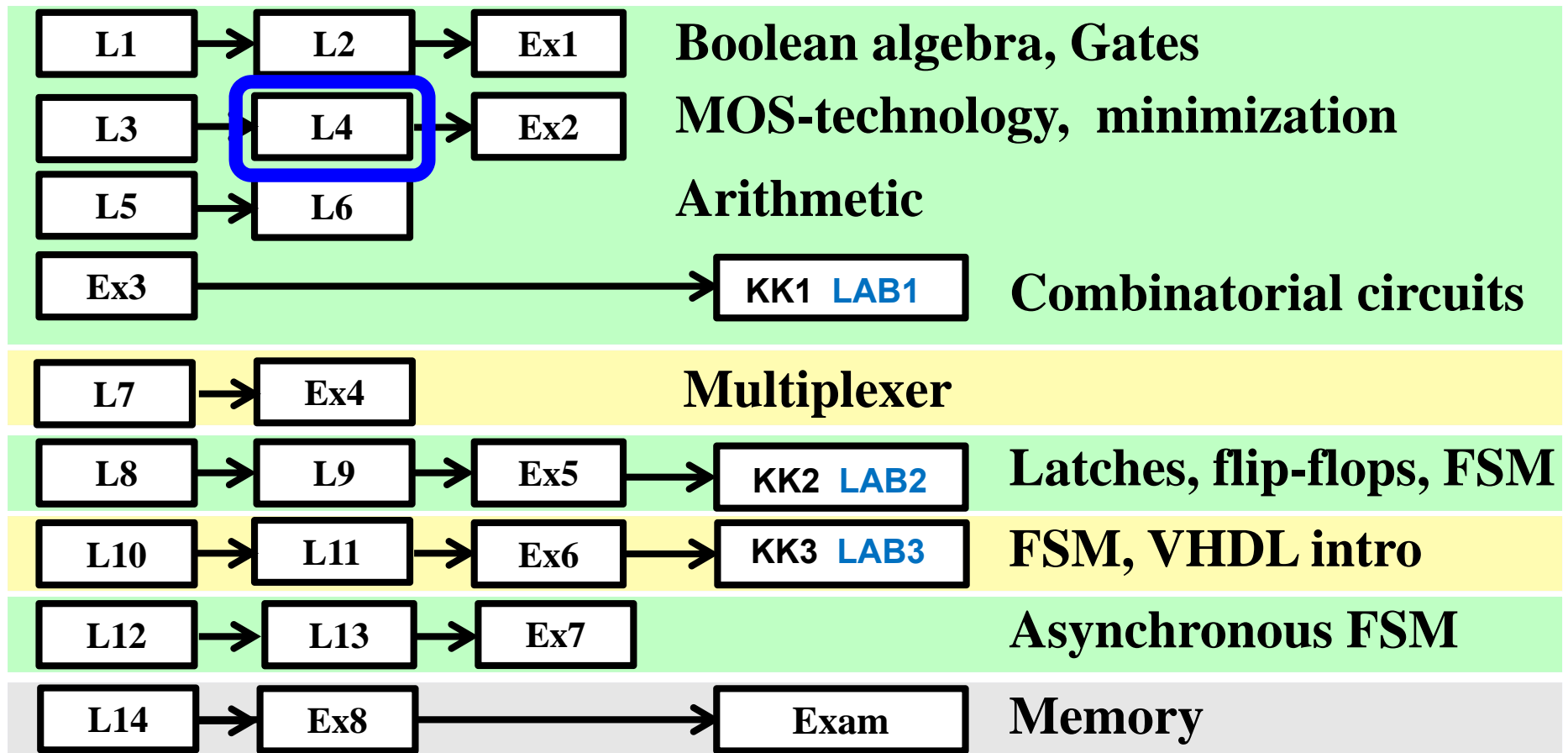


Combinatorial system

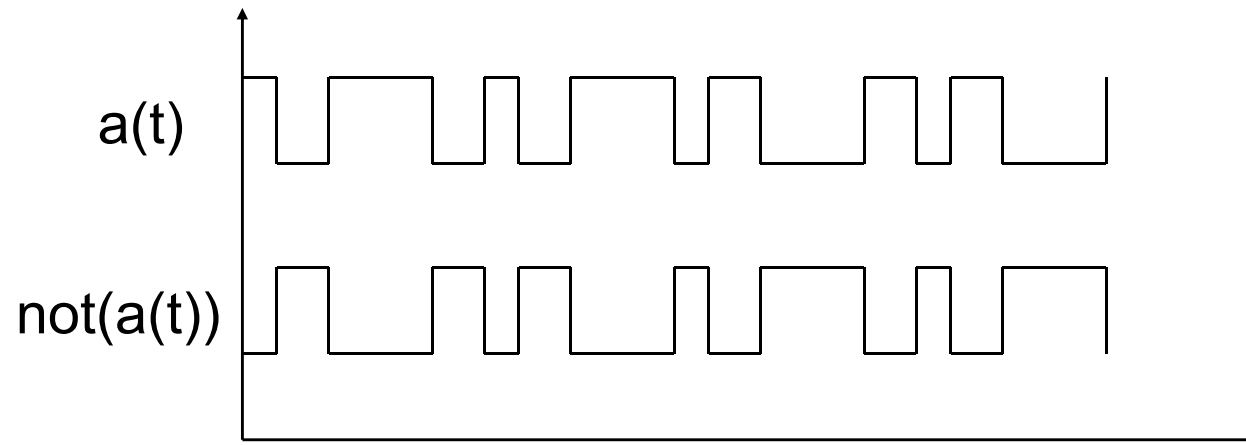

A combinatorial system has no memory - its output depends therefore **ONLY** on the **PRESENT** value of the input signal

Lecture 4 - Lecture 7

Sequential system

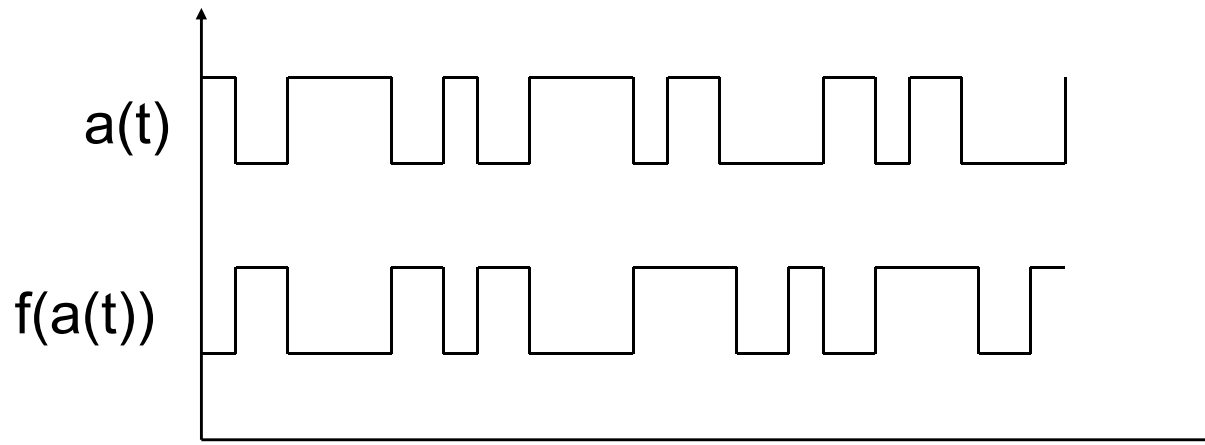

A sequential system has a built-in memory - its output depends therefore **BOTH** on the **PRESENT** and **PREVIOUS** value(s) of the input signal

Lecture 8 - Lecture 13

This lecture covers ...


- BV pp. 168-211

Minterms

- A minterm MUST contain all variables, otherwise it is not a minterm
- A minterm represents the combination of values of function's variables for which the function evaluates to 1

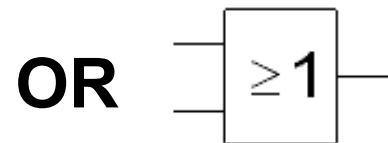Example:

$$f = \sum m(1,2,3) = \bar{x}_1 x_0 + x_1 \bar{x}_0 + x_1 x_0$$




	x_1	x_0	f
0	0	0	0
1	0	1	1
2	1	0	1
3	1	1	1

Minimization with Boolean algebra

Using Boolean algebra, we can shorten the expression to:
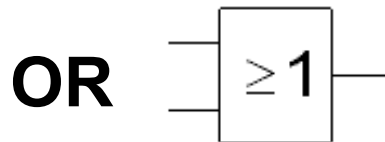
$$\begin{aligned} f &= \bar{x}_1 x_0 + x_1 \bar{x}_0 + x_1 x_0 = \bar{x}_1 x_0 + x_1 (\bar{x}_0 + x_0) \\ &= \bar{x}_1 x_0 + x_1 (1) = \bar{x}_1 x_0 + x_1 (1 + x_0) = \\ &= \bar{x}_1 x_0 + x_1 + x_1 x_0 = x_0 (\bar{x}_1 + x_1) + x_1 = x_0 (1) + x_1 \\ &= \boxed{x_1 + x_0} \quad \textit{As expected!} \end{aligned}$$




	x_1	x_0	f
0	0	0	0
1	0	1	1
2	1	0	1
3	1	1	1

Maxterm

- A maxterm MUST contain all variables, otherwise it is not a maxterm
- A minterm represents the combination of values of function's variables for which the function evaluates to 0

Example:


$$f = \prod M(0) = x_0 + x_1$$

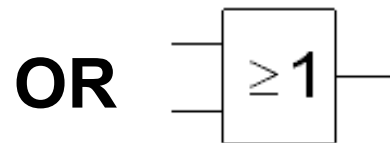

	x_1	x_0	f
0	0	0	0
1	0	1	1
2	1	0	1
3	1	1	1

Graphical minimization method

OR

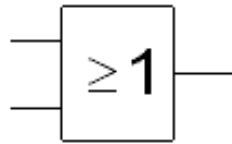

	x_1	x_0	f
0	0	0	0
1	0	1	1
2	1	0	1
3	1	1	1

		x_0	
		0	1
x_1	0	0	1
	1	1	1

		x_0	
		0	1
x_1	0	m_0	m_1
	1	m_2	m_3

$$\boxed{m_2 + m_3} = x_1 \bar{x}_0 + x_1 x_0 =$$


$$= x_1 (\bar{x}_0 + x_0) = \boxed{x_1}$$

$$\boxed{m_1 + m_3} = \bar{x}_1 x_0 + x_1 x_0 =$$


$$= x_0 (\bar{x}_1 + x_1) = \boxed{x_0}$$

$$f = x_1 + x_0$$

Graphical minimization method

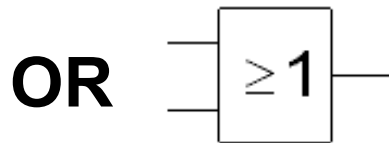

	x_1	x_0	f
0	0	0	0
1	0	1	1
2	1	0	1
3	1	1	1

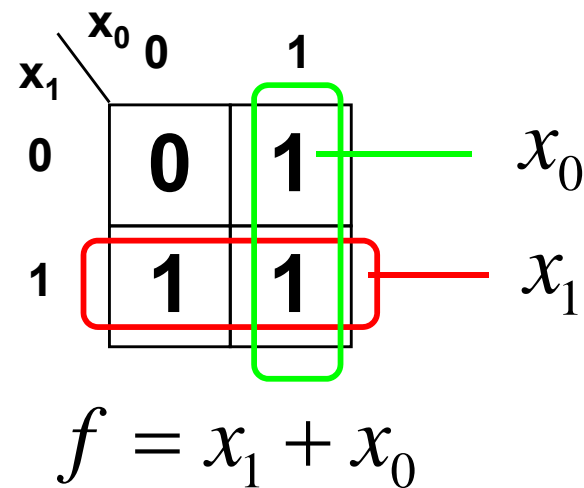

"Group" two ones that are "neighbors" (vertically or horizontally).

Minterms could then be reduced to "what they have in common".

Commonly used functions in two-dimensional table-form

AND

$x_1 \backslash x_0$	0	1
0	0	0
1	0	1

$$x_1 \cdot x_0$$

OR

$x_1 \backslash x_0$	0	1
0	0	1
1	1	1

$$x_1 + x_0$$

XOR

$x_1 \backslash x_0$	0	1
0	0	1
1	1	0

$$x_1 x_0 + x_1 \bar{x}_0$$

NOT

x_0	0	1
1	1	0

$$\bar{x}_0$$

NAND

$x_1 \backslash x_0$	0	1
0	1	1
1	1	0

$$\overline{x_1 + x_0} = \overline{x_1 + x_0} = \overline{x_1 \cdot x_0}$$

NOR

$x_1 \backslash x_0$	0	1
0	1	0
1	0	0


$$\overline{x_1 \cdot x_0} = \overline{x_1 \cdot x_0} = \overline{x_1 + x_0}$$

XNOR


$x_1 \backslash x_0$	0	1
0	1	0
1	0	1

$$\overline{x_1 x_0 + x_1 \bar{x}_0}$$

3-dimensional Boolean space

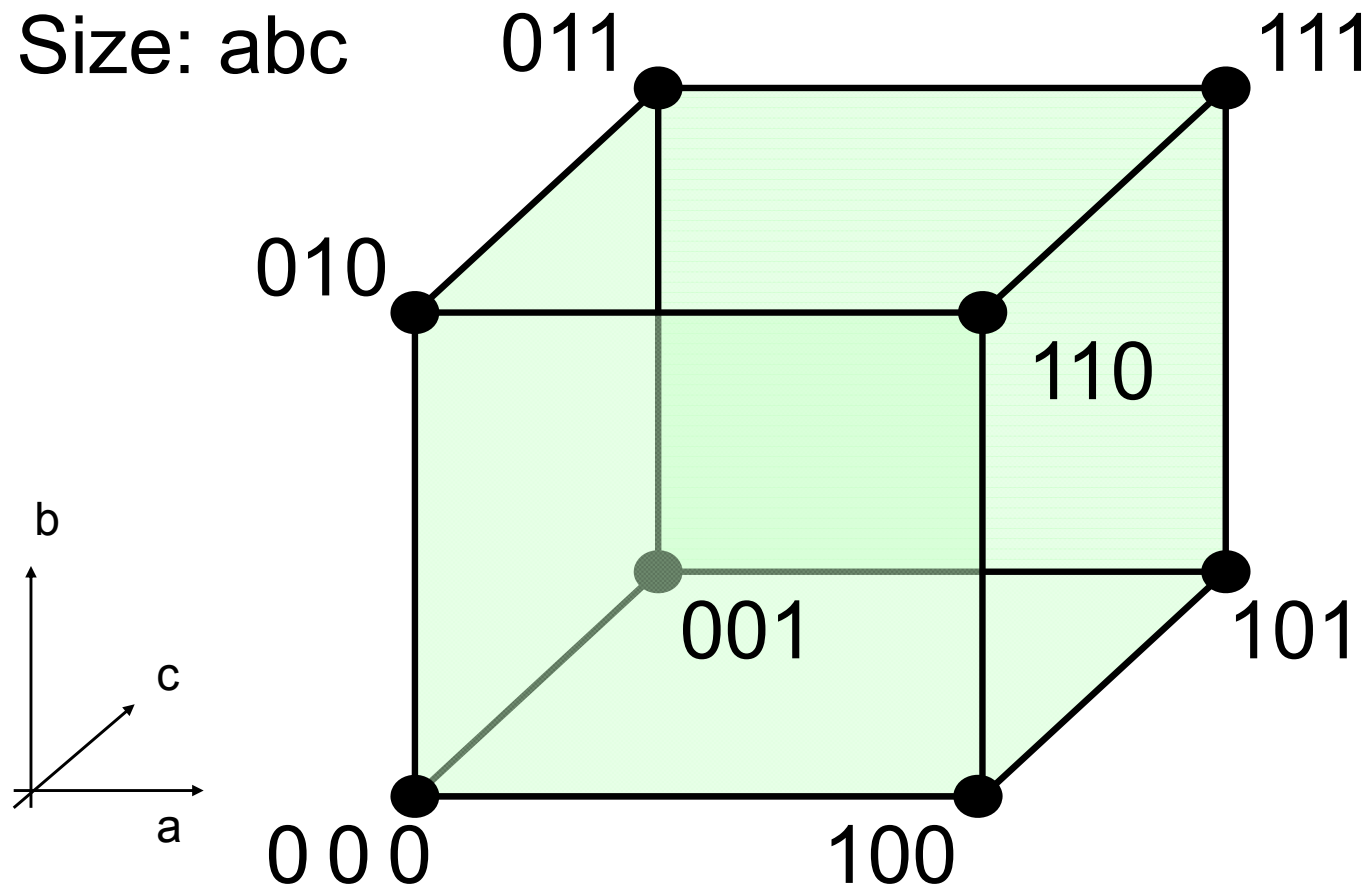


3-dimensional Boolean space

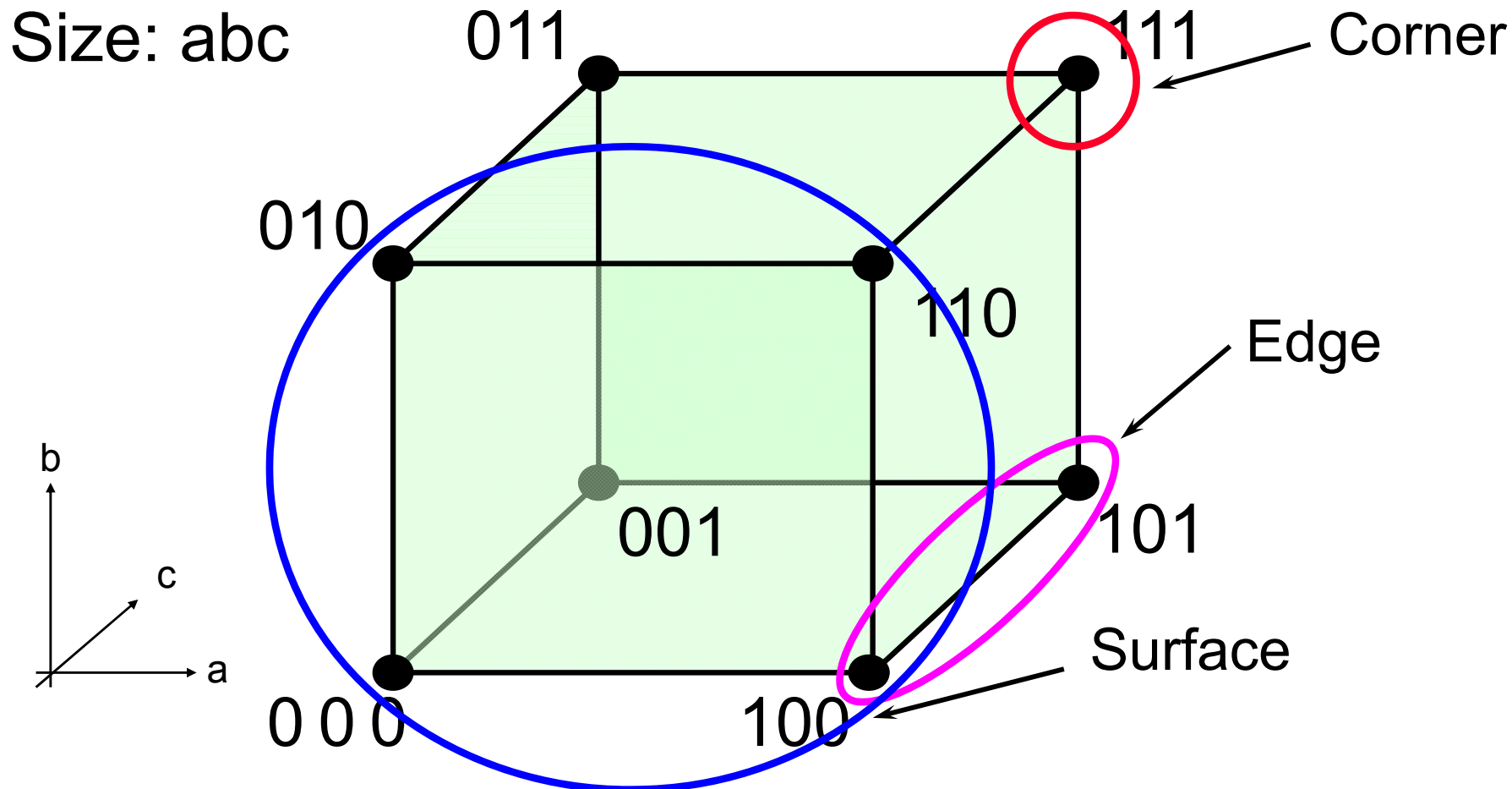


- Cube methods can be generalized to "Hyper Cubes" with any number of variables.

Minimization with cube

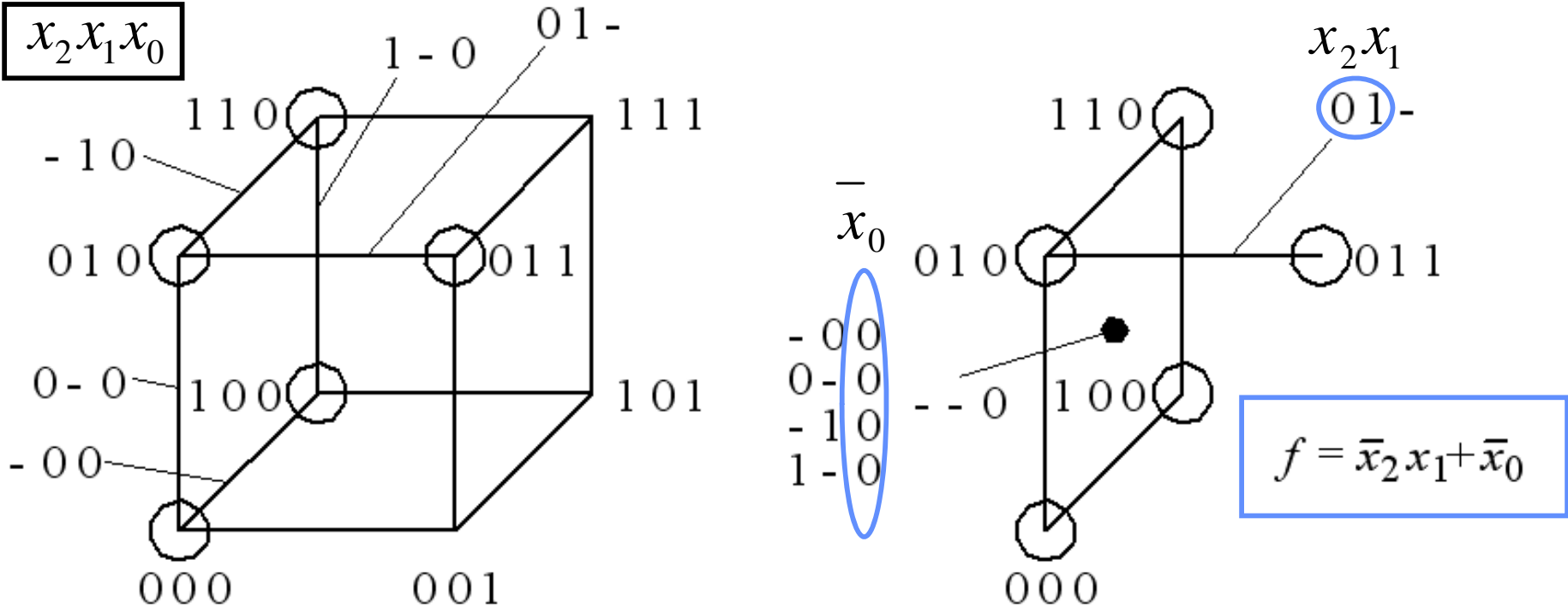

- A **surface** is represented by a **variable**.
- An **edge** is represented by a **product term with two variables**.
- A **corner** is represented by a **minterm with three variables**.

Graycode is a mirrored binarycode

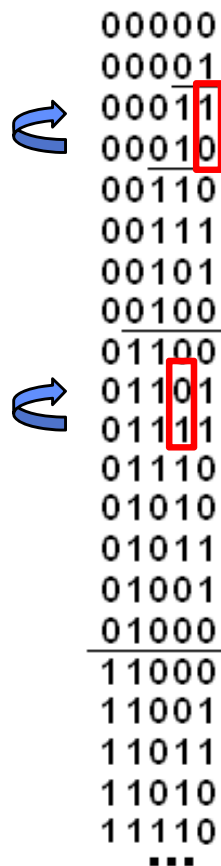

```
00000
00001
00011
00010
00110
00111
00101
00100
01100
01101
01111
01110
01010
01011
01001
01000
11000
11001
11011
11010
11110
...
```


One can easily construct a Gray code with an arbitrary number of bits needed for numbering the "corners" in "hypercubes" with!

Graycode is a mirrored binarycode


0	0	00	00	000	000	0000	0000	00000
1	<u>1</u>	<u>01</u>	<u>01</u>	<u>001</u>	<u>001</u>	<u>0001</u>	<u>0001</u>	<u>00001</u>
	1	11	11	011	011	0011	0011	00011
	0	10	<u>10</u>	<u>010</u>	<u>010</u>	<u>0010</u>	<u>0010</u>	<u>00010</u>
			10	110	110	0110	0110	00110
			11	111	111	0111	0111	00111
			01	101	101	0101	0101	00101
			00	100	<u>100</u>	<u>0100</u>	<u>0100</u>	<u>00100</u>
					100	1100	1100	01100
					101	1101	1101	01101
					111	1111	1111	01111
					110	1110	1110	01110
					010	1010	1010	01010
					011	1011	1011	01011
					001	1001	1001	01001
					000	1000	<u>1000</u>	<u>01000</u>
							1000	11000
							1001	11001
							1011	11011
							1010	11010
							1110	11110
						

3D-cube \Rightarrow Karnaugh map

$a \ b \ c$

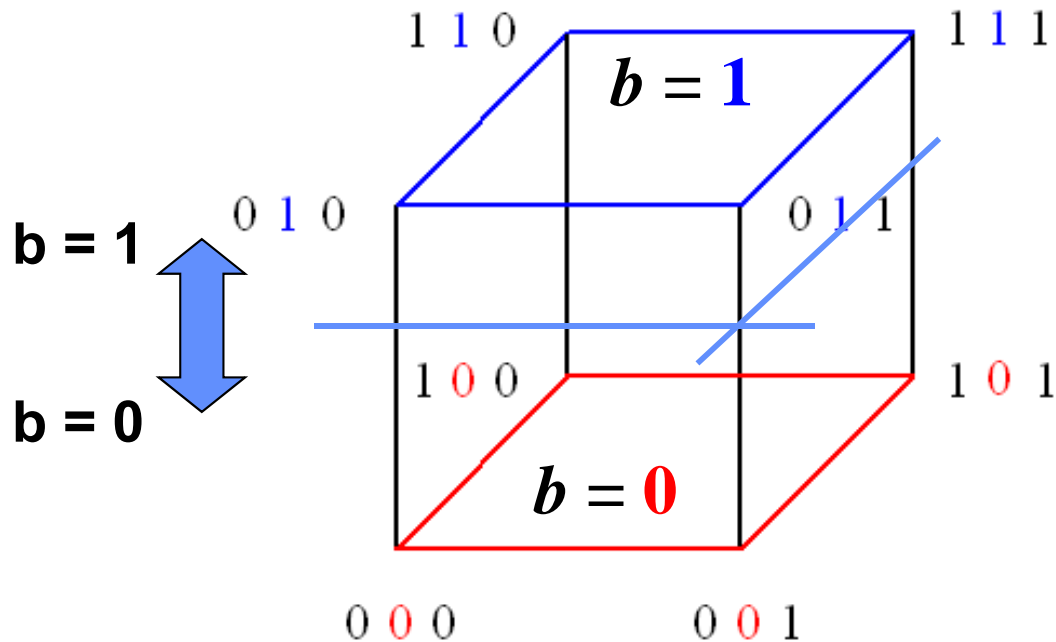

Gray-code \rightarrow mirror

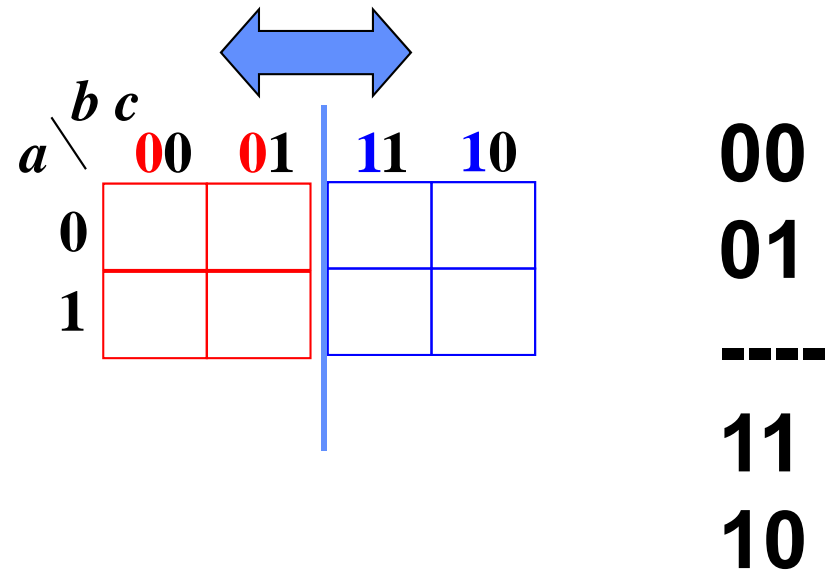

Gray code

A function of four variables a b c d

Truth Table with 11 "1" and 5 "0". The function can be expressed in SoP-form with 11 minterms or in PoS-form with 5 maxterms.

	abcd	f
0	0000	1
1	0001	1
2	0010	1
3	0011	1
4	0100	1
5	0101	1
6	0110	1
7	0111	1
8	1000	1
9	1001	0
10	1010	1
11	1011	0
12	1100	0
13	1101	1
14	1110	0
15	1111	0

$$f(a,b,c,d) = \sum (0,1,2,3,4,5,6,7,8,10,13)$$

$$f = \bar{a}\bar{b}\bar{c}\bar{d} + \bar{a}\bar{b}\bar{c}d + \bar{a}\bar{b}c\bar{d} + \bar{a}\bar{b}cd + \bar{a}b\bar{c}\bar{d} + \bar{a}b\bar{c}d + \bar{a}bc\bar{d} + \bar{a}bcd + a\bar{b}\bar{c}\bar{d} + a\bar{b}\bar{c}d + a\bar{b}c\bar{d} + a\bar{b}cd + ab\bar{c}\bar{d} + ab\bar{c}d + abc\bar{d} + abcd$$


$$f(a,b,c,d) = \prod (9,11,12,14,15)$$

$$f = (\bar{a}+b+c+\bar{d}) \cdot (\bar{a}+b+\bar{c}+\bar{d}) \cdot (\bar{a}+\bar{b}+c+d) \cdot (\bar{a}+\bar{b}+\bar{c}+d) \cdot (\bar{a}+\bar{b}+\bar{c}+\bar{d})$$

4D-cube \Rightarrow 2D-map

The Karnaugh map is the truth table lined up in a different way.

	abcd
0	0000
1	0001
2	0010
3	0011
4	0100
5	0101
6	0110
7	0111
8	1000
9	1001
10	1010
11	1011
12	1100
13	1101
14	1110
15	1111

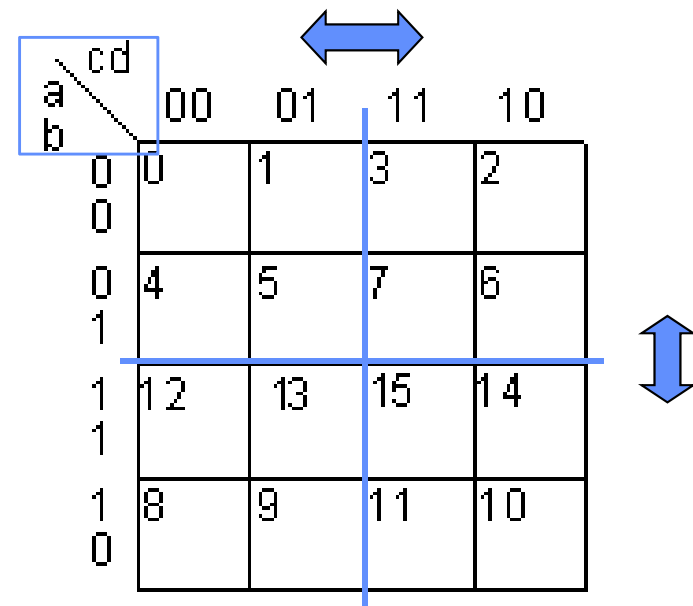


The frames are ordered in such way that only one bit changes between two vertical frames or horizontal frames. This order is called **Gray-code**.

Two "neighbors"

The frames "5" and "13" are "neighbors" in the Karnaugh map (but they are distant from each other in the truth table).

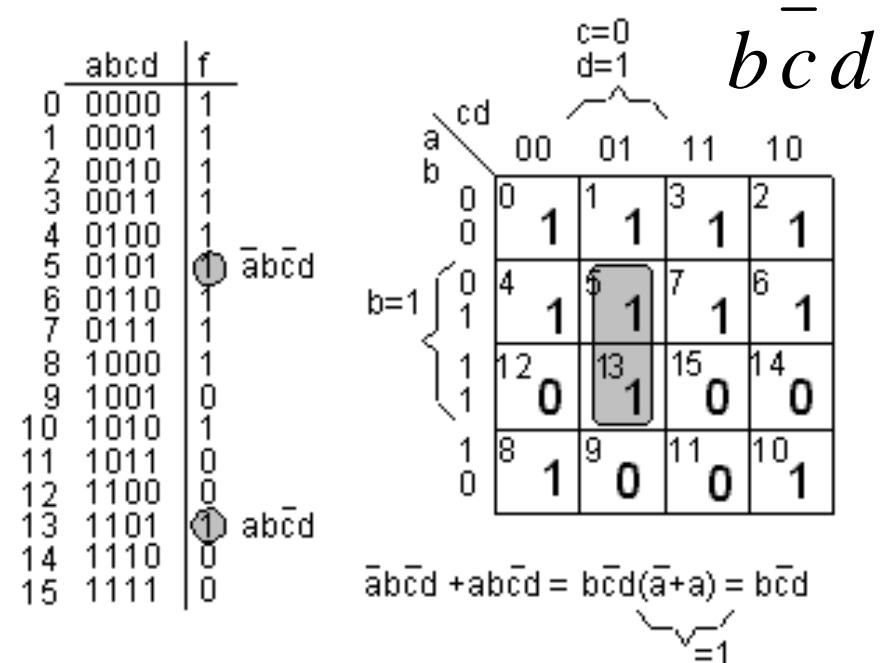They correspond to *two* minterms with *four* variables. With Boolean algebra, they can be reduced to one term with *three* variables.




What the two frames have in common is that $b = 1$, $c = 0$ and $d = 1$; and the reduced term expresses just that.

Everywhere in the Karnaugh map where one can find two ones that are "neighbors" (vertically or horizontally) the minterms could be reduced to "what they have in common". This is called a **grouping**.

Four "neighbors"

Frames "1" "3" "5" "7" is a group of four frames with "1" that are "neighbors" to each other.

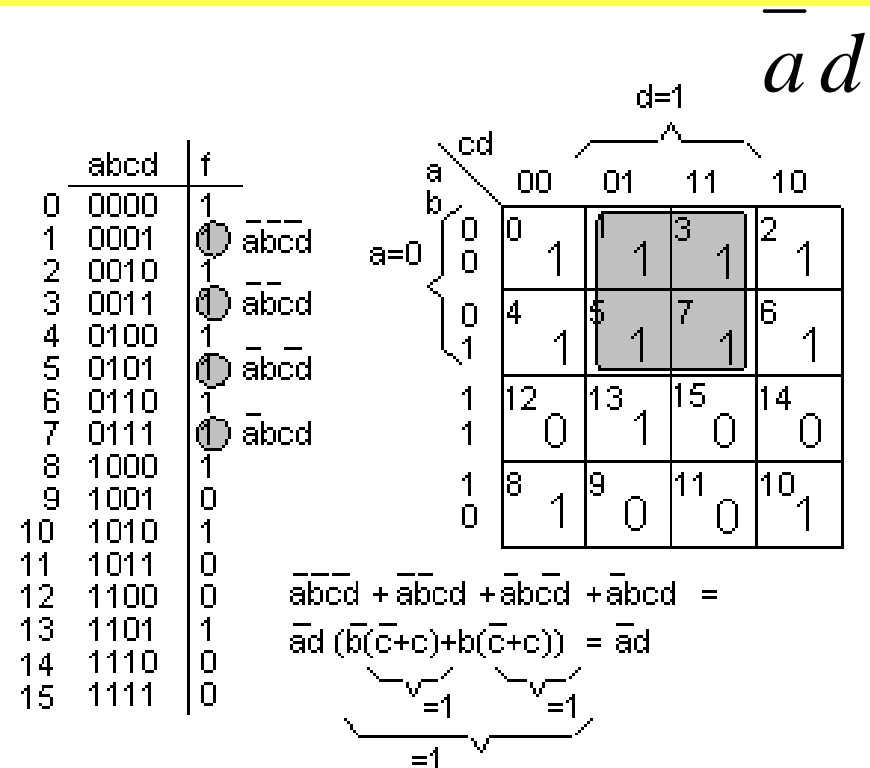The four minterms could be reduced to a term that expresses what is common for the frames, namely that $a = 0$ and $d = 1$.



Everywhere in Karnaugh map where one can find such groups of four ones such simplifications can be done, grouping of four.

Eight "neighbors"

\overline{a}


		cd			
		00 01 11 10			
a=0 {	b	0	1	3	2
	0	0	1	1	1
	0	4	5	7	6
	1	1	1	1	1
	1	12	13	15	14
	1	0	1	0	0
	1	8	9	11	10
	0	1	0	0	1

\overline{a}

All groups of 2, 4, 8, (... 2^N ie. powers of 2) frames containing ones can be reduced to a term, with what they have in common, grouping of n.

Karnaugh - torus


		cd			
		00	01	11	10
a b	0 0	0 1	1 1	3 1	2 1
	0 1	4 1	5 1	7 1	6 1
	1 1	12 0	13 1	15 0	14 0
	1 0	8 1	9 0	11 0	10 1

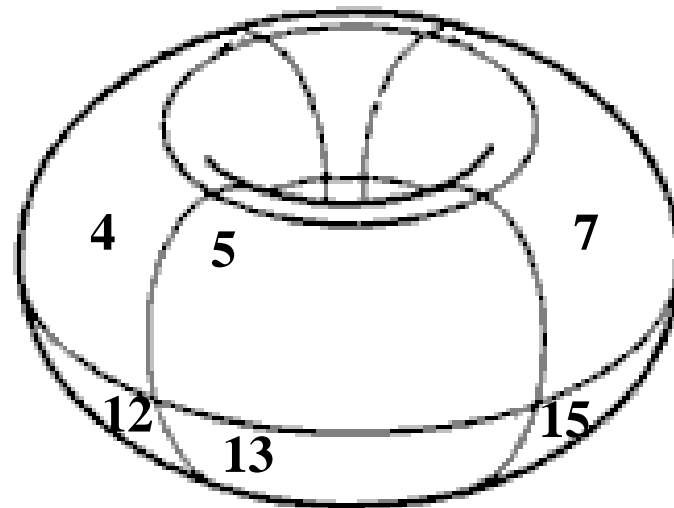

The Karnaugh map should be drawn on a torus (a donut). When we reach an edge, the graph continues from the opposite side! Frame 0 is the "neighbor" with frame 2, but also the "neighbor" with frame 8 which is "neighbor" to frame 10.

The optimal groupings

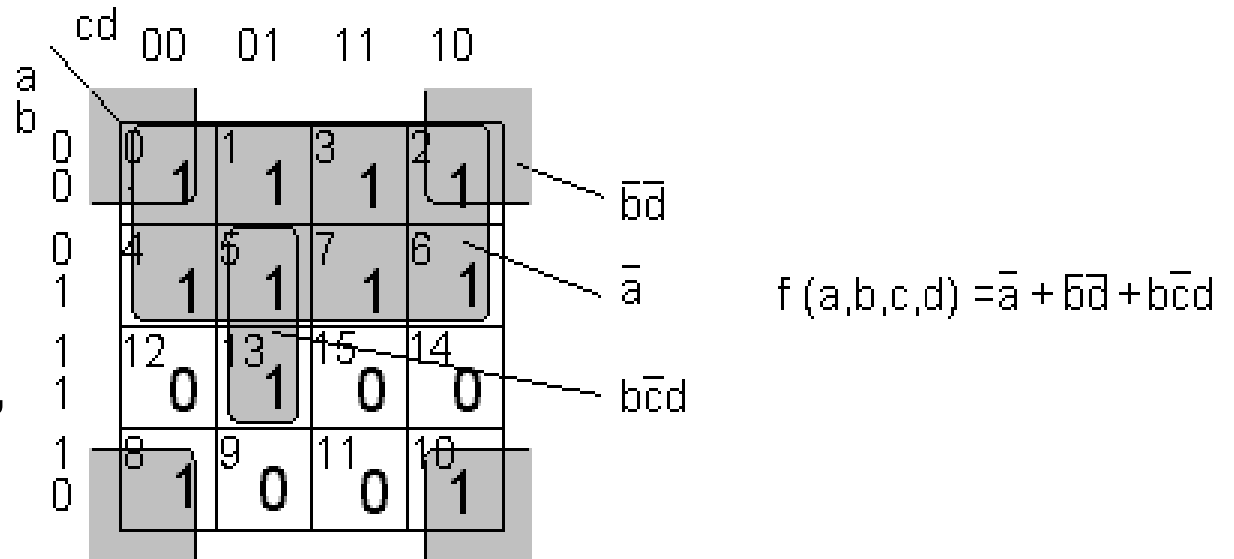
One is looking for the biggest grouping as possible. In the example, there is a grouping with eight ones (frames 0, 1, 3, 2, 4, 5, 7, 6). Corners (0, 2, 8, 10) is a group of four ones.



Two of the frames (0,10) has already been included in the first group, but it does not matter if a minterm is included multiple times. All ones in the logic function must either be in a grouping, or be included as a minterm. The "1" in frame 13 may form a group with "1" in frame 5, unfortunately there are no bigger grouping for this "1".

$$f(a,b,c,d) = \bar{a} + \bar{b}\bar{d} + b\bar{c}d$$

Grouping of "0"

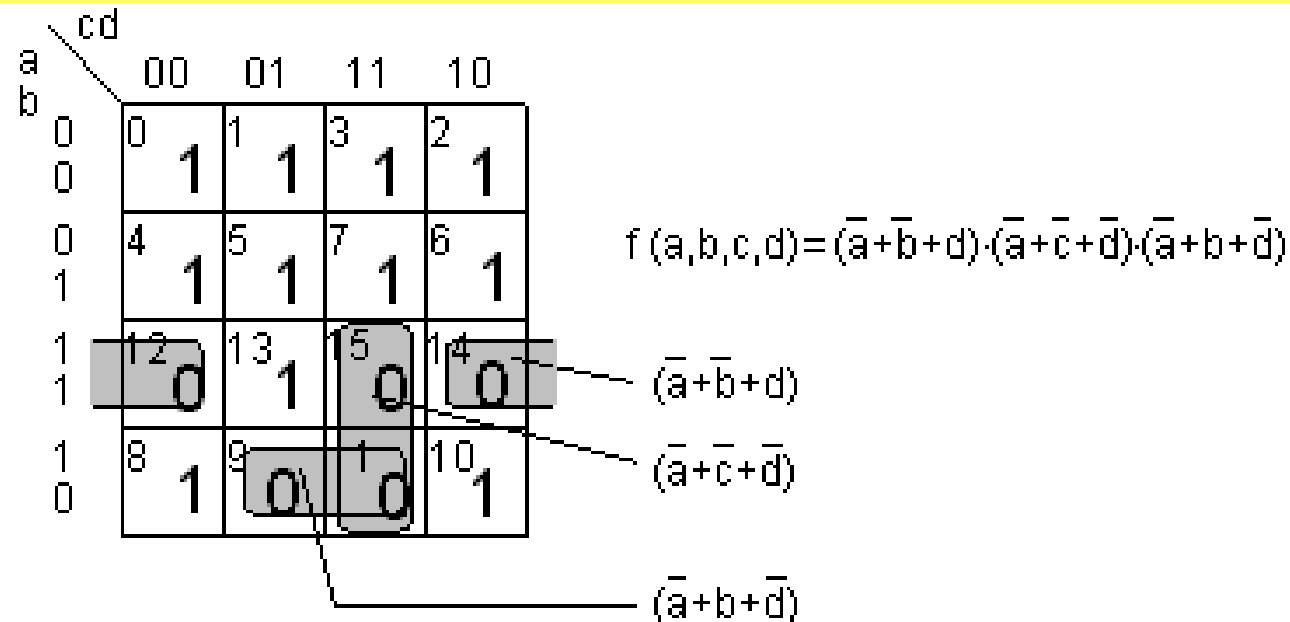

The Karnaugh map is also useful for groupings of 0's. The groupings may include the same number of frames as the case of groupings of 1's. In this example, 0's are grouped together in pairs with their "neighbors". Maxterms are simplified to what is in common for the frames.

$$f(a,b,c,d) = (\bar{a} + \bar{b} + d)(\bar{a} + \bar{c} + \bar{d})(\bar{a} + b + \bar{d})$$

Maps for other number of variables

	c	b	a
0	0	0	0
1	0	0	1
2	0	1	0
3	0	1	1
4	1	0	0
5	1	0	1
6	1	1	0
7	1	1	1

	ba			
c	00	01	11	10
0	0	1	3	2
1	4	5	7	6

	b	a
0	0	0
1	0	1
2	1	0
3	1	1

	a	
b	0	1
0	0	1
1	2	3

Karnaugh maps with three and two variables are also useful.

The Karnaugh map can conveniently be used for functions of up to four variables, and with a little practice up to six variables.

Maps for different number of variables

	abcd
0	0000
1	0001
2	0010
3	0011
4	0100
5	0101
6	0110
7	0111
8	1000
9	1001
10	1010
11	1011
12	1100
13	1101
14	1110
15	1111

		cd			
a	b	00	01	11	10
		0	1	3	2
0	0				
0	1	4	5	7	6
1	0	12	13	15	14
1	1	8	9	11	10

Literals and Product-Terms

- A given product-term consists of several variables (like $a\bar{b}\bar{c}$)
 - Each of the variables may appear complemented or uncomplemented
 - These variables are called literals (like a, \bar{b}, \bar{c})
- $$f(a,b,c) = \bar{a}\bar{b}\bar{c} + ab + bc$$

Minterms and product-terms

- A minterm always contains all variables of a function
 - Examples of minterms for three variable functions:
 $abc, \bar{a}\bar{b}\bar{c}$
- A product-term may contain less variables
 - Examples of product-terms for three variable functions:
 abc, ab, a

Implicants and Covers


- **Implicant** - A product-term for which the function evaluates to 1
- **Prime implicant** - An implicant which is not contained in any other implicant
 - A prime implicants cannot be expanded into a larger implicant
- **Cover** is a set of implicants which contains all minterms for which the function evaluates to 1

More implicant terminology

- A prime implicant is **essential** if there is a minterm covered by that implicant, but no other prime implicant
 - Essential implicants will always be included in a cover of a function
- If we can remove an implicant, but all minterms are still covered, then such an implicant is called **redundant**

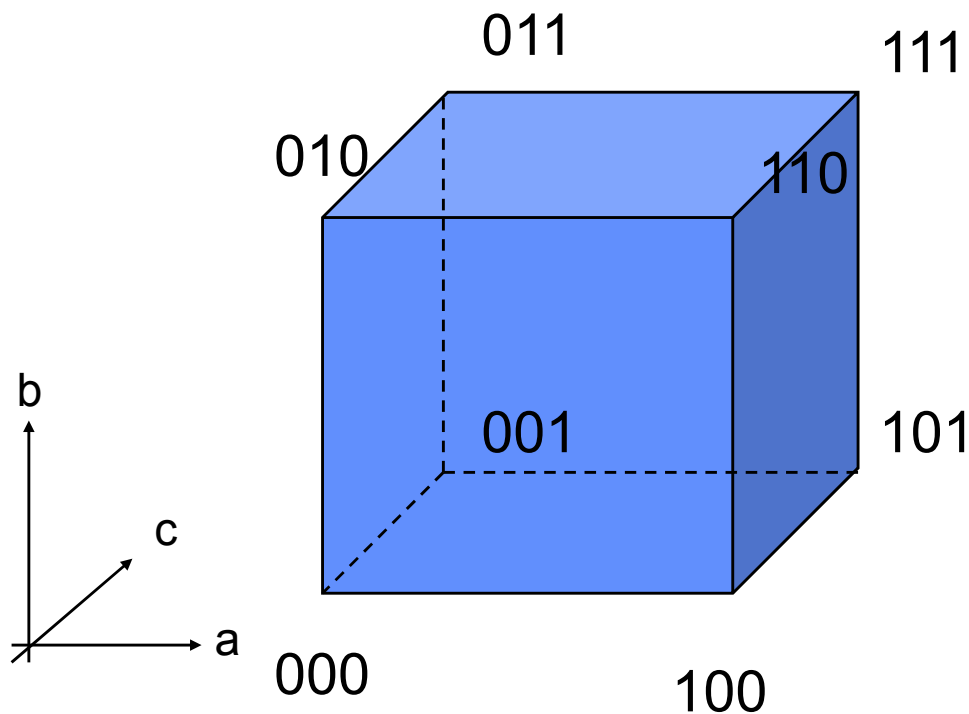Example

Redundant implicants -
both are not necessary
to cover the function





		bc			
		00	01	11	10
a	0	1		1	1
	1		1	1	

$$f(a, b, c) = \Sigma m(0, 2, 3, 5, 7)$$

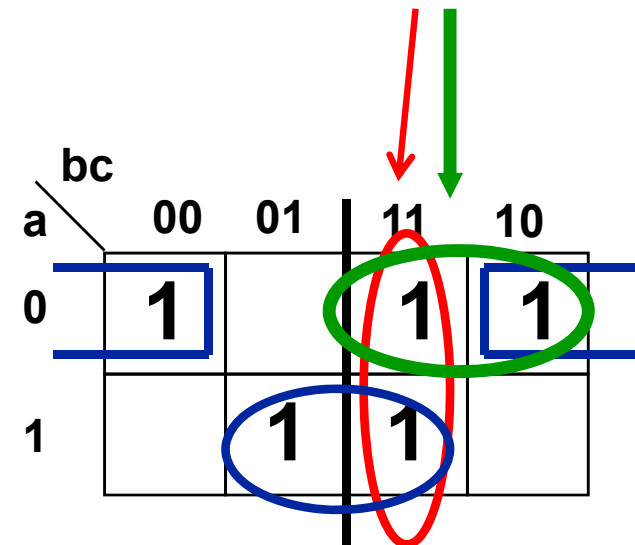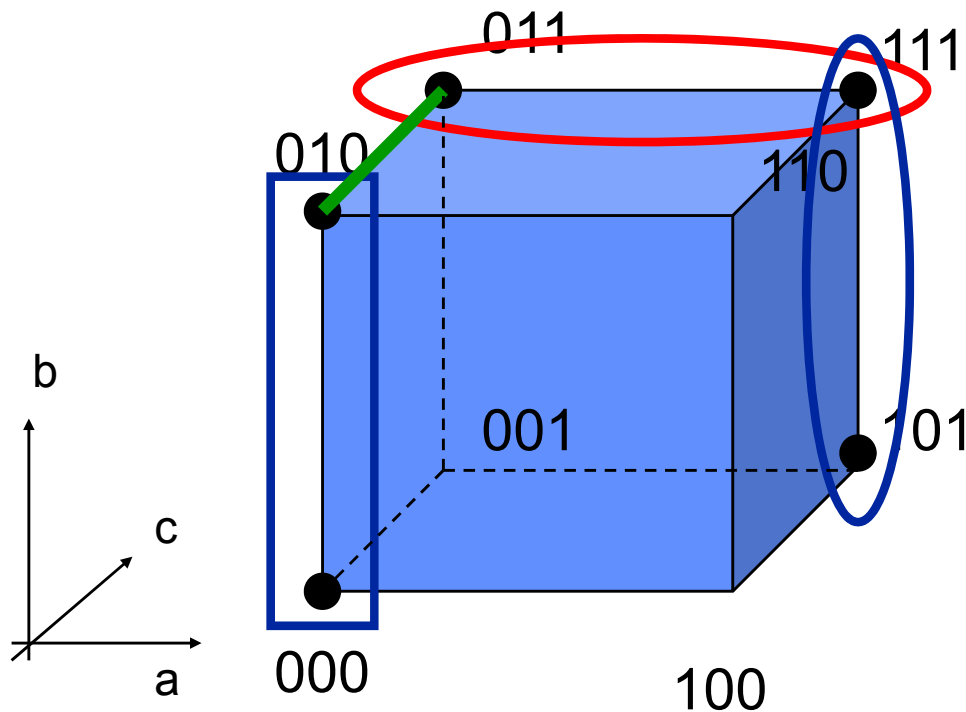Example


Redundant implicants -
both are not necessary
to cover the function




$$f(a, b, c) = \Sigma m(0, 2, 3, 5, 7)$$

Two-level minimization

Minimum sum-of-product implementation

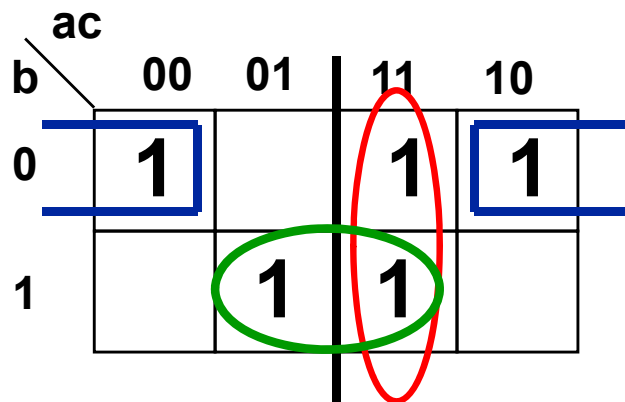


$$f = \bar{b}\bar{c} + ac + bc$$

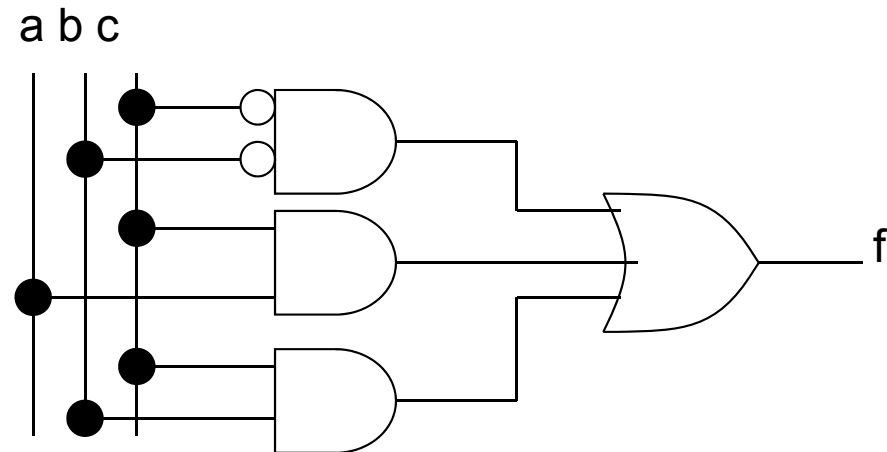


Programmable Logic Array (PLA)

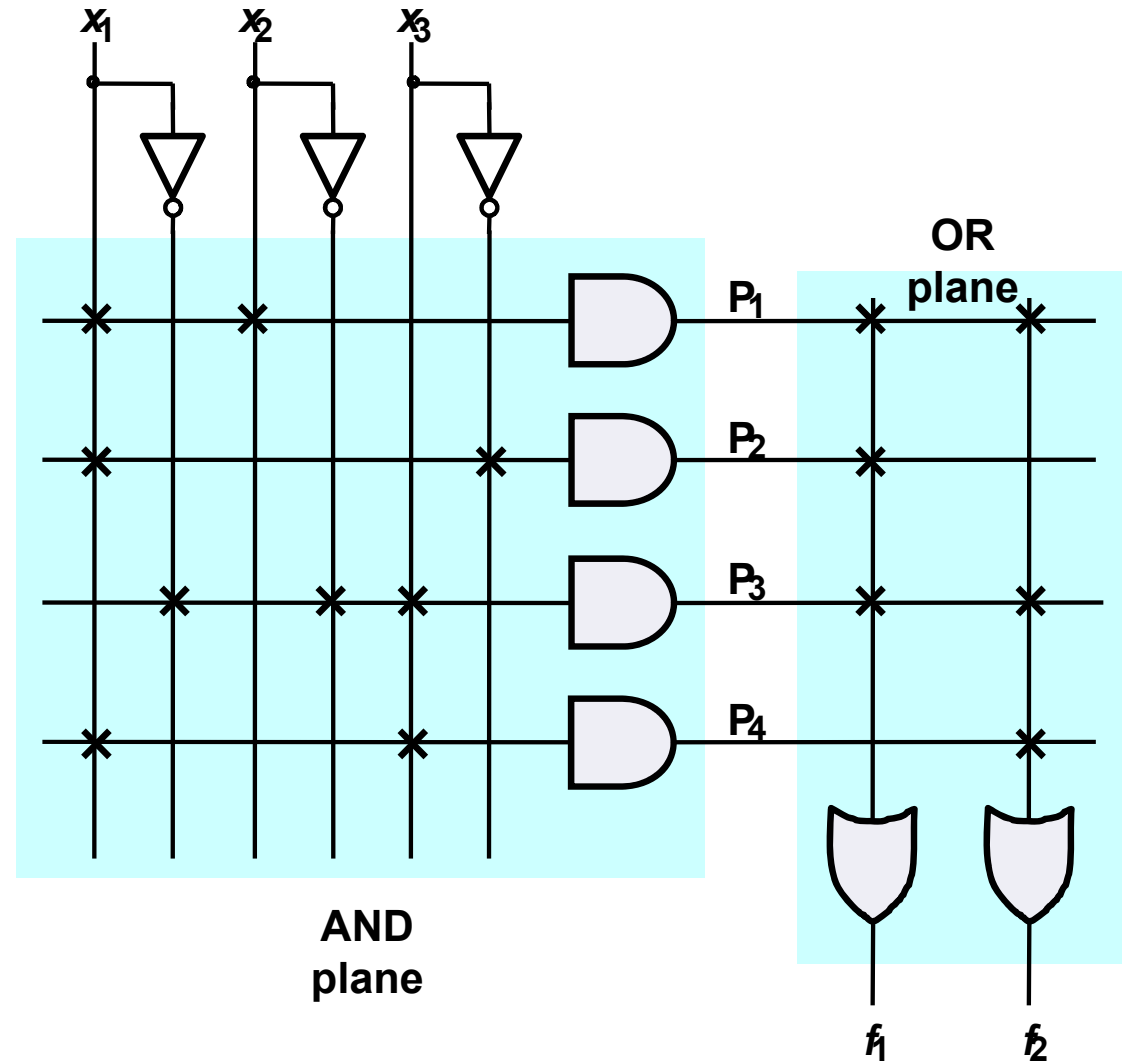- Both AND and OR arrays are programmable




Programmable Array Logic (PAL)

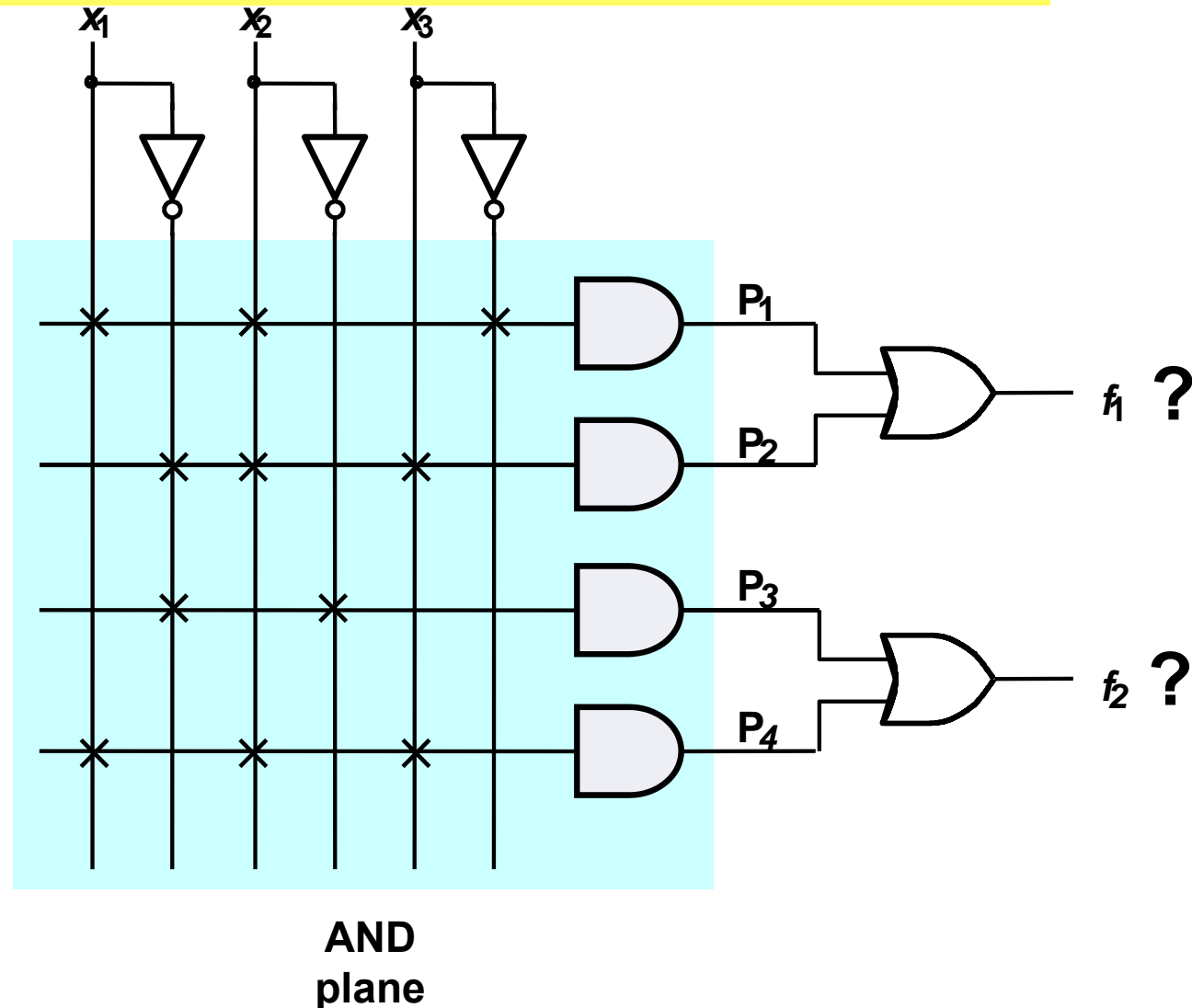- Only the AND arrays are programmable
- Which functions P_1 , P_2 , P_3 and P_4 represent ?



Karnaugh map with 4 variables

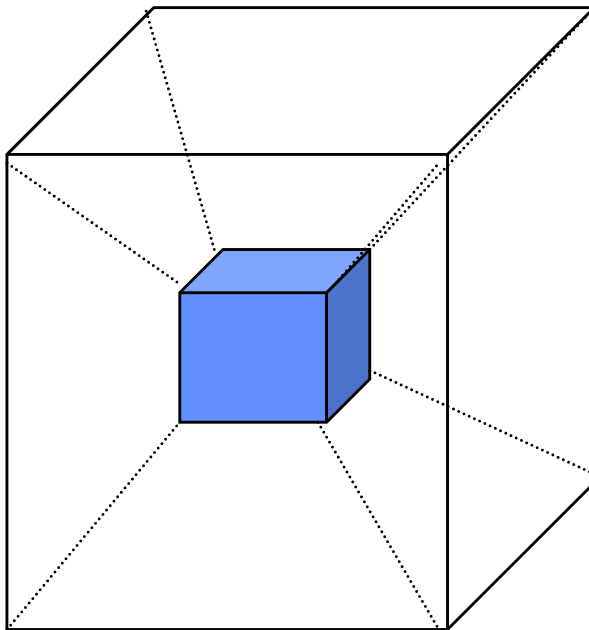

x_1x_0		00	01	11	10
x_3x_2	00				
	01				
	11	1	1	1	1
	10	1	1	1	1

$f = x_3$

We always circle an entire sub-space (as large as possible) !!!

XOR/XNOR function?

If two groups of four minterms can not form a group of eight, the XOR / XNOR function may be helpful.

x_1x_0		x_3x_2			
		00	01	11	10
00	00	1			1
	01		1	1	
11	11		1	1	
	10	1			1

This is under the assumption that there exists an efficient implementation of the XOR function.

$$f = \overline{x_2} \overline{x_0} + x_2 x_0 = \overline{x_2 \oplus x_0}$$

Order of minterms

$$f(x_3, x_2, x_1, x_0) = \sum m(0, 3, 7, 14)$$

Diagram illustrating the order of minterms in a 4-variable Karnaugh map. The variables are labeled as follows:

- x_3 is the MSB (Most Significant Bit).
- x_0 is the LSB (Least Significant Bit).
- x_1x_0 is the label for the columns.
- x_3x_2 is the label for the rows.

$x_3x_2 \backslash x_1x_0$	00	01	11	10
00	0	1	3	2
01	4	5	7	6
11	12	13	15	14
10	8	9	11	10

Example

- Example: $f(a, b, c, d) = ?$

		ab			
		00	01	11	10
cd	00	0	0	0	0
	01	0	1	1	0
	11	1	1	1	1
	10	0	0	1	0

Example

- Example: $f(a, b, c, d) = abc + bd + cd$

		ab			
cd		00	01	11	10
	00	0	0	0	0
	01	0	1	1	0
	11	1	1	1	1
c	10	0	0	1	0

Example

- Example: $f(a, b, c, d) = abc + bd + cd$

		b			
		ab			
cd		00	01	11	10
	00	0	0	0	0
	01	0	1	1	0
	11	1	1	1	1
	10	0	0	1	0

Example

- Example: $f(a, b, c, d) = abc + bd + cd$

		ab			
		00	01	11	10
cd	00	0	0	0	0
	01	0	1	1	0
	11	1	1	1	1
	10	0	0	1	0

Example

- Example: $f(a, b, c, d) = abc + bd + cd$

cd \ ab		ab			
		00	01	11	10
00		0	0	0	0
01		0	1	1	0
11		1	1	1	1
10		0	0	1	0

Example

x_1x_0		00	01	11	10
x_3x_2	00	1	1	1	1
	01	1	0	1	1
	11	1	1	1	1
	10	1	1	1	1

Alternative: Circle 0s

$x_3x_2 \backslash x_1x_0$	00	01	11	10
00	1	1	1	1
01	1	0	1	1
11	1	1	1	1
10	1	1	1	1

$x_3x_2 \backslash x_1x_0$	00	01	11	10
00	1	1	1	1
01	1	0	1	1
11	1	1	1	1
10	1	1	1	1

$$\overline{x_3 x_2 x_1 x_0} =$$

$$x_3 + \overline{x_2} + x_1 + \overline{x_0}$$

Circle the zeros as zeros are less than ones !!!

Karnaugh map with 5 variables

x_4

Approach A

$x_4 = 0$

$x_3x_2 \backslash x_1x_0$					
		00	01	11	10
x_3x_2	00				
	01			1	
	11				
	10				

$x_4 = 1$

$x_3x_2 \backslash x_1x_0$					
		00	01	11	10
x_3x_2	00				
	01			1	
	11				
	10				

Same in both diagrams, independent of x_4 . $\bar{x}_3 x_2 x_1 x_0$

Karnaugh map with 6 variables

$$x_4 = 0$$

$$x_4 = 1$$

Approach A

$$x_5 = 0$$

		x_1x_0			
		00	01	11	10
x_3x_2	00				
	01			1	
	11				
	10				

		x_1x_0			
		00	01	11	10
x_3x_2	00				
	01			1	
	11				
	10				

$$x_5 = 1$$


		x_1x_0			
		00	01	11	10
x_3x_2	00				
	01			1	
	11				
	10				

		x_1x_0			
		00	01	11	10
x_3x_2	00				
	01			1	
	11				
	10				

$$\overline{x_3x_2x_1x_0}$$

Independent
of x_5 and x_4 .

Karnaugh map with 5 variables

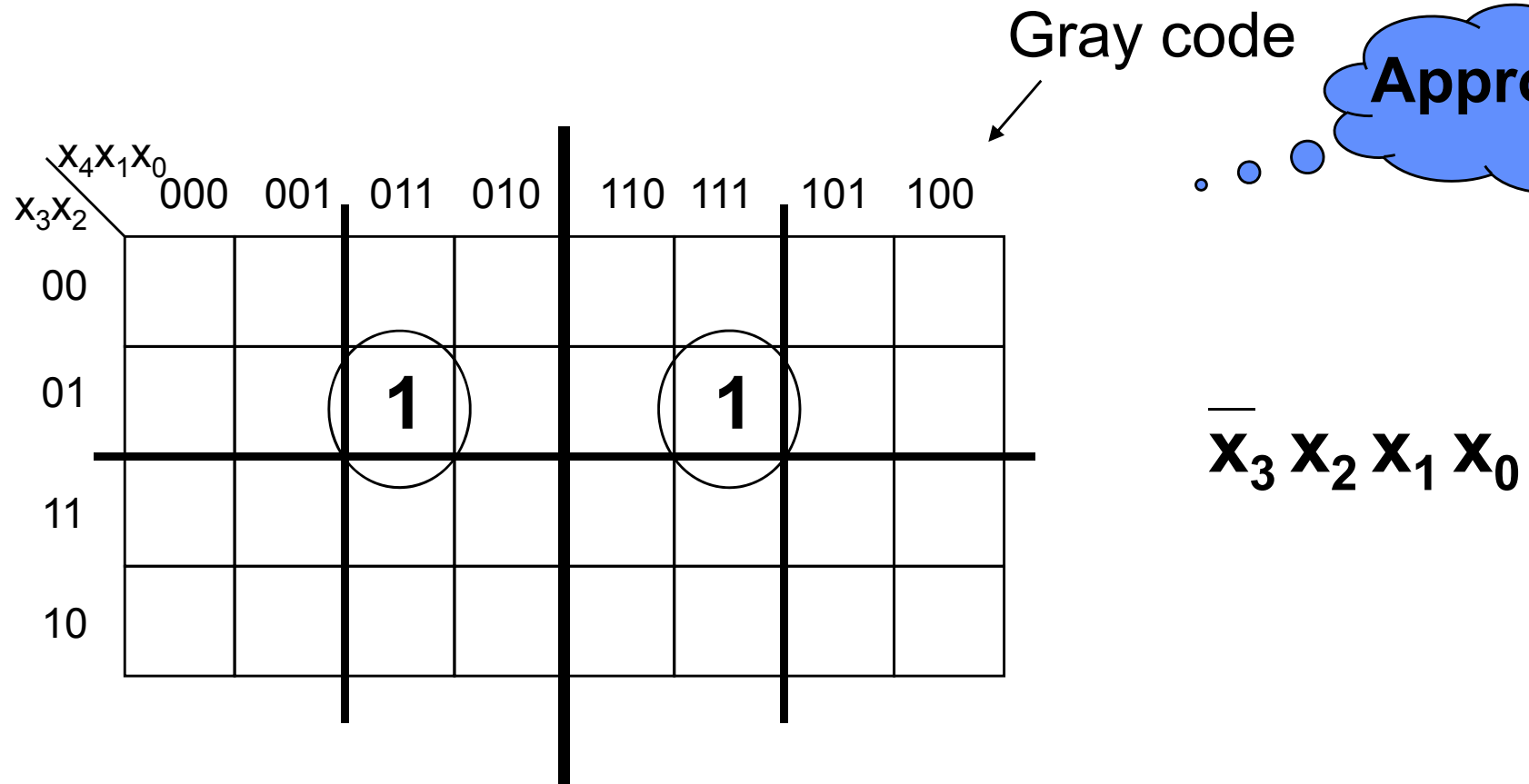

Example


$x_4x_3 \backslash x_2x_1x_0$	000	001	011	010	110	111	101	100
00						1		
01								
11								
10						1		

Approach B

$\overline{x_3} x_2 x_1 x_0$

Karnaugh map with 6 variables

Note!

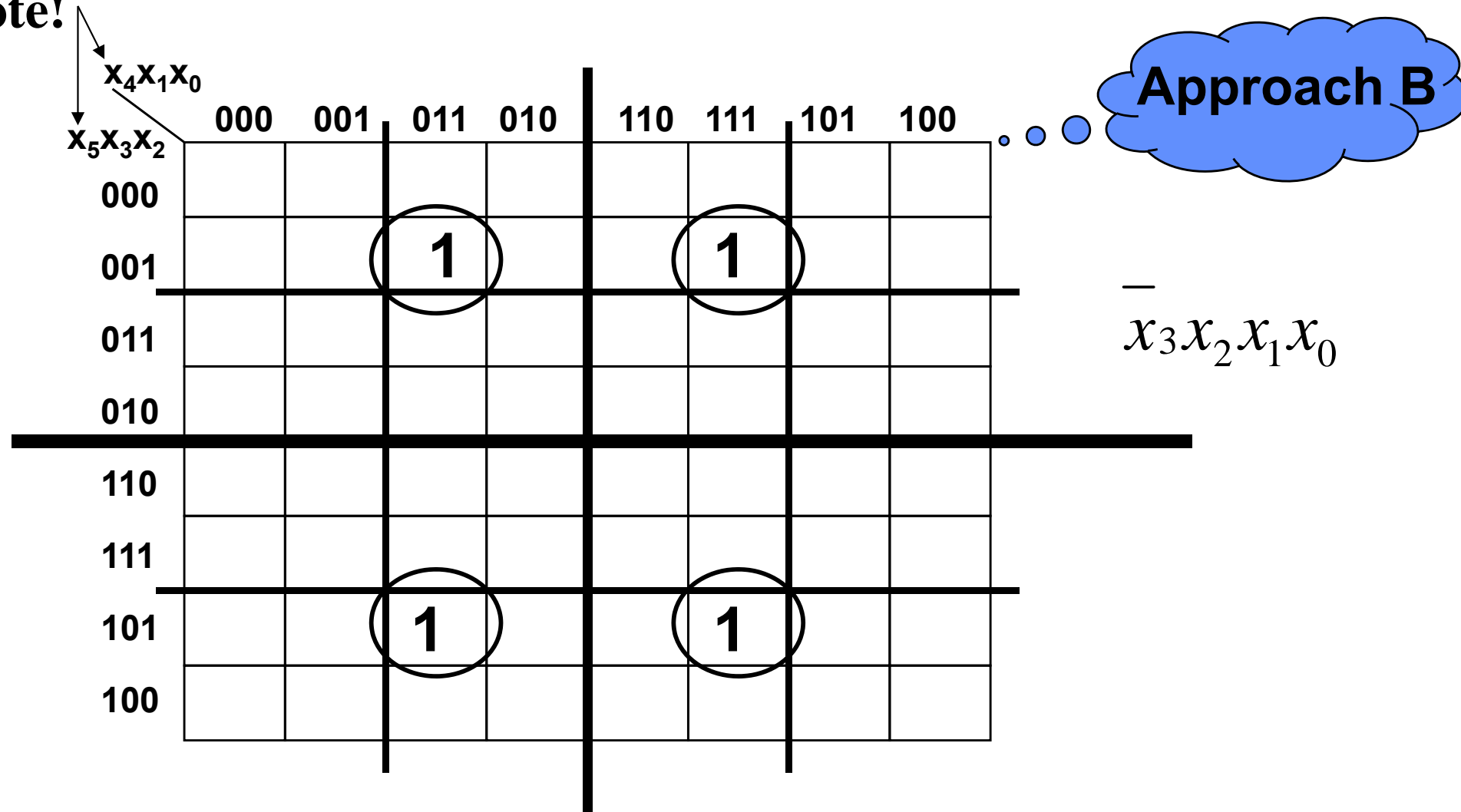

Example

$x_5 x_4 x_3$ \ $x_2 x_1 x_0$	000	001	011	010	110	111	101	100
000						1		
001								
011								
010						1		
110						1		
111								
101								
100						1		


... Approach B

$\overline{x}_3 x_2 x_1 x_0$


Incomplete functions with don't cares

- Often you can simplify a specification of the logic function knowing that some input combinations never occur
- For these combinations, we use the value "don't care"
- There are different symbols for "don't care"
 - 'd', 'D', '-', ' ϕ ', 'x'

Specification of incomplete functions

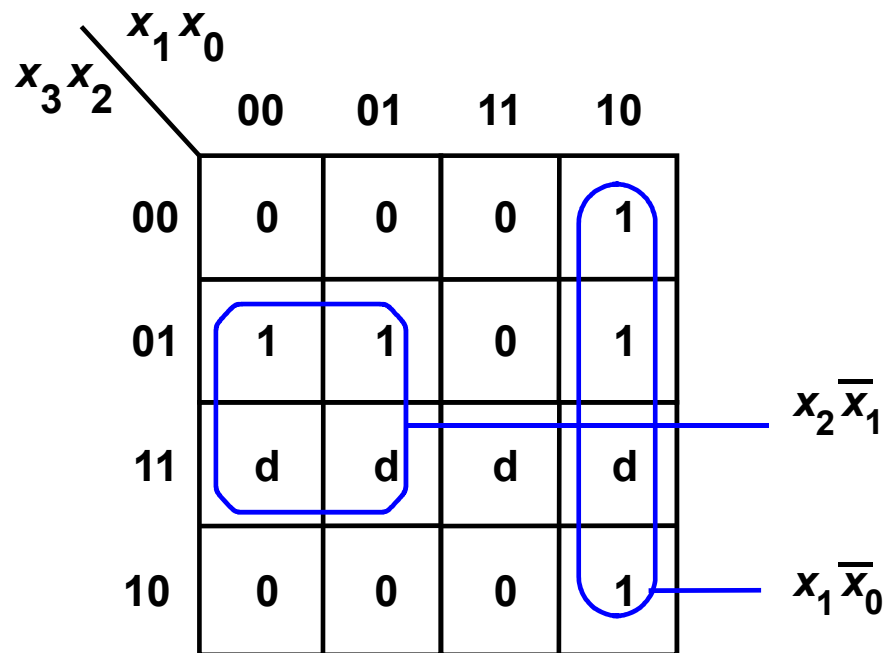


(A) SOP implementation

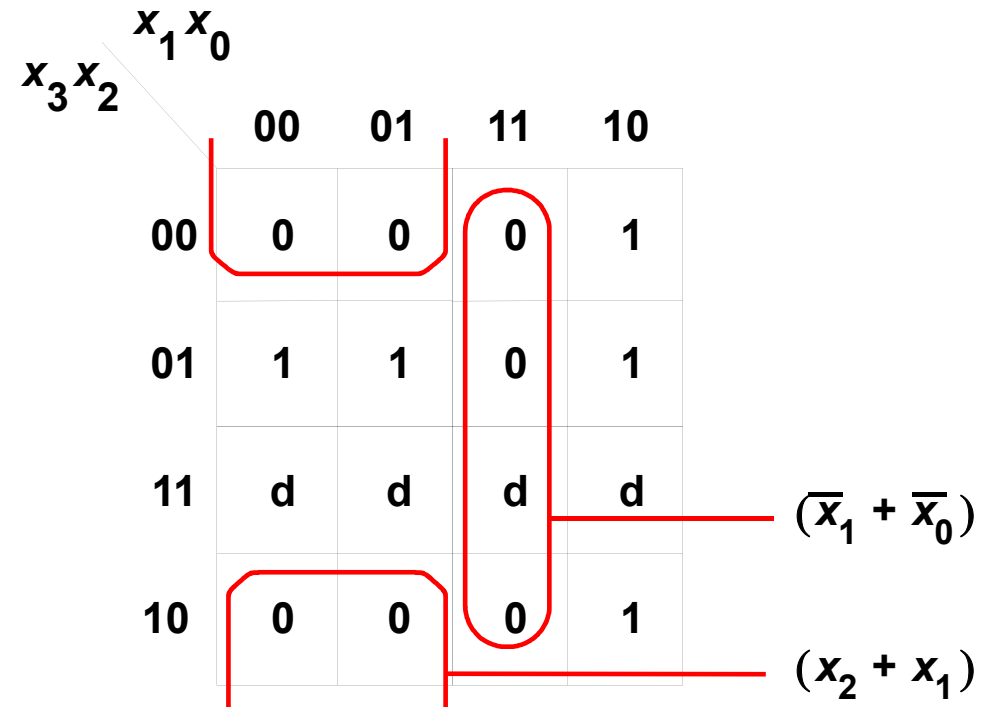


(B) POS implementations

Two implementations of the function
 $f(x_3, \dots, x_0) = \sum m(2, 4, 5, 6, 10) + D(12, 13, 14, 15).$

Alternative notation

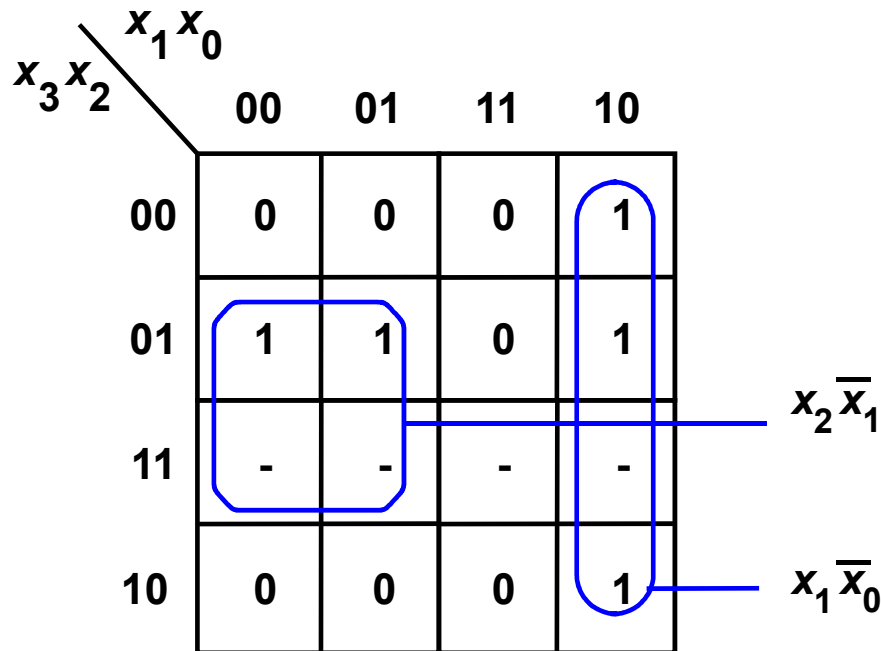

(A) SOP implementation

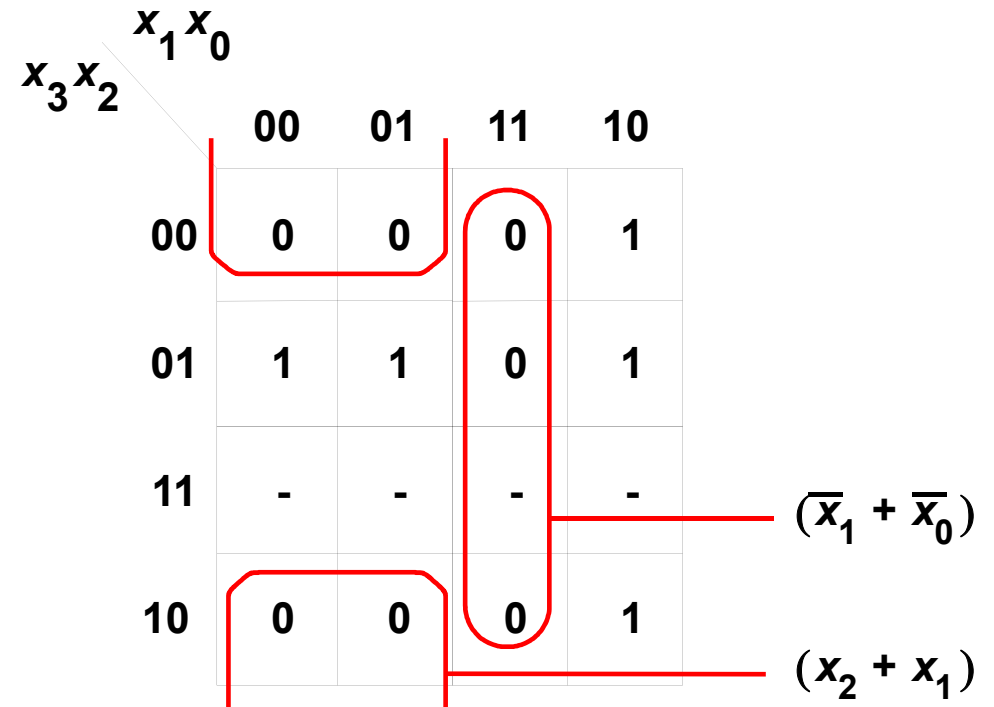

(B) POS implementations

Two implementations of the function
 $f(x_3, \dots, x_0) = \sum m(2, 4, 5, 6, 10) + D(12, 13, 14, 15).$

Functions with multiple outputs

		f_0						f_1			
		x_1x_0						x_1x_0			
x_3x_2	00	1	0	1	1			1	0	1	1
	01	0	0	0	1			0	0	0	1
	11	0	0	0	1			1	0	0	1
	10	1	0	1	1			1	0	1	1

Different outputs can share implicants!

Functions with multiple outputs

f_0

x_1x_0	00	01	11	10
x_3x_2 00	1	0	1	1
01	0	0	0	1
11	0	0	0	1
10	1	0	1	1

f_1

x_1x_0	00	01	11	10
x_3x_2 00	1	0	1	1
01	0	0	0	1
11	1	0	0	1
10	1	0	1	1

$$f_1 = f_0 + x_3 \bar{x}_0$$

Different outputs can share implicants!

Multi-level minimization

Do we need multi-level logic?

- One can realize all the combinational circuits with two-level (AND-OR, OR-AND)
 - The assumption is that all inputs are also available in the inverted form (as in PAL, PLA)

Why multi-level logic?

- A multi-level implementation may have considerably less gates than a two-level implementation

Two strategies for multi-level logic

1. Factorization
2. Functional Decomposition

Factorization

- Suppose the following function is to be implemented


$$f = x_1 \bar{x}_2 x_3 \bar{x}_4 x_5 x_6 + x_1 x_2 \bar{x}_3 \bar{x}_4 \bar{x}_5 x_6$$

Factorization

- If we use the distributive rule (L2, s.21, 12a), we can get the following multi-level implementation:

$$\begin{aligned} f &= x_1 \bar{x}_2 x_3 \bar{x}_4 x_5 x_6 + x_1 x_2 \bar{x}_3 \bar{x}_4 \bar{x}_5 x_6 \\ &= x_1 \bar{x}_4 x_6 \cdot (\bar{x}_2 x_3 x_5 + x_2 \bar{x}_3 \bar{x}_5) \end{aligned}$$

Factorization

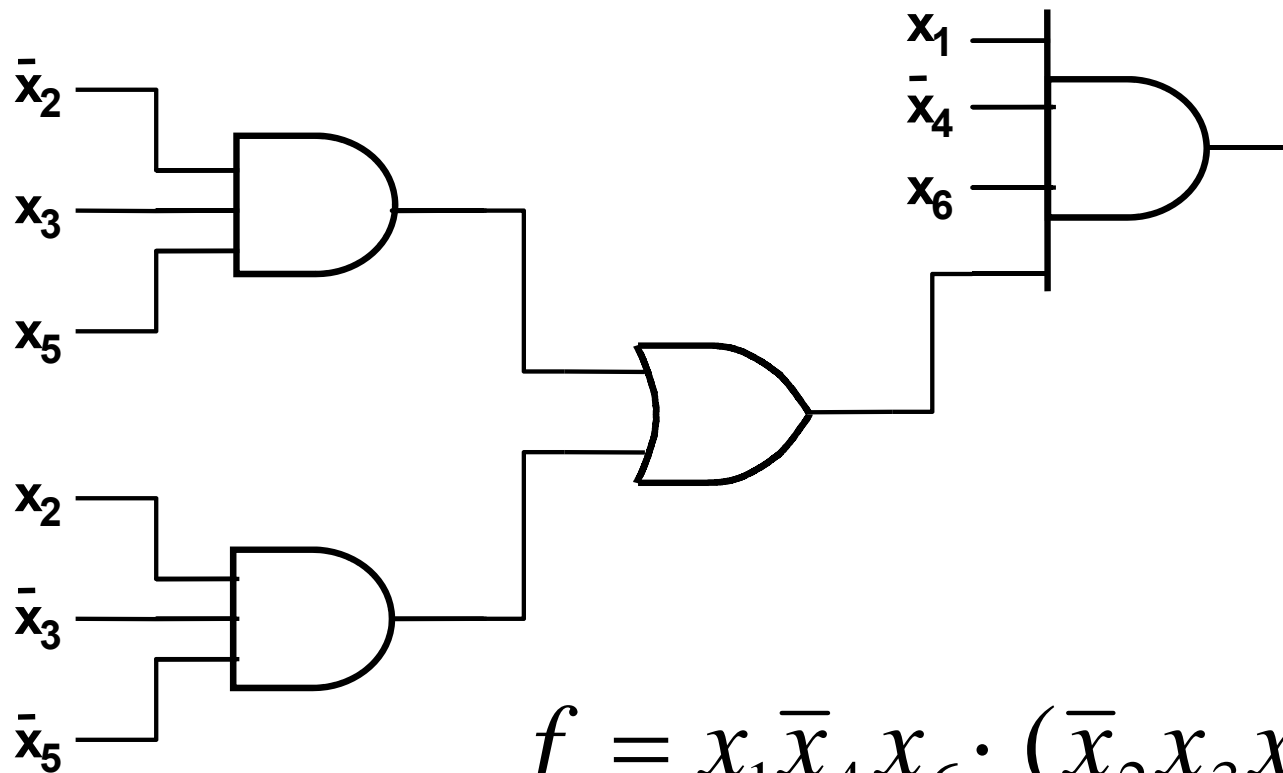

$$f = x_1 \bar{x}_4 x_6 \cdot (\bar{x}_2 x_3 x_5 + x_2 \bar{x}_3 \bar{x}_5)$$

Functional decomposition

- One can often reduce the complexity of a logic function by reusing its sub-functions several times
- For implementation it means to *share sub-circuits* in its construction

Functional Decomposition

- How can the following function be implemented?

$$f = \bar{x}_1 x_2 x_3 + x_1 \bar{x}_2 x_3 + x_1 x_2 x_4 + \bar{x}_1 \bar{x}_2 x_4$$

Functional Decomposition

- Factorization gives us

$$\begin{aligned} f &= \bar{x}_1 x_2 x_3 + x_1 \bar{x}_2 x_3 + x_1 x_2 x_4 + \bar{x}_1 \bar{x}_2 x_4 \\ &= (\underbrace{\bar{x}_1 x_2 + x_1 \bar{x}_2}_{\text{XOR}}) x_3 + (\underbrace{x_1 x_2 + \bar{x}_1 \bar{x}_2}_{\text{XNOR}}) x_4 \\ &\quad \quad \quad = g \quad \quad \quad = \bar{g} \end{aligned}$$

- If we define a sub-function g as

$$g = \bar{x}_1 x_2 + x_1 \bar{x}_2$$

Functional Decomposition

- So, we get


$$f = gx_3 + \bar{g}x_4$$

- where

$$g = \bar{x}_1x_2 + x_1\bar{x}_2 = \overline{x_1x_2 + \bar{x}_1\bar{x}_2}$$


Functional Decomposition

Implementation

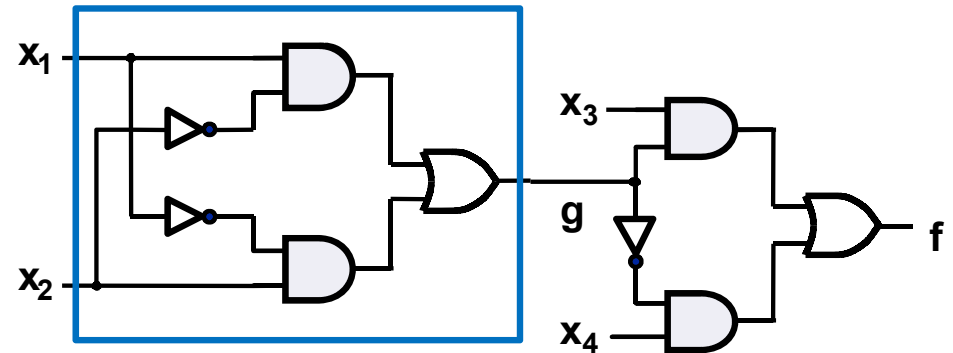

$$f = gx_3 + \bar{g}x_4$$
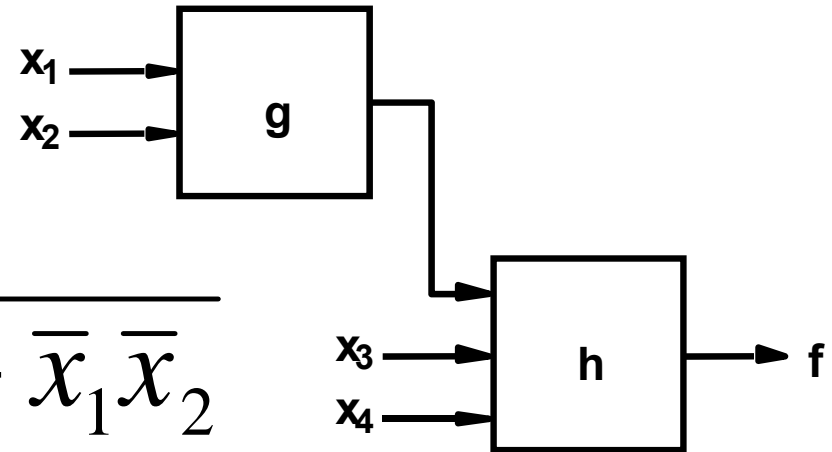
$$g = \bar{x}_1x_2 + x_1\bar{x}_2 = \overline{x_1x_2 + \bar{x}_1\bar{x}_2}$$



Algorithms for minimization

- Karnaugh map minimization gives a good insight into how to minimize logic functions
- But to minimize the complex functions with the help of computer, there are better algorithms
- Chapter 4.9 and 4.10 in Brown/Vranesic provides an introduction to the minimization algorithms (for the interested student)

Summary

- Karnaugh maps are a good tool for minimizing logic functions with a few variables
- There are algorithms for both two-level and multi-level minimization
- Next lecture: BV pp. 250-280