

IE1204/5 Digital Design **example exam**

- **Part A1** (10p in total) eight short *Analysis* tasks, 1p or 2p each
 - They are corrected only as **Right/Wrong!**
 - You need to get at least 6p on A1, otherwise parts A2 and B will not be marked at all!
- **Part A2** (10p in total) two *Methodology* tasks.
Marked only if there is at least 6p in part A1.
- **Part B** (10p in total) two *Design problems*.
Marked Only if there is at least 11p in parts A1+A2.

Pass-limit for the entire exam is at least **11p**, A1+A2+(B).
You can pass with no points from part B.

Grading scale


A1 10p A2 10p B 10p

Less than 11p på A1+A2 \Rightarrow F

Part B will not be marked!

Max 30

0 –	11 –	16 –	19 –	22 –	25
F	E	D	C	B	A

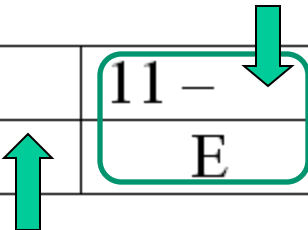

Less than 6p at A1 \Rightarrow F

Part A'' will not be marked!



- You can theoretical get grade C *without* solving part B.

Part A1 Analysis

- Right or wrong, 0p / 1p / 2p
- Minimum 6p out of 10p,
otherwise parts A2 and B will
not be marked at all!

?: Part **A1** (**2/1/0**) task **1**.

$$f(x, y, z) = z(\bar{x} + x\bar{y}) + xy\bar{z} + xyz = \{SoP\}_{\min} = ?$$

!: Part A1 (2/1/0) task 1.

$$f(x, y, z) = z(\bar{x} + x\bar{y}) + xy\bar{z} + xyz = \{SoP\}_{\min} = ?$$

$$f(x, y, z) = \bar{x}\bar{y}z + \bar{x}yz + x\bar{y}z + xyz + xy\bar{z}$$

!: Part A1 (2/1/0) task 1.

$$f(x, y, z) = z(\bar{x} + x\bar{y}) + xy\bar{z} + xyz = \{SoP\}_{\min} = ?$$

$$f(x, y, z) = \bar{x}\bar{y}z + \bar{x}yz + x\bar{y}z + xyz + xy\bar{z}$$




		yz				f
		00	01	11	10	
x	0		$\bar{x}\bar{y}z$	$\bar{x}yz$		
	1		$x\bar{y}z$	xyz	$xy\bar{z}$	

!: Part A1 (2/1/0) task 1.

$$f(x, y, z) = z(\bar{x} + x\bar{y}) + xy\bar{z} + xyz = \{SoP\}_{\min} = ?$$

$$f(x, y, z) = \bar{x}\bar{y}z + \bar{x}yz + x\bar{y}z + xyz + xy\bar{z}$$

		f			
x	yz	00	01	11	10
0			$\bar{x}\bar{y}z$	$\bar{x}yz$	
1			$x\bar{y}z$	xyz	$xy\bar{z}$

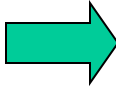


		f			
x	yz	00	01	11	10
0			1	1	
1			1	1	1

!: Part A1 (2/1/0) task 1.

$$f(x, y, z) = z(\bar{x} + x\bar{y}) + xy\bar{z} + xyz = \{SoP\}_{\min} = ?$$

$$f(x, y, z) = \bar{x}\bar{y}z + \bar{x}yz + x\bar{y}z + xyz + xy\bar{z}$$

		f				
		yz	00	01	11	10
x	0		$\bar{x}\bar{y}z$	$\bar{x}yz$		
	1		$x\bar{y}z$	xyz	$xy\bar{z}$	

 

		f			
		yz	00	01	11
x	0		1	1	
	1		1	1	1



$$f(x, y, z) = \{SoP\}_{\min} = z + xy$$

?: Part A1 (1/0) task 2.

2's complement-representation
of an 8-bit number .


--	--	--	--	--	--	--	--

$$(B7)_{16} - (A6)_{16} = ?_{16}$$

$$\pm ?_{10} - \pm ?_{10} = \pm ?_{10}$$

!: Part A1 (1/0) task 2.

 2's complement-representation
of an 8-bit number .



Signbit!

$$(B7)_{16} - (A6)_{16} = ?_{16}$$

$$\pm ?_{10} - \pm ?_{10} = \pm ?_{10}$$

$$(B7)_{16} = (10110111)_2 = (-01001001)_2 = (-49)_{16} = (-73)_{10}$$

$$(A6)_{16} = (10100110)_2 = (-01011010)_2 = (-5A)_{16} = (-90)_{10}$$

$$(B7)_{16} - (A6)_{16} = (B7)_{16} + (5A)_{16} = (11)_{16}$$

$$(-73)_{10} - (-90)_{10} = (17)_{10}$$

!: Part A1 (2/1/0) task 3.

	$x_3x_2x_1x_0$	f		$x_3x_2x_1x_0$	f
0	0000	1	8	1000	1
1	0001	0	9	1001	–
2	0010	1	10	1010	–
3	0011	–	11	1011	0
4	0100	0	12	1100	1
5	0101	1	13	1101	0
6	0110	0	14	1110	–
7	0111	0	15	1111	0

$$f(x_3x_2x_1x_0) = \{PoS\}_{\min} = ?$$

!: Part A1 (2/1/0) task 3.

	$x_3x_2x_1x_0$	f		$x_3x_2x_1x_0$	f
0	0000	1	8	1000	1
1	0001	0	9	1001	-
2	0010	1	10	1010	-
3	0011	-	11	1011	0
4	0100	0	12	1100	1
5	0101	1	13	1101	0
6	0110	0	14	1110	-
7	0111	0	15	1111	0



$f(x_3x_2x_1x_0) = \{PoS\}_{\min} = ?$
Groupings of 0:es


		x_1x_0			
		00	01	11	10
x_3x_2	00	⁰ 1	¹ 0	³ -	² 1
	01	⁴ 0	⁵ 1	⁷ 0	⁶ 0
	11	¹² 1	¹³ 0	¹⁵ 0	¹⁴ -
	10	⁸ 1	⁹ -	¹¹ 0	¹⁰ -



$$f(x_3x_2x_1x_0) =$$

$$(\bar{x}_0 + x_2)(\bar{x}_0 + \bar{x}_3)(\bar{x}_0 + \bar{x}_1)(x_0 + \bar{x}_2 + x_3)$$

?: Part A1 (1/0) task 4.

 


$A, B, C, D = ?$

!: Part A1 (1/0) task 4.


Lookup-table!

x	y	XOR	
0	0	0	$= D$
0	1	1	$= B$
1	0	1	$= C$
1	1	0	$= A$

 


$A = 0 \quad B = 1 \quad C = 1 \quad D = 0$

?: Part A1 (1/0) task 5.

 

$$Q(A, B) = ?$$

!: Part A1 (1/0) task 5.

 


$$Q(A, B) = ?$$

PullDown-circuit


$$\overline{Q} = A \cdot \overline{B} \Rightarrow Q = \overline{A \cdot \overline{B}} = \{dM\} = \overline{A} + B$$

?: Part A1 (1/0) task 6.

 

$(q_1q_0) = 00 \rightarrow ?? \rightarrow ?? \rightarrow ?? \rightarrow ?? \dots$

!: Part A1 (1/0) task 6.

 

Next state

$$q_1^+ = \bar{q}_1 \cdot \bar{q}_0$$

$$q_0^+ = q_1$$

$q_1 q_0$	$q_1^+ = \bar{q}_1 \cdot \bar{q}_0$	$q_0^+ = q_1$	$q_1^+ q_0^+$
00	1 = 1 · 1	0	10
10	0 = 0 · 1	1	01
01	0 = 1 · 0	0	00


$(q_1 q_0) = 00 \rightarrow 10 \rightarrow 01 \rightarrow 00 \dots$

?: Part A1 (1/0) task 7.

Complete this flow chart (for an asynchronous sequential circuit) with circles around stable states and by crossing out the conditions that can not be reached.

		$Q_1^+ Q_0^+$			
$Q_1 Q_0$	AB	00	01	11	10
a		a	a	d	a
b		a	a	c	b
c		c	c	c	b
d		c	c	d	a

!: Part A1 (1/0) task 7.

 

Inexpensive point for all those who did not "skip" section on asynchronous sequential circuits ...

- **Conclusion:** Do not skip any sections of the course!

?: Part A1 (1/0) task 8.


```
-- comment: example of buzzer circuit
entity BUZZER is
    port (DOOR, IGNITION, SBELT: in std_logic;
          WARNING: out std_logic);
end BUZZER;

architecture behavioral of BUZZER is
begin
    WARNING <= (not DOOR and IGNITION) or
               (not SBELT and IGNITION);
end behavioral;
```

- Draw entity-box with signal names and circuit diagram ...

!: Part A1 (1/0) task 8.
 
```
entity BUZZER is
    port (DOOR, IGNITION, SBELT: in std_logic;
          WARNING: out std_logic);
end BUZZER;
```




!: Part A1 (1/0) task 8.

architecture behavioral **of** BUZZER **is**
begin

```
    WARNING <= (not DOOR and IGNITION) or  
               (not SBELT and IGNITION);
```

end behavioral;

 


Part A2 Methodology

- Will be marked if you get at least 6p in part A1
- You need to get at least 11 p in A1 + A2 for the part B to be marked


?: Part A2 (5p) task 9.

- First, complete the full adder truth table.
- Then construct a full adder from two 4:1 MUXes.
- We assume the Carry signal c_{in} also available in the complemented form (as shown on Figure).


a	b	c_{in}	C_{out}	S
0	0	0	0	0
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

 

!: Part A2 (5p) task 9.

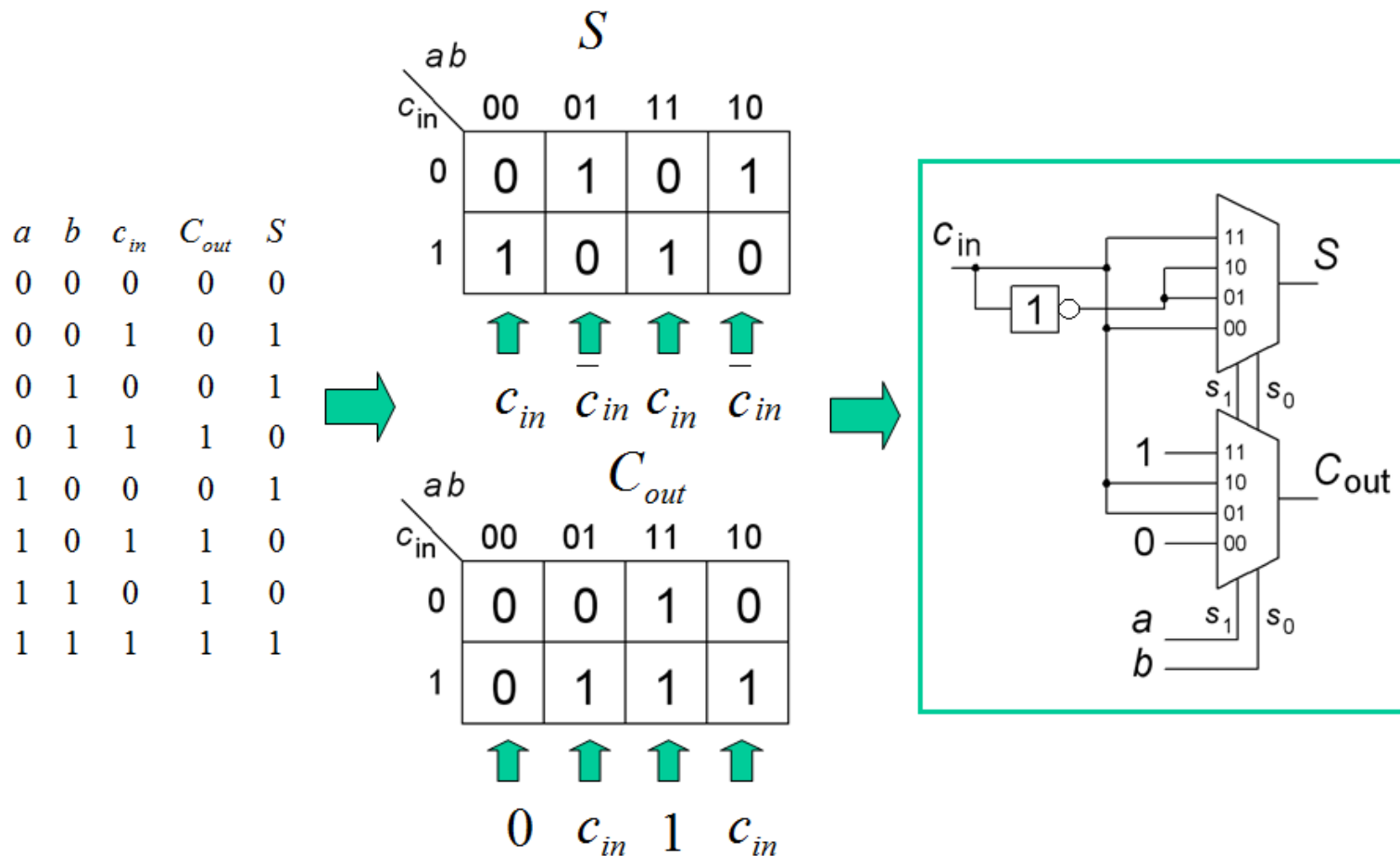


?: Part A2 (5p) task 10.

 



- A coffee machine has two input signals: **coin** from the coin slot to indicate that a coin passed a photocell there and **full** from a user who observes the plastic cup to be filled. **Coin = 1** when the coin passed the photocell. **full = 1** when the cup is full.
- The coffee machine has two output signals: **drop_cup** to a unit containing plastic cups and **coffee** to a magnetic valve for filling the coffee. The cup unit drops a cup as soon as **drop_cup** becomes "1" and coffee is filled as long as **coffee = 1**.

?: Part A2 (5p) task 10.

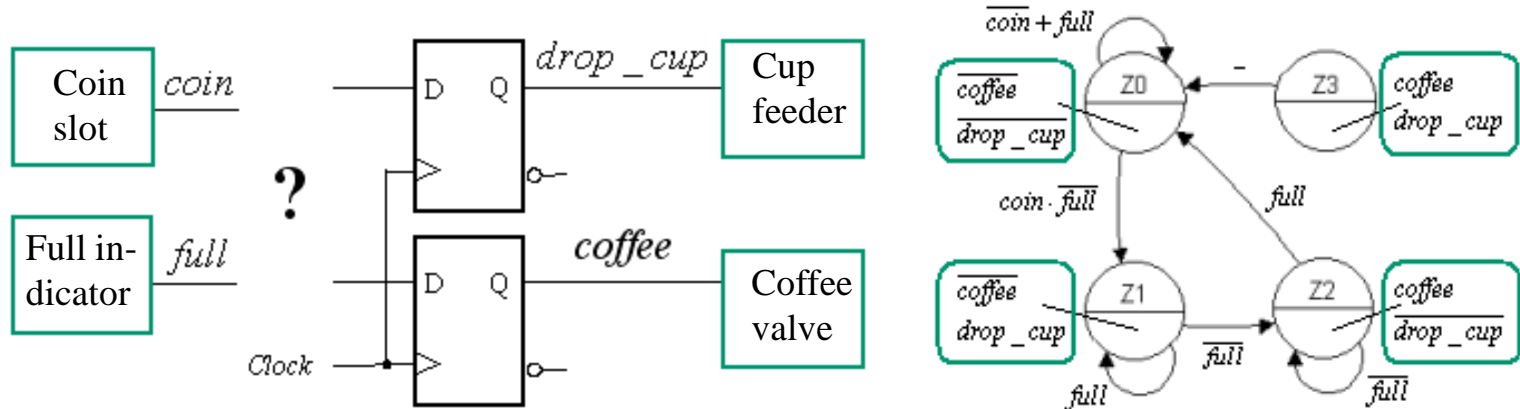

- Construct a synchronous Moore machine that follows the given state diagram.
- State assignments must control the outputs directly. No output decoder is used.
- Use positive edge-triggered D flip-flops and gates of your choice.
- Draw a complete circuit diagram.

!: Part A2 (5p) task 10.

  

full coin

		$i_1 i_0$					
$q_1 q_0$		00	01	11	10	$\overline{\text{coffee}}$	$\overline{\text{drop_cup}}$
Z0: 00		0	0	0	0	0	0
Z1: 01		1	0	0	1	0	1
Z3: 11		0	0	0	0	0	0
Z2: 10		1	0	0	0	0	0

$q_1^+ q_0^+$



q_1^+

$q_1 q_0$	$i_1 i_0$			
	00	01	11	10
00	0	0	0	0
01	1	1	0	0
11	0	0	0	0
10	1	1	0	0





q_0^+

$q_1 q_0$	$i_1 i_0$			
	00	01	11	10
00	0	1	0	0
01	0	0	1	1
11	0	0	0	0
10	0	0	0	0

$$q_1^+ = \overline{q_1} \overline{q_0} \overline{i_1} + q_1 \overline{q_0} \overline{i_1}$$

$$q_0^+ = \overline{q_1} \overline{q_0} \overline{i_1} i_0 + \overline{q_1} q_0 i_1$$

!: Part A2 (5p) task 10.

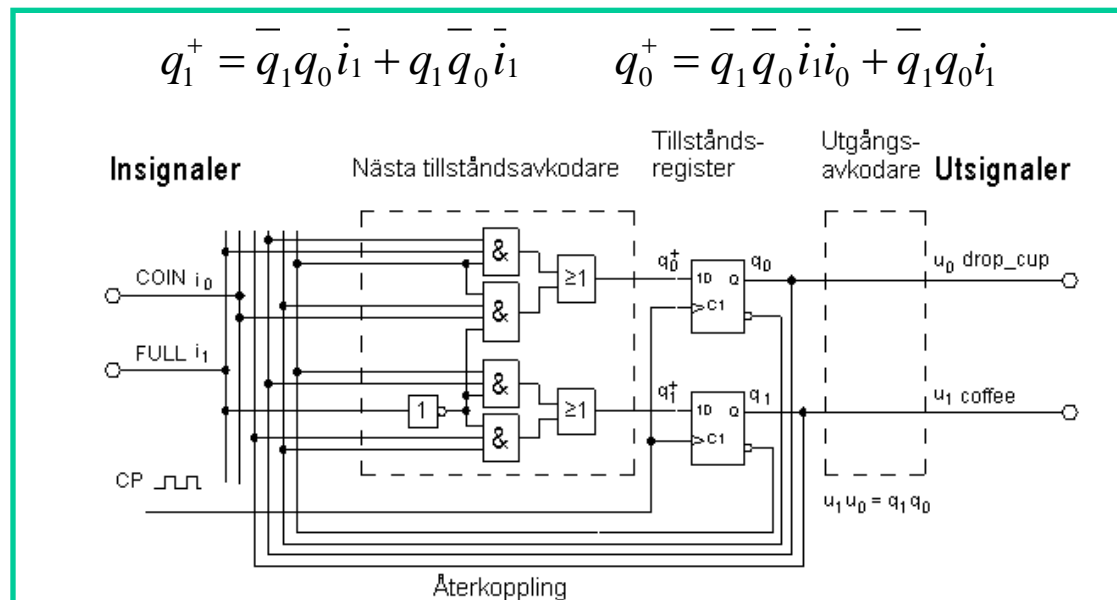 


Part B Design

- We mark part B (10p) if you get at least 11p at A1 + A2
- Tasks can always be solved in different ways. We mark as far as possible taking into account possible errors from previous steps
- Digital design is a creative process

?: Part B (5p) task 13.

Sequence Detector.

 


Obtain a minimal state table (show that it is minimal) for a synchronous sequential circuit of Moore-type with an input signal (w), and an output signal (z). The sequence net will generate the output 1 if it detects either input sequence 110 or 101, also overlapping sequences are valid (eg. 1101, is 110 followed by 101, will give output 00011). Derive the state diagram.

- a) (4p) Set up the circuit's **state table**, **show** that it is **minimal**, and draw the **state diagram**.
- b) (2p) Use Gray code to encode the states and set up the **encoded state table**. Obtain the **minimized expressions** for the **next state** and **output value**. No schematic of the circuit is needed to be drawn.

!: Part B (5p) task 13.

a) (4p)

	present $w = 0$	next $w = 1$	out z
A	A	B	0
B	E	C	0
C	D	C	0
D	A	F	1
E	A	F	0
F	E	C	1

 

Minimal number of states

$(ABCE)(DF)$
 $A_0 \rightarrow (\underline{A}BCE) \quad A_1 \rightarrow (A\underline{B}CE)$
 $B_0 \rightarrow (ABC\underline{E}) \quad B_1 \rightarrow (AB\underline{C}E)$
 $C_0 \rightarrow (\underline{D}F) \quad C_1 \rightarrow (AB\underline{C}E)$
 $E_0 \rightarrow (\underline{A}BCE) \quad E_1 \rightarrow (D\underline{F})$
 $(AB)(C)(DF)(E)$

$(AB)(C)(DF)(E)$
 $A_0 \rightarrow (\underline{A}B) \quad A_1 \rightarrow (A\underline{B})$
 $B_0 \rightarrow (E) \quad B_1 \rightarrow (C)$
 $(A)(B)(C)(DF)(E)$
 $D_0 \rightarrow (A) \quad D_1 \rightarrow (D\underline{F})$
 $F_0 \rightarrow (E) \quad F_1 \rightarrow (C)$
 $(A)(B)(C)(D)(E)(F)$

Was minimal
from the
beginning!

!: Part B (5p) task 13.

	present $w=0$	next $w=1$	out z
A	A	B	0
B	E	C	0
C	D	C	0
D	A	F	1
E	A	F	0
F	E	C	1

Gray code



	present $q_2 q_1 q_0$	next $q_2^+ q_1^+ q_0^+$ $w=0 \quad w=1$	out
A	000	000 001	0
B	001	110 011	0
C	011	010 011	0
D	010	000 111	1
E	110	000 111	0
F	111	110 011	1



$q_2^+ q_1^+ q_0^+ = f(q_2, q_1, q_0, w)$				
$q_1 q_0$	00	01	11	10
$w q_2$				
00	000	110	010	000
01	---	---	110	000
11	---	---	011	111
10	001	011	011	111

Kmap form

$$q_2^+ = f(q_2, q_1, q_0, w)$$

$q_1 q_0$	00	01	11	10
$w q_2$				
00	0	1	0	0
01	-	-	1	0
11	-	-	0	1
10	0	0	0	1

$$q_2^+ = \bar{q}_1 q_0 + \bar{w} q_2 + q_1 \bar{q}_0$$

$$q_1^+ = f(q_2, q_1, q_0, w)$$

$q_1 q_0$	00	01	11	10
$w q_2$				
00	0	1	1	0
01	-	-	1	0
11	-	-	1	1
10	0	1	1	1


$$q_1^+ = q_0 + w q_1$$

$$q_0^+ = f(q_2, q_1, q_0, w)$$

$q_1 q_0$	00	01	11	10
$w q_2$				
00	0	0	0	0
01	-	-	0	0
11	-	-	1	1
10	1	1	1	1



$$q_0^+ = w$$

?: Part B (5p) task 12.

 

- In order to study the I²C data transfer we want to construct a Moore-equivalent asynchronous sequential circuit which gives output signal $busy = 1$ during the time from the start signal to the stop signal. When no data communication occurs $busy = 0$

!: Part B (5p) task 12.

  


- In a state *a* we "wait" for the start (*b*), therefore the input signal 10 is impossible (marked with *). The protocol prohibits the alteration of data *SDA* when *SCL* is **high**. Therefore, the input signal 01 is impossible in state *e* (marked with *). This gives two additional don't care positions in the table.

	<i>SDA SCL</i>				
	00	01	11	10	<i>q</i>
<i>a</i>	–	<i>b</i>	<i>a</i>	*	0
<i>b</i>	<i>c</i>	<i>b</i>	<i>a</i>	–	1
<i>c</i>	<i>c</i>	<i>b</i>	–	<i>d</i>	1
<i>d</i>	<i>c</i>	–	<i>e</i>	<i>d</i>	1
<i>e</i>	–	*	<i>e</i>	<i>d</i>	1

- One see immediately which states can be merged.



!: Del B (5p) uppg 12.

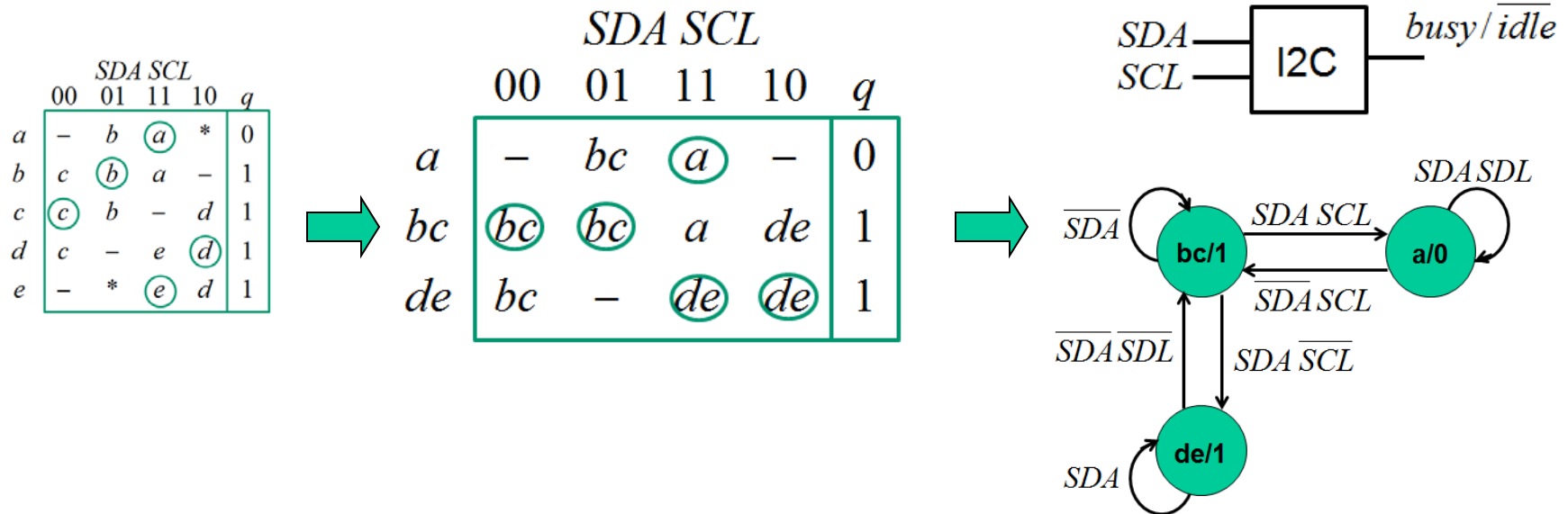

- We can use Gray code for state assignment: $a = 00$, $bc = 01$, $de = 11$. The unused state 01 can have any next state except 01.

!: Del B (5p) uppg 12.

	SDA SCL				
	00	01	11	10	q
a	–	bc	a	–	0
bc	bc	bc	a	de	1
de	bc	–	de	de	1

  

	SDA SCL				
$q_1 q_0$	00	01	11	10	$busy$
00	–	01	00	–	0
01	01	01	00	11	1
11	01	–	11	11	1
10	$\neq 10$	$\neq 10$	$\neq 10$	$\neq 10$	–

$q_1^+ q_0^+$

$busy =$
 $= q_0$

	SDA SCL				
$q_1 q_0$	00	01	11	10	
00	–	0	0	–	
01	0	0	0	1	
11	0	–	1	1	
10	–	–	–	–	

$q_1^+ = SDA(\overline{SCL} + q_1)$

	SDA SCL				
$q_1 q_0$	00	01	11	10	
00	–	1	0	–	
01	1	1	0	1	
11	1	–	1	1	
10	–	–	–	–	

$q_0^+ = (\overline{SDA} + \overline{SCL} + q_1)$

- Note that the resulting implementation is hazard-free because all adjacent 1's are covered by the same implicant.

Good Luck!