

Hands-on

Lectures 1-13

Masoumeh (Azin) Ebrahimi

## Lecture 1: Hands-on

Binary to Decimal:

$$(1011010)_2 = ( \quad )_{10}$$

Octal to Decimal:

$$(567)_8 = ( \quad )_{10}$$

Binary to Octal:

$$(1011010)_2 = ( \quad )_8$$

Hexadecimal to Decimal:

$$(1AE)_{16} = ( \quad )_{10}$$

Binary to Hexadecimal:


$$(1011010)_2 = ( \quad )_{16}$$

Decimal to Binary

$$(35)_{10} = ( \quad )_2$$
 
## Lecture 2: Hands-on


Fill the truth table based on the given circuit:



$f =$

| $x_1$ | $x_2$ | $f(x_1, x_2)$ |
|-------|-------|---------------|
| 0     | 0     |               |
| 0     | 1     |               |
| 1     | 0     |               |
| 1     | 1     |               |

 Fill the truth table based on the given circuit:



$f =$



| $x_1$ | $x_2$ | $f(x_1, x_2)$ |
|-------|-------|---------------|
| 0     | 0     |               |
| 0     | 1     |               |
| 1     | 0     |               |
| 1     | 1     |               |

Draw the logic circuit for the following truth table:

| $x_1$ | $x_2$ | $f(x_1, x_2)$ |
|-------|-------|---------------|
| 0     | 0     | 1             |
| 0     | 1     | 1             |
| 1     | 0     | 0             |
| 1     | 1     | 1             |

Show that consensus property holds using Venn diagram:
  
$$x \cdot y + y \cdot z + \bar{x} \cdot z = x \cdot y + \bar{x} \cdot z$$




Write the function using minterms and maxterms.

| $x_1$ | $x_2$ | $x_3$ | $f$ |
|-------|-------|-------|-----|
| 0     | 0     | 0     | 0   |
| 0     | 0     | 1     | 1   |
| 0     | 1     | 0     | 1   |
| 0     | 1     | 1     | 0   |
| 1     | 0     | 0     | 1   |
| 1     | 0     | 1     | 0   |
| 1     | 1     | 0     | 0   |
| 1     | 1     | 1     | 1   |


Draw the logic circuit.
 
## Lecture 3: Hands-on

What kind of function the following CMOS circuit implements?



 Implement the function  $f = x_1x_2 + \overline{x_2}x_3$



## Lecture 4: Hands-on

Find the minimum number of groups that cover all “1”. Groups should be in their biggest size.

|   |   | bc |    |    |    |
|---|---|----|----|----|----|
|   |   | 00 | 01 | 11 | 10 |
| a | 0 | 1  |    | 1  | 1  |
|   | 1 |    | 1  | 1  |    |

Find the minimum cost implementation for the following K-map:

|    |    | ab |    |    |    |
|----|----|----|----|----|----|
|    |    | 00 | 01 | 11 | 10 |
| cd | 00 | 0  | 0  | 0  | 0  |
|    | 01 | 0  | 1  | 1  | 0  |
|    | 11 | 1  | 1  | 1  | 1  |
|    | 10 | 0  | 0  | 1  | 0  |

Write the logic function of  $f_0$  and  $f_1$ :

|          |    | $f_0$    |    |    |    |
|----------|----|----------|----|----|----|
|          |    | $x_1x_0$ |    |    |    |
| $x_3x_2$ | 00 | 00       | 01 | 11 | 10 |
|          | 00 | 1        | 0  | 1  | 1  |
|          | 01 | 0        | 0  | 0  | 1  |
|          | 11 | 0        | 0  | 0  | 1  |
|          | 10 | 1        | 0  | 1  | 1  |

|          |    | $f_1$    |    |    |    |
|----------|----|----------|----|----|----|
|          |    | $x_1x_0$ |    |    |    |
| $x_3x_2$ | 00 | 00       | 01 | 11 | 10 |
|          | 00 | 1        | 0  | 1  | 1  |
|          | 01 | 0        | 0  | 0  | 1  |
|          | 11 | 1        | 0  | 0  | 1  |
|          | 10 | 1        | 0  | 1  | 1  |

Find the minimized function:

| $x_3x_2 \backslash x_1x_0$ | 00 | 01 | 11 | 10 |
|----------------------------|----|----|----|----|
| 00                         | 1  | 1  | 1  | 1  |
| 01                         | 1  | 0  | 1  | 1  |
| 11                         | 1  | 1  | 1  | 1  |
| 10                         | 1  | 1  | 1  | 1  |

## Lecture 5: Hands-on

Represent -10 in 2's complement scheme when the number of bits is 5.

Represent -10 in 2's complement scheme when the number of bits is 8.

Find the 2's complement of 110010 in two ways:


- 1) Complement each bit, then add 1:
- 2) Start from the right-hand side, then copy all the bits that are 0 and the first bit that is 1. Finally complement all other bits

Perform subtractions in the 2's complement scheme:

$$\begin{array}{r} (+5) \\ - (-2) \\ \hline (+7) \end{array}$$

$$\begin{array}{r} (-5) \\ - (-2) \\ \hline (-3) \end{array}$$

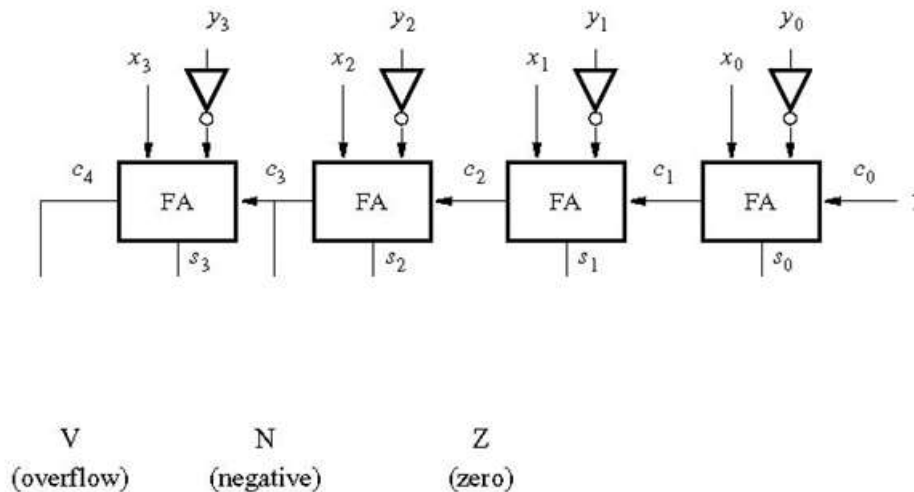How to recognize overflow, negative numbers and zero values in the following circuit? Make the connections.





## Lecture 6: Hands-on

Multiply -5 by +2 in binary by first converting -5 to the positive number and then keeping track of the result's sign.

Multiply  $13 * 8$  in binary.

Divide 1011 by 10 (binary).


Multiply 010100 by 4:

Divide 010100 by 4:

## Lecture 7: Hands-on


How to connect the inputs of the MUX in order to implement an inverter?

Desired function:  $z = \bar{x}$

 

How to connect the inputs of the MUX in order to implement an AND gate?

Desired function:  $z = xy$

 


Connect the inputs of the MUX in order to implement OR and XOR gates.




Connect the inputs of the MUX in order to implement the following function:  $f = \bar{z}\bar{x} + \bar{x}y + zy$

|   | xy |    |    |    |
|---|----|----|----|----|
| z | 00 | 01 | 11 | 10 |
| 0 | 1  | 1  | 0  | 0  |
| 1 | 0  | 1  | 1  | 0  |


 


Connect the inputs of the MUX in order to implement the following function in the table:

| x \ yz | 00 | 01 | 11 | 10 |
|--------|----|----|----|----|
| 0      | 0  | 1  | 0  | 1  |
| 1      | 1  | 0  | 1  | 0  |

 

 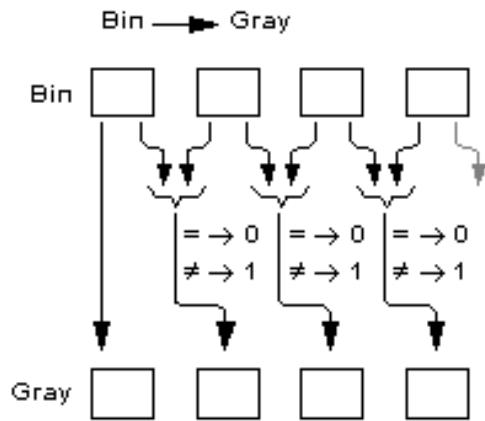Convert 0101 from binary to gray code. Also convert 0010 from gray code to binary code.




## Lecture 8: Hands-on

Fill the characteristic table of the following SR-latch when

$S=0$  and  $R=1$

$S=1$  and  $R=0$

 If you have enough time then try the case when  $S=1$  and  $R=1$ .




| S | R | $Q_a$ | $Q_b$ |
|---|---|-------|-------|
| 0 | 0 | 1     | 1     |
| 0 | 1 |       |       |
| 1 | 0 |       |       |
| 1 | 1 |       |       |



Prohibited input combination

What is the value of  $Q(t+1)$  when  $\text{clk}=1$  and  $D=1$ ?

 
What is the value of  $Q(t+1)$  when  $\text{clk}=0$ ?



  Complete the timing diagram for the following Latch, Positive edge triggered flipflop, and Negative edge triggered flipflop




Complete the timing diagram:

 
 
## Lecture 9: Hands-on

Assuming the following state diagram to detect two or more consecutive ones, we want to synthesis the circuit. Let's assume that A, B and C are coded as: A=00; B=01, and C=11.




Given the above state diagram, fill the state table and state-assigned table:

| Present state | Next state |         | Output<br>$z$ |
|---------------|------------|---------|---------------|
|               | $w = 0$    | $w = 1$ |               |
| A             |            |         | 0             |
| B             |            |         | 0             |
| C             |            |         | 1             |

A  
B  
C

| Present state<br>$y_2y_1$ | Next state |          | Output<br>$z$ |
|---------------------------|------------|----------|---------------|
|                           | $w = 0$    | $w = 1$  |               |
|                           | $Y_2Y_1$   | $Y_2Y_1$ |               |
| 00                        |            |          |               |
| 01                        |            |          |               |
| 11                        |            |          |               |
| 10                        |            |          |               |

 
Extract the function of  $Y_2$ ,  $Y_1$  and  $z$  and based on these functions, synthesis the circuit.



## Lecture 10: Hands-on
 
### Synthesizing the circuit and state minimization.

From the state diagram fill the state table.



| Present state | Next state |       | Output z |
|---------------|------------|-------|----------|
|               | w = 0      | w = 1 |          |
| A             | B          | C     | 1        |
|               |            |       |          |
|               |            |       |          |
|               |            |       |          |
|               |            |       |          |
|               |            |       |          |

Partition the states with different outputs and find the 0- and 1- successor of each state.

**P1= (ABCDEFGG)**

**P2=( ) ( )**

**First block**

**0-successor:**

**1-successor:**

**Second block**

**0-successor:**

**1-successor:**

**P3 = (ABD) (CEG) (F)**

**P4 = (AD) (B) (CEG) (F)**


**P5 = P4 = (AD) (B) (CEG) (F)**

Fill the final state table and draw the new state diagram.


| Present state | Next State |       | Output z |
|---------------|------------|-------|----------|
|               | w = 0      | w = 1 |          |
| A             | B          | C     | 1        |
|               |            |       |          |
|               |            |       |          |
|               |            |       |          |
|               |            |       |          |
|               |            |       |          |
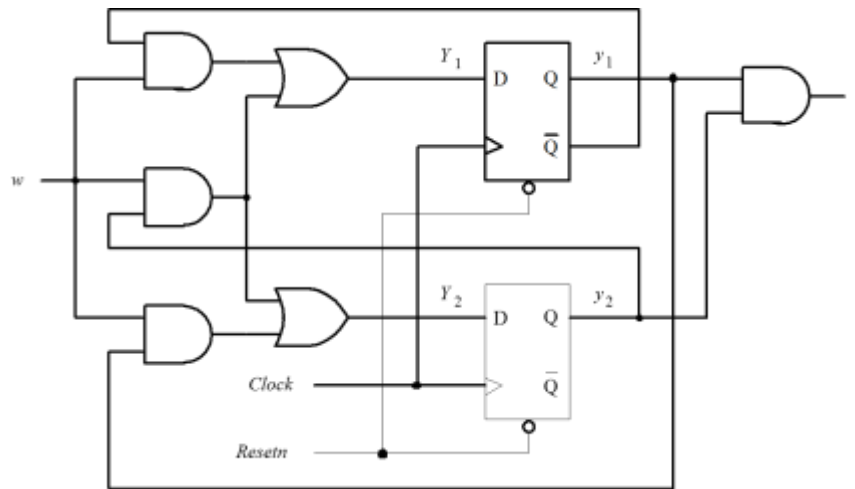
## Analysis of synchronous sequential circuits:

Get expressions for next state decoder (Y1 and Y2) and output decoder (z).



 Fill in the Karnaugh maps and merge the Karnaugh maps into a coded state table:



Fill the state-assigned and state tables:

| State-assigned table      |            |          |               |
|---------------------------|------------|----------|---------------|
| Present state<br>$y_2y_1$ | Next State |          | Output<br>$z$ |
|                           | $w = 0$    | $w = 1$  |               |
|                           | $Y_2Y_1$   | $Y_2Y_1$ |               |
| 00                        |            |          |               |
| 01                        |            |          |               |
| 10                        |            |          |               |
| 11                        |            |          |               |


A:"00" B:"01" C:"10" D:"11"

| State table   |            |         |               |
|---------------|------------|---------|---------------|
| Present state | Next state |         | Output<br>$z$ |
|               | $w = 0$    | $w = 1$ |               |
|               |            |         |               |
|               |            |         |               |
|               |            |         |               |
|               |            |         |               |

Draw the state diagram and realize the function.



## Lecture 11: Hands-on

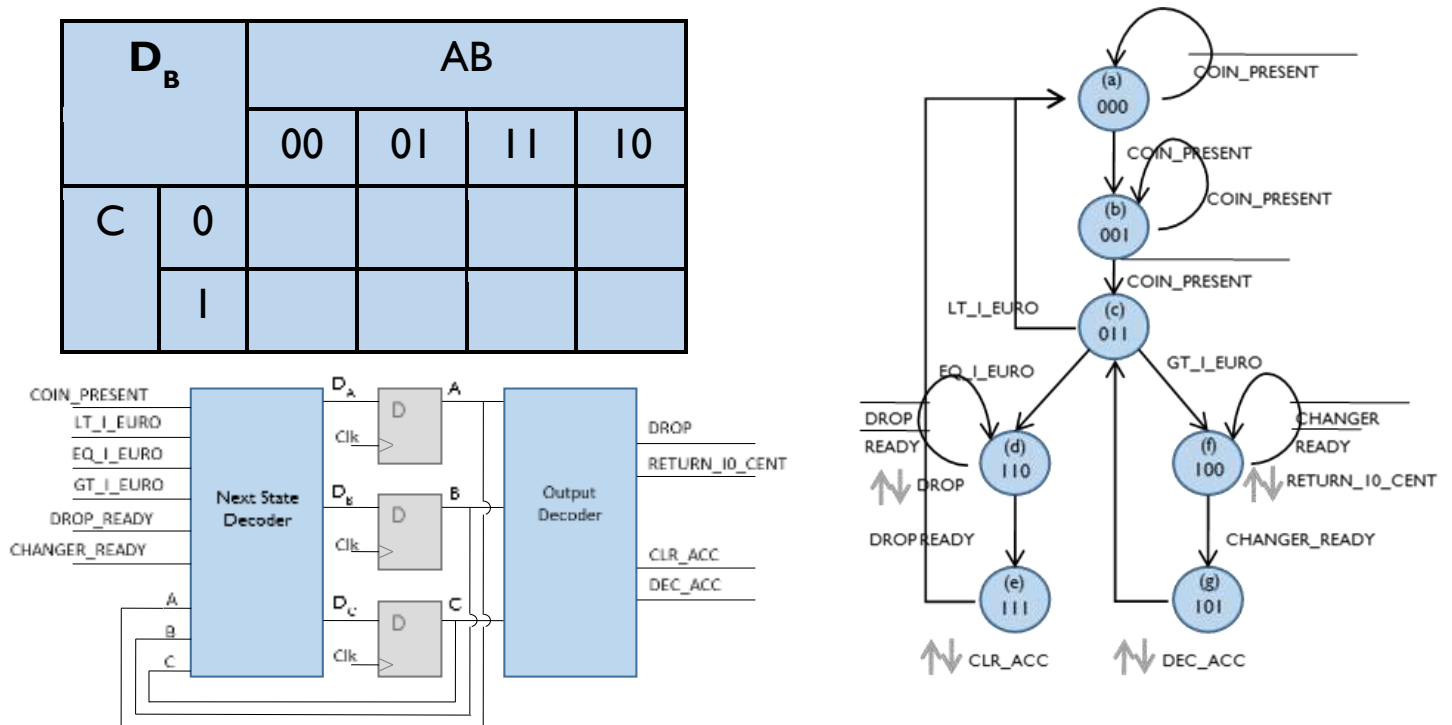

```

LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;

```

```

ENTITY Vending_Machine IS
  PORT (
    -- Inputs
    coin_present : IN std_logic;

```

```

    -- Outputs
    dec_acc      : OUT std_logic;

  );
END Vending_Machine;

```

---

```

ARCHITECTURE Moore_FSM OF Vending_Machine IS

```

```

  TYPE state_type IS (a, b, c, d, e, f, g);
  SIGNAL current_state, next_state: state_type;

BEGIN -- Moore_FSM

```

```


NEXTSTATEDECODER: PROCESS (current_state, coin_present, gt_1_euro, eq_1_euro,
lt_1_euro, drop_ready, changer_ready)

```

```

BEGIN  -- PROCESS NEXT_STATE
CASE current_state IS
  WHEN a => IF coin_present = '1' THEN
    next_state <= b;
  ELSE
    next_state <= a;
  END IF;
  WHEN b => IF coin_present = '0' THEN
    next_state <= c;
  ELSE
    next_state <= b;
  END IF;

```

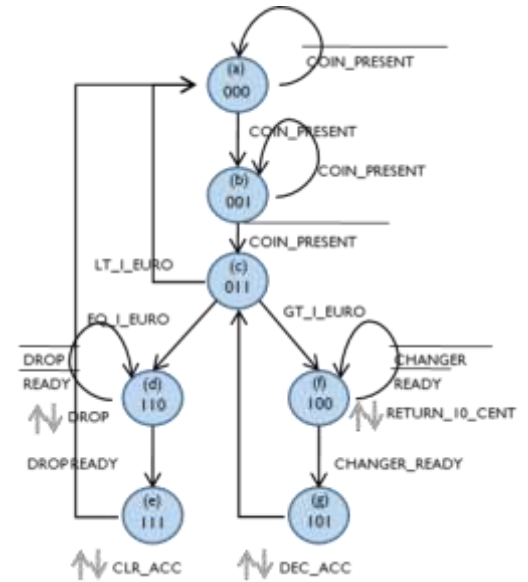

```

  WHEN OTHERS => next_state <= a;
END CASE;
END PROCESS NEXTSTATE;

```

```

OUTPUTDECODER: PROCESS (current_state)
BEGIN  -- PROCESS OUTPUT
  drop <= '0';

```

```

CASE current_state IS
  WHEN d => drop <= '1';

  WHEN OTHERS => NULL;
END CASE;
END PROCESS OUTPUT;

```

```

CLOCK: PROCESS (clk, reset_n)
BEGIN  -- PROCESS CLOCK
  IF reset_n = '0' THEN -- asynchronous reset (active low)
    current_state <= a;
  ELSIF clk'event AND clk = '1' THEN -- rising clock edge
    current_state <= next_state;
  END IF;
END PROCESS CLOCK;

```

```

END Moore_FSM;

```

# Lecture 12: Hands-on

## State reduction

## Equivalence classes

- Outputs must have the same value
- Stable states must be at the same positions
- Don't cares for next state must be in the same positions

## Merging equivalence groups

- Successors must be in the same classes

### Primitive flow table

| Pres<br>state | Next State |     |     |     | Q |
|---------------|------------|-----|-----|-----|---|
|               | X=00       | 01  | 10  | 11  |   |
| A             | (A)        | F   | C   | -   | 0 |
| B             | A          | (B) | -   | H   | 1 |
| C             | G          | -   | (C) | -   | 0 |
| D             | -          | F   | -   | (D) | 1 |
| E             | G          | -   | (E) | D   | 1 |
| F             | -          | (F) | -   | K   | 0 |
| G             | (G)        | B   | J   | -   | 0 |
| H             | -          | L   | E   | (H) | 1 |
| J             | G          | -   | (J) | -   | 0 |
| K             | -          | B   | E   | (K) | 1 |
| L             | A          | (L) | -   | K   | 1 |


### Reduced flow table

| Pres<br>state | Next State |    |    |    | Q |
|---------------|------------|----|----|----|---|
|               | X=00       | 01 | 10 | 11 |   |
|               |            |    |    |    |   |

## Finding compatible states and merging them

- both  $S_i$  and  $S_j$  have the same successor, or
- both  $S_i$  and  $S_j$  are stable, or
- the successor of  $S_i$  or  $S_j$ , or both, is unspecified

Moreover, both  $S_i$  and  $S_j$  must have the same output whenever specified

 
[illegible]

# Lecture 13: Hands-on
 
## Static Hazard

$$f = x_1x_2 + \bar{x}_1x_3$$

What is the value of f under the input of  $x_3x_2x_1=111$  and  $x_3x_2x_1=110$ . Complete the timing diagram for the following circuit by considering a delay for each gate.



## Dynamic Hazard

$$f = x_1 \bar{x}_2 + \bar{x}_3 x_4 + x_1 x_4$$

What is the value of f under the input of  $x_4x_3x_2x_1=1110$  and  $x_4x_3x_2x_1=1111$ . Complete the timing diagram for the following circuit by considering a delay for each gate.

