



**KTH Informations- och
kommunikationsteknik**

IE1204 Digital Design


L2: Logic gates and circuits, Boolean Algebra

Masoumeh (Azin) Ebrahimi

KTH/ICT




mebr@kth.se

IE1204 Digital Design

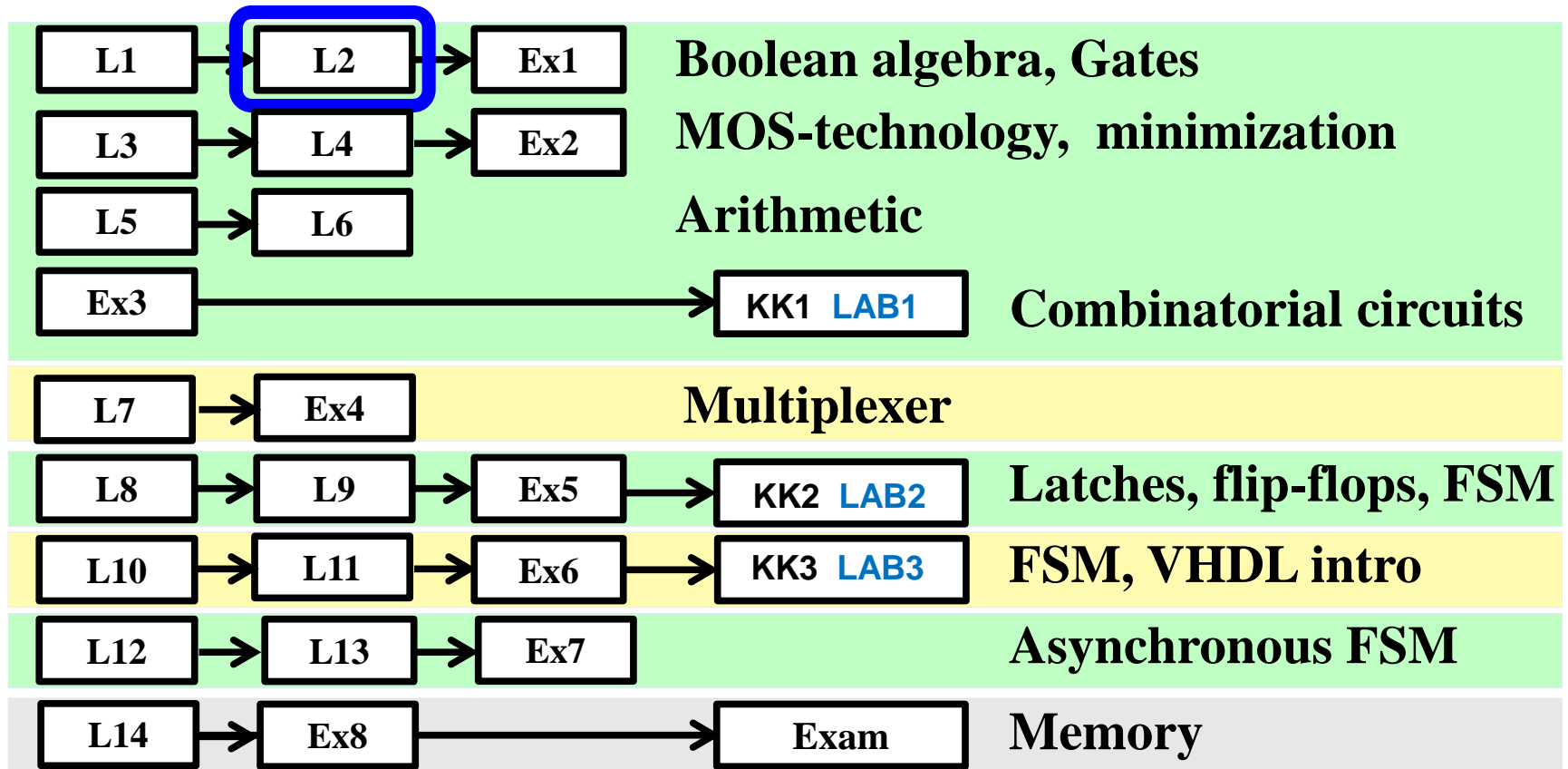


Switch

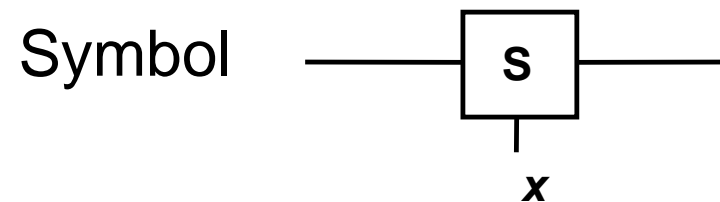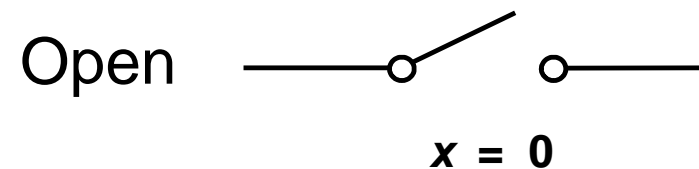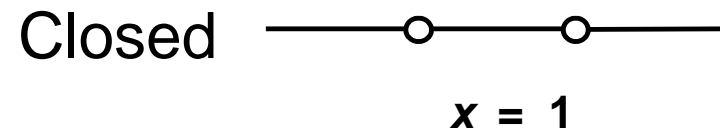- A switch has two positions
 - Closed/On
 - Open/Off



Implementation of logic functions

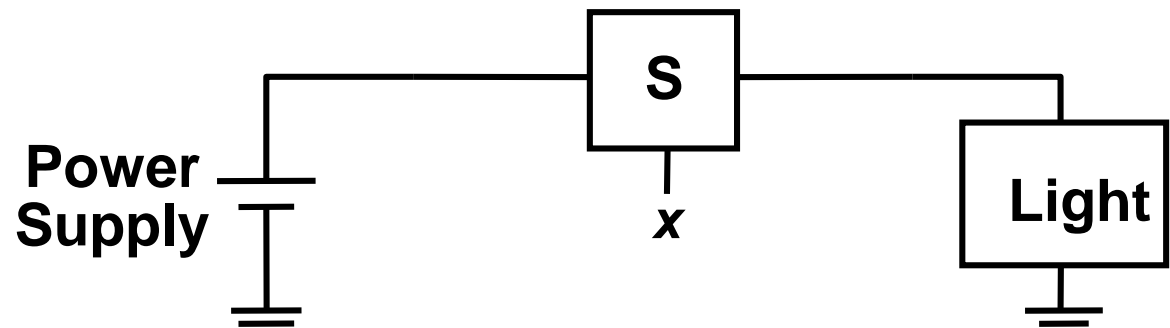- A switch can be used to implement logic functions




$L(x)$ is a logic function
 x is a logic variable

$$L(x) = \begin{cases} 0 & \text{Light Off} \\ 1 & \text{Light On} \end{cases}$$

Operation AND

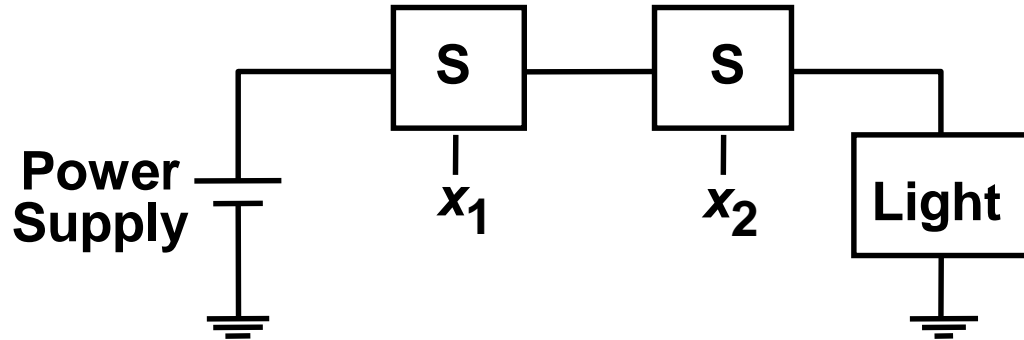
- The AND operation (\cdot) is achieved by switches that are connected in series



$$L(x) = x_1 \cdot x_2$$

Operation OR

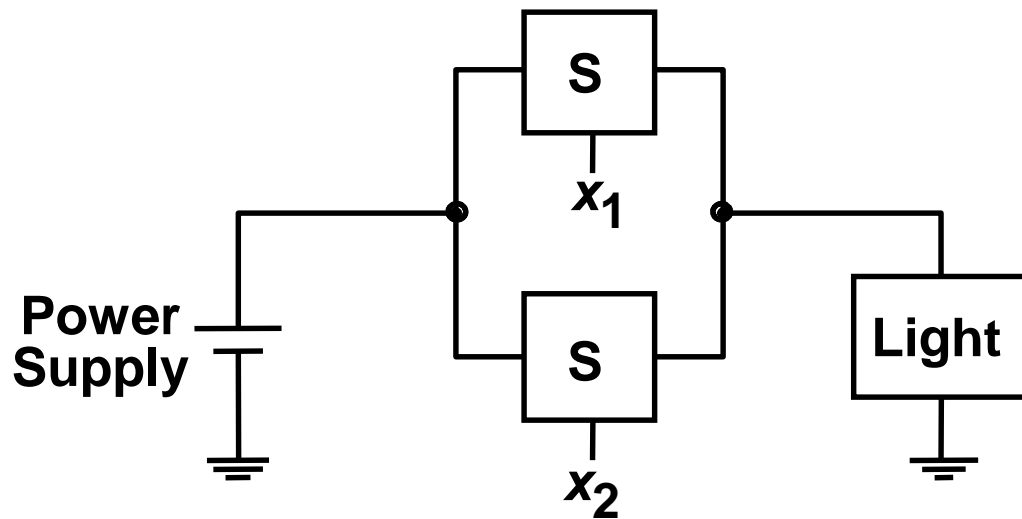
- The OR operation (+) is achieved by switches connected in parallel



$$L(x) = x_1 + x_2$$

Operation NOT

- NOT function inverts the logic value

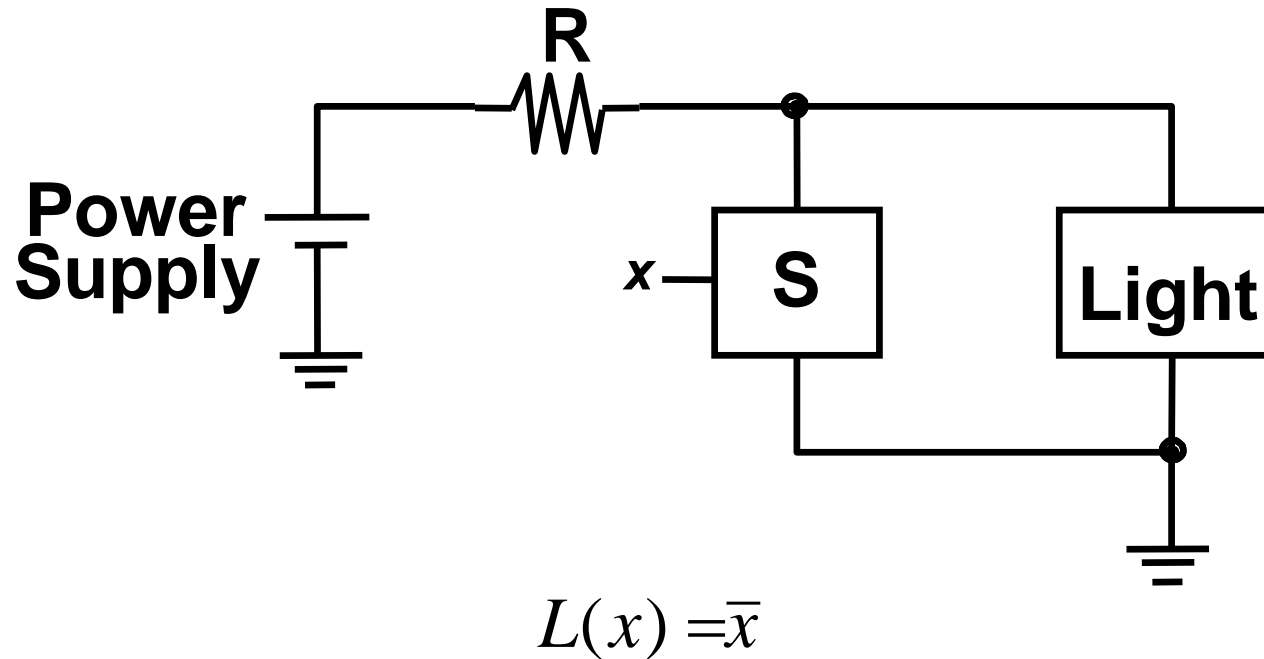

Truth Table

- A logic function can also be described by a *truth table*

x_1	x_2	$x_1 \cdot x_2$	$x_1 + x_2$
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	1

AND

OR

1 stands for true
0 stands for false


Logic gates

AND gate


A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

$$Y = A \cdot B$$

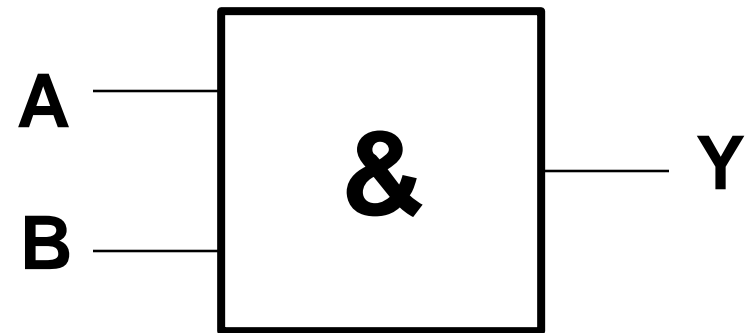IEC symbol
(International Electrotechnical Commission)



Traditional (American)
Symbol

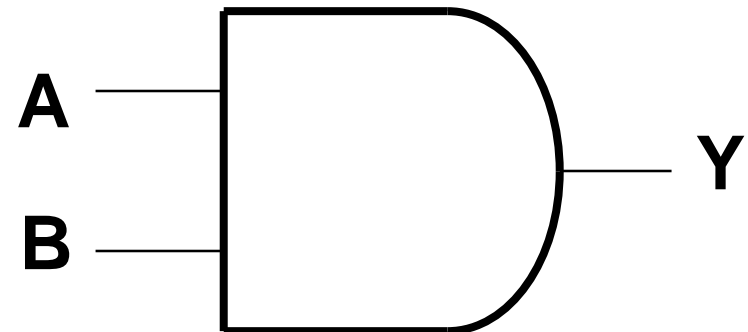


Logic gates

OR gate


A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

$$Y = A + B$$

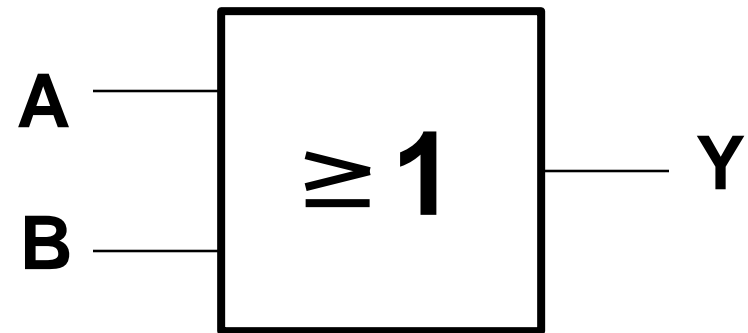IEC symbol
(International Electrotechnical Commission)



Traditional (American)
Symbol

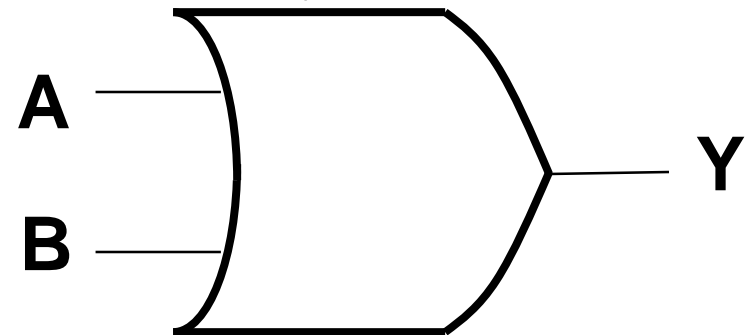


Logic gates

Inverter (NOT gate)


A	Y
0	1
1	0

$$Y = \bar{A}$$

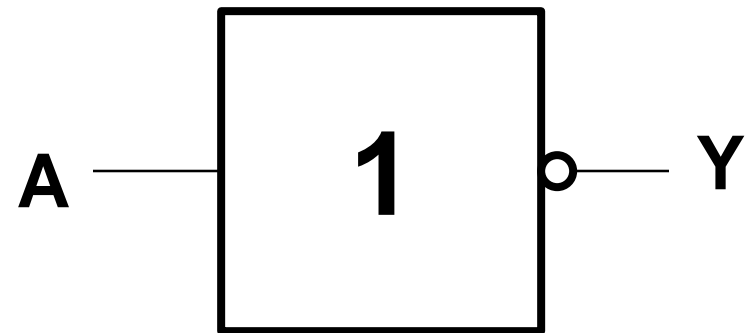
IEC symbol
(International Electrotechnical Commission)



Traditional (American)
Symbol

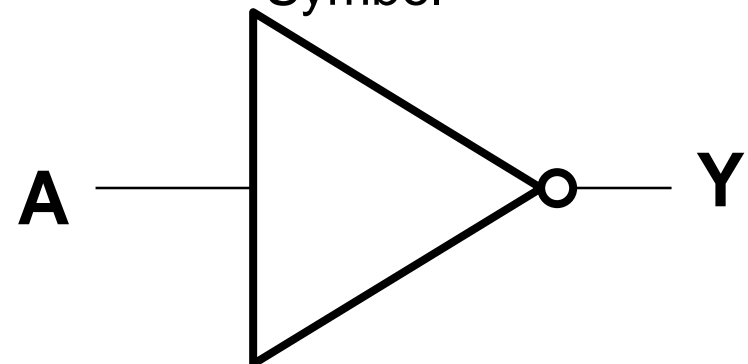

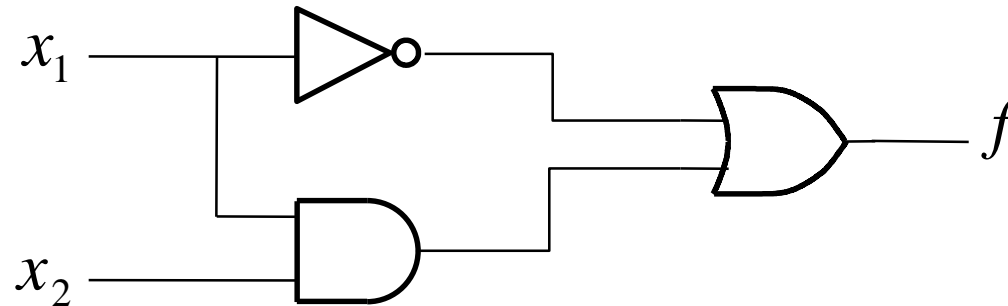
Which function is implemented by this logic circuit?



x_1	x_2	$f(x_1, x_2)$
0	0	
0	1	
1	0	
1	1	




Truth Table


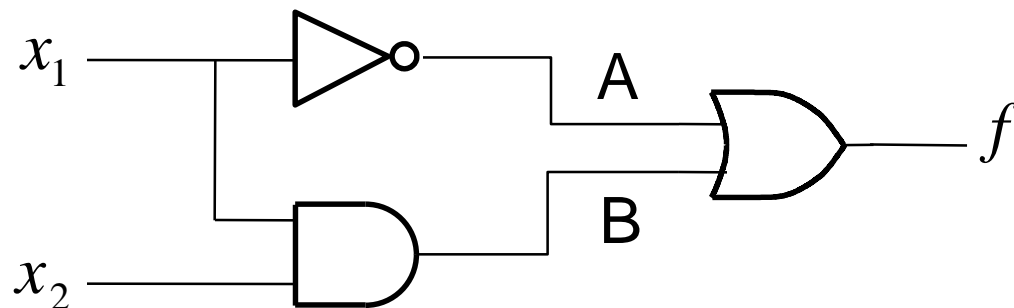


x_1	x_2	$f(x_1, x_2)$	A	B
0	0	1	1	0
0	1	1	1	0
1	0	0	0	0
1	1	1	0	1

Timing Chart

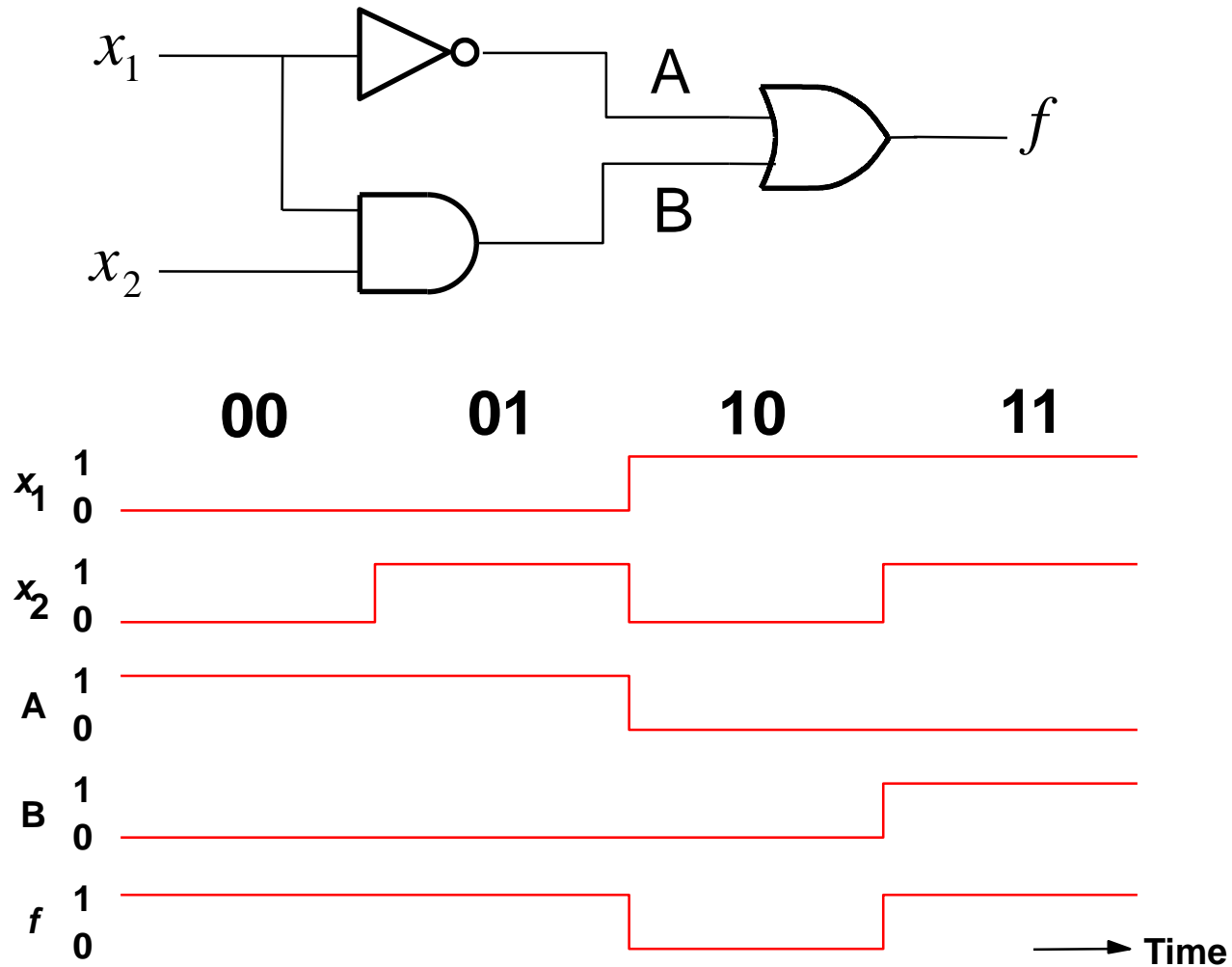

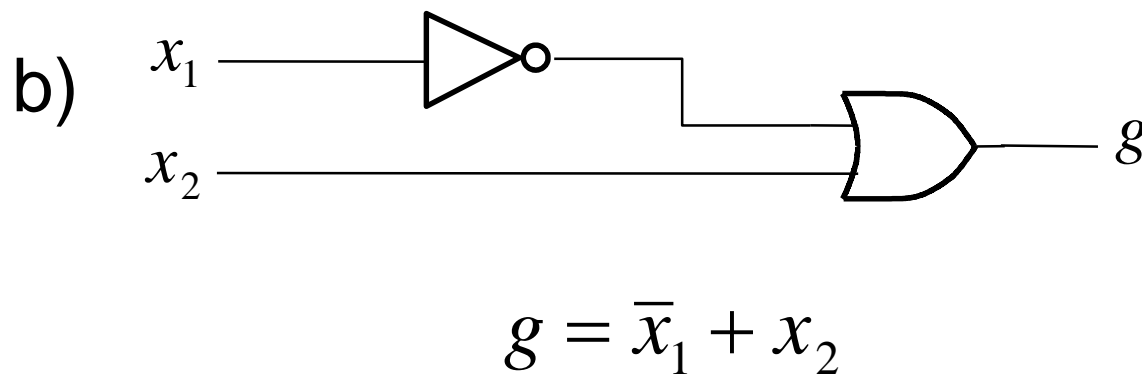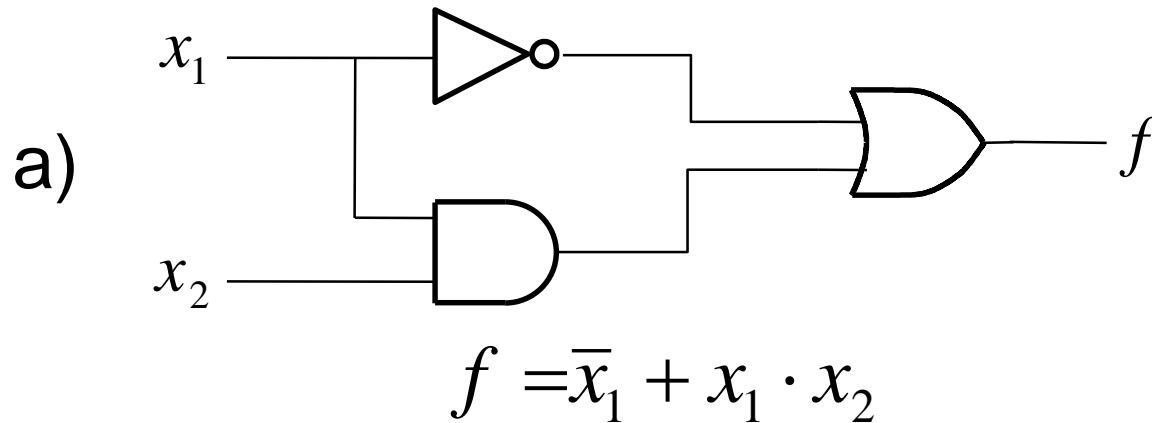Different logic circuits can implement the same function



x_1	x_2	$f(x_1, x_2)$
0	0	1
0	1	1
1	0	0
1	1	1

Boolean algebra


- Since several logic circuits can implement the same function, we want to find the most cost-effective implementation
- Logic circuits can be very large
- A mathematical base is needed so that the optimization of logic circuits can be performed using computers

Axioms of Boolean algebra


Axiomer	
(1a) $0 \cdot 0 = 0$	(1b) $1 + 1 = 1$
(2a) $1 \cdot 1 = 1$	(2b) $0 + 0 = 0$
(3a) $0 \cdot 1 = 1 \cdot 0 = 0$	(3b) $1 + 0 = 0 + 1 = 1$
(4a) If $x = 0$, then $\bar{x} = 1$	(4b) If $x = 1$, then $\bar{x} = 0$

Venn Diagrams

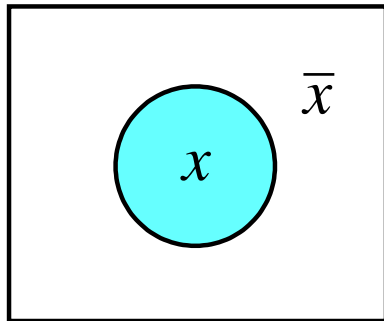
- Venn diagrams can be used to illustrate the logic operations



x

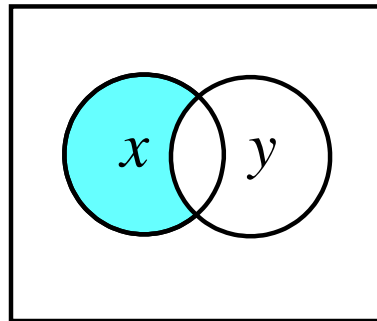


$x \cdot \bar{y}$

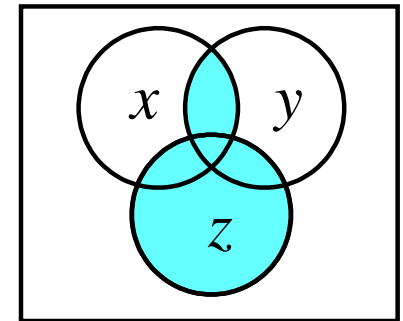

$x \cdot y + z$

Boolean algebra

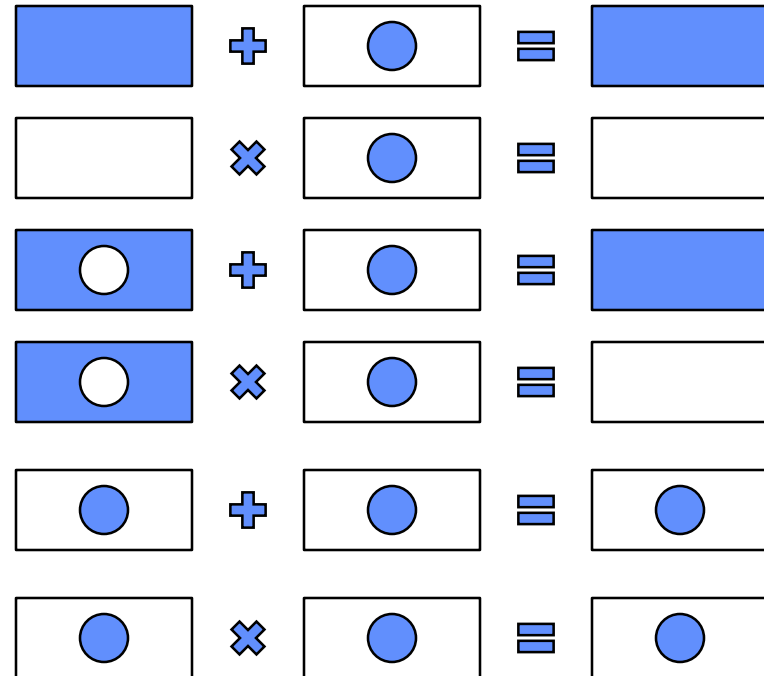- $1 + A = 1$
- $0 \cdot A = 0$
- $\bar{A} + A = 1$
- $\bar{A} \cdot A = 0$
- $A + A = A$
- $A \cdot A = A$



Other properties of Boolean algebra with single variable

- Using the axioms, we can derive new properties

Räknelagar	
(5a) $x \cdot 0 = 0$	(5b) $x + 1 = 1$
(6a) $x \cdot 1 = x$	(6b) $x + 0 = x$
(7a) $x \cdot x = x$	(7b) $x + x = x$
(8a) $x \cdot \bar{x} = 0$	(8b) $x + \bar{x} = 1$
(9a) $\overline{\bar{x}} = x$	

Duality principle

- If we have a valid Boolean expression, we can get another valid expression by changing
 - All 0s to 1s and all 1s to 0s
 - All ANDs to ORs and all ORs to ANDs

x_1	x_2	$x_1 \cdot x_2$	x_1	x_2	$x_1 + x_2$
0	0	0	1	1	1
0	1	0	1	0	1
1	0	0	0	1	1
1	1	1	0	0	0

Boolean algebra

properties with multiple variables

Räknelagar		
(10a) $x \cdot y = y \cdot x$	(10b) $x + y = y + x$	<i>kommutativ</i> <i>associativ</i> <i>distributiv</i> <i>absorption</i>
(11a) $x \cdot (y \cdot z) = (x \cdot y) \cdot z$	(11b) $x + (y + z) = (x + y) + z$	
(12a) $x \cdot (y + z) = x \cdot y + x \cdot z$	(12b) $x + y \cdot z = (x + y) \cdot (x + z)$	
(13a) $x + x \cdot y = x$	(13b) $x \cdot (x + y) = x$	
(14a) $x \cdot y + x \cdot \bar{y} = x$	(14b) $(x + y) \cdot (x + \bar{y}) = x$	<i>DeMorgan</i>
(15a) $\overline{x \cdot y} = \bar{x} + \bar{y}$	(15b) $\overline{x + y} = \bar{x} \cdot \bar{y}$	
(16a) $x + \bar{x} \cdot y = x + y$	(16b) $x \cdot (\bar{x} + y) = x \cdot y$	<i>consensus</i>
(17a) $x \cdot y + y \cdot z + \bar{x} \cdot z$ $= x \cdot y + \bar{x} \cdot z$	(17b) $(x + y) \cdot (y + z) \cdot (\bar{x} + z)$ $= (x + y) \cdot (\bar{x} + z)$	

Proof that consensus property holds

$$17a. \quad x \cdot y + y \cdot z + \bar{x} \cdot z = x \cdot y + \bar{x} \cdot z$$

$$x \cdot y + y \cdot z + \bar{x} \cdot z \quad (\text{left side})$$

$$= x \cdot y \cdot (z + \bar{z}) + (x + \bar{x}) \cdot y \cdot z + \bar{x} \cdot (y + \bar{y}) \cdot z$$

$$= \underbrace{x \cdot y \cdot z}_{\text{blue}} + x \cdot y \cdot \bar{z} + \underbrace{x \cdot y \cdot z}_{\text{blue}} + \underbrace{\bar{x} \cdot y \cdot z}_{\text{red}} + \underbrace{\bar{x} \cdot y \cdot z}_{\text{red}} + \bar{x} \cdot \bar{y} \cdot z$$

$$= x \cdot y \cdot z + x \cdot y \cdot \bar{z} + \bar{x} \cdot y \cdot z + \bar{x} \cdot \bar{y} \cdot z$$

$$= x \cdot y \cdot (z + \bar{z}) + \bar{x} \cdot z \cdot (y + \bar{y})$$

$$= x \cdot y + \bar{x} \cdot z \quad (= \text{right side})$$



Notation options

- Different books use different notations

\overline{x}	$x', !x, /x, \neg x$
<hr/>	
$x \cdot y$	$xy, x \wedge y$
<hr/>	
$x + y$	$x \vee y$

Analysis and synthesis

- Synthesis
 - Construction of a logic circuit that implements a given logic function
- Analysis
 - The derivation of the logic function for a given logic circuit

How can the following truth table be implemented by a logic circuit?

x_1	x_2	$f(x_1, x_2)$
0	0	1
0	1	1
1	0	0
1	1	1

How can the following truth table be implemented by a logic circuit?

x_1	x_2	$f(x_1, x_2)$
0	0	1
0	1	1
1	0	0
1	1	1


1. Write down the logic function:

$$f = \bar{x}_1 \bar{x}_2 + \bar{x}_1 x_2 + x_1 x_2$$

How can the following truth table be implemented by a logic circuit?

$$f = \bar{x}_1 \bar{x}_2 + \bar{x}_1 x_2 + x_1 x_2$$

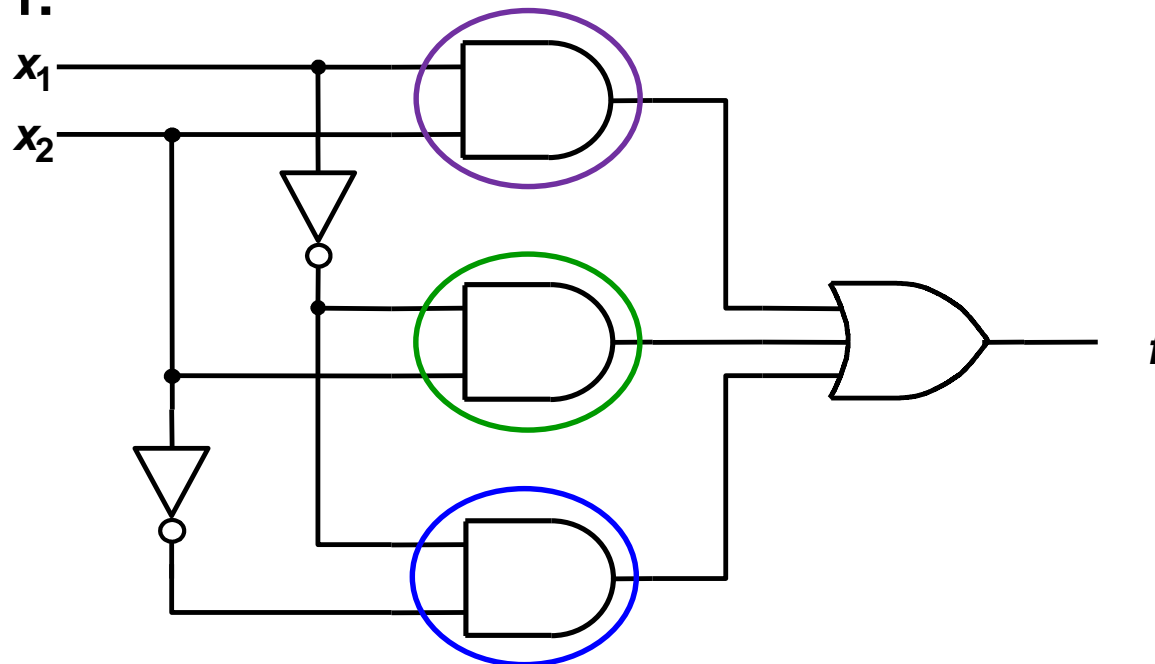2. Make a direct implementation of the logic function:



How can the following truth table be implemented by a logic circuit?


2. (Better) Minimize the logic function

$$\begin{aligned} f &= \bar{x}_1 \bar{x}_2 + \bar{x}_1 x_2 + x_1 x_2 \\ &= \bar{x}_1 \bar{x}_2 + \bar{x}_1 x_2 + \bar{x}_1 x_2 + x_1 x_2 && \text{Add redundant term } \bar{x}_1 x_2 \text{ (7b)} \\ &= \bar{x}_1 (\bar{x}_2 + x_2) + (\bar{x}_1 + x_1) x_2 && \text{Distributive rule (12a)} \\ &= \bar{x}_1 \cdot 1 + 1 \cdot x_2 && \text{(8b)} \\ &= \bar{x}_1 + x_2 \end{aligned}$$

How can the following truth table be implemented by a logic circuit?

3. Implement the minimized function

$$f = \bar{x}_1 + x_2$$

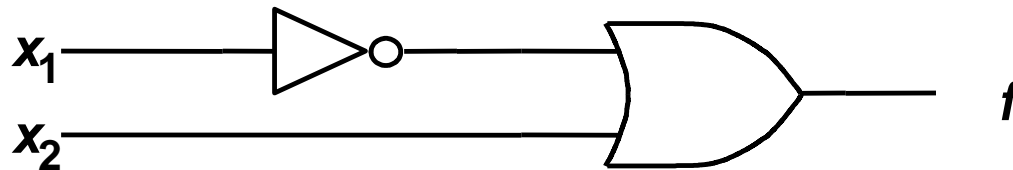

Much simpler implementation!

Discussion: Algebraic optimization

- Algebraic optimization of logic expressions can lead to efficient implementations
- But: For larger circuits, it can be very difficult to identify potential optimizations

We need a generic method that works for all logic circuits!

Minterms and Maxterms

- A **minterm** is a ***product*** term of a logic function in which *all* variables of the logic function are presented.
- A **maxterm** is a ***sum*** term for a logic function in which *all* variables of the logic function are presented.

Minterms and Maxterms

Row number	x_1	x_2	x_3	Minterm	Maxterm
0	0	0	0	$m_0 = \bar{x}_1 \bar{x}_2 \bar{x}_3$	$M_0 = x_1 + x_2 + x_3$
1	0	0	1	$m_1 = \bar{x}_1 \bar{x}_2 x_3$	$M_1 = x_1 + x_2 + \bar{x}_3$
2	0	1	0	$m_2 = \bar{x}_1 x_2 \bar{x}_3$	$M_2 = x_1 + \bar{x}_2 + x_3$
3	0	1	1	$m_3 = \bar{x}_1 x_2 x_3$	$M_3 = x_1 + \bar{x}_2 + \bar{x}_3$
4	1	0	0	$m_4 = x_1 \bar{x}_2 \bar{x}_3$	$M_4 = \bar{x}_1 + x_2 + x_3$
5	1	0	1	$m_5 = x_1 \bar{x}_2 x_3$	$M_5 = \bar{x}_1 + x_2 + \bar{x}_3$
6	1	1	0	$m_6 = x_1 x_2 \bar{x}_3$	$M_6 = \bar{x}_1 + \bar{x}_2 + x_3$
7	1	1	1	$m_7 = x_1 x_2 x_3$	$M_7 = \bar{x}_1 + \bar{x}_2 + \bar{x}_3$

Introduction to SOPs and POSs

- Describe the following logic function by a Boolean expression

Row number	x_1	x_2	x_3	$f(x_1, x_2, x_3)$
0	0	0	0	0
1	0	0	1	1
2	0	1	0	0
3	0	1	1	0
4	1	0	0	1
5	1	0	1	1
6	1	1	0	1
7	1	1	1	0

Sum-of-Products (SOPs)

Row number	x_1	x_2	x_3	$f(x_1, x_2, x_3)$
0	0	0	0	0
1	0	0	1	1 m_1
2	0	1	0	0
3	0	1	1	0
4	1	0	0	1 m_4
5	1	0	1	1 m_5
6	1	1	0	1 m_6
7	1	1	1	0

$$f = \bar{x}_1\bar{x}_2x_3 + x_1\bar{x}_2\bar{x}_3 + x_1\bar{x}_2x_3 + x_1x_2\bar{x}_3 = \sum m(1,4,5,6)$$

Sum-of-Products

- A ***sum-of-products*** is a logic expression which is obtained by adding minterms for which f equals to 1
 - Also called *disjunctive normal form (DNF)*

Product-of-Sums



Row number	x_1	x_2	x_3	$f(x_1, x_2, x_3)$
0	0	0	0	0 M_0
1	0	0	1	1
2	0	1	0	0 M_2
3	0	1	1	0 M_3
4	1	0	0	1
5	1	0	1	1
6	1	1	0	1
7	1	1	1	0 M_7

$$f = (x_1 + x_2 + x_3) \cdot (x_1 + \bar{x}_2 + x_3) \cdot (x_1 + \bar{x}_2 + \bar{x}_3) \cdot (\bar{x}_1 + \bar{x}_2 + \bar{x}_3) = \prod M(0,2,3,7)$$

Product-of-Sums

- A *product-of-sums* is a logic expression which is obtained by multiplying maxterms for which f equals to 0
 - Also called *conjunctive normal form (CNF)*

Duality: Minterms and Maxterms, SOP and POS

- For each minterm, there is a corresponding maxterm

$$\overline{m}_i = M_i$$

$$M_0 = \overline{m}_0 = \overline{\overline{x}_1 \cdot \overline{x}_2 \cdot \overline{x}_3} = \overline{\overline{x}_1} + \overline{\overline{x}_2} + \overline{\overline{x}_3} = x_1 + x_2 + x_3$$

(by DeMorgan 15a)

- For each SOP, there is a corresponding POS


$$f = \sum m(1,4,5,6) = \prod M(0,2,3,7)$$

Logic gates: NAND gate


A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

$$Y = \overline{A \cdot B}$$

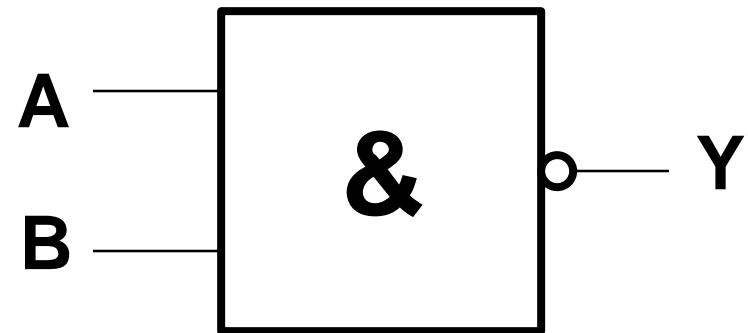IEC symbol
(International Electrotechnical Commission)



Traditional (American)
Symbol

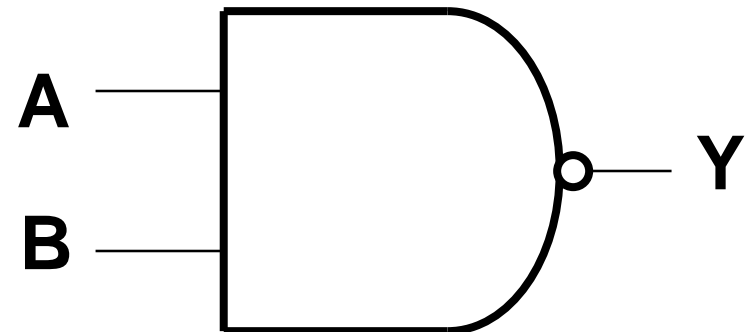


Logic gates: NOR gate


A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

$$Y = \overline{A + B}$$

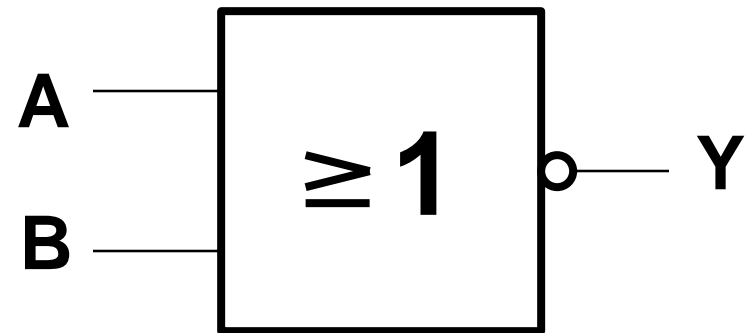IEC symbol
(International Electrotechnical Commission)



Traditional (American)
Symbol

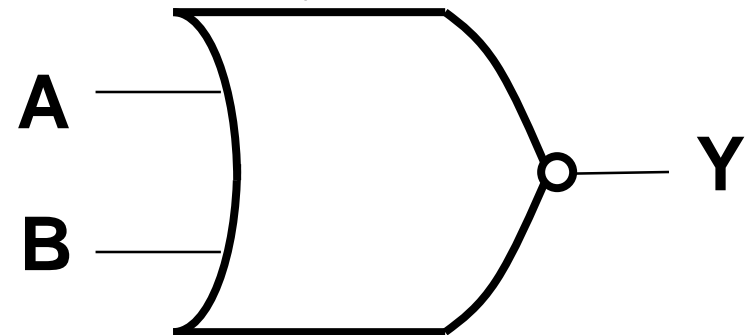

Only one gate is needed!

- All Boolean functions can be implemented using only NAND or NOR gates



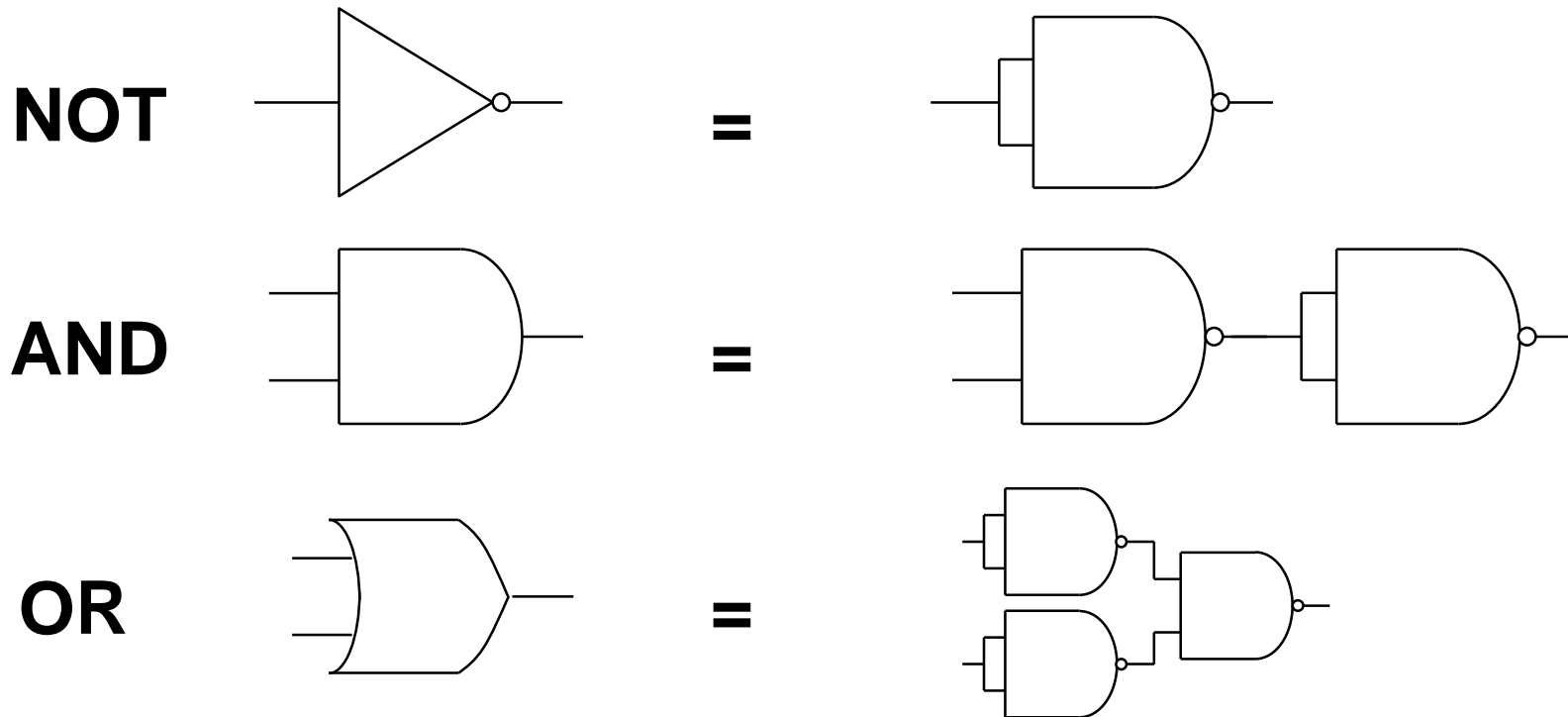


Illustration of DeMorgan's theorem


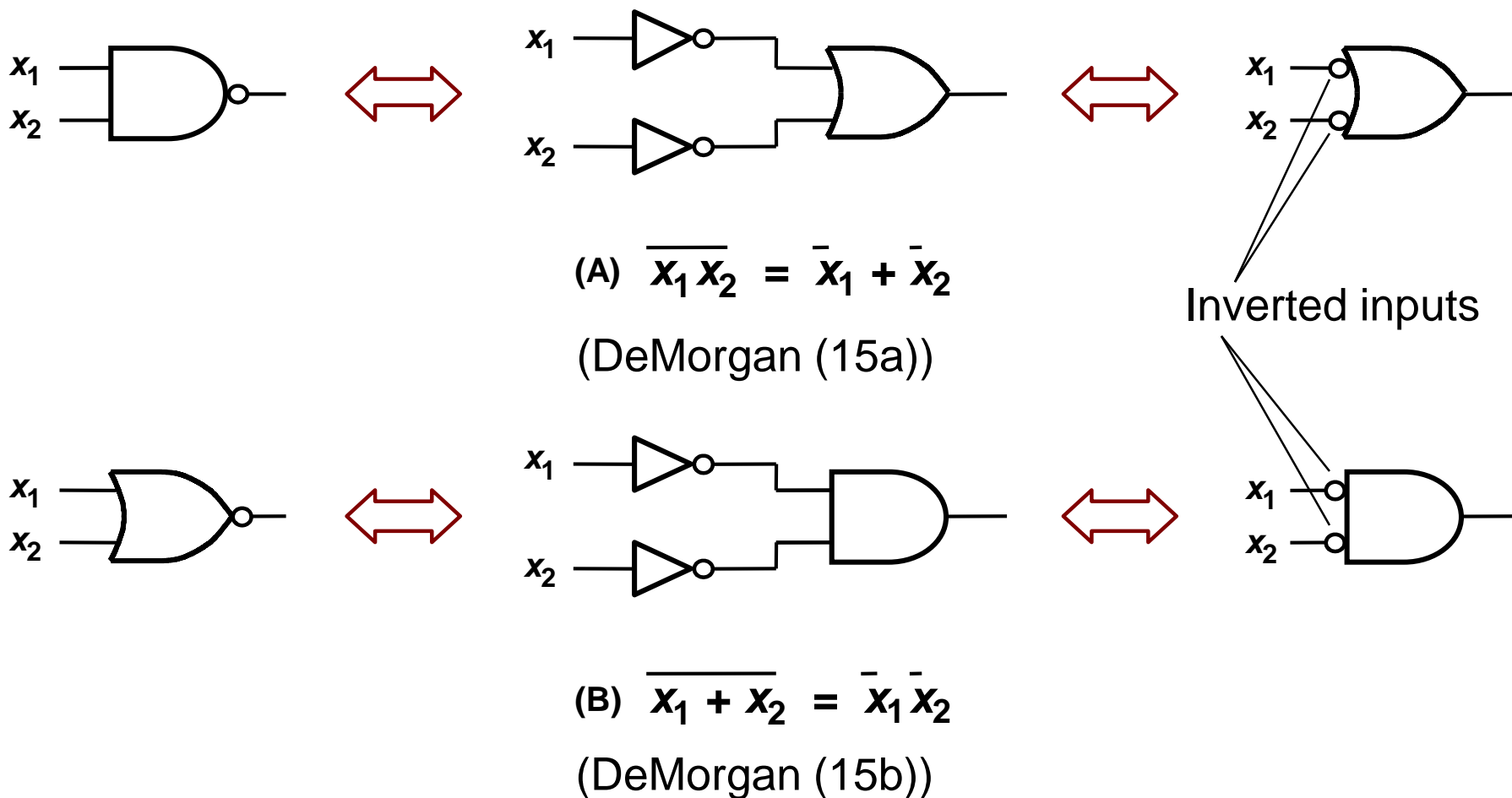


Inverter with NAND gates

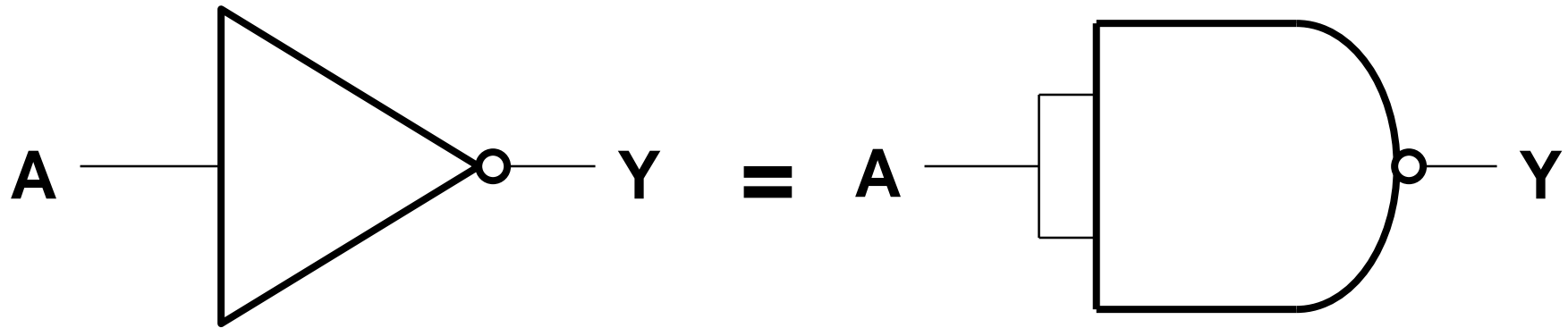


$$Y = \overline{A} = \overline{A \cdot A}$$

AND gate with NAND gates

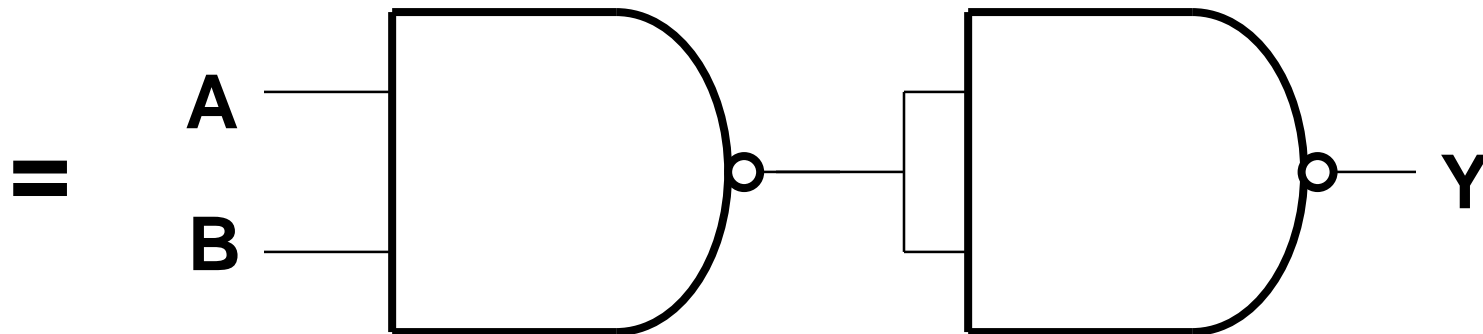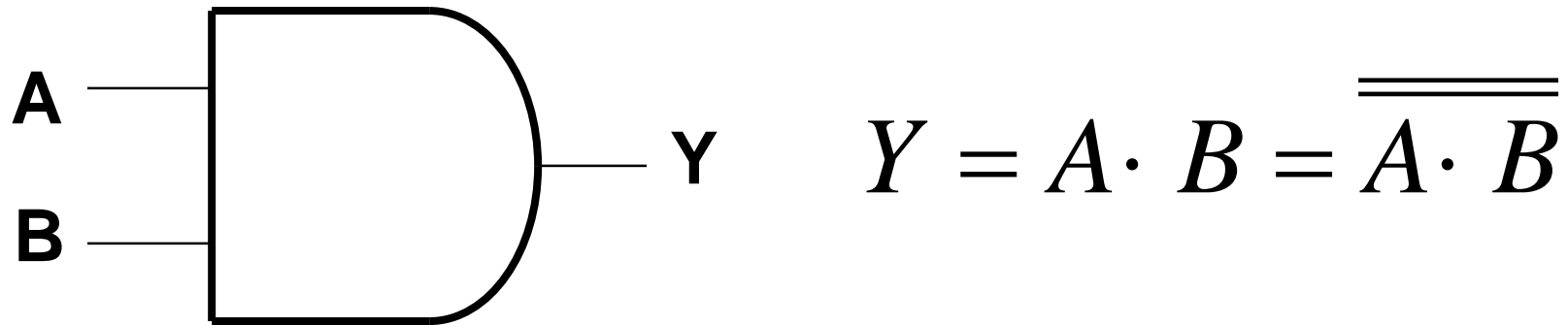


OR gate with NAND gates


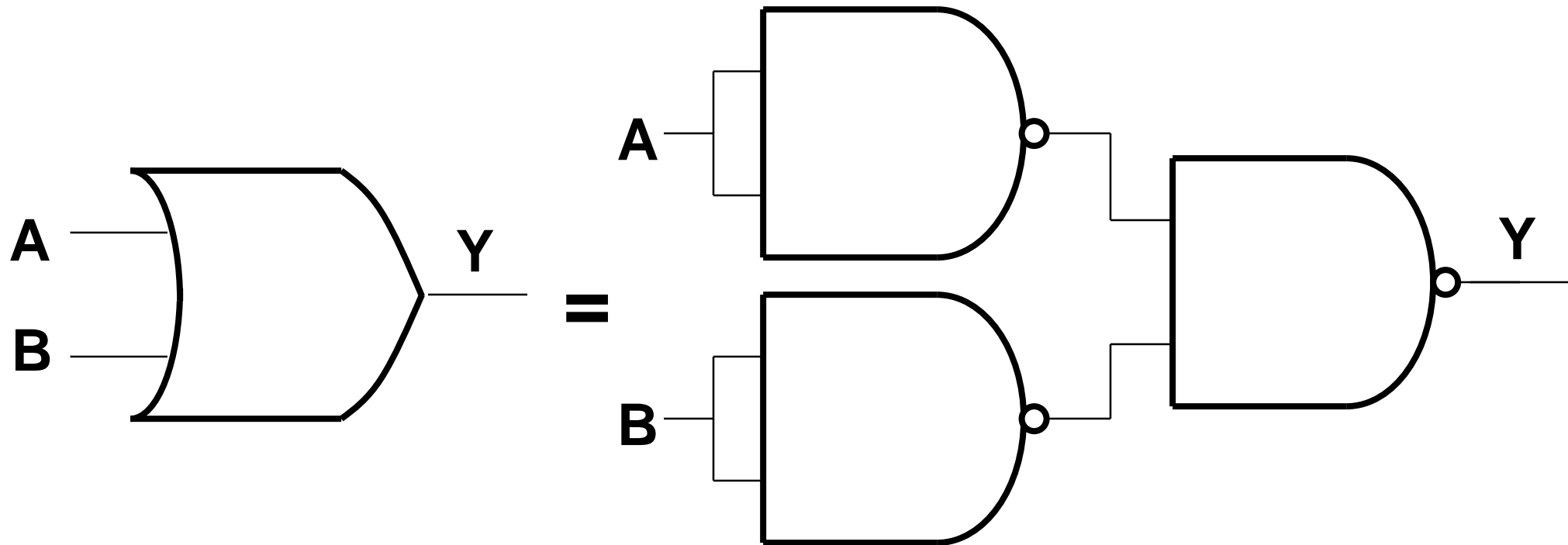


$$Y = A + B = \overline{\overline{A + B}} = \overline{\overline{A} \cdot \overline{B}} = \overline{\overline{A} \cdot \overline{A} \cdot \overline{B} \cdot \overline{B}}$$

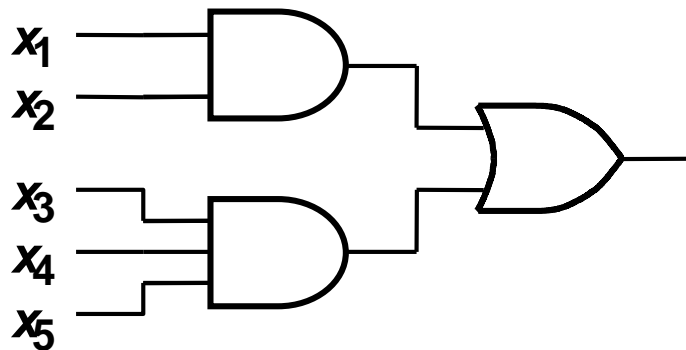Implementation of logic functions using only NAND gates



AND-OR function

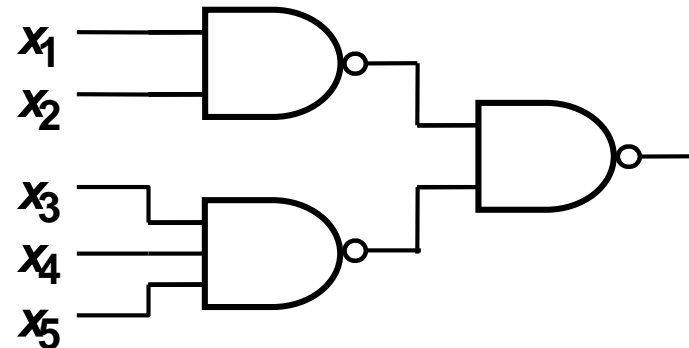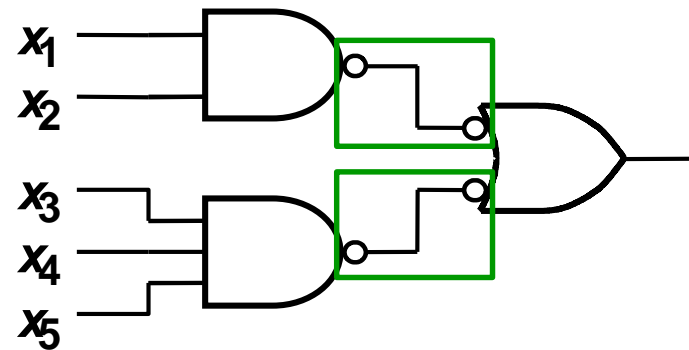

Universal sets of gates

- A set of gates called **universal** or **functionally complete** if all Boolean functions can be implemented using this set
- Examples of universal sets:

$\{\text{AND, OR, NOT}\} \rightarrow (\text{DeMorgan}) \rightarrow \{\text{AND, NOT}\} \rightarrow \{\text{NAND}\}$


$\{\text{AND, OR, NOT}\} \rightarrow (\text{DeMorgan}) \rightarrow \{\text{OR, NOT}\} \rightarrow \{\text{NOR}\}$

Logic gates: XOR gate (Exclusive OR)


A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

$$Y = A \oplus B = A \cdot \bar{B} + \bar{A} \cdot B$$

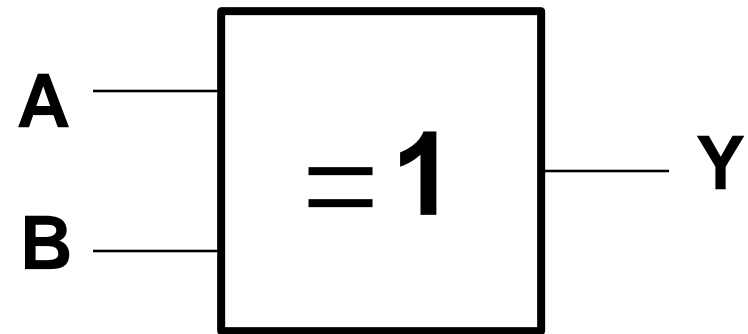IEC symbol
(International Electrotechnical Commission)



Traditional (American)
Symbol

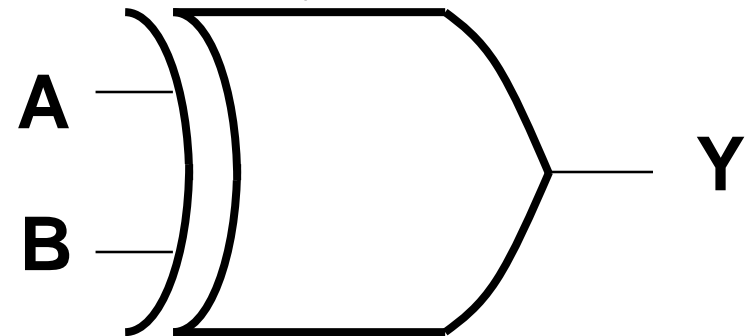


Logic gates: XNOR gate (Exclusive NOR)


A	B	Y
0	0	1
0	1	0
1	0	0
1	1	1

$$Y = \overline{A \oplus B} = \overline{A} \cdot \overline{B} + A \cdot B$$

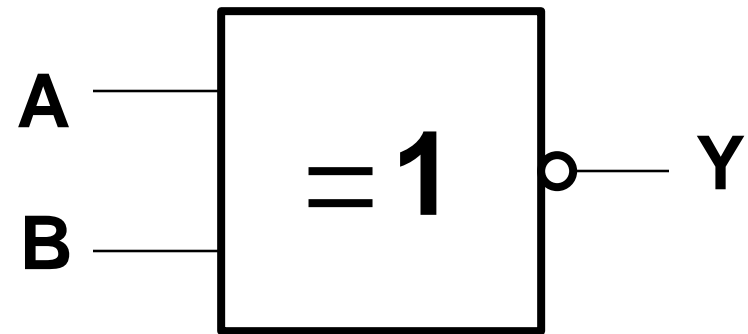IEC symbol
(International Electrotechnical Commission)





Traditional (American)
Symbol

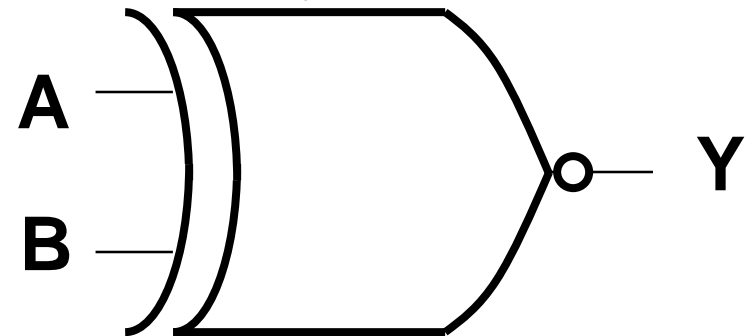

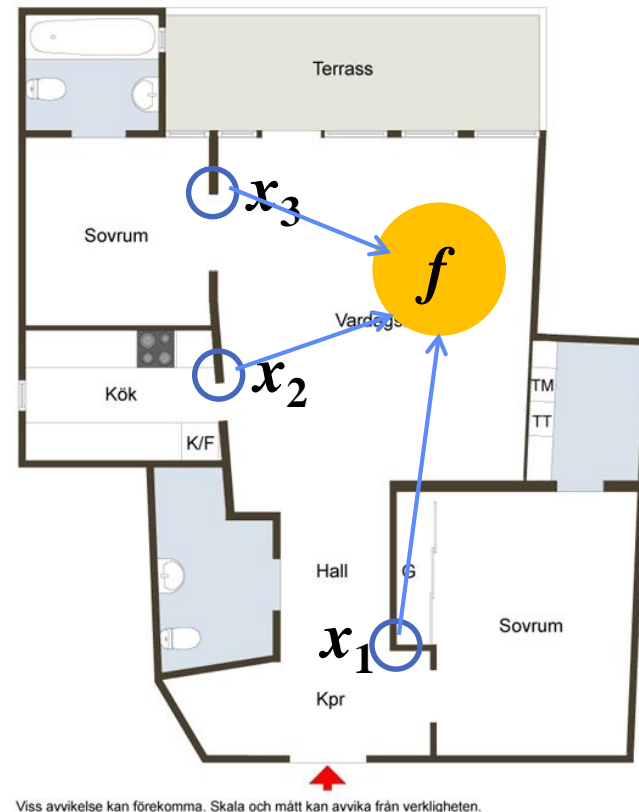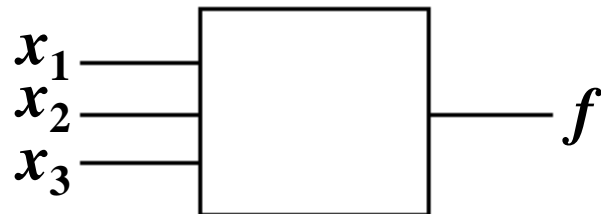
Example: Three-way light control

Brown/Vranesic: 2.8.1

Suppose that we need to be able to turn on / off the light from three different places.




Three-way light control

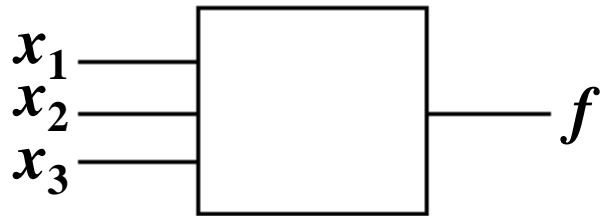

One should always be able to change the light by changing *any* switch.

x_1	x_2	x_3	f
0	0	0	0
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	


Three-way light control

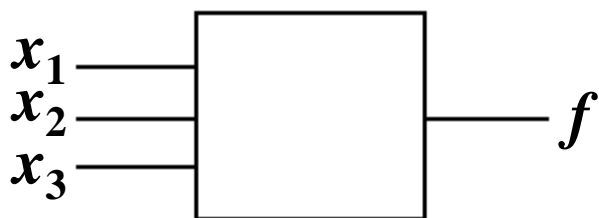

One should always be able to change the light by changing *any* switch.

x_1	x_2	x_3	f
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	
1	0	0	1
1	0	1	
1	1	0	
1	1	1	


Three-way light control

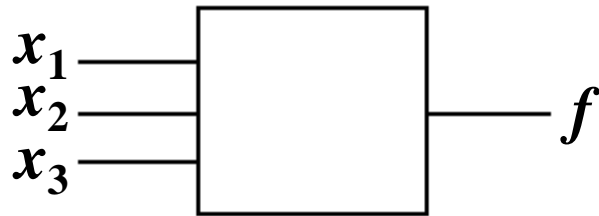

One should always be able to change the light by changing *any* switch.

x_1	x_2	x_3	f
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	
1	1	0	
1	1	1	


Three-way light control

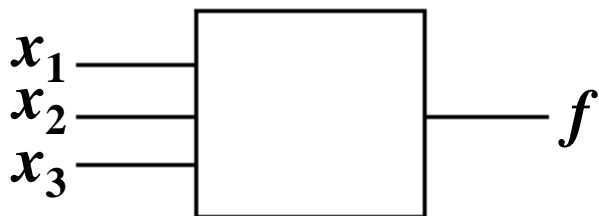

One should always be able to change the light by changing *any* switch.

x_1	x_2	x_3	f
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	

Three-way light control

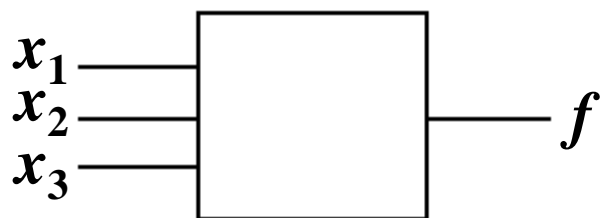

One should always be able to change the light by changing *any* switch.


The truth table now corresponds with the specifications!

x_1	x_2	x_3	f
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1



Three-way light control

x_1	x_2	x_3	f	
0	0	0	0	M_0
0	0	1	1	m_1
0	1	0	1	m_2
0	1	1	0	M_3
1	0	0	1	m_4
1	0	1	0	M_5
1	1	0	0	M_6
1	1	1	1	m_7

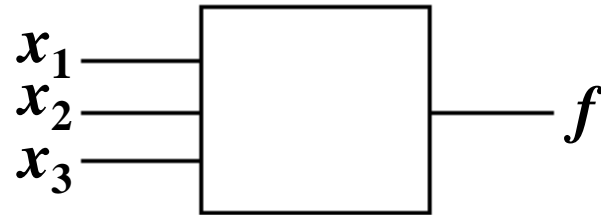

$$f = \sum m(1,2,4,7) =$$

$$= \bar{x}_1 \bar{x}_2 x_3 + \bar{x}_1 x_2 \bar{x}_3 + x_1 \bar{x}_2 \bar{x}_3 + x_1 x_2 x_3$$


or

$$f = \prod M(0,3,5,6) =$$

$$= (x_1 + x_2 + x_3) \cdot (x_1 + \bar{x}_2 + \bar{x}_3) \cdot (\bar{x}_1 + x_2 + \bar{x}_3) \cdot (\bar{x}_1 + \bar{x}_2 + x_3)$$

Three-way light control
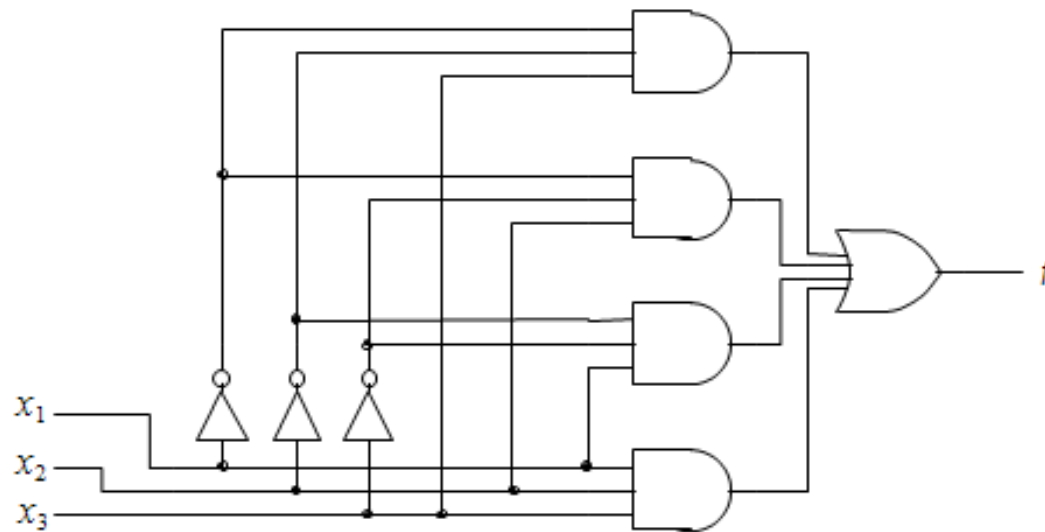
$$f = \sum m(1,2,4,7) = \bar{x}_1\bar{x}_2x_3 + \bar{x}_1x_2\bar{x}_3 + x_1\bar{x}_2\bar{x}_3 + x_1x_2x_3$$




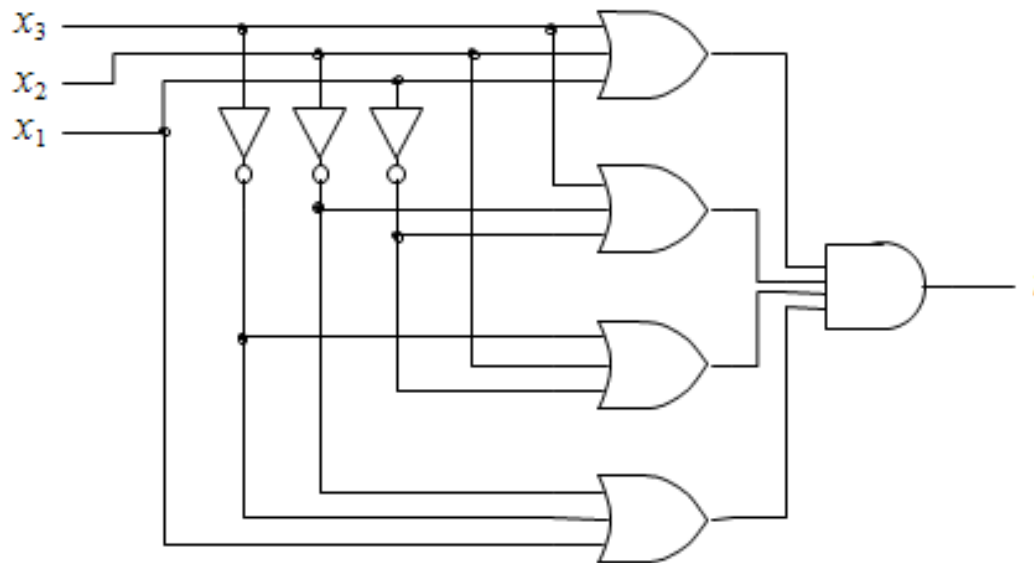(a) Sum-of-products realization



Three-way light control

$$f = \prod M(0,3,5,6) = (x_1 + x_2 + x_3) \cdot (x_1 + \bar{x}_2 + \bar{x}_3) \cdot (\bar{x}_1 + x_2 + \bar{x}_3) \cdot (\bar{x}_1 + \bar{x}_2 + x_3)$$



(b) Product-of-sums realization

Summary

- Logic functions can be described using rules of Boolean algebra
- There are logic gates for many two-variable Boolean functions
- A logic function can be expressed as
 - SOP form (Sum of minterms) or
 - POS form (Product of maxterms)