 


LAB VHDL-programing




With a breakoutboard one can use the breadboard with components that actually is intended for surface mounting on circuit boards. One can then easily try different couplings.

In this way, we use the same technique as in the previous lab - even though we now move on to more complex so-called CPLD circuitry and are programming them with the VHDL language.

MAX-chip



Figure 1. MAX 3000A Device Block Diagram

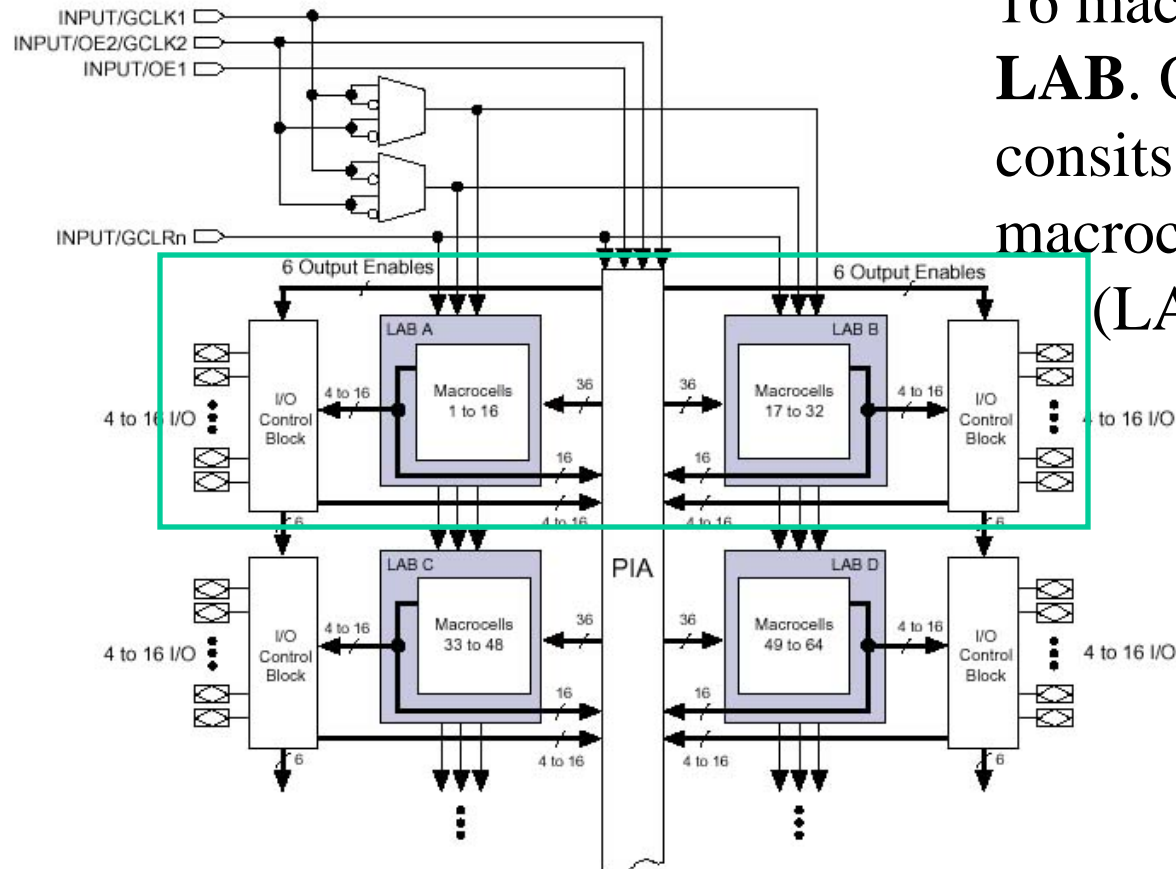



16 macrocells forms a **LAB**. Our lab-chip consists of 32 macrocells, 2 LAB's. (LAB A LAB B)

The block **PIA** is used to connect the LAB-units.



Laboration task - code lock



 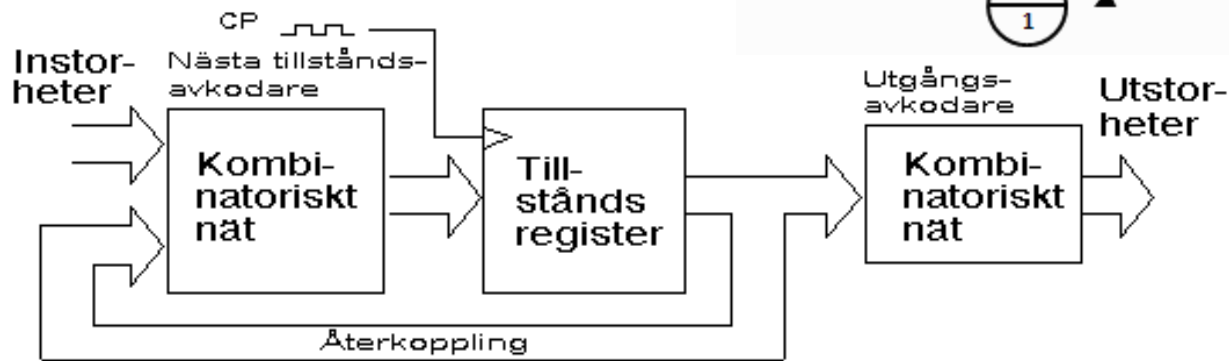- **Task:** to write VHDL code for a code lock that opens with the code "the last four digits of your social security number".
- **Help:** a VHDL "template" for a simplified code lock that opens with the code "number one".



LAB equipment with a MAX-chip

  


The keys are decoded as
"One of three" columns (**K**),
and "one of four" lines (**R**).

Quartus tutorial for MAX CPLD on school centrally administrated computers




QuartusII

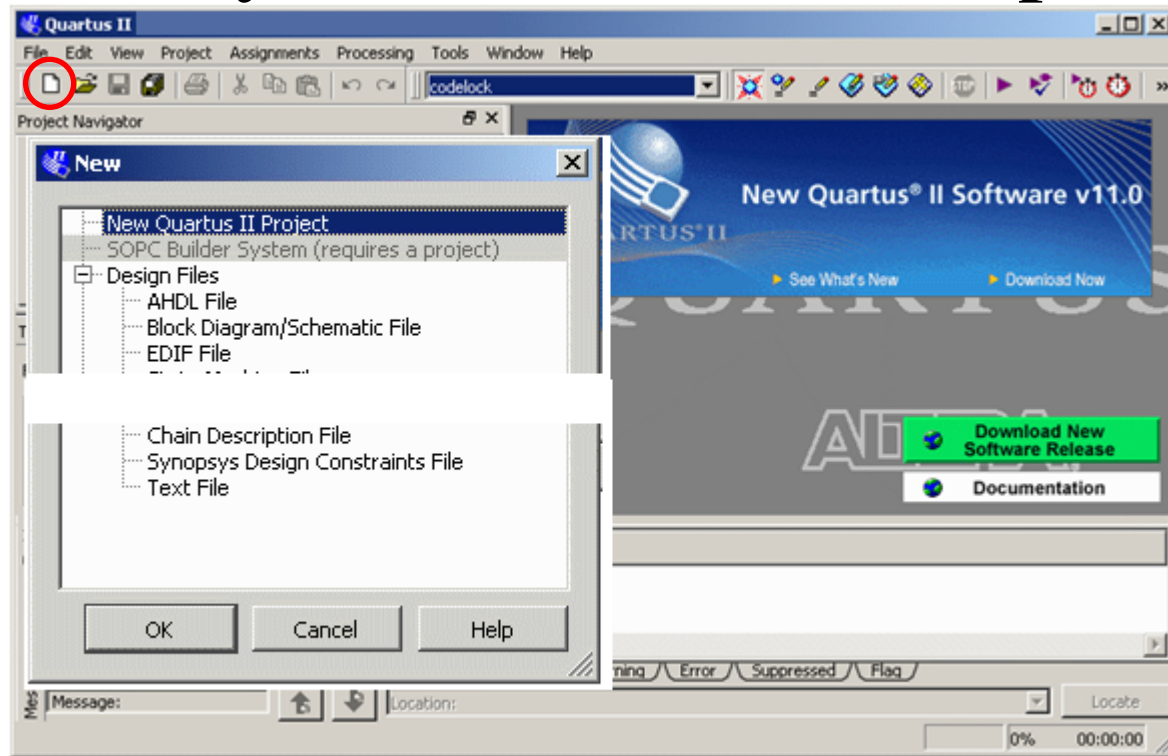

- Start with creating a new project.
File, New, New Quartus II Project

New Project Wizard

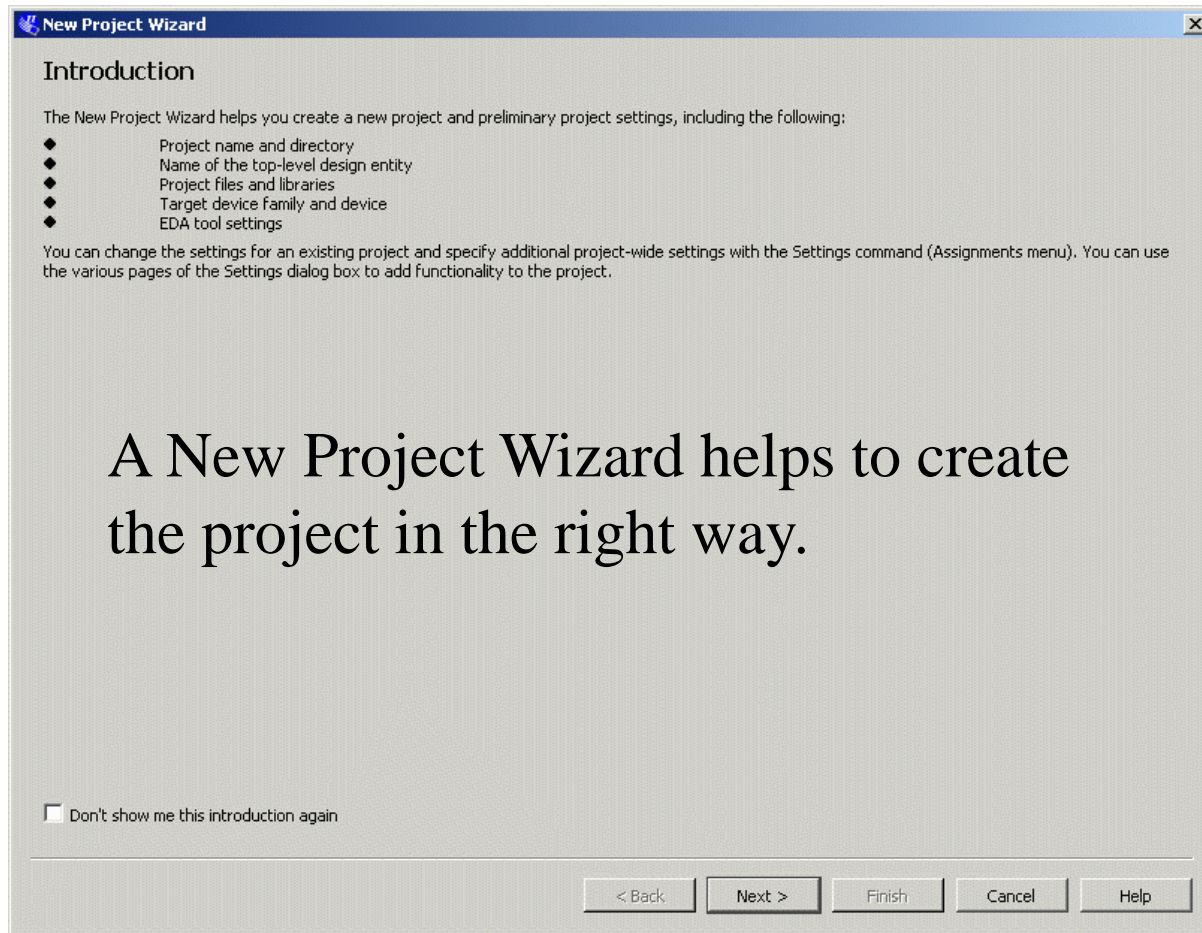

A New Project Wizard helps to create the project in the right way.

Project Name and Directory

New Project Wizard

Directory, Name, Top-Level Entity [page 1 of 5]

What is the working directory for this project?

H:/MAXwork

What is the name of this project?

codelock

What is the name of the top-level design entity for this project? This name is case sensitive and must exactly match the entity name in the design file.

codelock

Use Existing Project Settings...


< Back Next > Finish Cancel Help

At school the whole project must be on your **H: **

- **Name: codelock**
- **Top-Level Entity: codelock**

(NOTE **codelock** must "match" the name you later on is using for **entity** in your VHDL-file)

Add Files

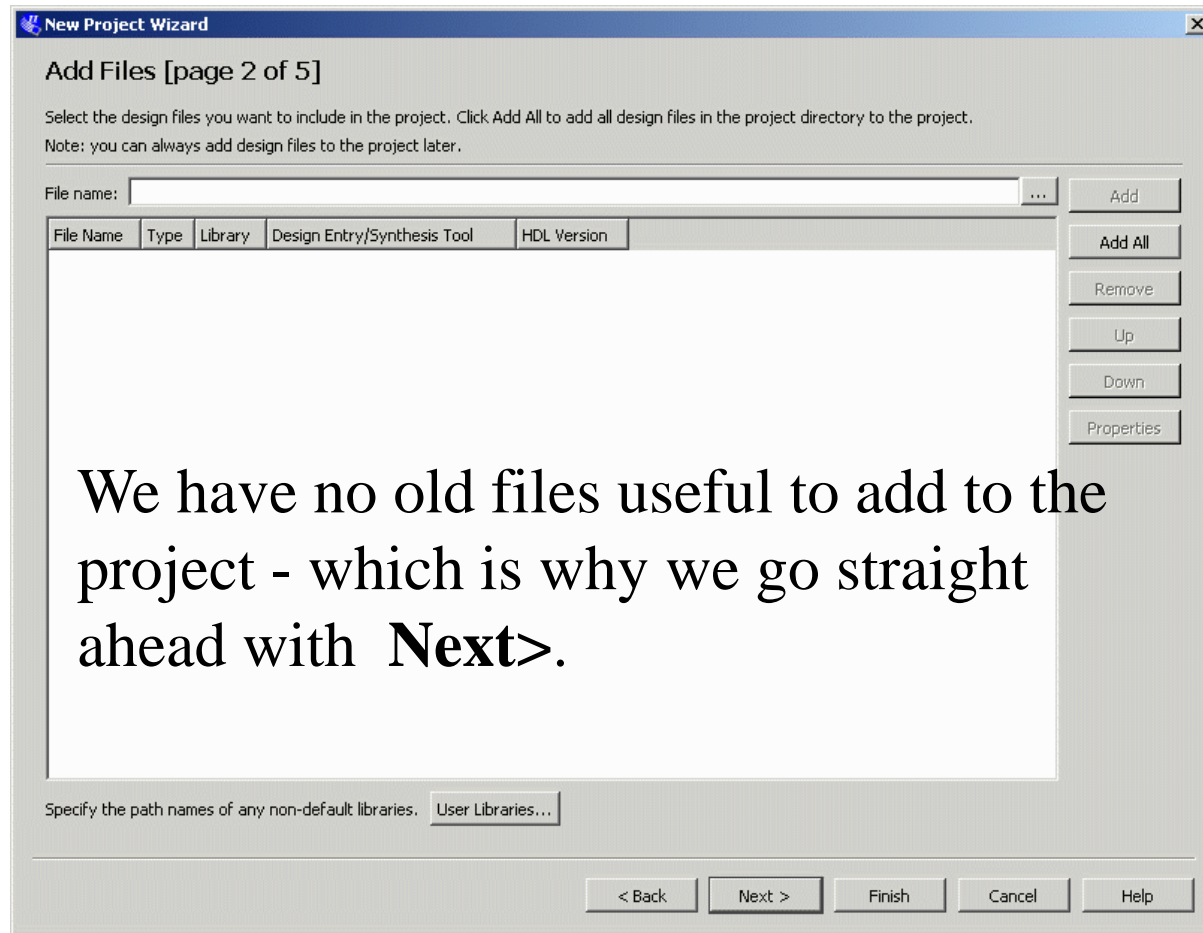

Family and Device Settings



New Project Wizard

Family & Device Settings [page 3 of 5]

Select the family and device you want to target for compilation.

Device family

Family:

Devices:

Target device

☐ Auto device selected by the Filter

☒ Specific device selected in 'Available devices' list

☐ Other: n/a

Show in 'Available devices' list

Package:

Pin count:

Speed grade:

☒ Show advanced devices

☐ HardCopy compatible only

Available devices:

Name	Core Voltage	Macrocells
EPM3032ALC44-4	3.3V	32
EPM3032ALC44-7	3.3V	32
EPM3032ALC44-10	3.3V	32
EPM3032ATC44-4	3.3V	32
EPM3032ATC44-7	3.3V	32
EPM3032ATC44-10	3.3V	32
EPM3032ATI44-10	3.3V	32
FPM3064AI C44-4	3.3V	64

Companion device

HardCopy:


☐ Limit DSP & RAM to HardCopy device resources

< Back Next > Finish Cancel Help

Family: MAX3000A Available devices: EPM3032ALC44-10

William Sandqvist william@kth.se

EDA Tool Settings

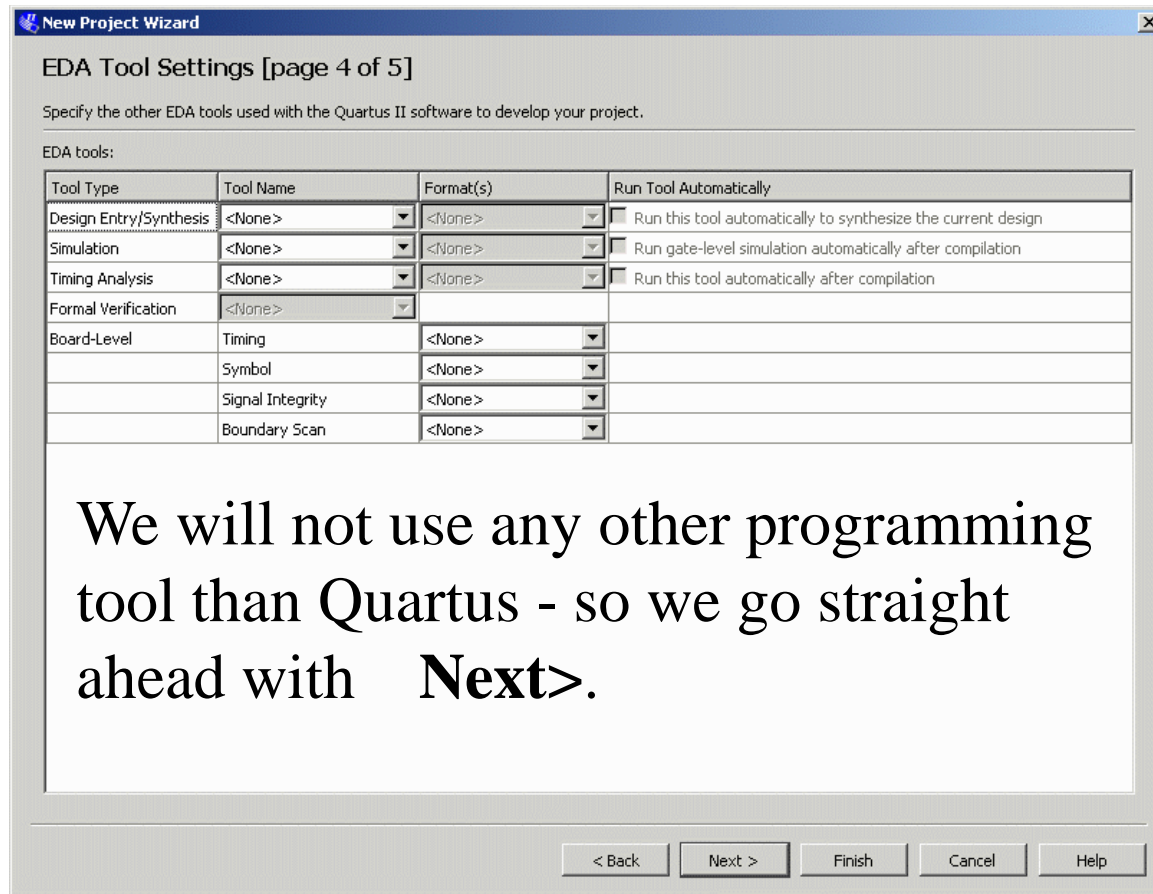

New Project Wizard

EDA Tool Settings [page 4 of 5]

Specify the other EDA tools used with the Quartus II software to develop your project.


EDA tools:

Tool Type	Tool Name	Format(s)	Run Tool Automatically
Design Entry/Synthesis	<None>	<None>	<input checked="" type="checkbox"/> Run this tool automatically to synthesize the current design
Simulation	<None>	<None>	<input type="checkbox"/> Run gate-level simulation automatically after compilation
Timing Analysis	<None>	<None>	<input checked="" type="checkbox"/> Run this tool automatically after compilation
Formal Verification	<None>		
Board-Level	Timing	<None>	
	Symbol	<None>	
	Signal Integrity	<None>	
	Boundary Scan	<None>	

We will not use any other programming tool than Quartus - so we go straight ahead with **Next>**.

< Back Next > Finish Cancel Help

Summary

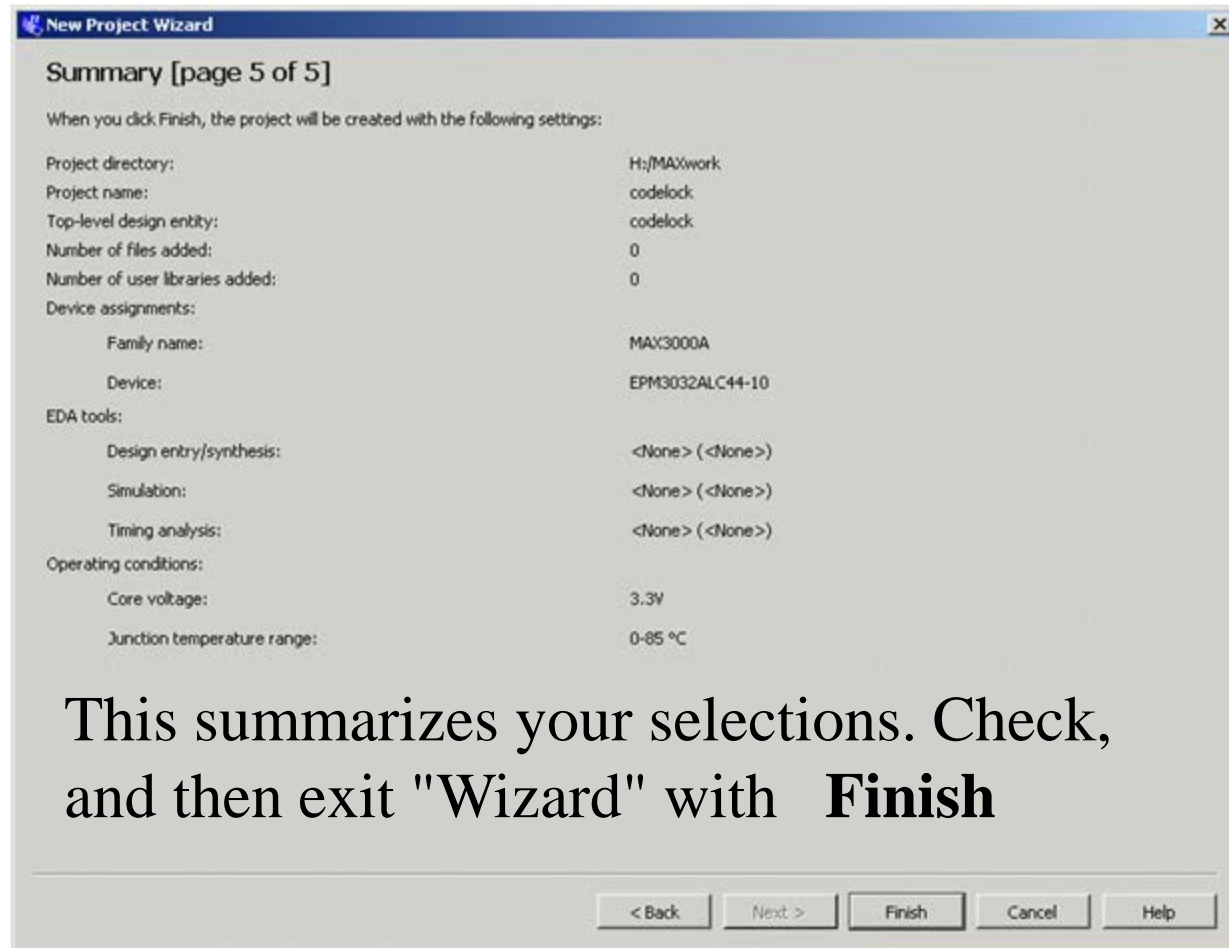


This summarizes your selections. Check, and then exit "Wizard" with **Finish**

Project is created



VHDL code

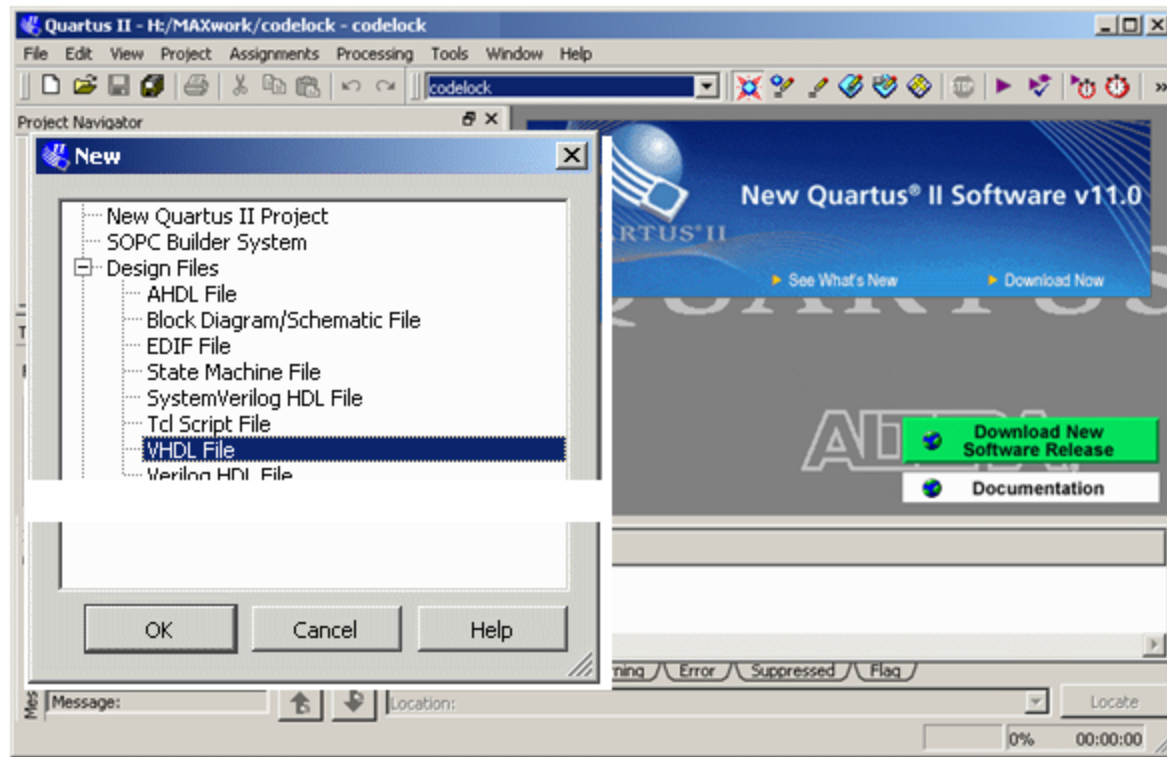

- Create a blank file for the VHDL-code. **File, New, VHDL File**
- The template program is complete (but it is to a simplified code lock).



Paste the VHDL code

NOTE that entity in VHDL-file must "matc" the project Top Level Entity!

Save the file: **File, Save As**

- Folder *must* be in H: \



Analysis and Synthesis

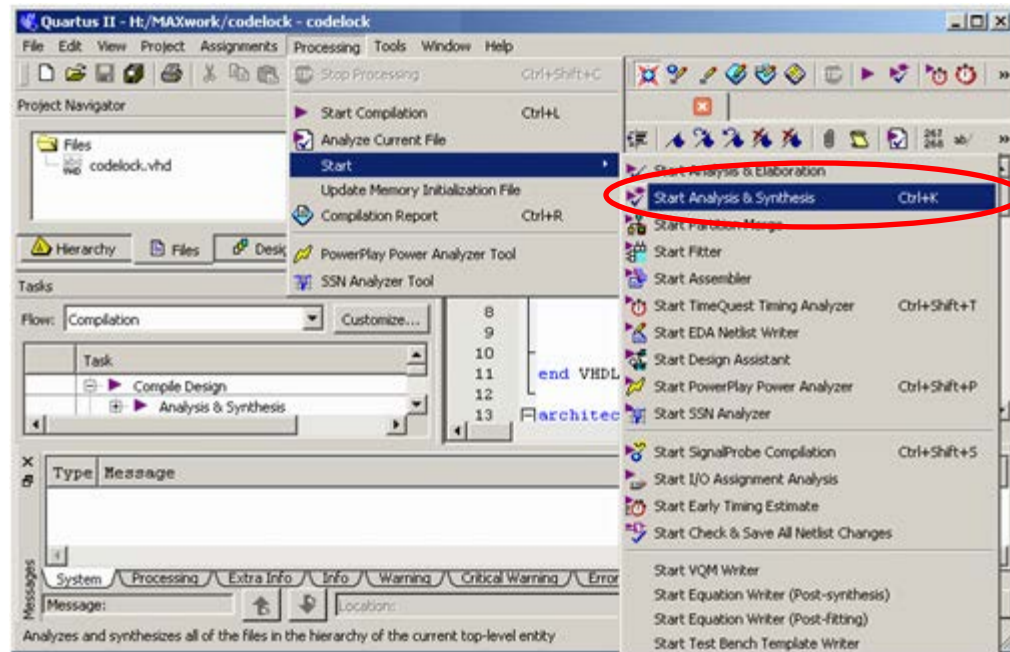 




When you have newly written code, it is unnecessary to run the entire tool chain - the chances are that there are errors along the way ...

- From start run only **Analysis & Synthesis**.

Analysis and Synthesis

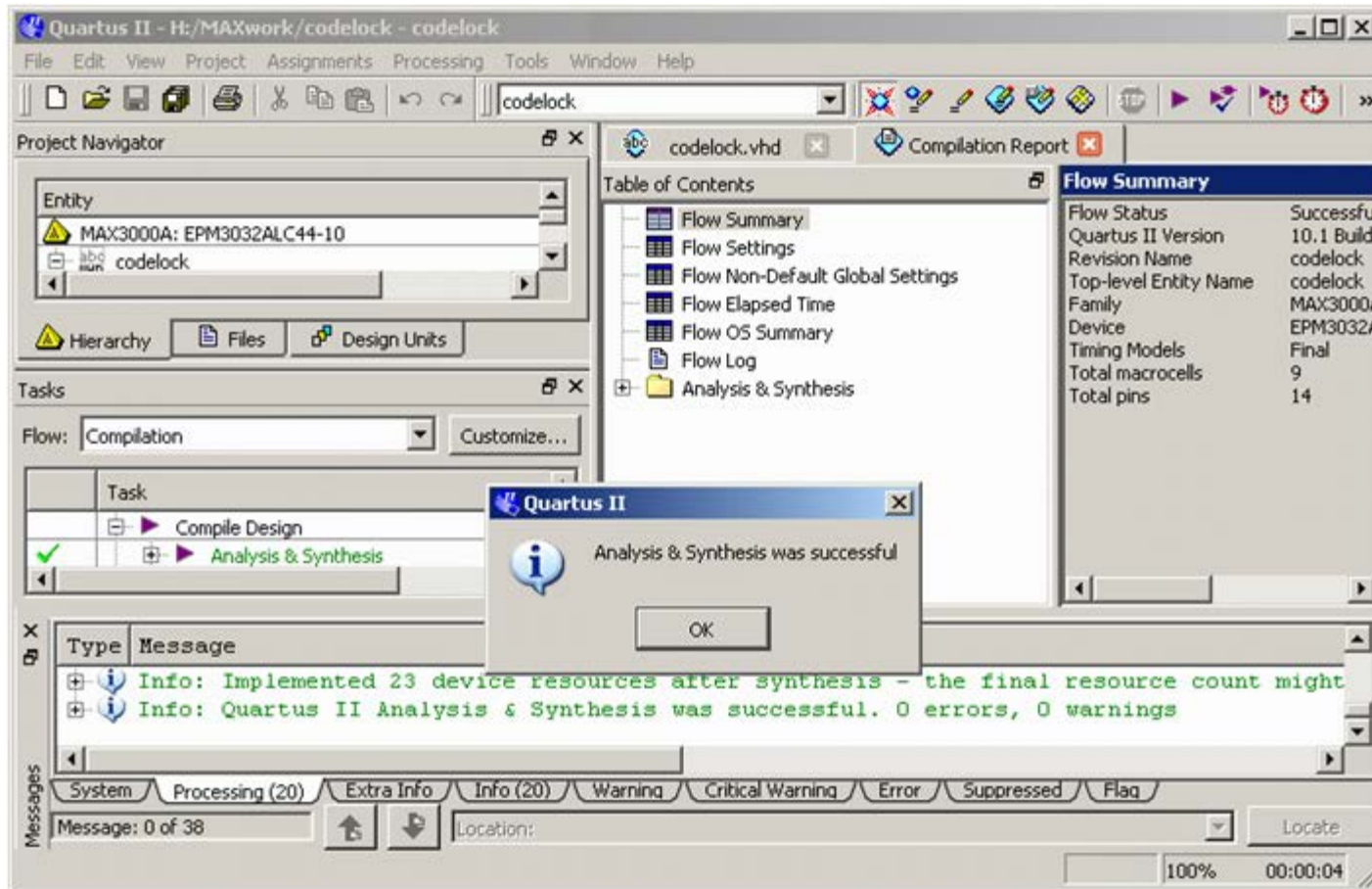
 


Lab equipment has *different* wiring!

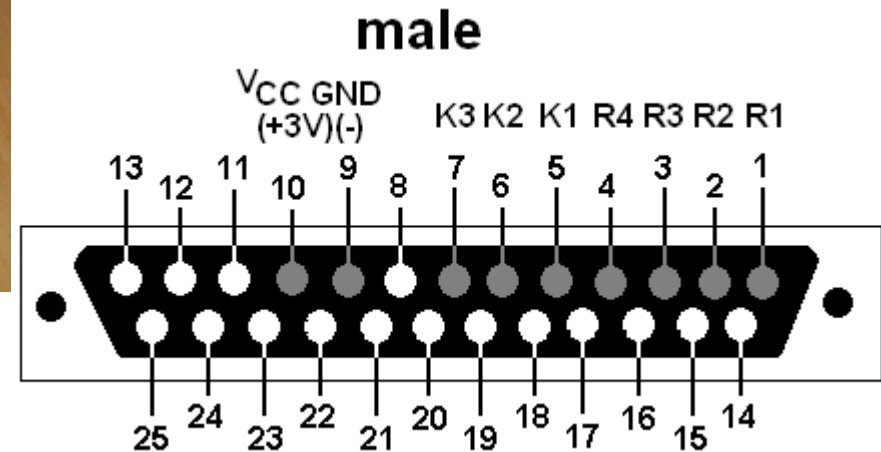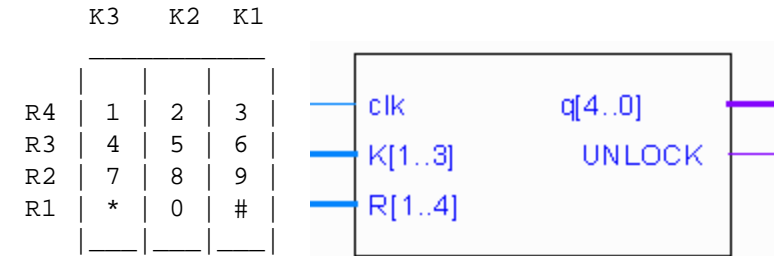 

It's DB25 connector pin No. 1 ... 10 that are used by the keys.

What applies for your equipment?

 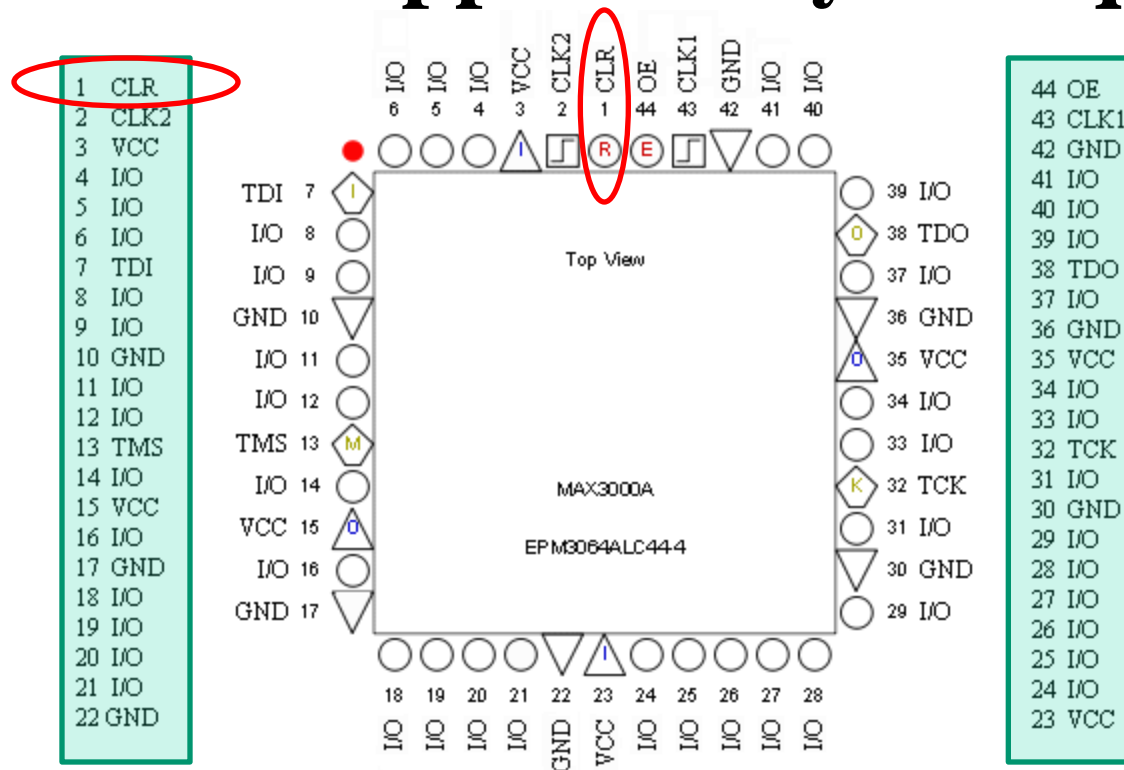


JTAG

TDI	-	TMS	TDO	TCK
GND	-	-	VCC	GND

This is how you identify pin number 1.





Pin Planner

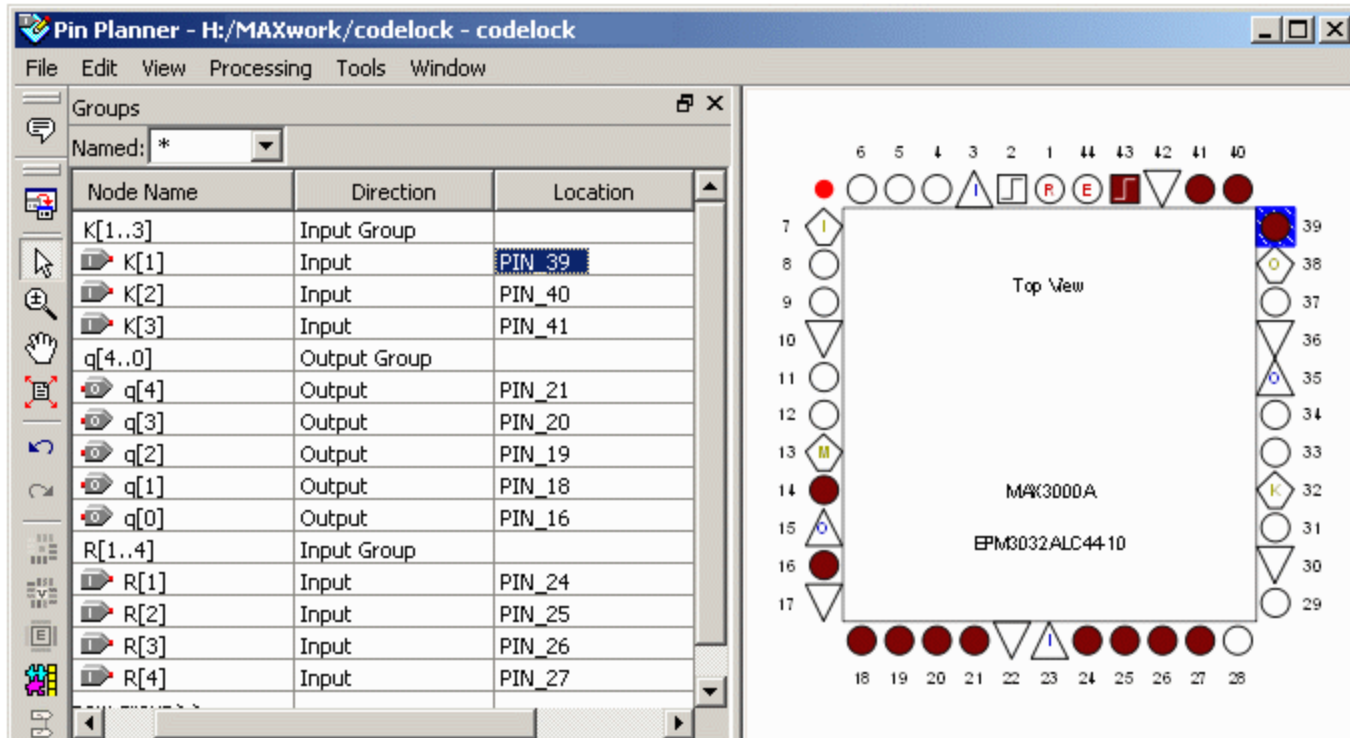



At the lab, all equipment are connected in different ways, so you have to make your own pin-planning for your lab equipment. The image pin-plan can only be seen as an example.

Start Compilation

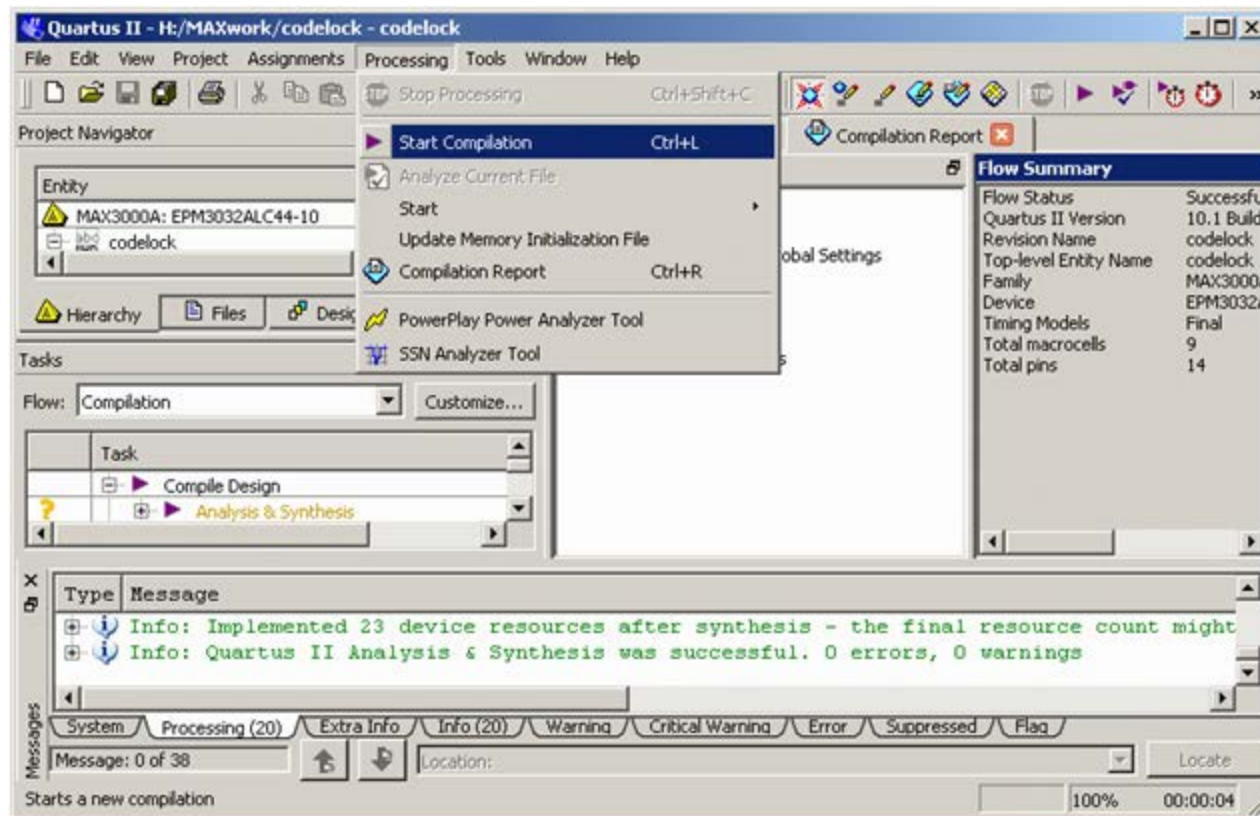 

- **Start Compilation** runs the *whole* tool-chain.

Compilation successful

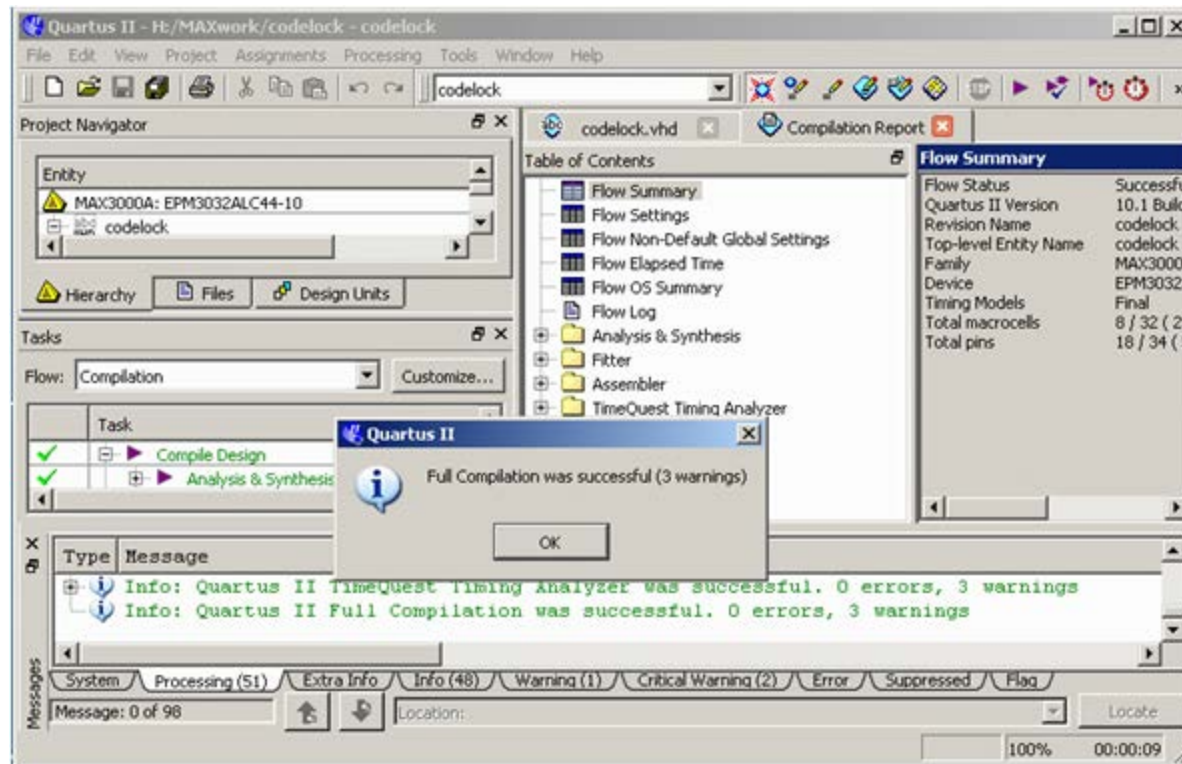 

The 3 warnings (more with other program versions) is about "tools" that are missing in our program version but that we do not need.

Chip-programming



JTAG



TDI	-	TMS	TDO	TCK
GND	-	-	VCC	GND



A **JTAG** contact is connected to the MAX-chip for "in circuit programming".

Chip-programming is done with a *USB-blast*er.

Try out the functioning!

  


Power
On/Off

Template application is for a simplified code lock that opens to the key "1", a little too easy it seems ...!

Open the lock with your social security number!

 
- *Now it's time to rewrite the VHDL code so that the lock opens to the last four digits of your social security number!*



(If you prepare the code for your social security number, then two in a group can contribute with half of the code at the lab).

Description of the code lock template

 The combination lock template is for a simplified lock that opens instantly when you press the key "1".




Virtually all digital design are now using high-level languages like VHDL / VERILOG. Our first course in digital technology does not allow space to teach VHDL language, however, you will be able to reshape "the template code lock" into useful VHDL code before the lab.

Do you think that the VHDL language seems interesting, so the school has several digital technology advanced courses

...

Moore machine
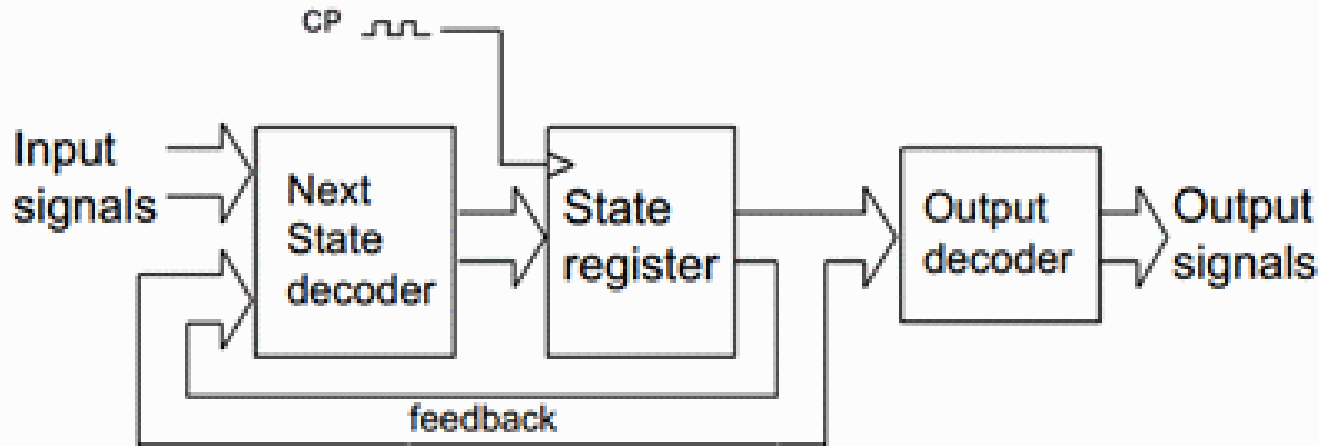
```
next_state_decoder: state_register: output_decoder:
```



The different blocks in the code are identified with "labels"

```
next_state_decoder:
```

```
output_decoder:
```

```
state_register:
```

VHDL process

With a "process" one can describe what a block is to perform without having to go into detail on how this should be done.

Label.

`next_state_decoder:`

`process(state, K, R)`

`begin`

`...`

`end process;`

Sensitivity list. Every *change* in one of these variables forces the process to be updated!

Body. What is to be done.

lockmall.vhd

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_arith.all;

start → entity codelock is
    port( clk:      in  std_logic;
          K:        in  std_logic_vector(1 to 3);
          R:        in  std_logic_vector(1 to 4);
          q:        out std_logic_vector(4 downto 0);
          UNLOCK:   out std_logic );
end codelock;

start → architecture behavior of codelock is
    subtype state_type is integer range 0 to 31;
    signal state, nextstate: state_type;

    begin
        nextstate_decoder: -- next state decoding part
        process(state, K, R)
        begin
            case state is
                when 0 => if (K = "100" and R ="0001")    then nextstate <= 1;
                           else nextstate <= 0;
                           end if;
                when 1 => if (K = "100" and R ="0001")    then nextstate <= 1;
                           elsif (K = "000" and R = "0000") then nextstate <= 2;
                           else nextstate <= 0;
                           end if;
                when 2 to 30 => nextstate <= state + 1;
                when 31      => nextstate <= 0;
            end case;
        end process;

        debug_output: -- display the state
        q <= conv_std_logic_vector(state,5);

        output_decoder: -- output decoder part
        process(state)
        begin
            case state is
                when 0 to 1  => UNLOCK <= '0';
                when 2 to 31 => UNLOCK <= '1';
            end case;
        end process;


        state_register: -- the state register part (the flipflops)
        process(clk)
        begin
            if rising_edge(clk) then
                state <= nextstate;
            end if;
        end process;
    end behavior;
end
```

entity
architecture
next_state_decoder:
output_decoder:
state_register:

Codelock VHDL

- **entity** Block-description, input signals and output signals
 
```
library IEEE;  
use IEEE.std_logic_1164.all;  
use IEEE.std_logic_arith.all;
```




start

```
entity codelock is  
  port( clk:      in  std_logic;  
        K:        in  std_logic_vector(1 to 3);  
        R:        in  std_logic_vector(1 to 4);  
        q:        out std_logic_vector(4 downto 0);  
        UNLOCK:   out std_logic );  
end codelock;
```

end

Bitvectors and bit's


 
You can customize the indexing of variables so that it is consistent with the data sheets - less risk of mistakes!



```
K: in std_logic_vector(1 to 3);
R: in std_logic_vector(1 to 4);
q: out std_logic_vector(4 downto 0);
```

1 2 3
K = "001" bit vector
K(3) = '1' bit

  4 3 2 1 0
q = "00001" bit vector
q(0) = '1' bit



Codelock VHDL ...

- **architecture**

Description of the
block behavior

start




```
architecture behavior of codelock is
  subtype state_type is integer range 0 to 31;
  signal state, nextstate: state_type;

begin;
```

Here we create a new data type, **state_type**, which can have integer values between 0 and 31. The compiler prevents us then from (accidentally) use other values. Signals **state** and **nextstate** are of this datatype.

Codelock VHDL ...

```
nextstate_decoder: -- next state decoding part
process(state, K, R)
begin
  case state is
    when 0 => if (K = "001" and R = "0001")      then nextstate <= 1;
               else nextstate <= 0;
               end if;
    when 1 => if (K = "001" and R = "0001")      then nextstate <= 1;
               elsif (K = "000" and R = "0000") then nextstate <= 2;
               else nextstate <= 0;
               end if;
    when 2 to 30 => nextstate <= state + 1;
    when 31      => nextstate <= 0;
  end case;
end process;
```

 

Codelock VHDL ...

To troubleshoot, we want to be able to follow the state machine is in ...

```
debug_output:  -- display the state  
q <= conv_std_logic_vector(state,5);
```

The function **conv_std_logic_vector()** converts **state** (an integer between 0...31) to a 5-bit bit vector **q**, **q(4) ... q(0)**.

Codelock VHDL ...


```
output_decoder: -- output decoder part
process(state)
begin
    case state is
        when 0 to 1  => UNLOCK <= '0';
        when 2 to 31 => UNLOCK <= '1';
    end case;
end process;
```

Codelock VHDL ...

```
state_register: -- the state register part (the flipflops)
process(clk)
begin
    if rising_edge(clk) then
        state <= nextstate;
    end if;
end process;
```


```
end behavior;
```

← end

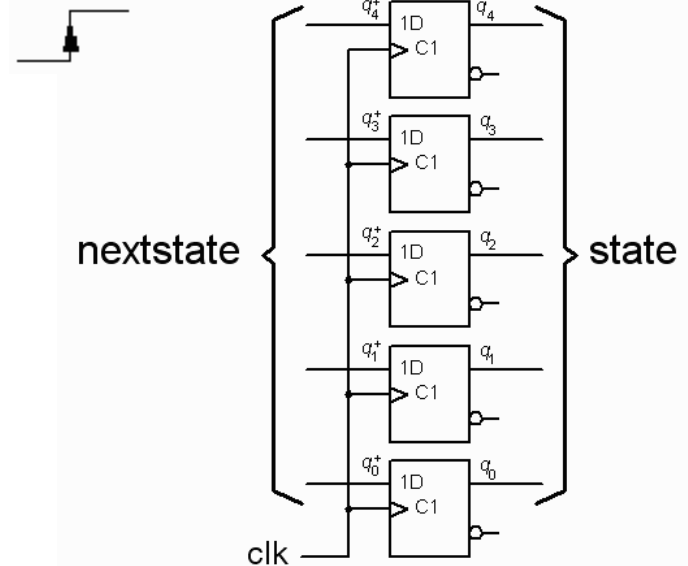

Open the lock with your social security number!

 - *Now it's time to rewrite the VHDL code so that the lock opens to the last four digits of your social security number!*




Simulate with ModelSim



ModelSim can be used to simulate the VHDL code, to determine whether it is "right" thought.

One can perform simulations that take into account "time delay" and other phenomena inside the intended target circuit.

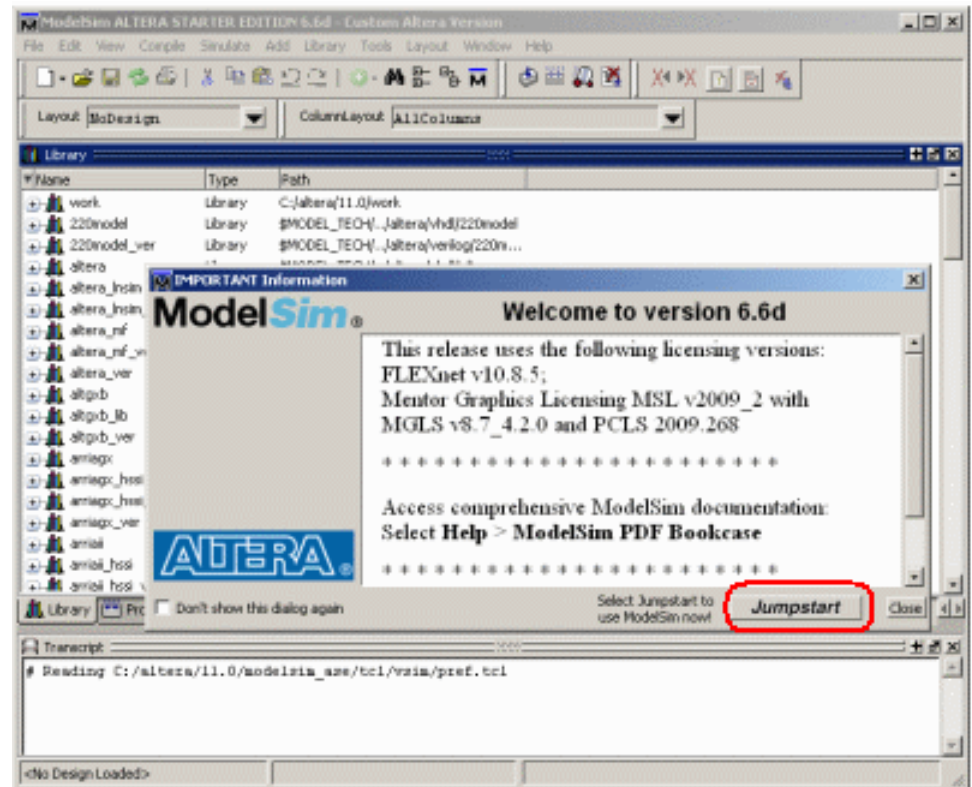Start **ModelSim**. Click on **Jumpstart** for help with setting up a project.



Create a project

 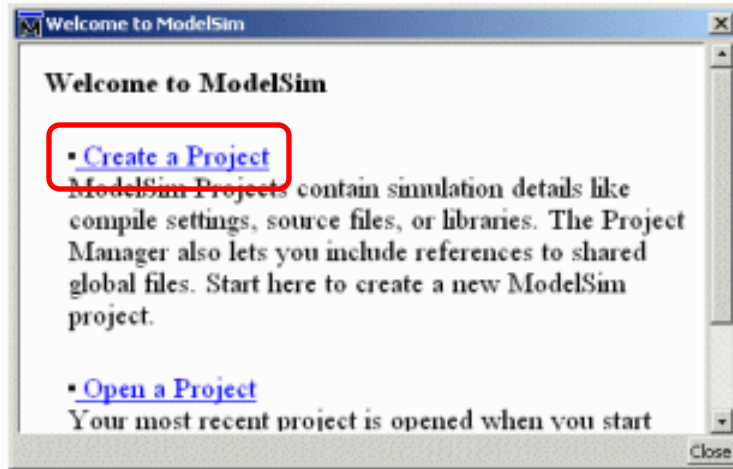


Project Name

MAXsim may be an appropriate name

Project location

H: /MAXwork browse to the *same working directory* you used for Quartus


Add a VHDL-file

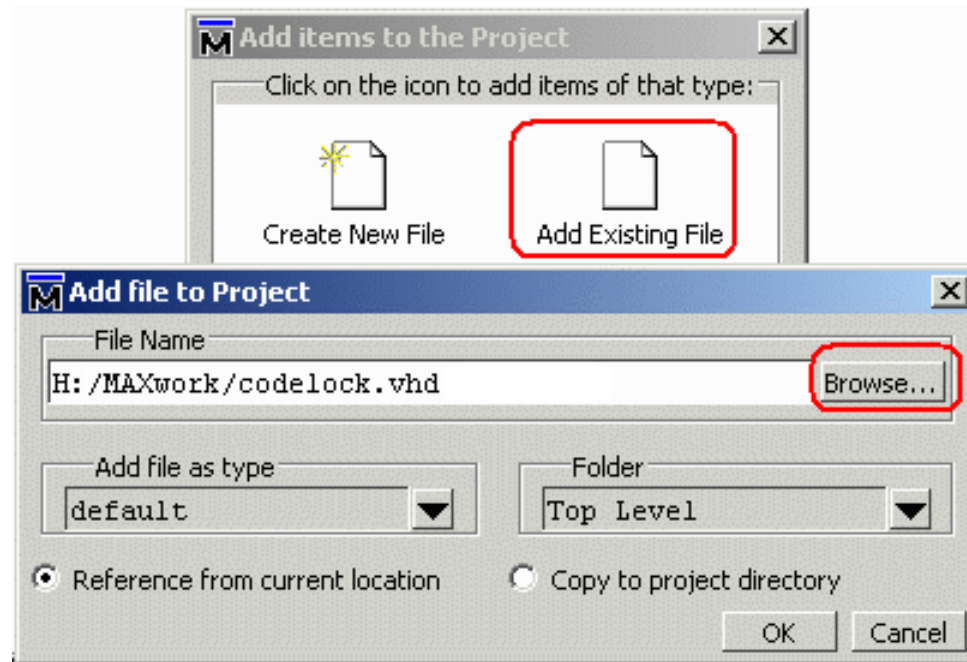

We choose "Add Existing File" to add a VHDL file to the project.



"Browse" to the file **codelock.vhd** as we created earlier with **Quartus**.

 Codelock template in ModelSim





Compile for simulation

ModelSim has its own compiler to produce the VHDL code for simulation. Though we have compiled the VHDL code in **Quartus** we must nevertheless compile it again with **ModelSim**.



Name	Status
 codelock.vhd	

Choose **Compile** menu, alternative **Compile All**.

Name	Status
 codelock.vhd	

Now the VHDL code is also compiled for modelsim. The status symbol changes from a blue question mark to a green check!

Simulate the code lock template

 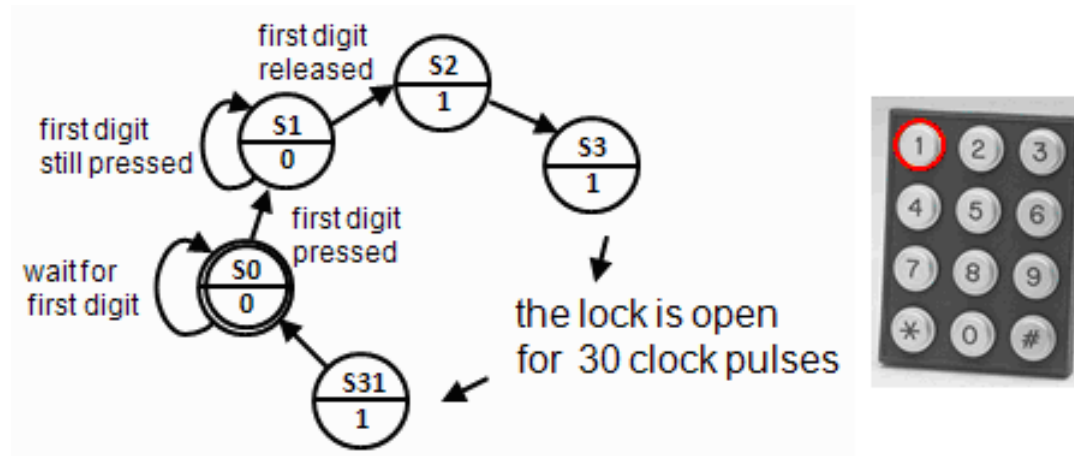


Download The design to the simulator. Select the Library tab, and open the folder work. Double click on the "Entity" **code lock**.

Transcript-window

A series of commands are now resulting in that the design is loaded into the simulator.

In the **Transcript** window, you can follow the commands that are executed.

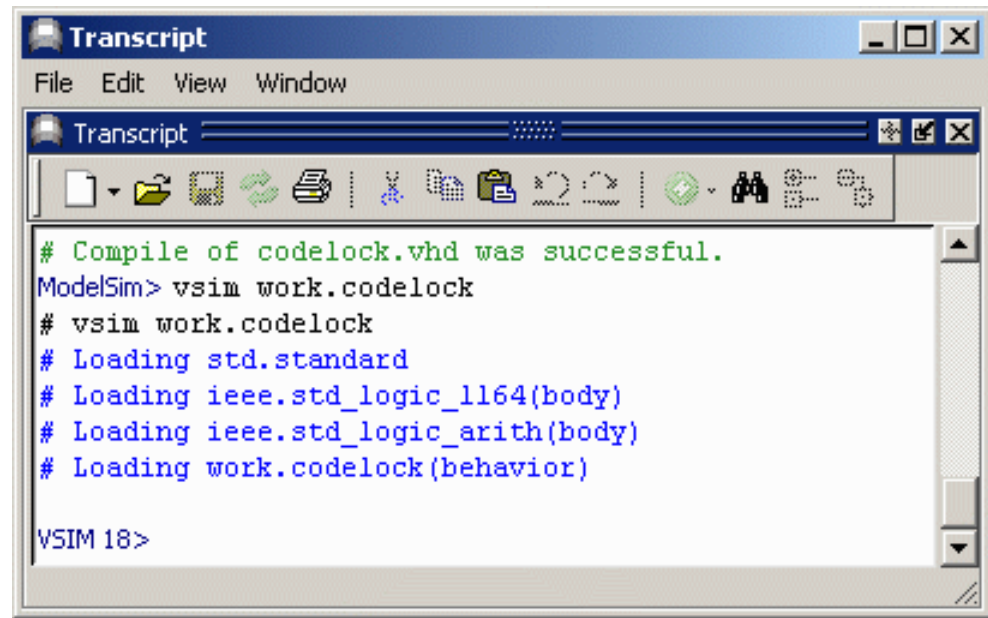Transcript window is a terminal window where you give commands, but you can also give most commands by menu selection, or by clicking the buttons.



```
Transcript
File Edit View Window

# Compile of codelock.vhd was successful.
ModelSim> vsim work.codelock
# vsim work.codelock
# Loading std.standard
# Loading ieee.std_logic_1164(body)
# Loading ieee.std_logic_arith(body)
# Loading work.codelock(behavior)

VSIM 18>
```

Commands are, however, always printed in the Transcript window, no matter how they are delivered. William Sandqvist william@kth.se

Prepare the simulation

We need to have a number of windows open in order to follow the simulation.


Give commands in the Transcript window. Or click on the View menu.

```
VSIM> view objects
```

```
VSIM> view locals
```


```
VSIM> view source
```

```
VSIM> view wave -undock
```

 

Modelsim consists of "windows". It can be difficult to see everything at the same time. The **Zoom / Unzoom** enlarges the window. With the button **Dock / Undock** the window can be moved to any location. The **Close** button closes the window.

Signals in Wave-window

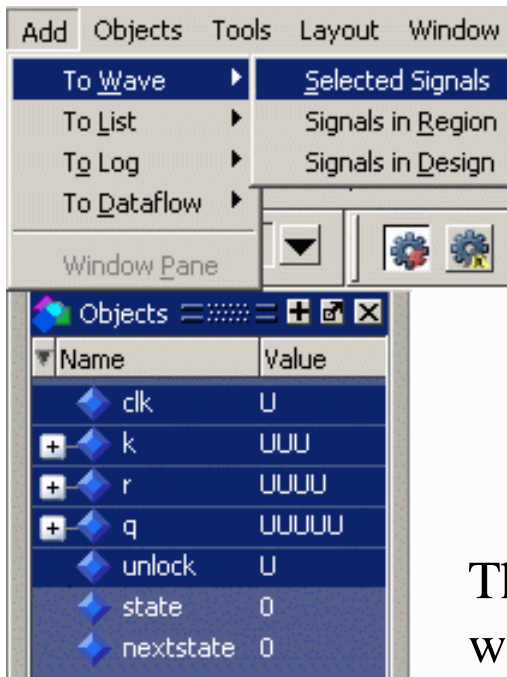

Signals in Wave

If you have many signals, it is a good idea to select the signals you are interested to join in the **Wave** window, but here we choose to follow all:


add wave *

There are several ways to add signals to the **Wave** window:

- Choose signals in **Object**-window and “drag and drop” the selection to the **Wave** window.
- Right click in the **Object**-window and choose **Add to Wave**.

Format, Radix, Hexadecimal

 The statevariable q has 32 different states, such a variable is easier to follow if it is defined as a hexadecimal digit, 00 ... 1F instead of a five bit binary number.



UUUUU is exchanged to **xx** in **Wave**-window. The other variables are best suited as a binary number.

Create stimuli


Stimuli. Input signals as clock pulses or keystrokes, are created with the command **force** in the **Transcript**-window.

```
Transcript
VSIM 3> force codelock/clk 1 0ns, 0 10ns -repeat 20ns
VSIM 4> force codelock/k 000
VSIM 5> force codelock/r 0000
VSIM 6> run 100ns
```


The default time resolution in **Wave** is nanoseconds, ns.
A suitable clock frequency for a code lock may however be as low as 5 Hz, or a cycle time of 0.2 sec. It will be easiest to use a unrealistic high clock frequency with a period of 20 ns.

force codelock/clk 1 0ns, 0 10ns -repeat 20ns

Generates clockpulses for ever.

 


Simulate key-press

 



```
force codelock/k 000
force codelock/r 0000
run 100ns
force codelock/k 001
force codelock/r 0001
run 30ns
```

```
force codelock/k 000
force codelock/r 0000
run 800ns
```

Find in the Wave-window

 

Add a Cursor. Search for "Signal Value".

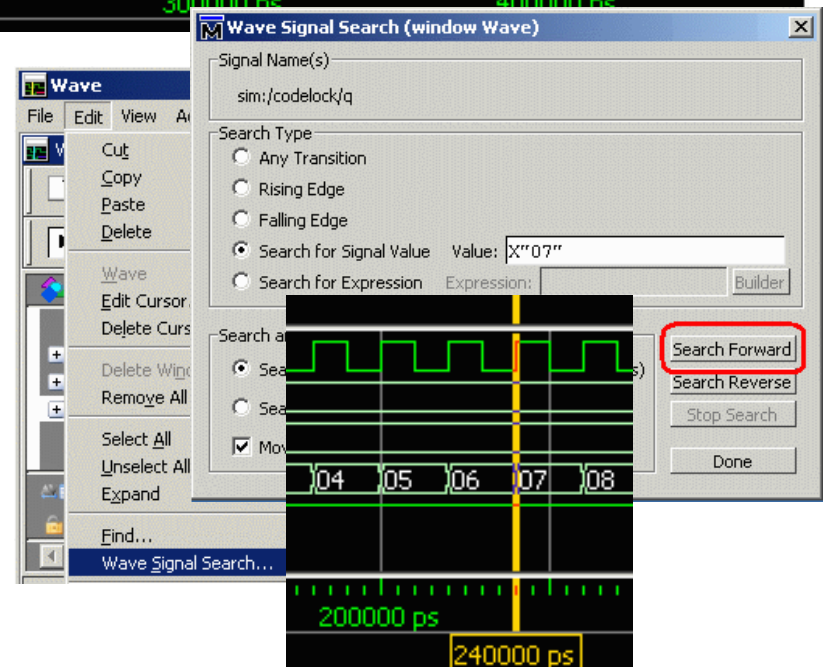 



Practice at home for the lab!

VHDL testbench

Template program - state diagram





  The lock opens when the key "1" is pressed and then released.



Keypad and Statecounter

  *Good choice of
data types makes
the code self-
explanatory!*



```
K: in std_logic_vector(1 to 3);
```

```
R: in std_logic_vector(1 to 4);
```

1 2 3
K = "001" bitvector

K(3) = '1' bit

1 2 3 4
R = "0001" bitvector

R(4) = '1' bit

4 3 2 1 0
Statecounter: q = "00001" bitvector
q(0) = '1' bit

lockmall.vhd

This code is given



```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_arith.all;

entity codelock is
    port( clk:      in  std_logic;
          K:        in  std_logic_vector(1 to 3);
          R:        in  std_logic_vector(1 to 4);
          q:        out std_logic_vector(4 downto 0);
          UNLOCK: out std_logic );
end codelock;
```

```
architecture behavior of codelock is
    subtype state_type is integer range 0 to 31;
    signal state, nextstate: state_type;
```

```
begin
    nextstate_decoder: -- next state decoding part
    process(state, K, R)
    begin
```


```
        case state is
            when 0 => if (K = "100" and R = "0001") then nextstate <= 1;
                       else nextstate <= 0;
                       end if;
            when 1 => if (K = "100" and R = "0001") then nextstate <= 1;
                       elsif (K = "000" and R = "0000") then nextstate <= 2;
                       else nextstate <= 0;
                       end if;
            when 2 to 30 => nextstate <= state + 1;
            when 31 => nextstate <= 0;
        end case;
    end process;
```

```
    debug_output: -- display the state
    q <= conv_std_logic_vector(state,5);
```

```
output_decoder: -- output decoder part
process(state)
begin
    case state is
        when 0 to 1 => UNLOCK <= '0';
        when 2 to 31 => UNLOCK <= '1';
    end case;
end process;
```

```
state_register: -- the state register part (the flipflops)
process(clk)
begin
    if rising_edge(clk) then
        state <= nextstate;
    end if;
end process;
end behavior;
```

It's easy to see that this is correct!

 

lockmall_with_error.vhd

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_arith.all;

entity codelock is
    port( clk:        in  std_logic;
          K:          in  std_logic_vector(1 to 3);
          R:          in  std_logic_vector(1 to 4);
          q:          out std_logic_vector(4 downto 0);
          UNLOCK: out std_logic );
end codelock;

architecture behavior of codelock is
    subtype state_type is integer range 0 to 31;
    signal state, nextstate: state_type;

begin
    nextstate_decoder: -- next state decoding part
    begin
        nextstate_decoder: -- next state decoding part
        process(state, K, R)
        begin
            case state is
                when 0 => if(((R(2)='0') and (R(3)='0') and (K(2)='0') and (K(3)='1')) and
                    ( not (( not ((K(1)='0') and (R(1)='0') and (R(4)='1')) and
                    ( not ((K(1)='1') and (R(1)='1') and (R(4)='0'))))))))
                    then nextstate <= 1;
                    else nextstate <= 0;
                    end if;
                when 1 => if(((R(2)='0') and (R(3)='0') and (K(2)='0') and (K(3)='1')) and
                    ( not (( not ((K(1)='0') and (R(1)='0') and (R(4)='1')) and
                    ( not ((K(1)='1') and (R(1)='1') and (R(4)='0'))))))))
                    then nextstate <= 1;
                    elsif (K = "000" and R = "0000") then nextstate <= 2;
                    else nextstate <= 0;
                    end if;
                when 2 to 30 => nextstate <= state + 1;
                when 31      => nextstate <= 0;
            end case;
        end process;

        debug_output: -- display the state
        q <= conv_std_logic_vector(state,5);

        output_decoder: -- output decoder part
        process(state)
        begin
            case state is
                when 0 to 1  => UNLOCK <= '0';
                when 2 to 31 => UNLOCK <= '1';
            end case;
        end process;

        state_register: -- the state register part (the flipflops)
        process(clk)
        begin
            if rising_edge(clk) then
                state <= nextstate;
            end if;
        end process;
    end behavior;
end codelock;
```

Now it's hard to see if this is correct or not?

lockmall_with_error.vhd

Means both expressions the same thing?

```
( K = "100" and R = "0001" )
```

Is this really the same thing?

```
(( (R(2)='0') and (R(3)='0') and (K(2)='0') and (K(3)='1')) and  
( not (( not ((K(1)='0') and (R(1)='0') and (R(4)='1')) and  
( not ((K(1)='1') and (R(1)='1') and (R(4)='0'))))))))
```

*Someone "promises" that the code is correct -
but how can you know if this is absolutely
true?*

Testbench

thank's to: *Francesco Robino*

tb_lockmall.vhd

`tb_lockmall.vhd`

We need to write a VHDL testbench

A test bench applications can test every possible key combinations and report if a problem occurs ...

It can automatically loop through all possible key-presses and report on whether the lock is trying to open.

There are $2^7 = 128$ possible key combinations and we would be completely exhausted if we tried to try them all by hand.

entity – a testbench has no ports

```
entity tb_codelock is  
    -- entity tb_codelock has no ports  
    -- because it's for simulation only  
end tb_codelock;
```


Some internal signals are needed

```
signal      clk : std_logic := '0';
signal      K_test : std_logic_vector(1 to 3);
signal      R_test : std_logic_vector(1 to 4);
signal prev_K_test : std_logic_vector(1 to 3);
signal prev_R_test : std_logic_vector(1 to 4);
signal      q : std_logic_vector(4 downto 0);
signal      unlock : std_logic;
```

Our codelock is used as a component

-- we use our codelock as a component

component codelock

port(clk : **in** std_logic;

 K : **in** std_logic_vector(1 **to** 3);


 R : **in** std_logic_vector(1 **to** 4);

 q : **out** std_logic_vector(4 **downto** 0);

 UNLOCK : **out** std_logic);

end component;

Generate a simulation clock

 


```
-- generate a simulation clock  
clk <= not clk after 10 ns;
```

Instantiation and signal mapping

```
-- instantiation of the device under test,  
-- mapping of signals  
inst_codelock:  
  codelock  
  port map (  
      clk => clk,  
      K  => K_test,  
      R  => R_test,  
      q  => q,  
      UNLOCK => unlock );
```

A nested loop creates keystrokes


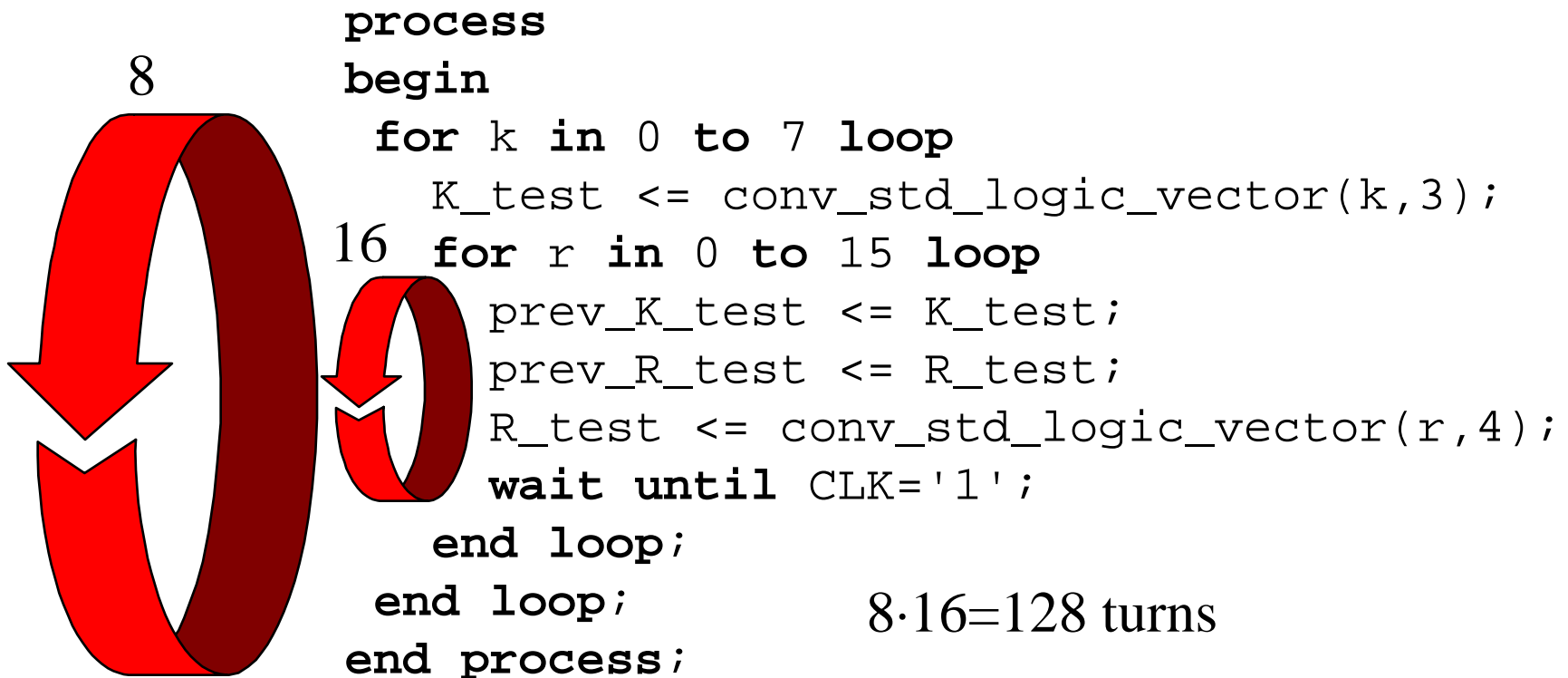


report, severity **note**, severity **error**

Tests if state $q = "00001"$ will be reached by any combination.

check:

```
process(q)
begin if ((q = "00001") and
          (prev_K_test = conv_std_logic_vector(1,3)) and
          (prev_R_test = conv_std_logic_vector(1,4)))
  then assert false report
    "Lock tries to open for the right sequence!"
    severity note;
  else if ((q = "00001"))
  then
    assert false report
    "Lock tries to open with the wrong sequence!"
    severity error;
  else report "Lock closed!" severity note;
  end if;
end if;
end process check;
```

  

Simulate and find the error!

What else besides pressing the "1" key
could open the lock?

?



