



**KTH Informations- och
kommunikationsteknik**

IE1204 Digital Design


L7: Combinational circuits, Introduction to VHDL

Masoumeh (Azin) Ebrahimi

KTH/ICT

mebr@kth.se

IE1204 Digital Design


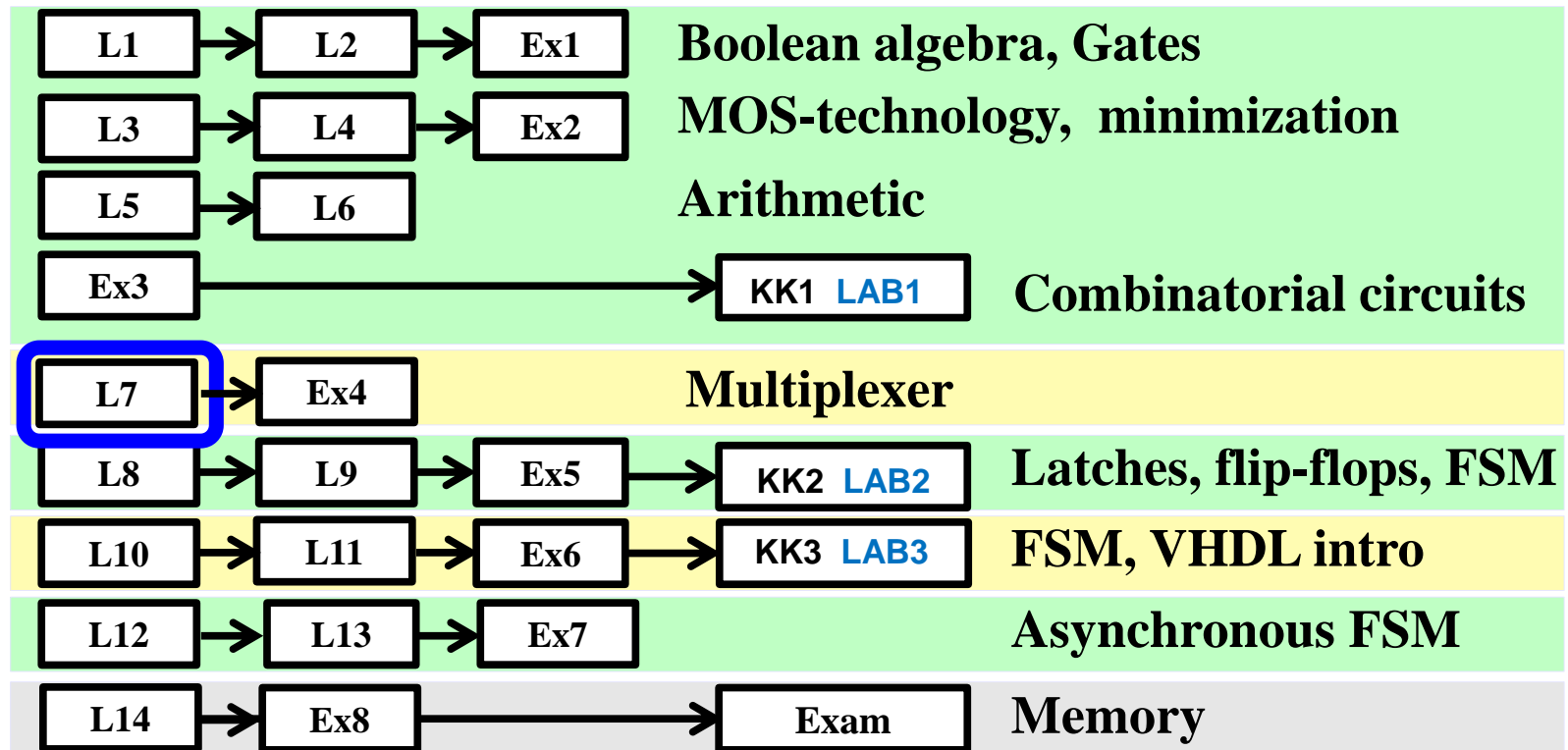


This lecture


- BV 318-339, 60-65, 280-291, 341-365

PLD (eg. PAL)

Technology: AND-OR array

  



Fan-in issue

 

Large programmable circuits

Therefore in order to be able to build large programmable circuits in CMOS technology there is a need for other techniques that are not based on gates with many inputs!

FPGA (eg. Cyclone II)

  


Typically **50000** logic elements

Technology : MUX tree

The multiplexer (MUX)

 
- The multiplexer can select which input you are going to connect to the output
- "If S then X, else Y"



$$Z = SX + \bar{S}Y$$

The multiplexer (MUX)

 
- The multiplexer can select which input you are going to connect to the output
- "If S then X, else Y"



$$Z = SX + \bar{S}Y$$

The multiplexer (MUX)

 - The multiplexer can select which input you are going to connect to the output
- "If S then X, else Y"




$$Z = SX + \bar{S}Y$$

Implementation of functions using MUXes

How can the following functions be implemented with a 2:1 multiplexer?

 - $Z = \bar{B}$ (INV)
- $Z = AB$ (AND)
- $Z = A + B$ (OR)
- $Z = A \oplus B$ (XOR)




$$Z = SX + \bar{S}Y$$

Quickie Question ...




- How to connect the inputs of the MUX in order to implement an inverter?***


Desired function: $z = \overline{x}$

 

Alt: A

 

Alt: B

 


Alt: C


Inverter implemented with a MUX

Specification:
 
```
if input = '1' then result <= '0';  
if input = '0' then result <= '1';
```


 
$$\begin{aligned} Z &= S \cdot X + \bar{S} \cdot Y = \\ &= x_0 \cdot 0 + \bar{x}_0 \cdot 1 = \bar{x}_0 \quad \text{NOT} \end{aligned}$$




Quickie Question ...




- How to connect the inputs of the MUX in order to implement an AND gate?***


Desired function: $z = xy$

 

Alt: A

 

Alt: B

 


Alt: C

AND implemented with a MUX

- Specification:


$x_1 \backslash x_0$	0	1
0	0	0
1	0	1

 


$$Z = SX + \bar{S}Y = x_1 \cdot \boxed{x_0} + \bar{x}_1 \cdot \boxed{0} = x_1 \cdot x_0$$

AND implemented with a MUX

- Specification:

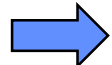


		x_0	
		0	1
x_1	0	0	0
	1	0	1

 


$$Z = SX + \bar{S}Y = x_1 \cdot \boxed{x_0} + \bar{x}_1 \cdot 0 = x_1 \cdot x_0$$

AND implemented with a MUX

- Specification:

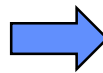

		x_0	
		0	1
x_1	0	0	0
	1	0	1

 


$$Z = SX + \bar{S}Y = x_1 \cdot x_0 + \bar{x}_1 \cdot \boxed{0} = x_1 \cdot x_0$$

OR implemented with a Mux

- Specification:

x_1	x_0	
	0	1
0	0	1
1	1	1

 


$$\begin{aligned} Z &= x_1 x_0 + \bar{x}_1 x_0 + x_1 \bar{x}_0 = \\ &= \{SX + \bar{S}Y\} = x_1 (x_0 + \bar{x}_0) + \bar{x}_1 \cdot x_0 = \\ &= x_1 \cdot 1 + \bar{x}_1 \cdot x_0 \end{aligned}$$




OR implemented with a Mux

- Specification:

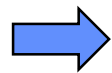

	x_0	0	1
x_1	0	0	1
	1	1	1

 


$$\begin{aligned} Z &= x_1 x_0 + \bar{x}_1 x_0 + x_1 \bar{x}_0 = \\ &= \{SX + \bar{S}Y\} = x_1 (x_0 + \bar{x}_0) + \bar{x}_1 \cdot x_0 = \\ &= x_1 \cdot 1 + \bar{x}_1 \cdot \boxed{x_0} \end{aligned}$$

XOR implemented with a Mux

- Specification:

		x_0		0	1
x_1	0	0	1	0	1
	1	1	0	0	1

 


$$\begin{aligned} Z &= SX + \bar{S}Y = \\ &= x_1 \cdot \bar{x}_0 + \bar{x}_1 \cdot x_0 = x_1 \oplus x_0 \end{aligned}$$

XOR implemented with a Mux

- Specification:

→


		x_0	
	x_1	0	1
0		0	1
1		1	0

 


$$\begin{aligned} Z &= SX + \bar{S}Y = \\ &= x_1 \cdot \boxed{\bar{x}_0} + \bar{x}_1 \cdot x_0 = x_1 \oplus x_0 \end{aligned}$$

XOR implemented with a Mux

- Specification:

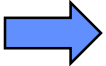


	x_0	0	1
x_1	0	0	1
	1	1	0

 


$$\begin{aligned} Z &= SX + \bar{S}Y = \\ &= x_1 \cdot \bar{x}_0 + \bar{x}_1 \cdot \boxed{x_0} = x_1 \oplus x_0 \end{aligned}$$

Hierarchy of MUXes

 


Hierarchy of MUXes

 

Implementation of larger functions with MUXes


		xy			
		00	01	11	10
z	0	1	1	0	0
	1	0	1	1	0

$$f = \bar{z}\bar{x} + \bar{x}y + zy$$

 


Implementation of larger functions with MUXes

 Choose any of the inputs as address inputs ...



$$f = \bar{z}\bar{x} + \bar{x}y + zy$$

 



... And minimize/implement function for each input.
Draw new Karnaugh diagrams if necessary.

An (n + 1)-input function can be implemented with a MUX that has n select inputs!

Mapping into MUXes:

Shannon decomposition (BV 6.1.2)

  - Any Boolean function $f(x_n, \dots, x_1, x_0)$ can be partitioned as
$$f(x_n, \dots, x_1, \boxed{x_0}) = x_0 f_1(x_n, \dots, x_1, 1) + \overline{x_0} f_0(x_n, \dots, x_1, 0)$$
- The function can then be implemented with a multiplexer





Mapping into MUXes:

Shannon decomposition (BV 6.1.2)

- Any Boolean function $f(x_n, \dots, x_1, x_0)$ can be partitioned as
  
$$f(x_n, \dots, x_1, x_0) = x_0 f_1(x_n, \dots, x_1, 1) + \overline{x_0} f_0(x_n, \dots, x_1, 0)$$
- The function can then be implemented with a multiplexer





Mapping into MUXes:

Shannon decomposition (BV 6.1.2)

- Any Boolean function $f(x_n, \dots, x_1, x_0)$ can be partitioned as

  
$$f(x_n, \dots, x_1, x_0) = x_0 f(x_n, \dots, x_1, 1) + \bar{x}_0 f(x_n, \dots, x_1, 0)$$
- The function can then be implemented with a multiplexer



Mapping to MUXes: Shannon decomposition

- Any Boolean function $f(x_n, \dots, x_1, x_0)$ can be decomposed (recursively) as
 
$$\begin{aligned} f(x_n, \dots, x_1, x_0) &= x_0 f_1(x_n, \dots, x_1, 1) + \bar{x}_0 f_0(x_n, \dots, x_1, 0) \\ &= x_1 x_0 f_{11}(x_n, \dots, x_2, 1, 1) + x_1 \bar{x}_0 f_{10}(x_n, \dots, x_2, 1, 0) \\ &\quad + \bar{x}_1 x_0 f_{01}(x_n, \dots, x_2, 0, 1) + \bar{x}_1 \bar{x}_0 f_{00}(x_n, \dots, x_2, 0, 0) \end{aligned}$$



Proof


$$\overbrace{f(x_n, \dots, x_1, x_0)}^{\text{Left-hand side}} = \underbrace{x_0 \cdot f(x_n, \dots, x_1, 1)}_{\text{Left term}} + \underbrace{\bar{x}_0 \cdot f(x_n, \dots, x_1, 0)}_{\text{Right term}} \quad \overbrace{\hspace{10em}}^{\text{Right-hand side}}$$

- Right-hand side:
 - If $x_0 = 1$ then the right term is zero. Then f is equal to the left term.
 - If $x_0 = 0$, the left term is zero. Then f is equal to the right term.
- Left-hand side:
 - if $x_0 = 1$, then f is equal to $f(x_n, \dots, x_1, 1)$ (= left term on the right-hand side)
 - if $x_0 = 0$ then f is equal to $f(x_n, \dots, x_1, 0)$ (= right term in the right-hand side)
- Left-hand side = Right-hand side


Mux circuits




		yz			
		00	01	11	10
x	0	0	1	0	1
	1	1	0	1	0

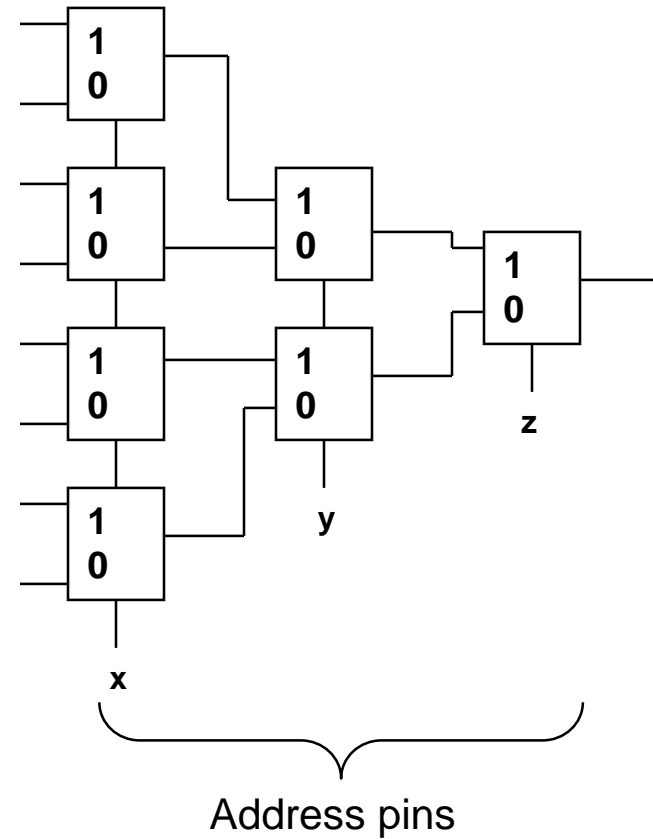


Mux circuits

 

**But this is a memory
(ROM, RAM ...)**


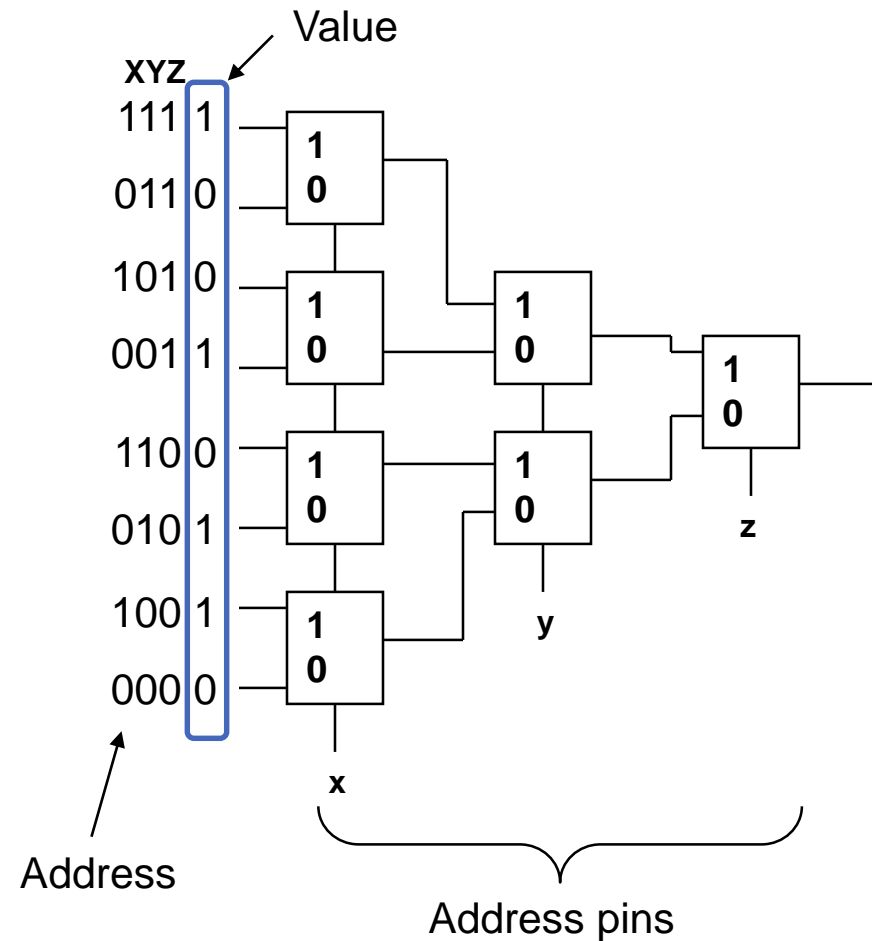


Look-up tables (LUT)

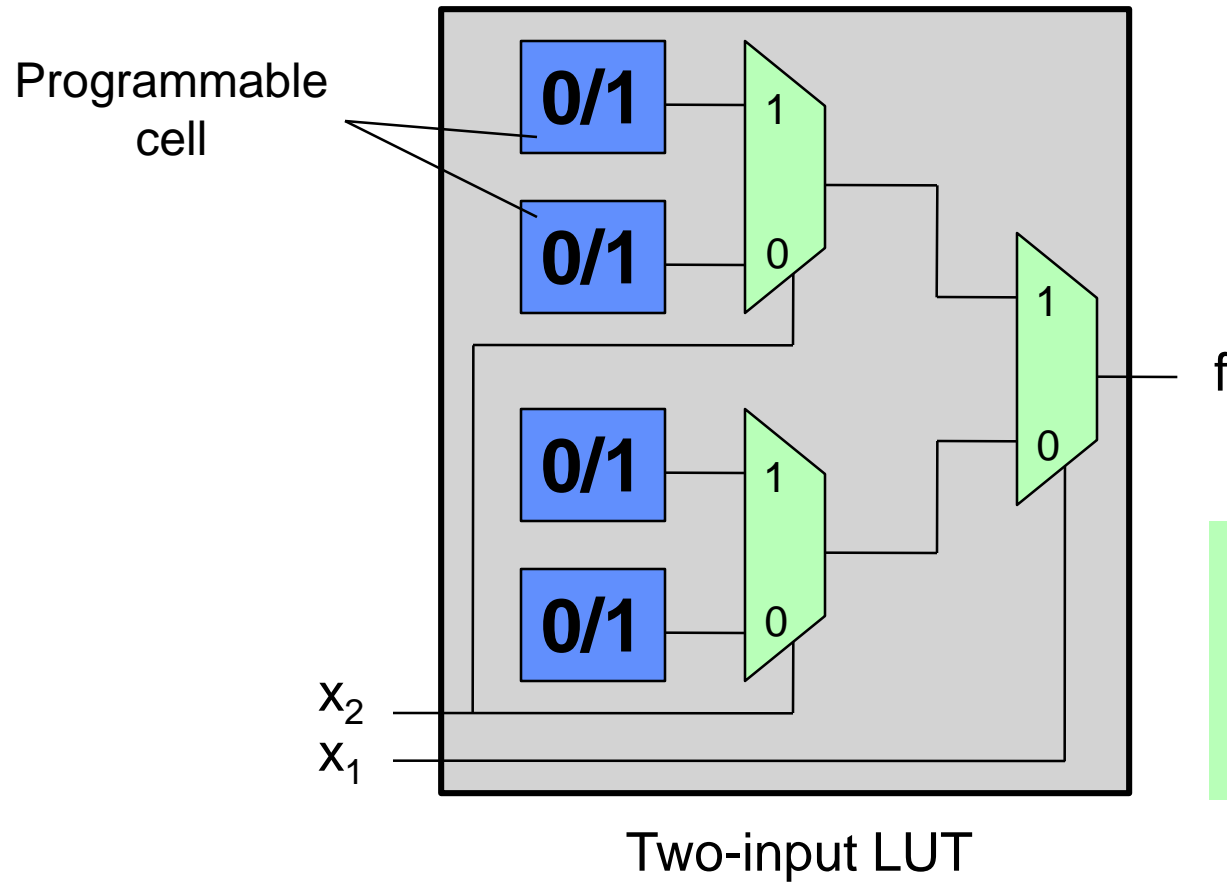


A LUT with n inputs can realize all combinational functions with up to n inputs

Example: XOR gate

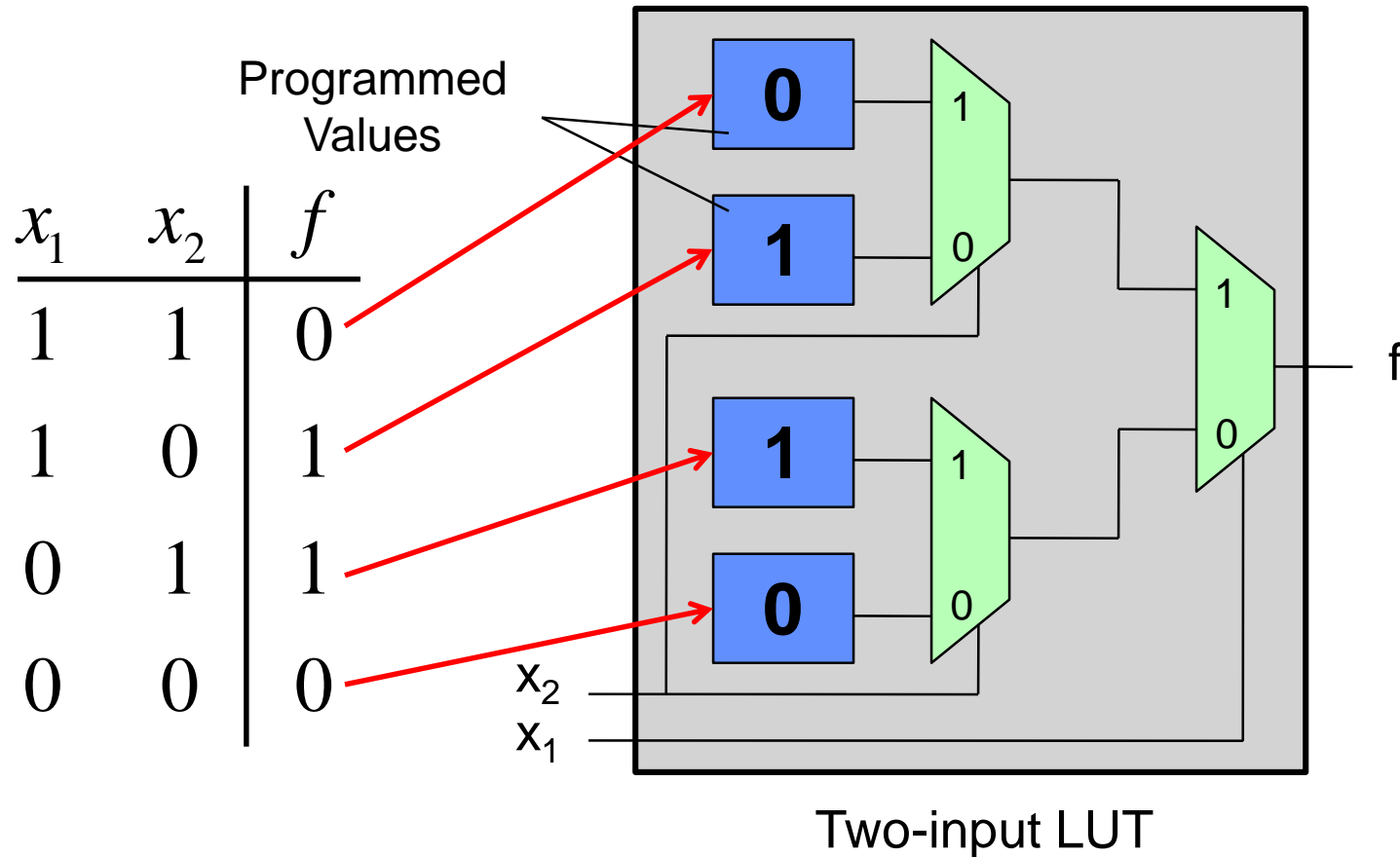 

A simple FPGA cell

 - The simplest FPGA cell consists of a single table (e.g. Look-Up-Table - LUT), a D flip-flop and a bypass MUX.



One way to identify functions...

$$f(x_3, x_2, x_1, x_0) = "0110100110010110" = f_{6996(H)}$$

MSB

LSB

Bit # 15

Bit # 1

Bit # 0

		$x_1 x_0$	00	01	11	10
x_3	0	0	0	1	3	2
x_2	0	0	0	1	3	2
	0	1	4	5	7	6
	1	1	12	13	15	14
	1	0	8	9	11	10

The functions that are stored in a LUT are usually numbered after the number that is made up of the 1's in the truth table / Karnaugh map.


n inputs $\Rightarrow 2^{(2^n)}$ possible different Boolean functions

LUT function number

$$f(x_3, x_2, x_1, x_0) = "0110100110010110" = f_{6996}$$

$x_1 x_0$					
x_3	x_2	00	01	11	10
	0	0	1	3	2
	1	4	5	7	6
	0	1	0	1	0
	1	12	13	15	14
	0	0	1	0	1
	1	8	9	11	10
	0	1	0	1	0

Odd parity

 


$$f_{6996} = x_3 \oplus x_2 \oplus x_1 \oplus x_0$$


With a LUT, all functions are realized in the same way, so all of them have the same cost

Decoder

 - Mostly used as address decoders
- Only one output is active when the 'enable' (En) signal is active
- The active output is selected by a_1a_0



En	a_1	a_0	y_0	y_1	y_2	y_3
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1
0	-	-	0	0	0	0



 


2-to-4 decoder


Demultiplexer

- The demultiplexer has basically the same function as the decoder, but it is drawn differently
- The input I is connected to a selected output

I	a_1	a_0	y_0	y_1	y_2	y_3
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1
0	-	-	0	0	0	0

   

Read-Only Memory

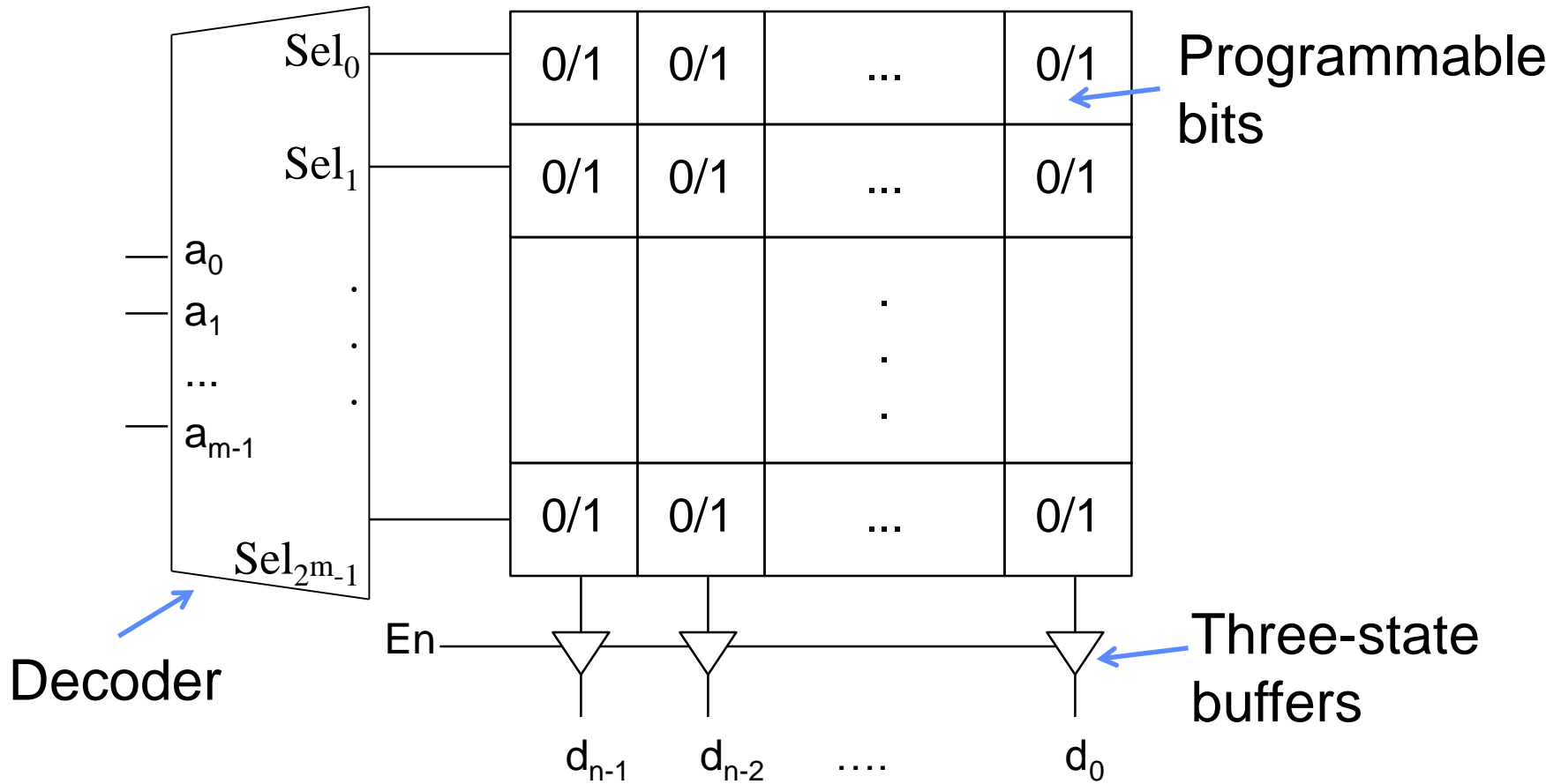


Encoders

- Encoder has the opposite function to a decoder, i.e. it translates 2^N bit input into an N -bit code.
 - The information is greatly reduced



w_0	w_1	w_2	w_3	y_1	y_0
1	0	0	0	0	0
0	1	0	0	0	1
0	0	1	0	1	0
0	0	0	1	1	1

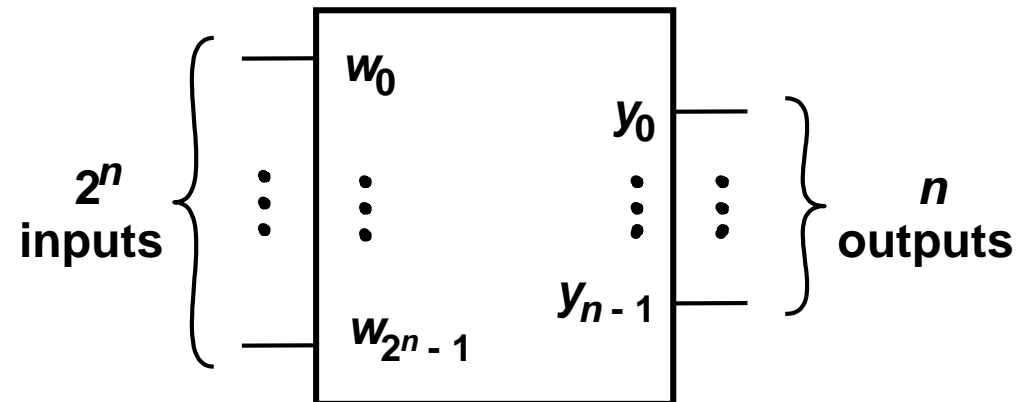

Priority Encoder

- A Priority Encoder gives back the address of the input with the lowest (or highest) indices that are set to 1 (or 0 depending on what you are looking for)
- If all inputs are 0, the output $z = 0$, else $z = 1$



w_0	w_1	w_2	w_3	z	y_1	y_0
1	-	-	-	1	0	0
0	1	-	-	1	0	1
0	0	1	-	1	1	0
0	0	0	1	1	1	1
0	0	0	0	0	-	-

The output is well-defined even if several inputs are active at the same time.

Overview




Multiplexer

  


Encoder

Demultiplexer

 


↔
Equivalent

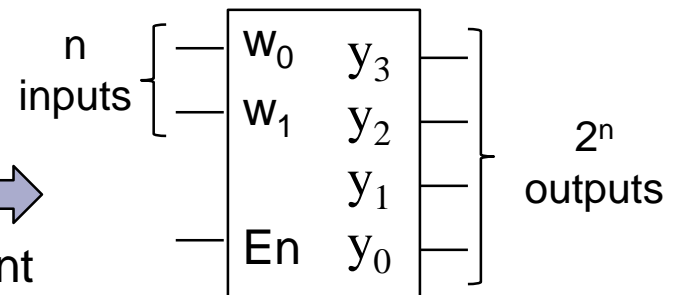

Decoder


Code converters

 - A code converter translates from one code to another. Typical examples are:
 - Binary to BCD (Binary-Coded Decimal)
 - Binary to Gray code
 - 7-4-2-1 code
 - BCD to seven-segment decoder



A variant of the 7-4-2-1 code is used today to store the bar code


BCD-to-seven segment decoder

 

w_3	w_2	w_1	w_0	a	b	c	d	e	f	g
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1

- BCD-to-7 segment decoder consists of 7 different combinatorial circuits, one for each segment
- To get optimal circuits, all 7 functions have to be minimized simultaneously so that common logic is shared

Disadvantage of binary codes

 

Binary code, adjacent code words:

1-2 double change

3-4 triple change

5-6 double change

7-8 quadruple change!

9-A double change

B-C quadruple change!

D-E double change


F-0 quadruple change!

Can two bits change at exactly the same time?


- For safe data registration use Gray code
- For data processing use binary code

Gray code

 - By changing the order of the codewords in a binary code, one constructs codes in which no more than one bit is changing at a time
- Such codes are called Gray codes



Conversion between binary and Gray

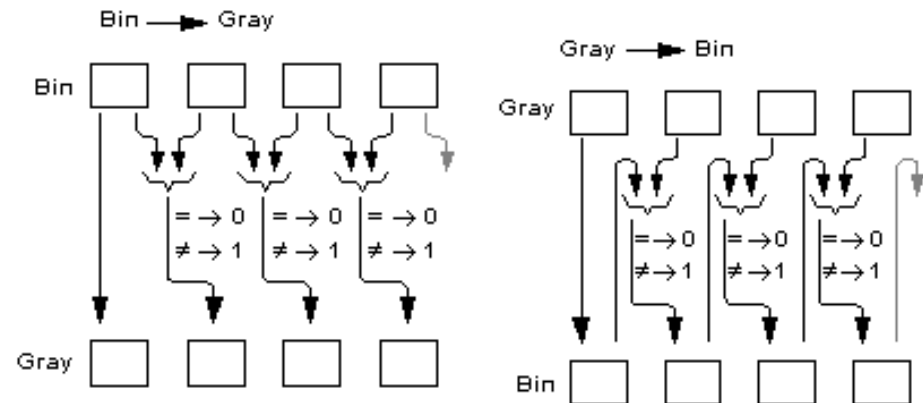

Binary \rightarrow Gray:

If Binary bit b_n and bit b_{n-1} are *different*, the Gray code bit g_{n-1} is "1", else "0".

Gray \rightarrow Binary (most common transformation direction):

If Binary bit b_n and Gray code bit g_{n-1} are *different* the Binary bit b_{n-1} is "1", else "0".


Logic for Gray to Binary conversion

XOR-gate is "1" if its inputs are *different*!

4 bit code converter
Gray code to Binary code

	Binär-kod	Gray-kod		Binär-kod	Gray-kod
0	0000	0000	8	1000	1100
1	0001	0001	9	1001	1101
2	0010	0011	10	1010	1111
3	0011	0010	11	1011	1110
4	0100	0110	12	1100	1010
5	0101	0111	13	1101	1011
6	0110	0101	14	1110	1001
7	0111	0100	15	1111	1000

Tabell med Binärkod och Graykod.

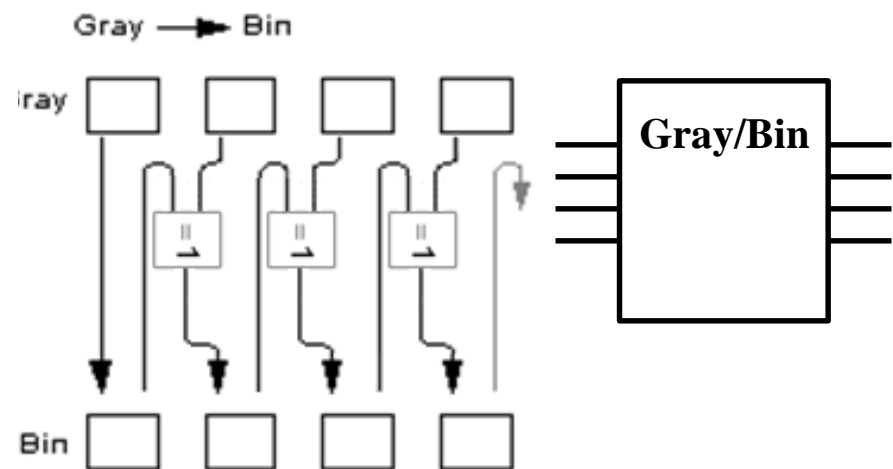


Logic for Gray to Binary conversion

XOR-gate is "1" if its inputs are *different*!

	Binär-kod	Gray-kod		Binär-kod	Gray-kod
0	0000	0000	8	1000	1100
1	0001	0001	9	1001	1101
2	0010	0011	10	1010	1111
3	0011	0010	11	1011	1110
4	0100	0110	12	1100	1010
5	0101	0111	13	1101	1011
6	0110	0101	14	1110	1001
7	0111	0100	15	1111	1000

Tabell med Binärkod och Graykod.

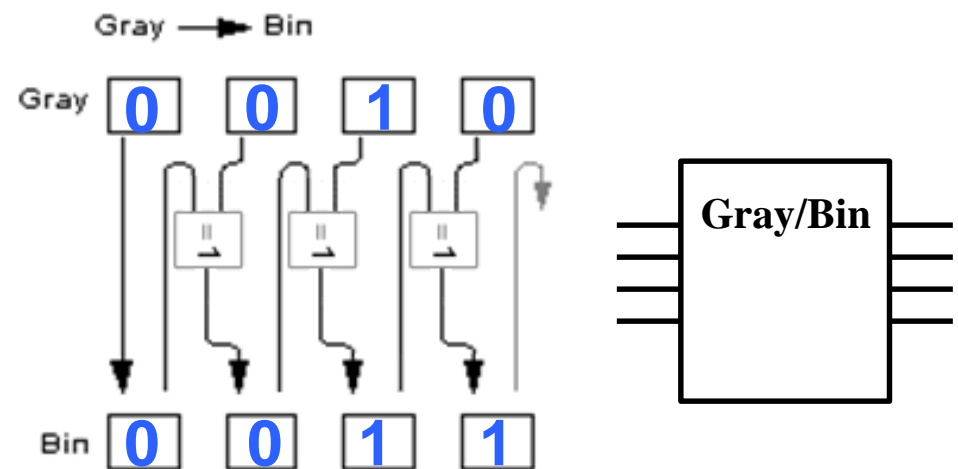4 bit code converter
Gray code to Binary code



Introduction to VHDL

- VHDL is a language used to specify the hardware
 - HDL - VHSIC Hardware Description Language
 - VHSIC - Very High Speed Integrated Circuit
 - Used mostly in Europe
- Verilog is another language used to specify the hardware
 - Used mostly in the United States

Why VHDL?


- VHDL is used to
 - Verifies that you have connected right by simulating the circuit
 - describes the large structures in a simple way and then generates the circuit by synthesis
 - allows for structured descriptions of a circuit

VHDL increases the level of abstraction!

Types of VHDL code

- There are two types of VHDL code
 - **VHDL for synthesis:** The code is used as an input to a synthesis tool which converts it into an implementation (for example FPGA or ASIC)
 - **VHDL modeling and simulation** code is used to describe a system at an early stage. Since the code can be simulated so you can check whether the intended functionality is correct


Entity (FA)

 

```
ENTITY fulladder IS
    PORT( A,B,Cin :  IN  STD_LOGIC;
          S,Cout   :  OUT STD_LOGIC);
END fulladder;
```

The *entity* describes the ports to the outside of the circuit.
The circuit as a block.

Architecture (FA)

 

ARCHITECTURE behave OF fulladder IS
BEGIN

$S \leq A \text{ xor } B \text{ xor } C_{in};$

$C_{out} \leq (A \text{ and } B) \text{ or } (A \text{ and } C_{in}) \text{ or } (B \text{ and } C_{in});$

END behave;

Architecture describes the function inside the circuit.

VHDL port

- PORT declaration establishes *interface* between the component and the outside world
- A port declaration contains three things:
 - The **name** of the port
 - The **direction** of the port
 - Port's **datatype**

- Example:

```
ENTITY test IS  
    PORT ( name : direction data_type);  
END test;
```


The most common data types

- Scalars (single-variable signals)
 - Bit ("0", "1")
 - Std_logic ('U', '0', '1', 'X', 'Z', 'L', 'H', 'W', '-')
 - Integer
 - Real
 - Time
- Vectors (many-variable signals)
 - BIT_VECTOR - vector of bits
 - STD_LOGIC_VECTOR - vector of std_logic

VHDL Example: 4/1 MUX


```
LIBRARY ieee;  
USE ieee.std_logic_1164.ALL;
```
 
```
ENTITY Multiplexer_41 IS  
  PORT (ce_n: IN std_logic; -- Chip Enable (active low)  
        data_in: IN std_logic_vector(3 DOWNTO 0);  
        sel: IN std_logic_vector(1 DOWNTO 0);  
        data_out: OUT std_logic); -- TriState Output  
END ENTITY Multiplexer_41;
```



VHDL Example: 4/1 MUX (cont.)

```
ARCHITECTURE RTL OF Multiplexer_41 IS
BEGIN
  PROCESS(ce_n, data_in, sel)
  BEGIN
    IF ce_n = '1' THEN
      data_out <= 'Z';
    ELSE
      CASE sel is
        WHEN "00"=> data_out <= data_in(0);
        WHEN "01"=> data_out <= data_in(1);
        WHEN "10"=> data_out <= data_in(2);
        WHEN "11"=> data_out <= data_in(3);
        WHEN OTHERS => null;
      END CASE;
    END IF;
  END PROCESS;
END ARCHITECTURE RTL;
```

 

More on VHDL

- The study material on synthesis shows a number of VHDL constructs and the resulting hardware
- The following slides contain extra material
The book gives many examples and detailed explanations of VHDL

Synthesis tool Quartus

- The course textbook contains a CD with the synthesis tool, Quartus
- You will use Quartus in Lab 3

Summary

- Implementation of functions with MUXes
 - Shannon decomposition
- Look-up tables, ROM
- Decoder, encoder, code converters
- Introduction to VHDL
- Next lecture: BV pp. 383-418, 469-471


VHDL (Not part of the exam)



Entity (XOR)

- An entity describes a component's *interface* with the outside world
- PORT-declaration indicates if it is an input or an output
- An *Entity* is a symbol of a component.

 
```
ENTITY xor_gate IS  
    PORT (x, y: IN BIT;  
          q: OUT BIT);  
END xor_gate;
```



Use English names for variable names in the code!

Architecture (XOR)

 - An *architecture* describes the operation of a component
- **An entity can have many architectures**, but only one can be active at a time
- An architecture corresponds to the component diagram or behavior



Code for Simulation

```
ARCHITECTURE behavior OF xor_gate IS
BEGIN
    q <= a xor b after 5 ns;
End behavior;
```

Signal declaration

Signal-declaration is used inside architectures to declare internal (local) signals:

```
signal a, b, c, d: bit;
```

```
signal a, b, sum: bit_vector (31 downto 0);
```

Signal-assignment is used to describe the behavior:

```
sum <= a + b; signal assignment without delay
```

Sequential vs Parallel Code


- There are two types of code execution in VHDL: sequential and parallel
 - Sequential code describes the hardware from a "programmer's" point of view and it is executed in the order which is defined
 - The parallel code is executed regardless of the order. It is *asynchronous*.

VHDL description styles

- Sequential (Behavioral)
 - similar to how to write desktop applications
- Data Flow (RTL)
 - Concurrent assignments
- Structural
 - similar to how to connect components

Sequential style


XOR gate

 

```
Process (x, y)
begin
    if (x /= y) then
        q <= '1';
    else
        q <= '0';
    end if;
end process;
```

Data flow style

XOR gate

 


```
q <= a xor b;
```

- Or in behavioral dataflow style

```
q <= '1' When a /= b else "0";
```

Structural style

 

```
u1: not_gate port map (x,xi);  
u2: not_gate port map (y,yi);  
u3: and_gate port map (xi,y,t3);  
u4: and_gate port map (yi,x,t4);  
u5: or_gate port map (t3,t4,q);
```


Structural style

Component declaration

- A component must be declared before it can be used

```
ARCHITECTURE Test OF test_entity
  COMPONENT and_gate
    Port (in1, in2: IN BIT;
          out1: BIT OUT);
  END COMPONENT;
... more statements...
```



- It is necessary, unless it is not in a library somewhere

Structural style


Component instantiation

- Component *instantiation ring* connects the component interface with the signals in the architecture
  
```
ARCHITECTURE Test OF test_entity
  COMPONENT and_gate
    Port (in1, in2: IN BIT;
          out1: BIT OUT);
  END COMPONENT;
  SIGNAL S1, S2, S3: BIT;
BEGIN
  Gate1: and_gate PORT MAP (S1, S2, S3);
END test;
```



Generate

 


- Generate-statement couples many similar elements

```

ENTITY adder IS
    GENERIC (N: integer)
    PORT (a, b: IN bit_vector (N-1 downto 0);
          sum: OUT bit_vector (N-1 downto 0));
END adder;

ARCHITECTURE OF structural adder IS
    COMPONENT full_adder
        PORT (a, b, cin: IN bit; cout, s: OUT bit);
    END COMPONENT;
    signal c: bit_vector (N-2 downto 0);
BEGIN
    G0: for i in 1 to N-2 Generate
        U0: full_adder PORT MAP (a (i), b (i), c (i-1), c (i), p (i));
    end Generate; - G0
    U0: full_adder PORT MAP (a(0), b(0), '0', c(0), p(0));
    UN: full_adder PORT MAP (a(n-1), b(n-1), c(n-2), OPEN, s(n-1));
END structural;
    
```

Generate n-bit adder

 

Five lines of code generates the ripple-carry n-bit adder from Lecture 5!

The test bench stimuli 1

The ENTITY is empty!

```
ENTITY testbench IS END testbench;
```

```
ARCHITECTURE xor_stimuli_1 of testbench IS
```

```
  COMPONENT xor_gate
```

```
    PORT(x,y:IN bit; q:OUT bit);
```

```
  END COMPONENT;
```

```
  signal x,y,ut1:bit;
```

```
BEGIN
```

```
  x <= not(x) after 10 ns;
```


```
  y <= not(y) after 20 ns;
```

```
  U1:xor_gate PORT MAP (x,y,ut1);
```

```
END example;
```

The circuit under test is used as a component of the test bench program

Here are the test signals generated

 

The test bench stimuli 2

```
ENTITY testbench IS END testbench;

ARCHITECTURE xor_stimuli_2 of testbench IS
    COMPONENT xor_gate
        PORT(x,y:IN bit;q:OUT bit);
    END COMPONENT;
    signal x,u1,u2,u3:bit; -- Endast en in-signal
    for U1:xor_gate use entity work.xor_gate(behave);
    for U2:xor_gate use entity work.xor_gate(data_flow);
    for U3:xor_gate use entity work.xor_gate(structural);
BEGIN
    x <= not(x) after 10 ns;
    U1:xor_gate PORT MAP (x,x,ut1);
    U2:xor_gate PORT MAP (x,x,ut2);
    U3:xor_gate PORT MAP (x,x,ut3);
END example;
```

Test bench

A test bench can mark when the desired events occur during the execution.



Or mark when unwanted events occur



The result of a run with a test bench can be saved in a file, as a proof that everything is ok - or as a troubleshooting aid if it did not go well.