

Vending machine

Design-exempel by *Ingo Sander*




William Sandqvist william@kth.se



System Control

We will design the block,
System Control

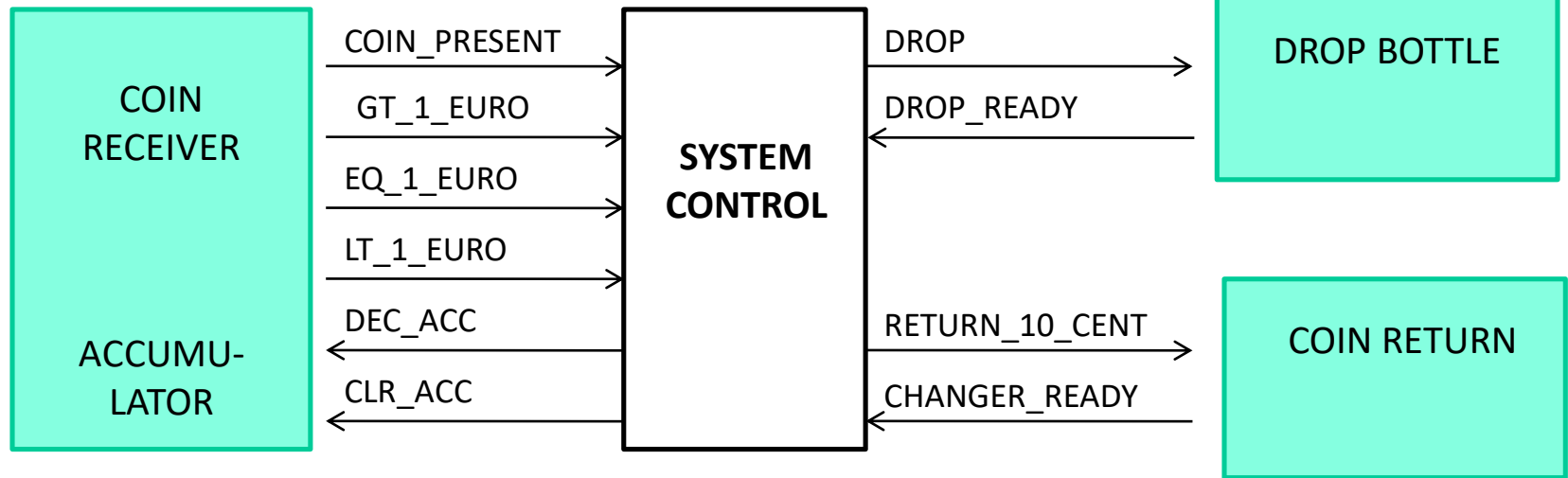


Return only 10 cents coin.



Coin Reciever

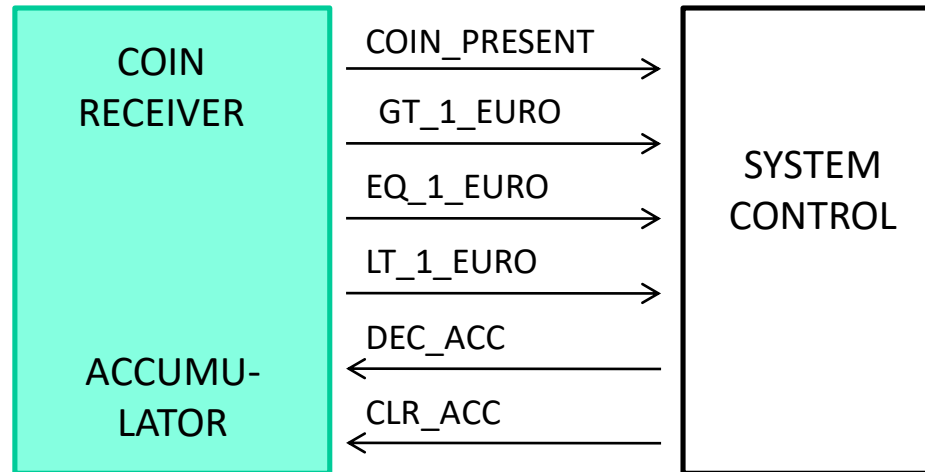
The **System Control** unit controls a number of subsystems from other suppliers. **Coin Reciever. Drop Bottle. Coin Return.**



An **ACCUMULATOR** counts up the amount of paid coins.


- Signal **COIN_PRESENT** indicates that there are coins and the "amount" is indicated by the signals **GT_1_EURO**, **EQ_1_EURO**, **LT_1_EURO**.
- With the signals **DEC_ACC** and **CLR_ACC** the systemcontrol unit can reduce the amount by 10 cents, or reset the **ACCUMULATOR**.

Coin Return

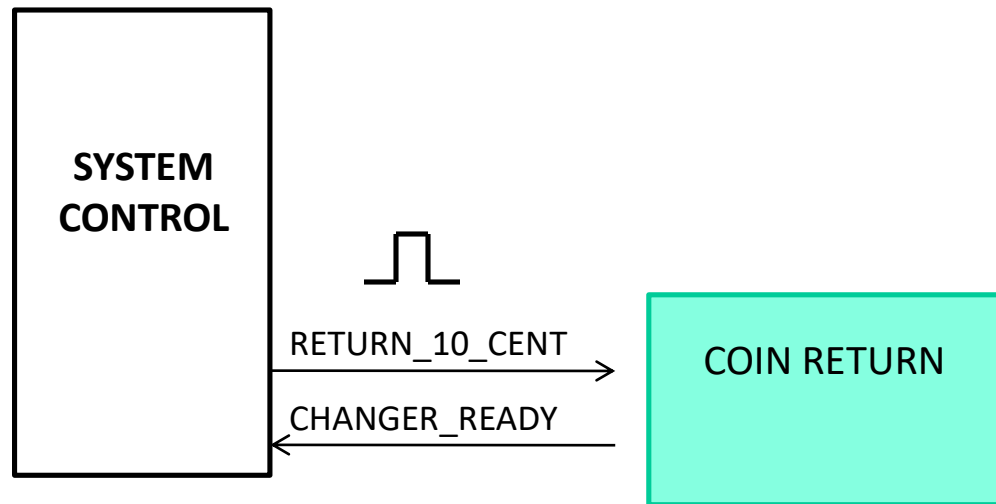


With a pulse on **RETURN_10_CENT** the coin return unit will eject 10 cent, and signal **CHANGER_READY** when this is done and the unit is ready for the next command.

Drop Bottle

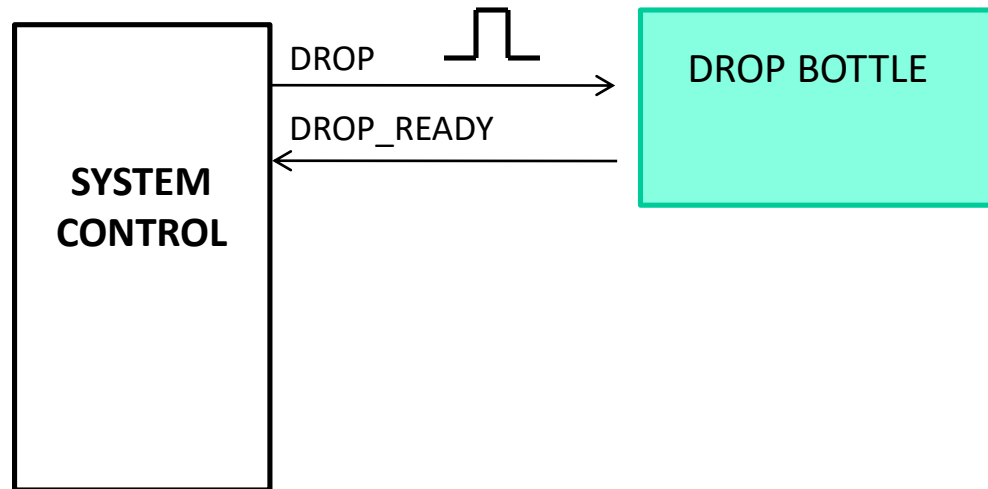

With a pulse on DROP the drop bottle unit will eject a bottle, and signals DROP_READY when this is done and the unit is ready for the next command.


Block diagram

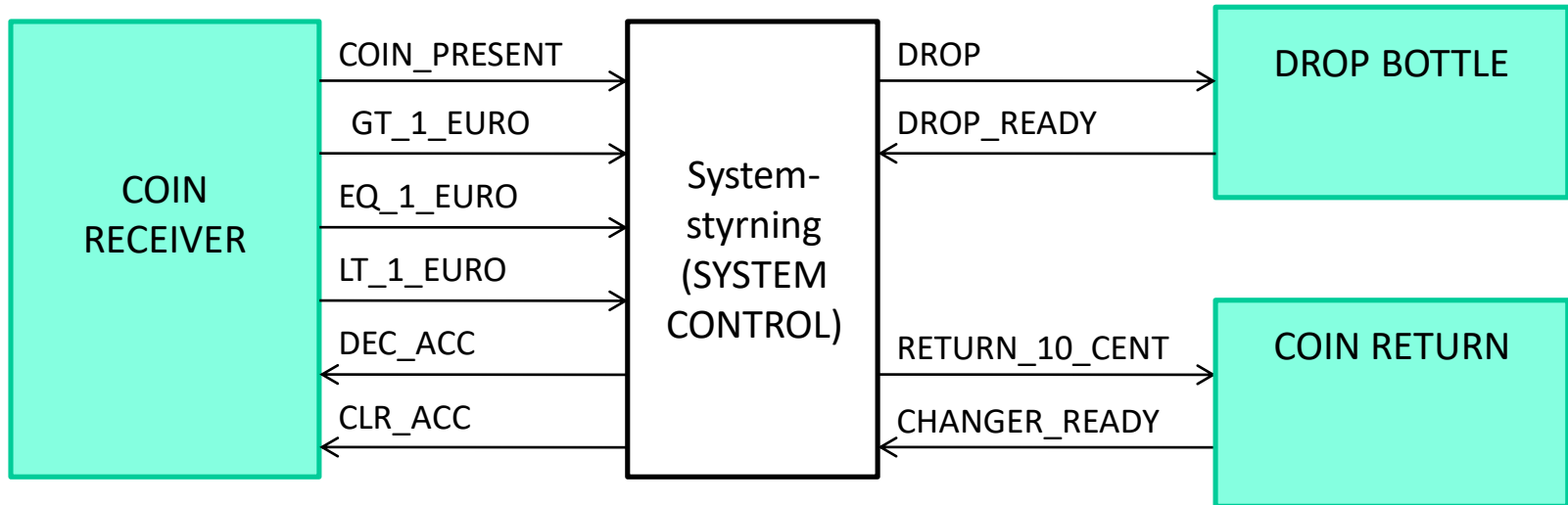

- Signal properties


- DROP_READY is active for a clockperiod after the bottle is ejected
- CHANGER_READY is active for a clockperiod after a 10 Cent coin is ejected
 - Because of the mechanical properties the following signals are active and inactive for several clock periods:
 - COIN_PRESENT (active for several clockperiods after the coin is inserted)
 - DROP_READY (active for several clockperiods at bottle ejection)
 - CHANGER_READY (inactive for several clockperiods at coin ejection)

Use a Moore-machine

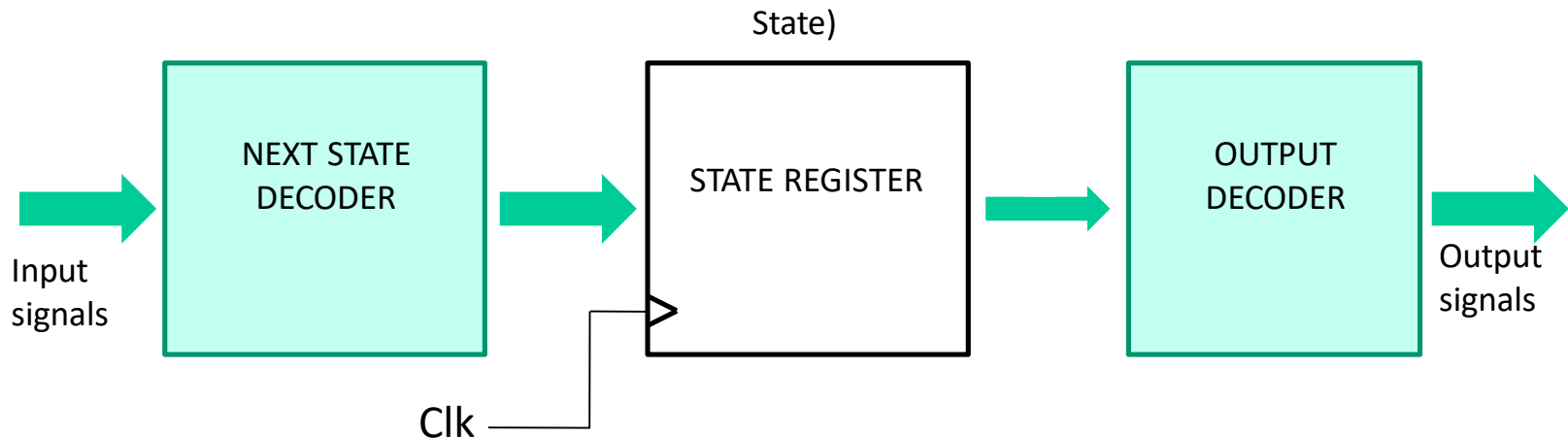


- Construction of a state machine for the controller of a vending machine
- Assumptions
 - Moore-Machine
 - - Stateregister implemented with D-flip-flops

Function diagram for vending machine

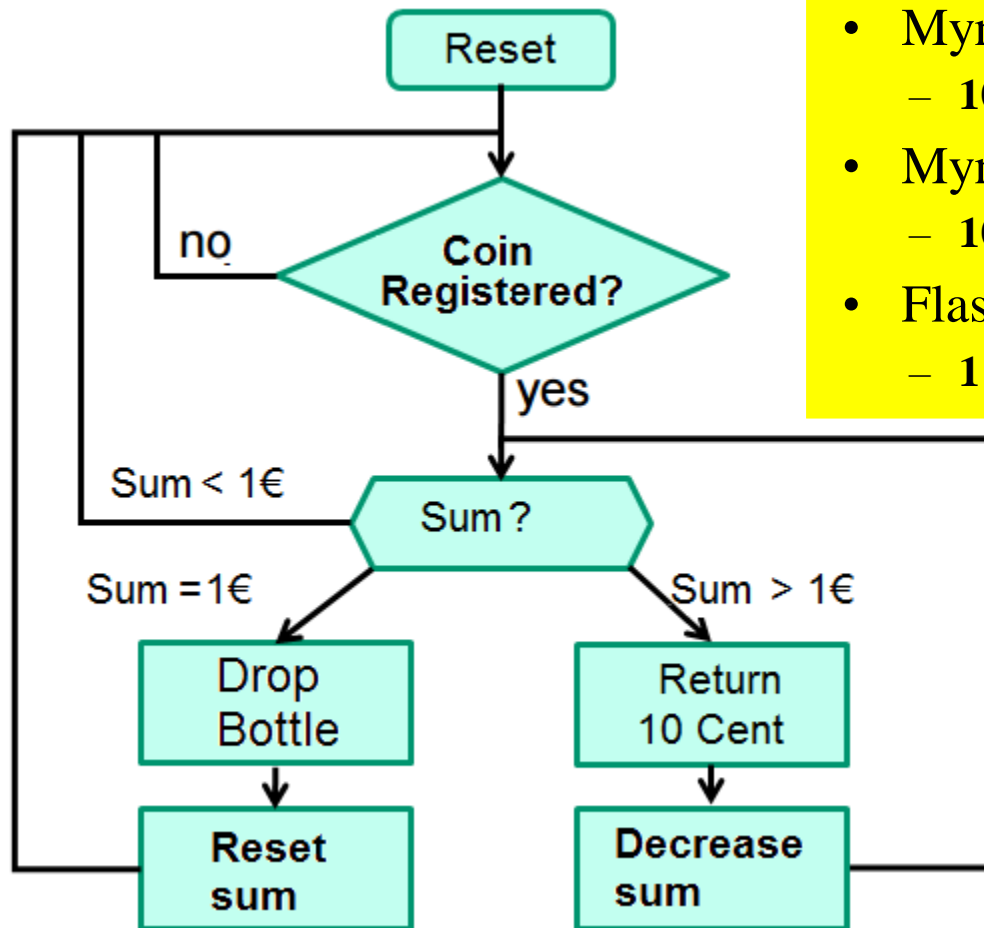


- Myntinkast
 - 10 Cent, 50 Cent, 1 Euro
- Myntutkast
 - 10 Cent
- Flaskpris
 - 1 Euro


State diagram

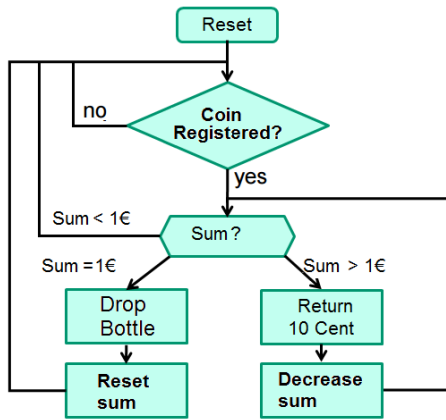

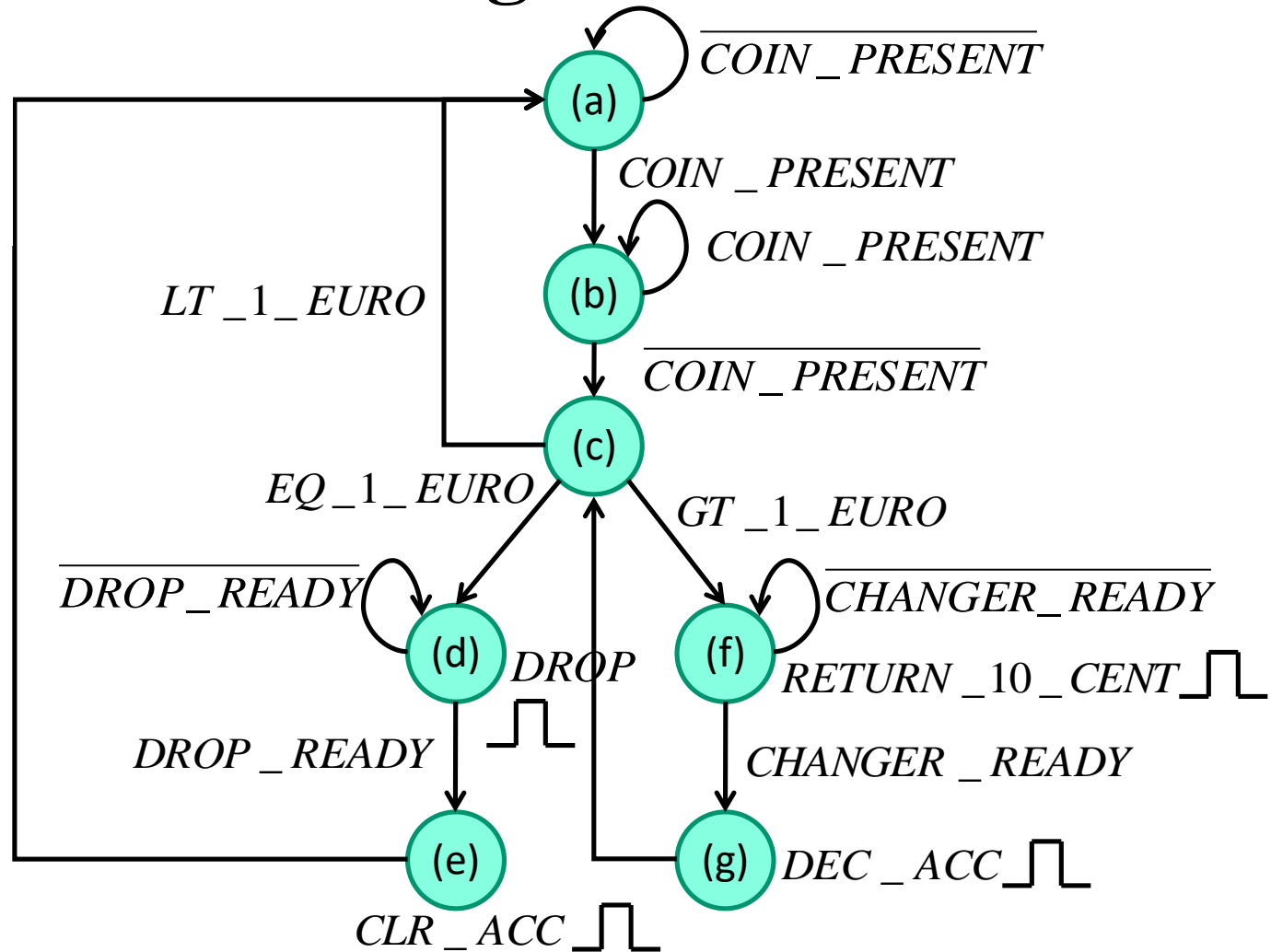We draw a state diagram from the functional diagram :




State diagram

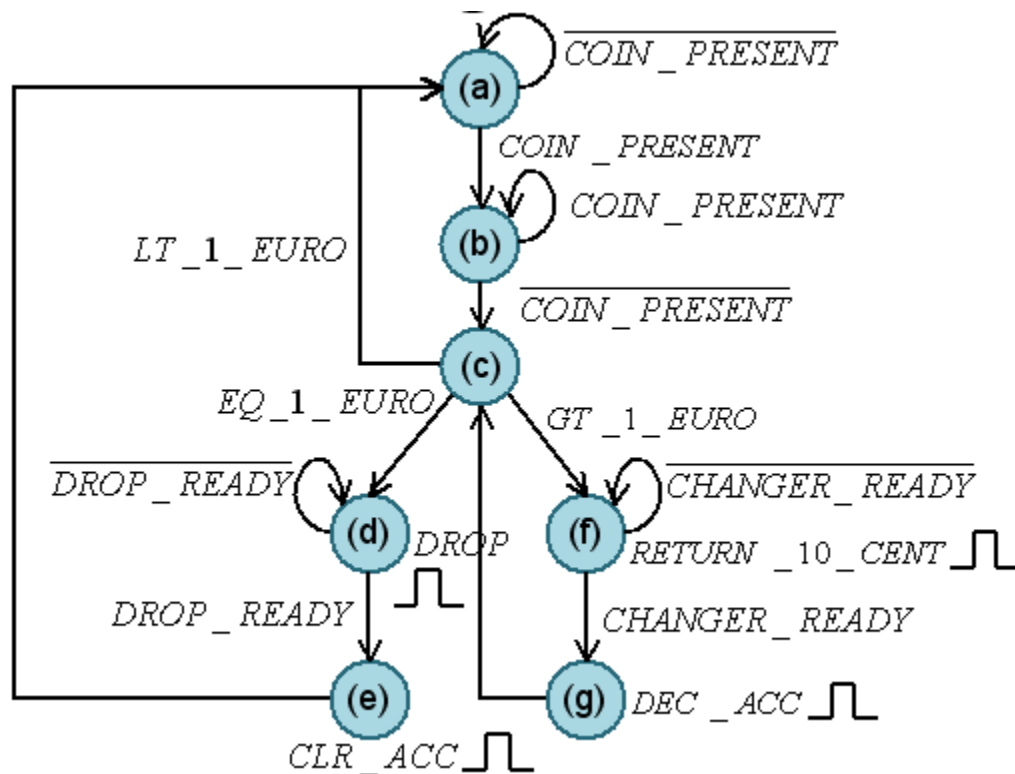

- (a) Wait for coin input
- (b) Register coin?
- (c) Coin is registered (3 cases)
- (d) Eject bottle
- (e) Reset sum
- (f) Return 10 Cent
- (g) Decrease sum 10 Cent

Block schematic

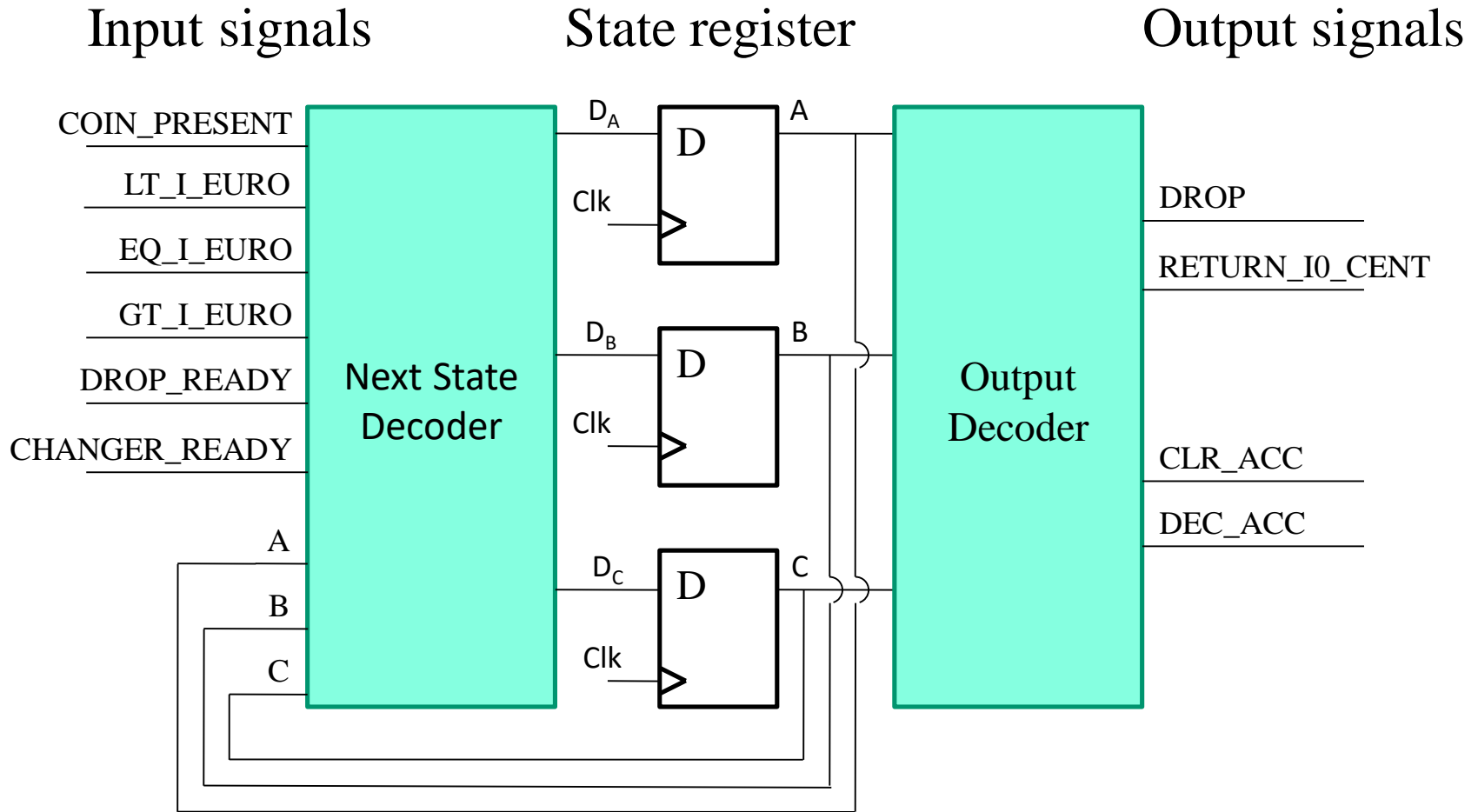

State encoding

Idea: Let the states that are close together in the state diagram have codes with unit distance.

(b) next to (c)

(d) next to (e)


(a) next to (b)

(f) next to (g)

7 states 3 state variables A, B, C are needed


		AB			
		00	01	11	10
C	0	a	Ø	d	f
	1	b	c	e	g

(Ø = don't care)

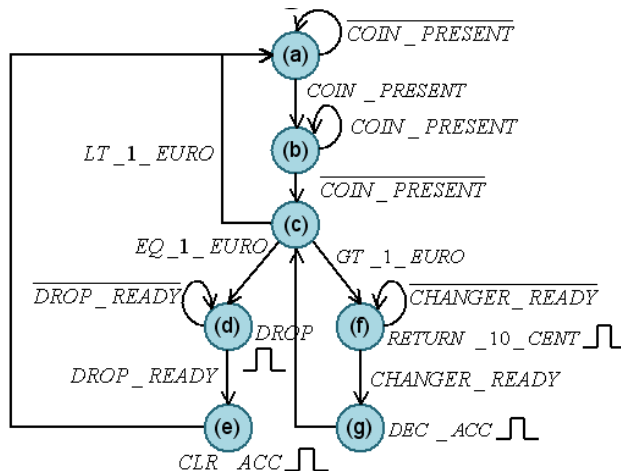

The number of inputs is large, 6, total there may be nine variables in Karnaugh maps ???

State encoding

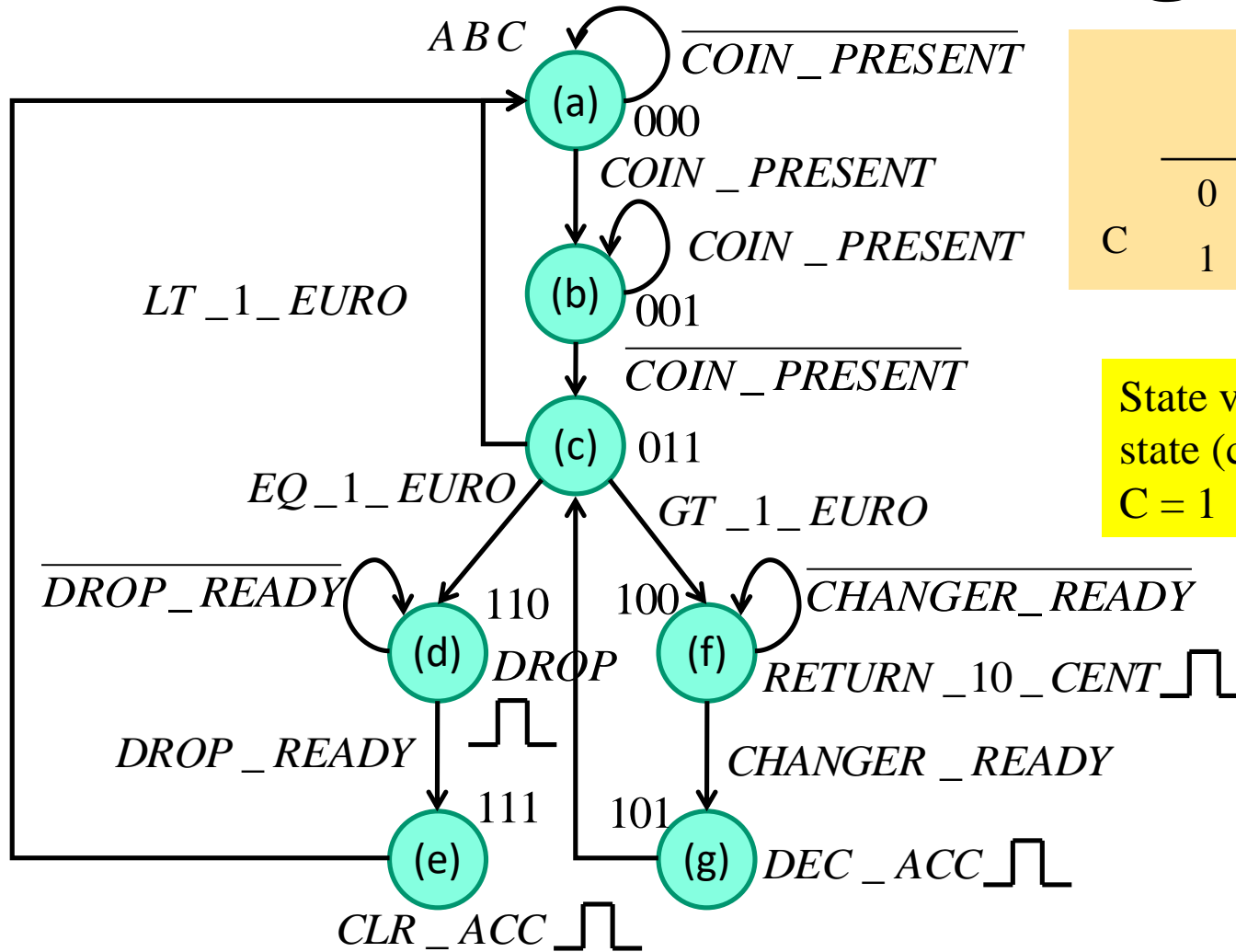

		AB			
		00	01	11	10
C	0	a	Ø	d	f
	1	b	c	e	g


(Ø = don't care)

State variables ABC, eg. in state (c) is A = 0, B = 1 and C = 1

Coded state table?

$$A^+B^+C^+ = f(ABC, CP, DR, CR, GT, LT, EQ)$$

		AB			
		00	01	11	10
C	0	(a): $\overline{CP} \rightarrow 000$ (a) $CP \rightarrow 001$ (b)	$\Phi: \Phi$	(d): $\overline{DR} \rightarrow 110$ (d') $DR \rightarrow 111$ (e)	(f): $\overline{CR} \rightarrow 100$ (f) $CR \rightarrow 101$ (g)
	1	(b): $CP \rightarrow 001$ (b) $\overline{CP} \rightarrow 011$ (c)	$GT \rightarrow 100$ (f) (c): $EQ \rightarrow 110$ (d) $LT \rightarrow 000$ (a)	(e): $\rightarrow 000$ (a)	(g): $\rightarrow 011$ (c)

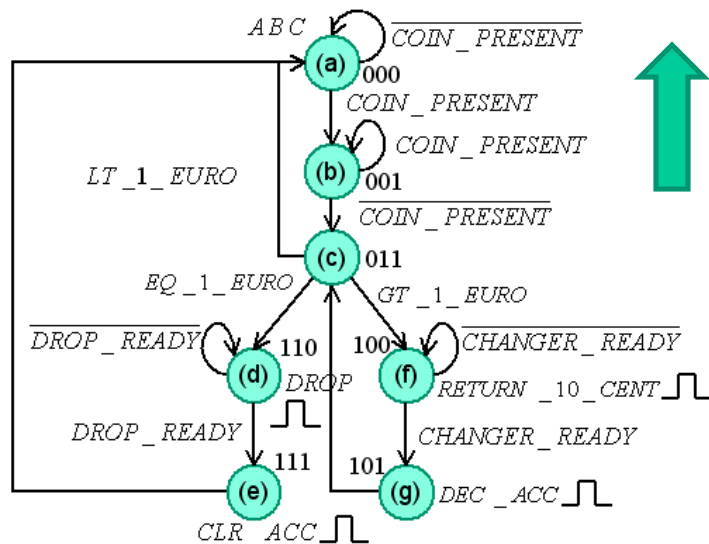

From the state diagram, you can set up the following coded state table.


How do we avoid the complexity of **nine** variables?

Variable-Entered Mapping (VEM)

Variable-Entered Mapping can be helpful when you need Karnaugh diagrams with many variables. You write functional expressions in the Karnaugh map.

$$A^+B^+C^+ = f(ABC, CP, DR, CR, GT, LT, EQ)$$

		AB			
		00	01	11	10
C	0	(a): $\overline{CP} \rightarrow 000$ (a) $CP \rightarrow 001$ (b)	$\Phi: \Phi$	(d): $\overline{DR} \rightarrow 110$ (d) $DR \rightarrow 111$ (e)	(f): $\overline{CR} \rightarrow 100$ (f) $CR \rightarrow 101$ (g)
	1	(b): $CP \rightarrow 001$ (b) $\overline{CP} \rightarrow 011$ (c)	$GT \rightarrow 100$ (f) (c): $EQ \rightarrow 110$ (d) $LT \rightarrow 000$ (a)	(e): $\rightarrow 000$ (a)	(g): $\rightarrow 011$ (c)

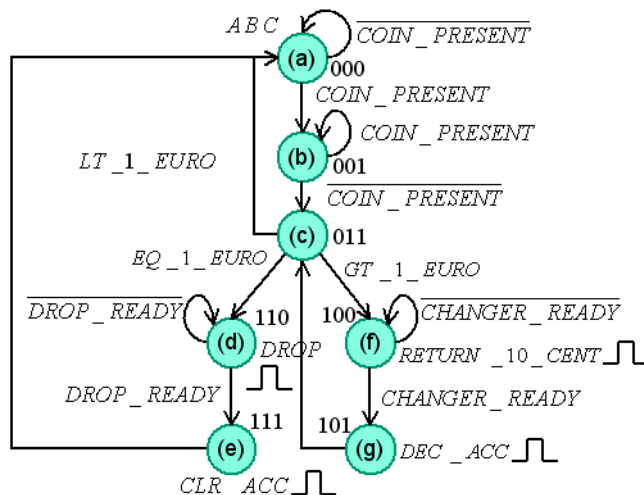

		AB			
		00	01	11	10
C	0	0	\emptyset	1	1
	1	0	EQ + GT	0	0

Variables

Next state - D_A

$$A^+ B^+ C^+ = f(ABC, CP, DR, CR, GT, LT, EQ)$$

		AB			
		00	01	11	10
C	0	(a): $\overline{CP} \rightarrow 000$ (a) $CP \rightarrow 001$ (b)	$\Phi: \Phi$	(d): $\overline{DR} \rightarrow 110$ (d) $DR \rightarrow 111$ (e)	(f): $\overline{CR} \rightarrow 100$ (f) $CR \rightarrow 101$ (g)
	1	(b): $CP \rightarrow 001$ (b) $\overline{CP} \rightarrow 011$ (c)	$GT \rightarrow 100$ (f) (c): $EQ \rightarrow 110$ (d) $LT \rightarrow 000$ (a)	(e): $\rightarrow 000$ (a)	(g): $\rightarrow 011$ (c)

$A^+ D_A$		AB			
		00	01	11	10
C	0	0	\emptyset	1	1
	1	0	EQ + GT	0	0

EQ : EQ_1_EURO
GT : GT_1_EURO

$$A^+ = D_A = \overline{A} \cdot B \cdot EQ + \overline{A} \cdot B \cdot GT + A \cdot \overline{C}$$

Next state - D_B

$$A^+B^+C^+ = f(ABC, CP, DR, CR, GT, LT, EQ)$$

		AB			
		00	01	11	10
C	0	(a): $\overline{CP} \rightarrow 000$ (a) $CP \rightarrow 001$ (b)	$\Phi: \Phi$	(d): $\overline{DR} \rightarrow 110$ (d) $DR \rightarrow 111$ (e)	(f): $\overline{CR} \rightarrow 100$ (f) $CR \rightarrow 101$ (g)
	1	(b): $CP \rightarrow 001$ (b) $\overline{CP} \rightarrow 011$ (c)	$GT \rightarrow 100$ (f) (c): $EQ \rightarrow 110$ (d) $LT \rightarrow 000$ (a)	(e): $\rightarrow 000$ (a)	(g): $\rightarrow 011$ (c)

$B^+ D_B$		AB			
		00	01	11	10
C	0	0	\emptyset	1	0
	1	\overline{CP}	EQ	0	1

EQ : EQ_1_EURO
CP : COIN_PRESENT

$$B^+ = D_B = \overline{A} \cdot B \cdot EQ + B \cdot \overline{C} + \overline{B} \cdot C \cdot \overline{CP} + A \cdot \overline{B} \cdot C$$

Easy to miss!

Next state - D_C

$$A^+B^+C^+ = f(ABC, CP, DR, CR, GT, LT, EQ)$$


		AB			
		00	01	11	10
C	0	$(a): \overline{CP} \rightarrow 000 (a)$ $CP \rightarrow 001 (b)$	$\Phi: \Phi$	$(d): \overline{DR} \rightarrow 110 (d)$ $DR \rightarrow 111 (e)$	$(f): \overline{CR} \rightarrow 100 (f)$ $CR \rightarrow 101 (g)$
	1	$(b): \overline{CP} \rightarrow 001 (b)$ $\overline{CP} \rightarrow 011 (c)$	$GT \rightarrow 100 (f)$ $(c): EQ \rightarrow 110 (d)$ $LT \rightarrow 000 (a)$	$(e): \rightarrow 000 (a)$	$(g): \rightarrow 011 (c)$

CP : COIN_PRESENT
 DR : DROP_READY
 CR : CHANGER_READY

$C^+ D_C$		AB			
		00	01	11	10
C	0	CP	\emptyset	DR	CR
	1	1	0	0	1

$$\begin{aligned}
 C^+ = D_C = & \overline{A} \cdot \overline{C} \cdot CP + B \cdot \overline{C} \cdot DR \\
 & + A \cdot \overline{B} \cdot CR + \overline{B} \cdot C
 \end{aligned}$$

Output signals

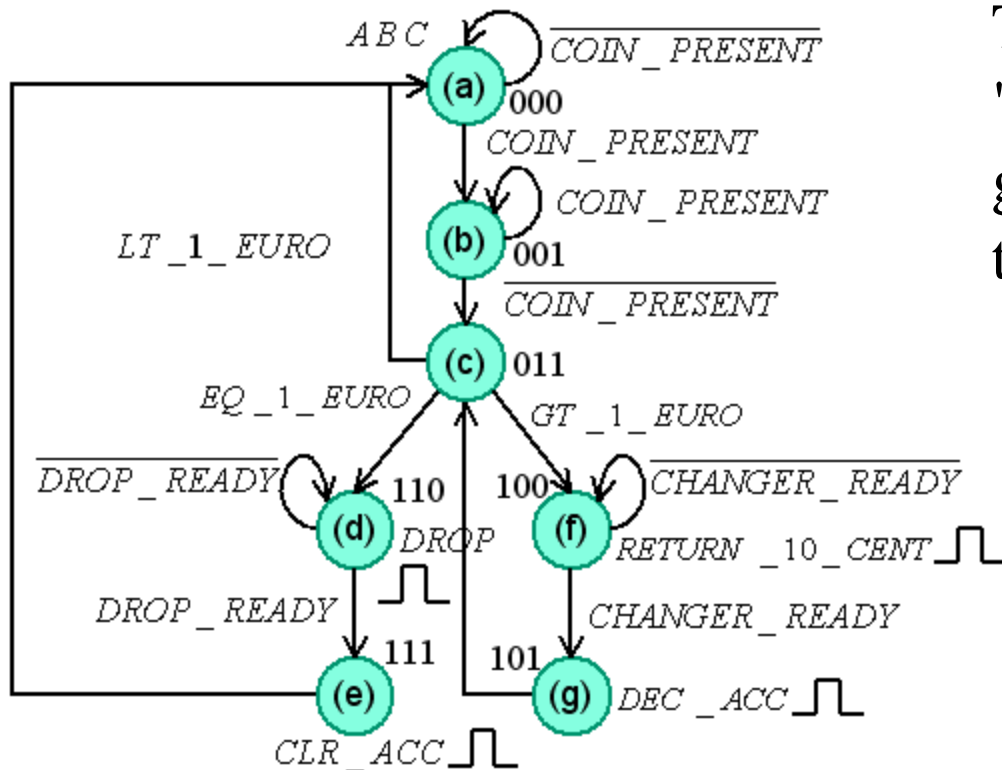

The output signals are "pulses" which are generated when passing through the states d, f, e, g.

$$DROP = \boxed{ABC\bar{C}}$$

$$CLR_ACC = \boxed{ABC}$$

$$RETURN_10_CENT = \boxed{\bar{A}\bar{B}\bar{C}}$$

$$DEC_ACC = \boxed{\bar{A}\bar{B}C}$$

Implementation of the vending machine

”students must master the the design of simple combinational and sequential digital systems”


You do that now!

***When they call from **CocaCola**, it's just for you all
”Digital Designers” to adopt the mission ...***

What will happen in state Φ ?

		AB			
		00	01	11	10
C	0	a	Ø	d	f
	1	b	c	e	g

$$\Phi = (010)_{ABC}$$

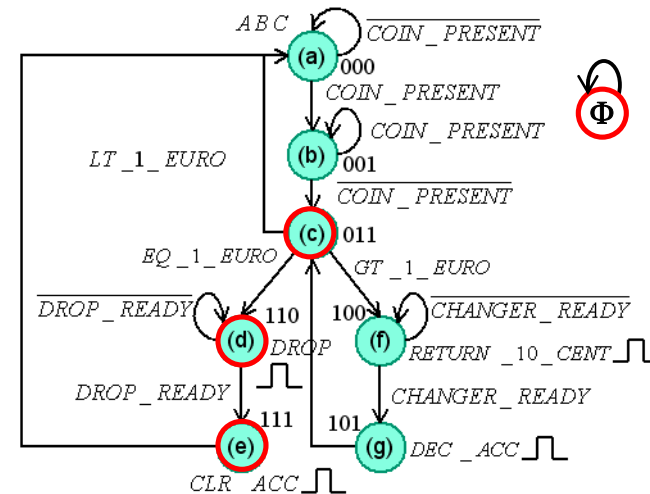

$$A^+ = \bar{A} \cdot B \cdot EQ + \bar{A} \cdot B \cdot GT + A \cdot \bar{C} \Rightarrow A^+(010)_{ABC} = 1 \cdot 1 \cdot EQ + 1 \cdot 1 \cdot GT + 0 \cdot 1 = EQ + GT$$

$$B^+ = \bar{A} \cdot B \cdot EQ + B \cdot \bar{C} + \bar{B} \cdot C \cdot \overline{CP} + A \cdot \bar{B} \cdot C \Rightarrow B^+(010)_{ABC} = 1 \cdot 1 \cdot EQ + 1 \cdot 1 + \dots = 1$$


$$C^+ = \bar{A} \cdot \bar{C} \cdot CP + B \cdot \bar{C} \cdot DR + A \cdot \bar{B} \cdot CR + \bar{B} \cdot C$$

$$\Rightarrow C^+(010)_{ABC} = 1 \cdot 1 \cdot CP + 1 \cdot 1 \cdot DR + 0 \cdot 0 \cdot CR + 0 \cdot 0 = CP + DR$$

$$A^+ B^+ C^+ = -1- = 010, 110, 011, 111 \rightarrow \Phi, d, c, e$$

What will happen in state Φ ?
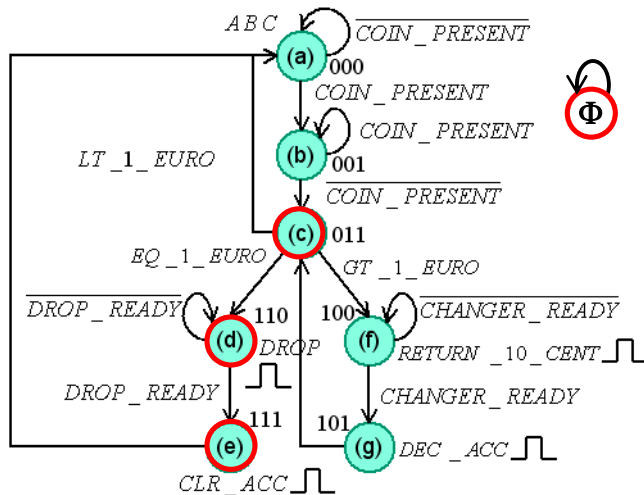
$$A^+B^+C^+ = -1- = 010, 110, 011, 111 \rightarrow \Phi, d, c, e$$



In Φ -state we are stuck, or we go to (c) and then on. Or we go to (d) and offers soft drinks, or we go to (e) and resets any previous payment.

Obviously, we need to purchase a reset circuit that ensures that the machine always starts in (a) **000**! Otherwise we will have legitimate complaints from the customers!



RESET-generator

