



KTH Informations- och
kommunikationsteknik

IE1204 Digital Design


F11: Programmable Logic, VHDL for Sequential Circuits

Masoumeh (Azin) Ebrahimi

KTH/ICT

mebr@kth.se

IE1204 Digital Design

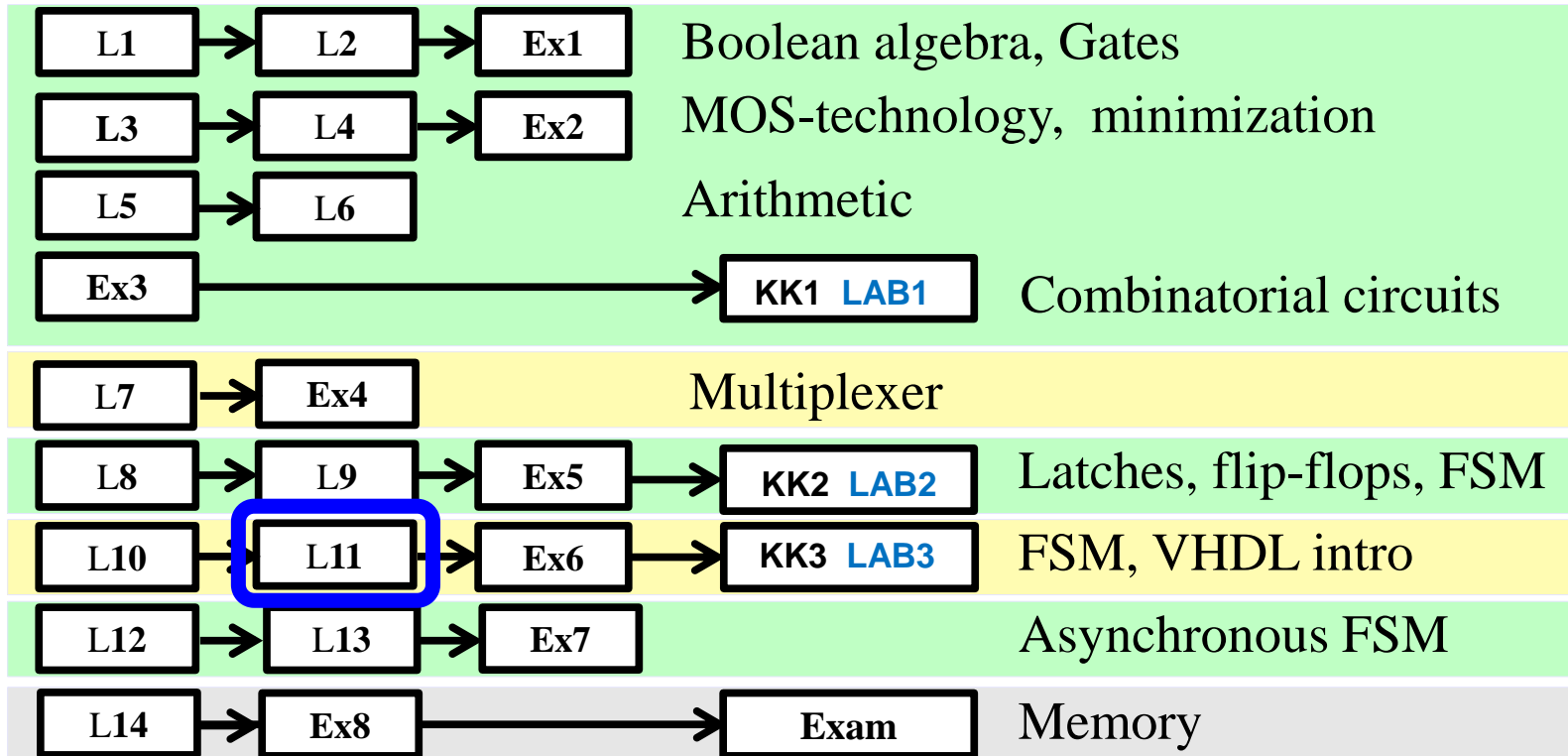


This lecture

- BV pp. 98-118, 418-426, 507-519

Programmable Logic Devices

- *Programmable logic devices (PLDs)* were introduced in the 1970s
- They are based on a structure with an AND-OR array that makes it easy to implement a sum-of-products expression

Structure of a PLD

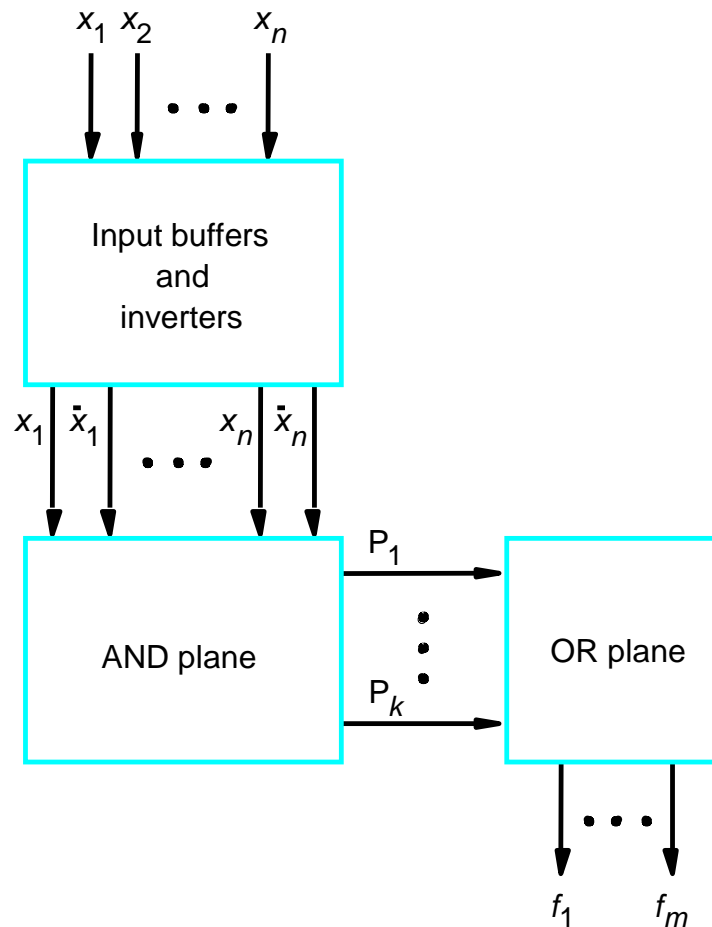


Programmable Logic Array (PLA)

- Both AND and OR arrays are programmable

$$f_1 = x_1x_2 + x_1\bar{x}_3 + \bar{x}_1\bar{x}_2x_3$$
 
$$f_2 = x_1x_2 + x_1\bar{x}_2x_3 + x_1x_3$$




Programmable Array Logic (PAL)

- Only the AND array is programmable

$$f_1 = x_1 x_2 \bar{x}_3 + \bar{x}_1 x_2 x_3$$

 
$$f_2 = \bar{x}_1 \bar{x}_2 + x_1 x_2 x_3$$



Combinatorial and register outputs

- In earlier PLDs there were
 - combinatorial outputs
 - register outputs (outputs with a flip-flop)
- For each circuit the number of combinational and register outputs was fixed
- To increase flexibility, *macrocells* were introduced
 - one can choose if an output is combinatorial or has a flip-flop

Macrocells in a PLD

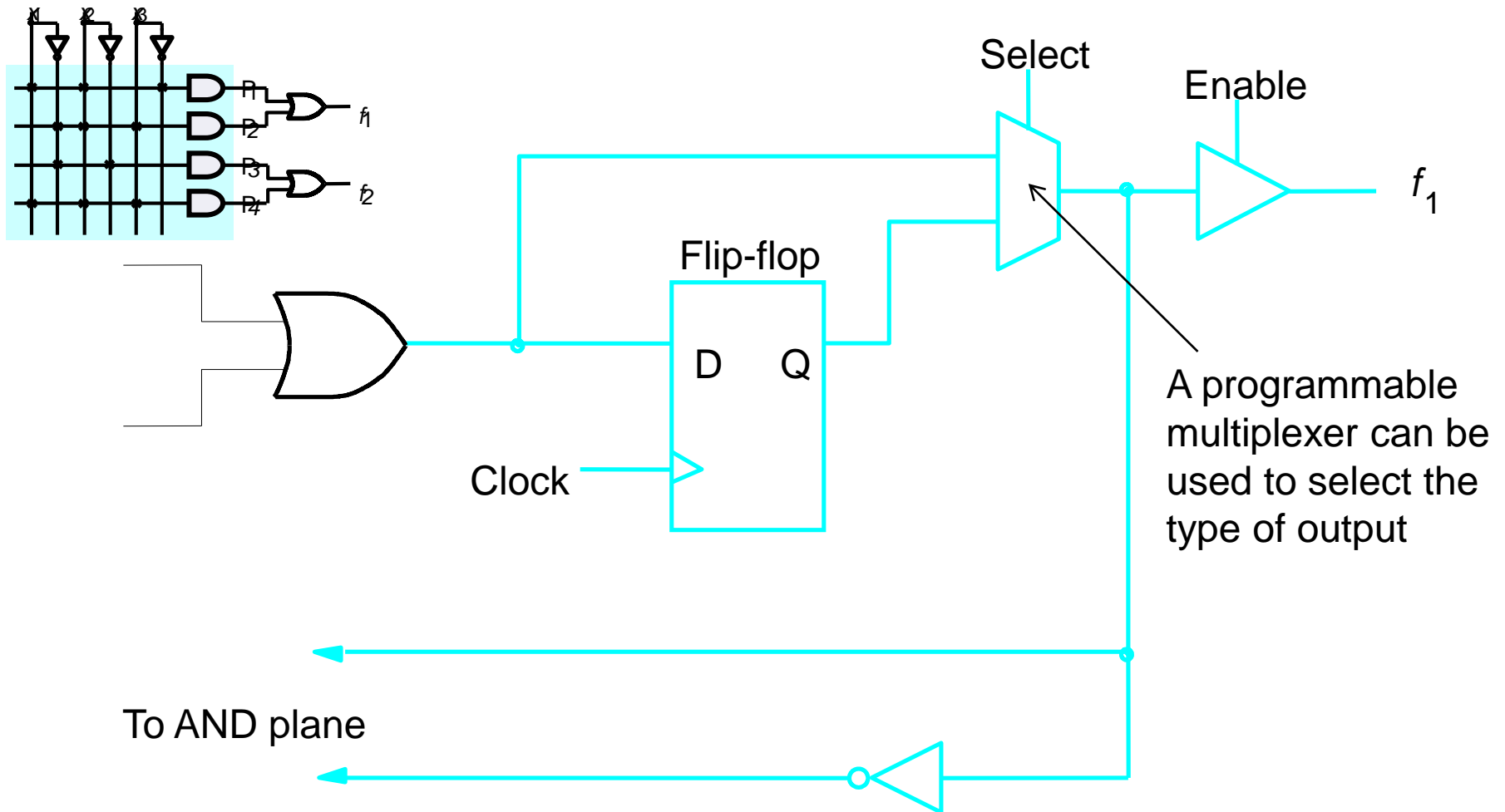


Programming of PLDs



Complex PLD's (CPLD)

- PLDs were quite small (PALCE 22V10 had 10 flip-flops)
- To program larger functions, structures consisting of several PLD-like blocks were developed called Complex PLD (CPLD)


CPLD Structure

 


Programming of CPLDs via the JTAG interface

- Modern CPLDs (and FPGAs) can be programmed by downloading circuit description (programming information) via a cable
- Download usually uses a standard port called *JTAG port* (Joint Test Action Group)

Programming via the JTAG port

 

 (a) CPLD in a Quad Flat Pack (QFP) package




(b) JTAG programming

You can program the chips when they are soldered to the circuit board - using the programmer you can select which chip you want to program through the JTAG port


Field Programmable Gate Arrays

- CPLDs are based on the AND-OR array
- It is difficult to make really large functions using CPLDs
- FPGAs use a different concept based on *logic blocks*

Structure of an FPGA

 


Look-up-tables (LUT)

 

A LUT with n inputs can realize all combinational functions with up to n inputs. The usual size of LUT in an FPGA is $n = 4$

Logic Block in a FPGA

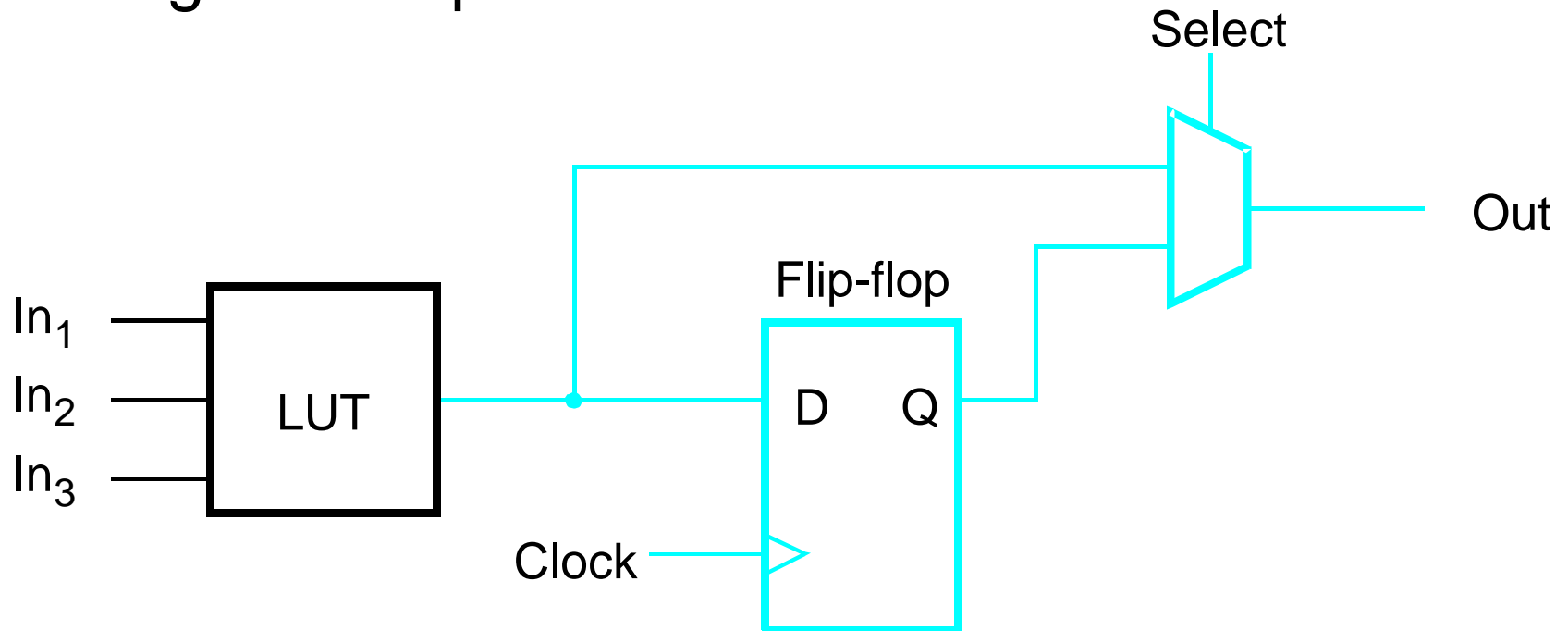- A logic block in an FPGA often consists of a LUT, a flip-flop and a multiplexer to select register output




Programming the LUT's and the connection matrix in an FPGA

- Blue cross: switch is programmed
- Black cross: switch is not programmed


$$f = f_1 + f_2$$

$$f = x_1 x_2 + \bar{x}_2 x_3$$

 


DE2 University Board

 - DE2 Board
 - Cyclone II EP2C35 FPGA (Datorteknik-course)
 - 4 Mbytes of flash memory
 - 512 Kbytes of static RAM
 - 8 Mbytes of SDRAM
 - Several I/O-Devices
 - 50 MHz oscillator



Cyclone II Logic Element

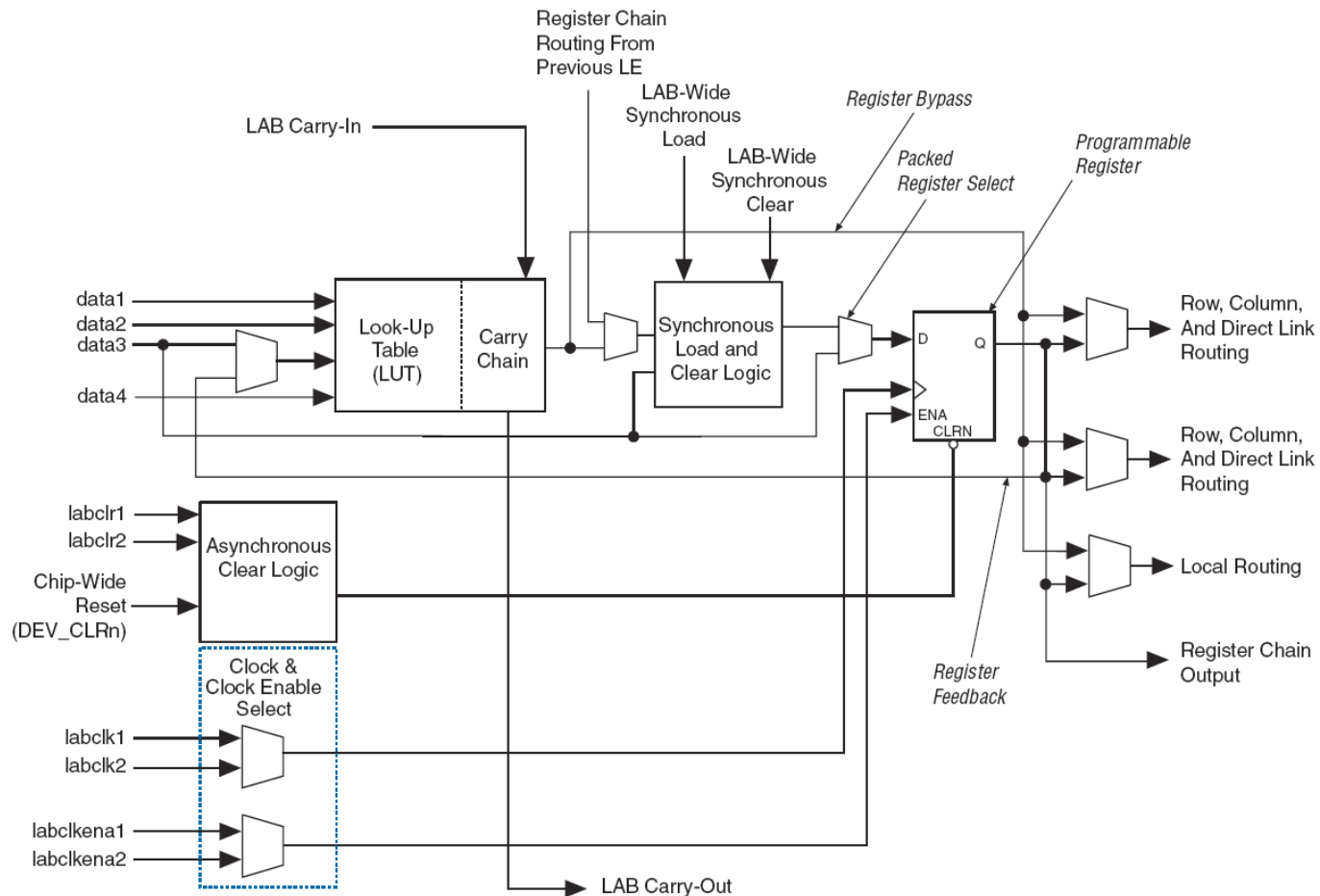

Cyclone II Family

Table 1–1. Cyclone II FPGA Family Features

Feature	EP2C5	EP2C8 (2)	EP2C15 (1)	EP2C20 (2)	EP2C35	EP2C50	EP2C70
LEs	4,608	8,256	14,448	18,752	33,216	50,528	68,416
M4K RAM blocks (4 Kbits plus 512 parity bits)	26	36	52	52	105	129	250
Total RAM bits	119,808	165,888	239,616	239,616	483,840	594,432	1,152,000
Embedded multipliers (3)	13	18	26	26	35	86	150
PLLs	2	2	4	4	4	4	4
Maximum user I/O pins	158	182	315	315	475	450	622

(3) Total Number of 18x18 Multipliers

DE2

Stratix III Family


Table 1–1. Stratix III FPGA Family Features

	Device/ Feature	ALMs	LEs	M9K Blocks	M144K Blocks	MLAB Blocks	Total Embedded RAM Kbits	MLAB RAM Kbits ⁽²⁾	Total RAM Kbits ⁽³⁾	18×18-bit Multipliers (FIR Mode)	PLLs
Stratix III Logic Family	EP3SL50	19K	47.5K	108	6	950	1,836	297	2,133	216	4
	EP3SL70	27K	67.5K	150	6	1,350	2,214	422	2,636	288	4
	EP3SL110	43K	107.5K	275	12	2,150	4,203	672	4,875	288	8
	EP3SL150	57K	142.5K	355	16	2,850	5,499	891	6,390	384	8
	EP3SL200	80K	200K	468	36	4,000	9,396	1,250	10,646	576	12
	EP3SE260	102K	255K	864	48	5,100	14,688	1,594	16,282	768	12
	EP3SL340	135K	337.5K	1,040	48	6,750	16,272	2,109	18,381	576	12
Stratix III Enhanced Family	EP3SE50	19K	47.5K	400	12	950	5,328	297	5,625	384	4
	EP3SE80	32K	80K	495	12	1,600	6,183	500	6,683	672	8
	EP3SE110	43K	107.5K	639	16	2,150	8,055	672	8,727	896	8
	EP3SE260 ⁽¹⁾	102K	255K	864	48	5,100	14,688	1,594	16,282	768	12

DE3 Board

Multiple processors can be implemented on an FPGA

 - Nios II is a so-called 'soft-processor' (32-bit) that can be implemented on Altera's FPGAs
- Today's FPGAs are so large that multiple processors can fit on a single FPGA chip




Very powerful multiprocessor systems can be created on an FPGA!

ASICs

- An ASIC (**Application Specific Integrated Circuit**) is a circuit which is manufactured at a semiconductor factory
- In a *full custom* integrated circuit, the entire circuit is customized
- In an ASIC, some design steps have already been made to reduce design time and cost
- There are several types of ASICs:
 - Gate array ASICs
 - Standard cell ASIC



ASICs: Gate Array

 - In a gate array ASIC, gates (or transistors) are already on silicon





ASICs: Gate Array

  - We only need to create the links between the inputs and outputs of gates







ASICs: Standard Cells

  - A standard cell can for example be AND, OR, Invert, XOR, XNOR, buffer, or a storage function as flip-flop or latch.




Comparison

FPGA, Gate Array, Standard Cell

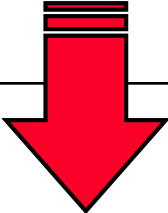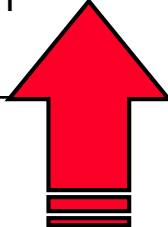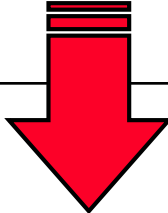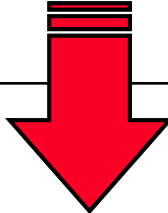
	Initial Cost	Cost per part	Performance	Fabrication Time
FPGA	Low 	High 	Low 	Short 
Gate Array (ASIC)				
Standard Cell (ASIC)	High	Low	High	Long

Design Trade-Offs

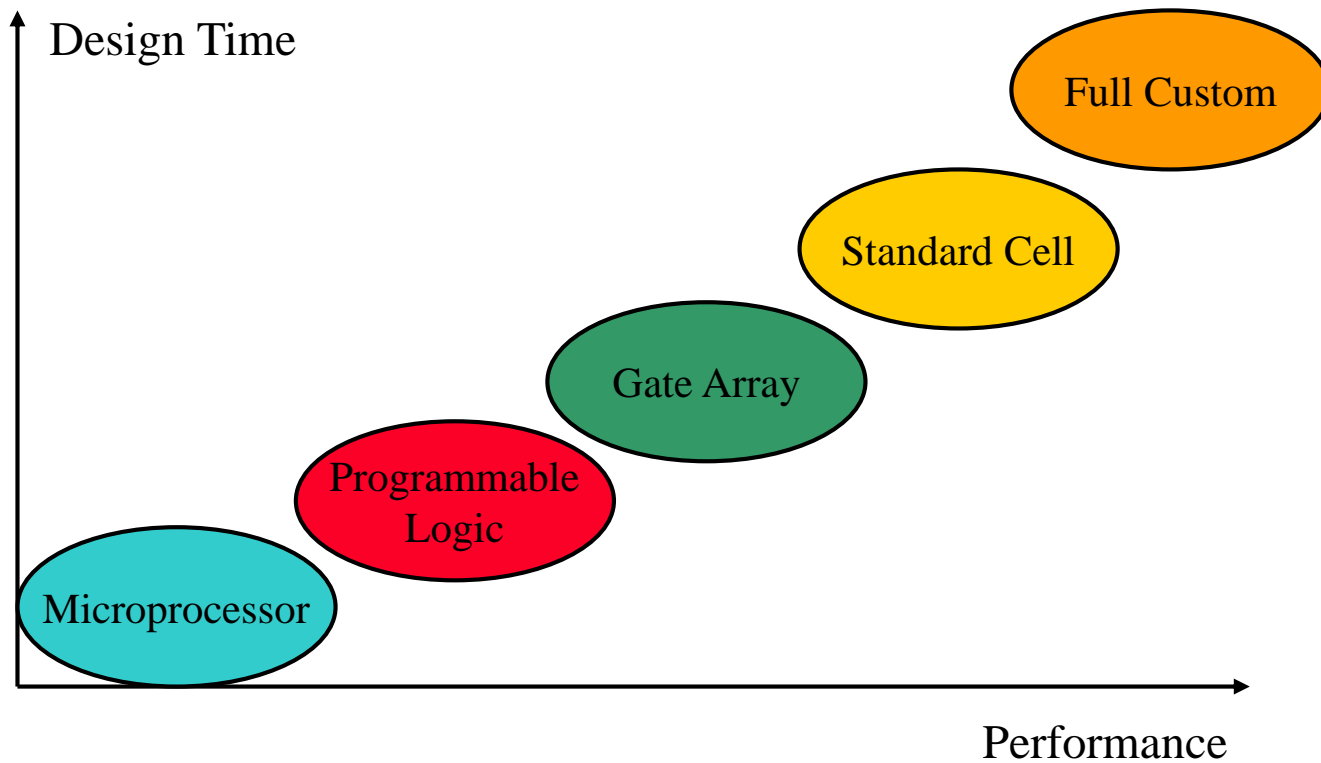

VHDL: Sequential circuits

Moore machine

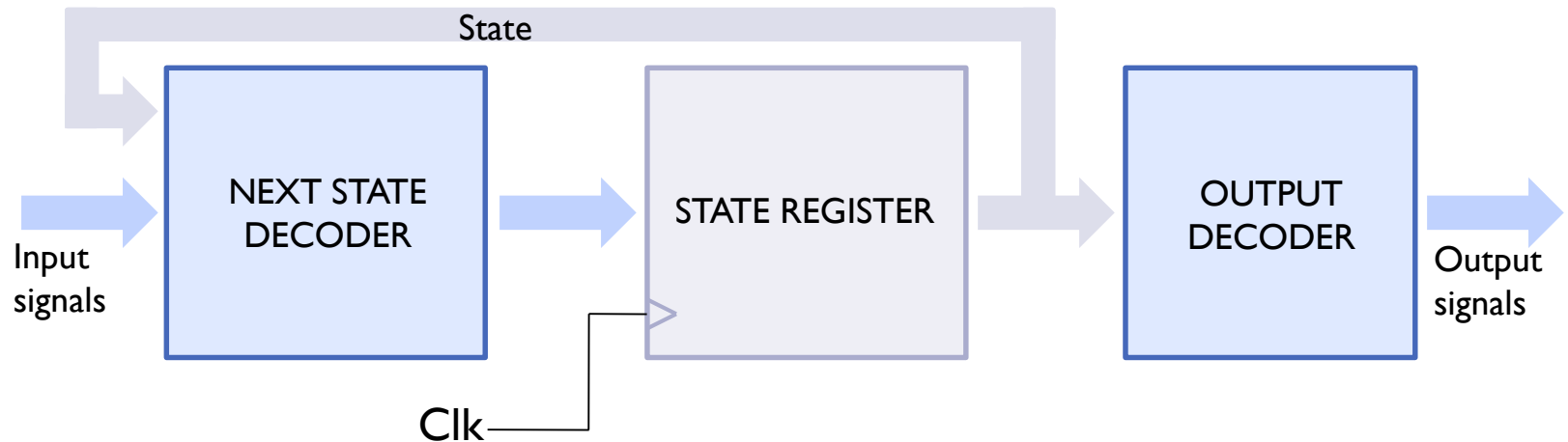

- In a Moore-type machine output signals depend only on the current state




How to model a state machine in VHDL?

- In a Moore machine, we have three blocks
 - Next state decoder
 - Output decoder
 - State register
- These blocks are executed in parallel

Quick question

- Which logic gate is represented by the following VHDL code?

```
q <= a and (not b) ;
```

   


Quick question

- Which logic gate is represented by the following VHDL code?


```
if (a /= b) then  
    q <= '1';  
else  
    q <= '0';  
end if;
```



Alt: A

 

Alt: B

 

Alt: C

Processes in VHDL

- A *architecture* in VHDL can contain multiple processes
- Processes are executed in parallel
- A process is written as a sequential program

Moore-machine processes


- For a Moore machine, we create three processes
 - Next state decoder
 - Output decoder
 - State register

Internal signals

- Moore machine contains internal signals for
 - Current state
 - Next state
- These signals are declared in the *architecture* description

Bottle dispenser vending machine in VHDL

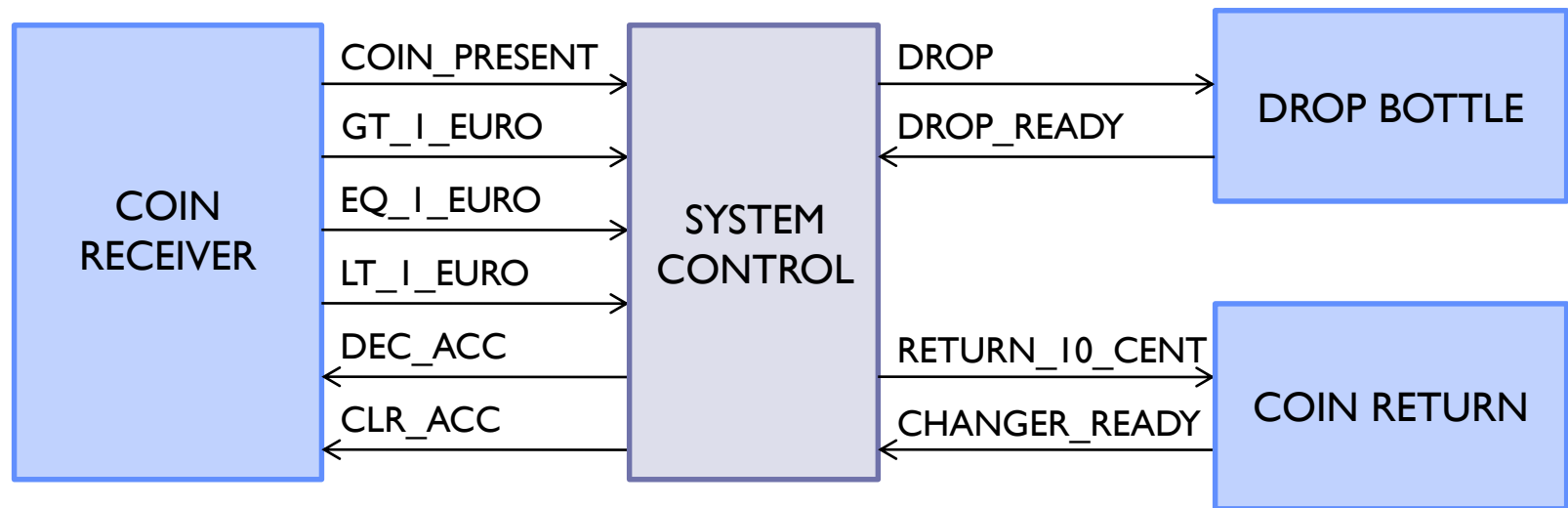- We use bottle dispenser vending machine as an example
- We describe its system controller in VHDL




Bottle dispenser

- Bottle dispenser consists of several parts
 - COIN RECEIVER
 - DROP BOTTLE
 - COIN RETURN
- Machine accepts only the following coins: 1 Euro, 50 Cent, 10 Cent
- The vending machine only returns 10 Cent coins




Flow diagram of control system

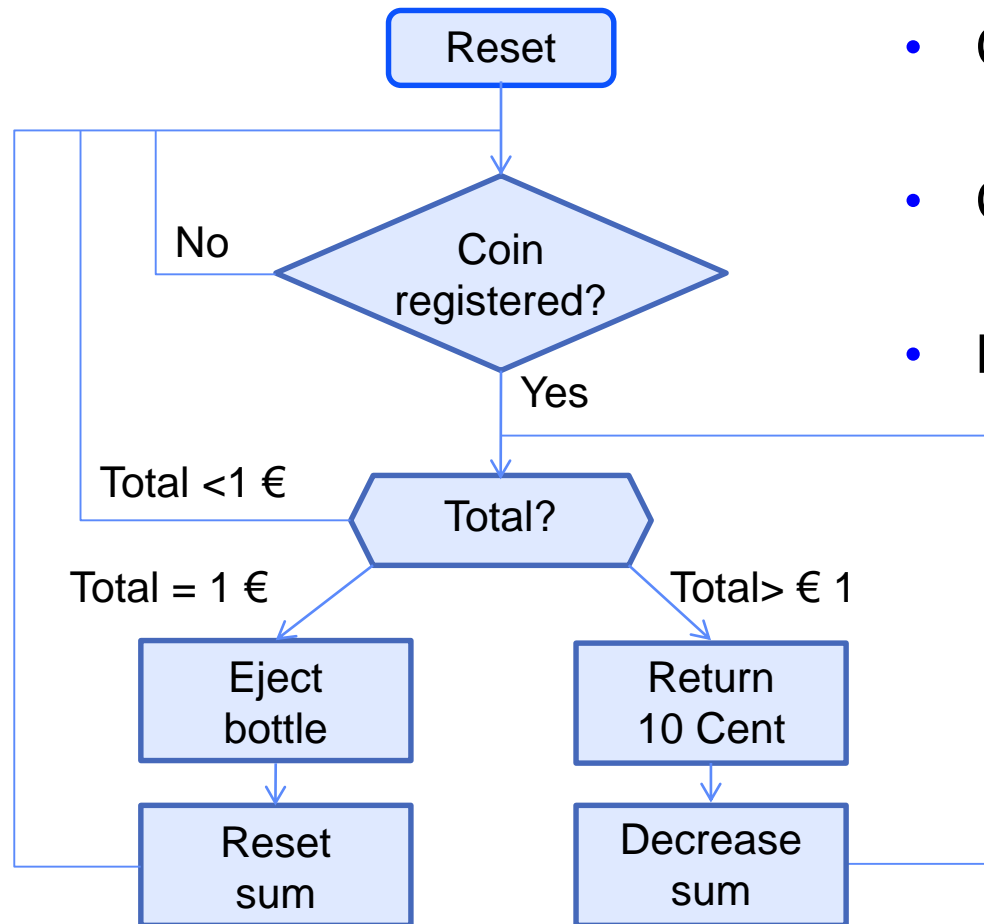

- Coin
 - 10 Cent, 50 Cent, 1 Euro
- Coin return
 - 10 Cent
- Bottle Price
 - 1 Euro


State diagram (Moore)

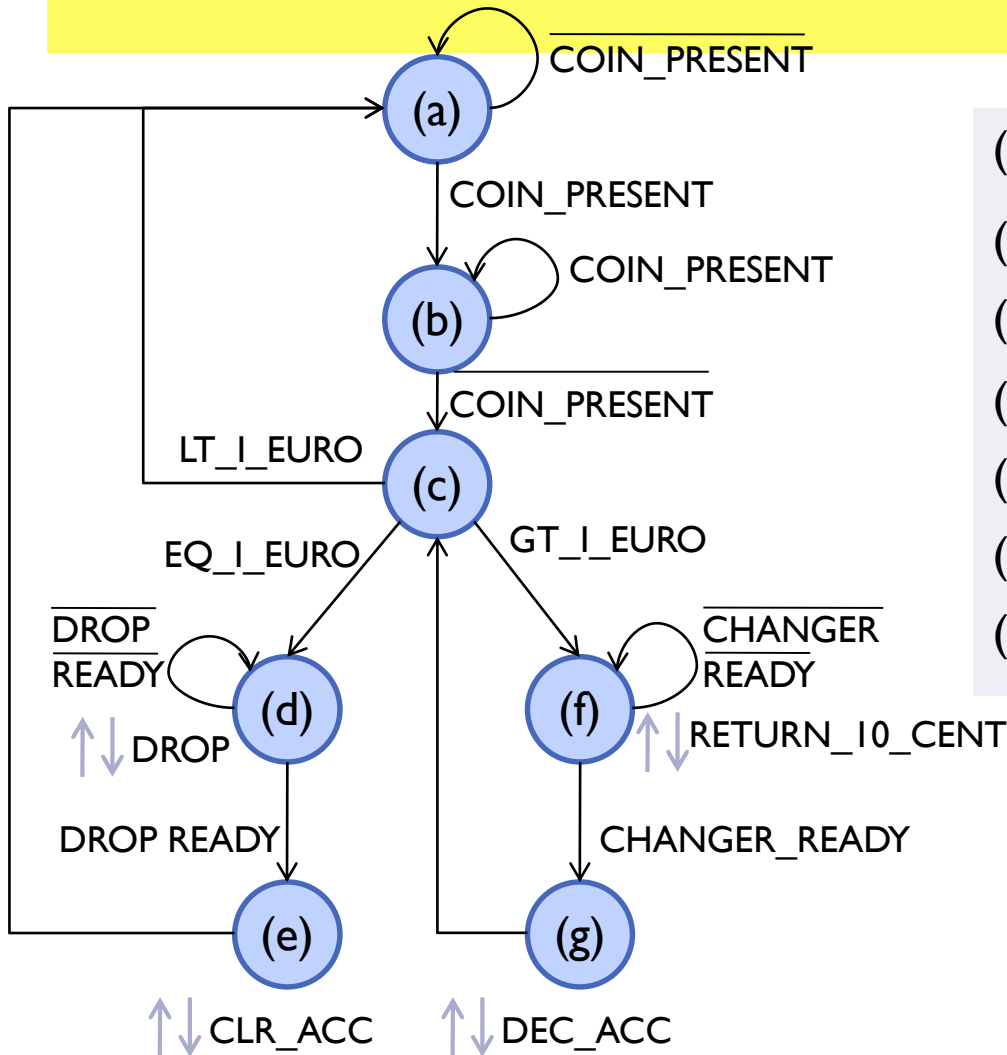

- (a) Wait for coin
- (b) Register coin
- (c) Coin is registered (3 cases)
- (d) Drop bottle
- (e) Reset sum
- (f) Return 10 Cent
- (g) Decrease sum with 10 Cent

- ↑ • Upon entry into the state, signal becomes active
- ↓ • When exiting the state, signal becomes inactive

State diagram

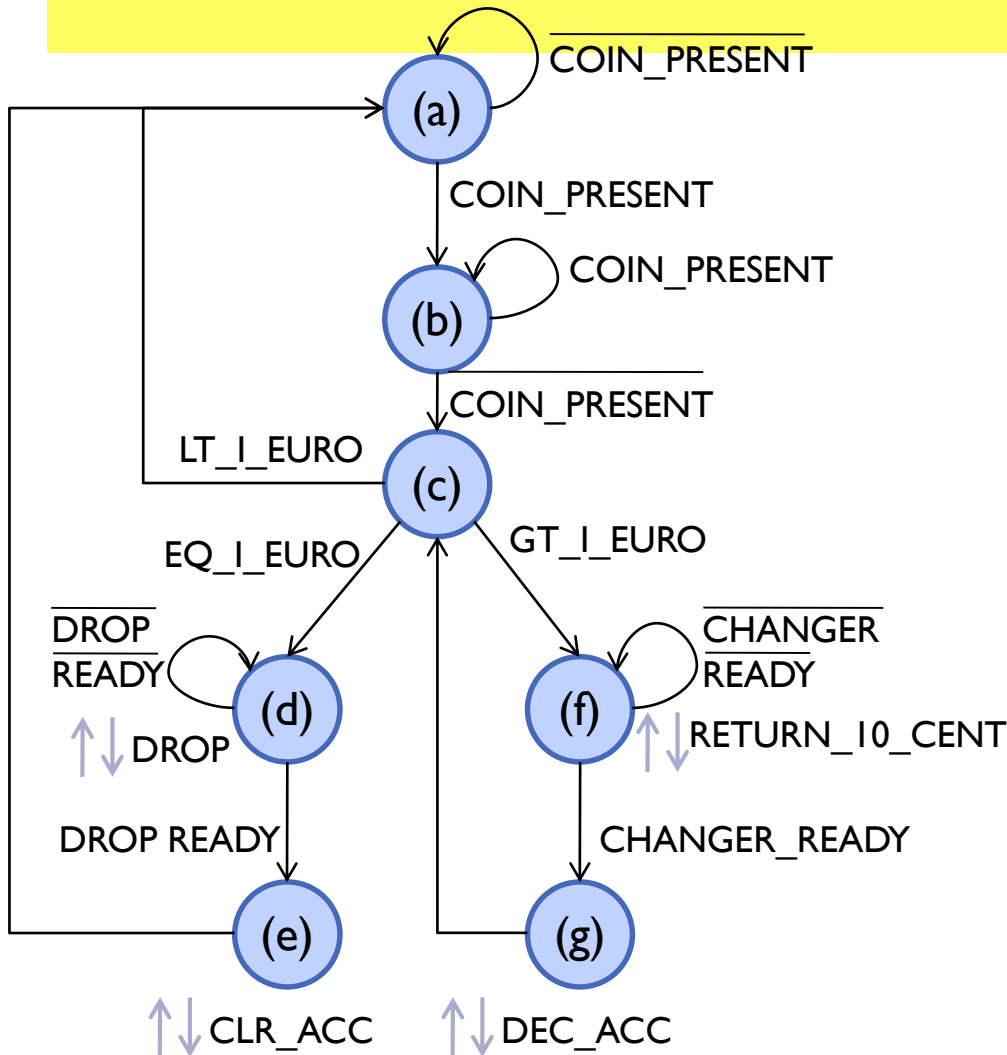


- State assignment with no claim for optimality (Ad hoc)
 - (a) next to (b)
 - (b) next to (c)
 - (d) next to (e)
 - (f) next to (g)
- For all these cases, only one variable changes

		AB			
		00	01	11	10
C	0	a	-	d	f
	1	b	c	e	g

("-" = don't care)


State diagram

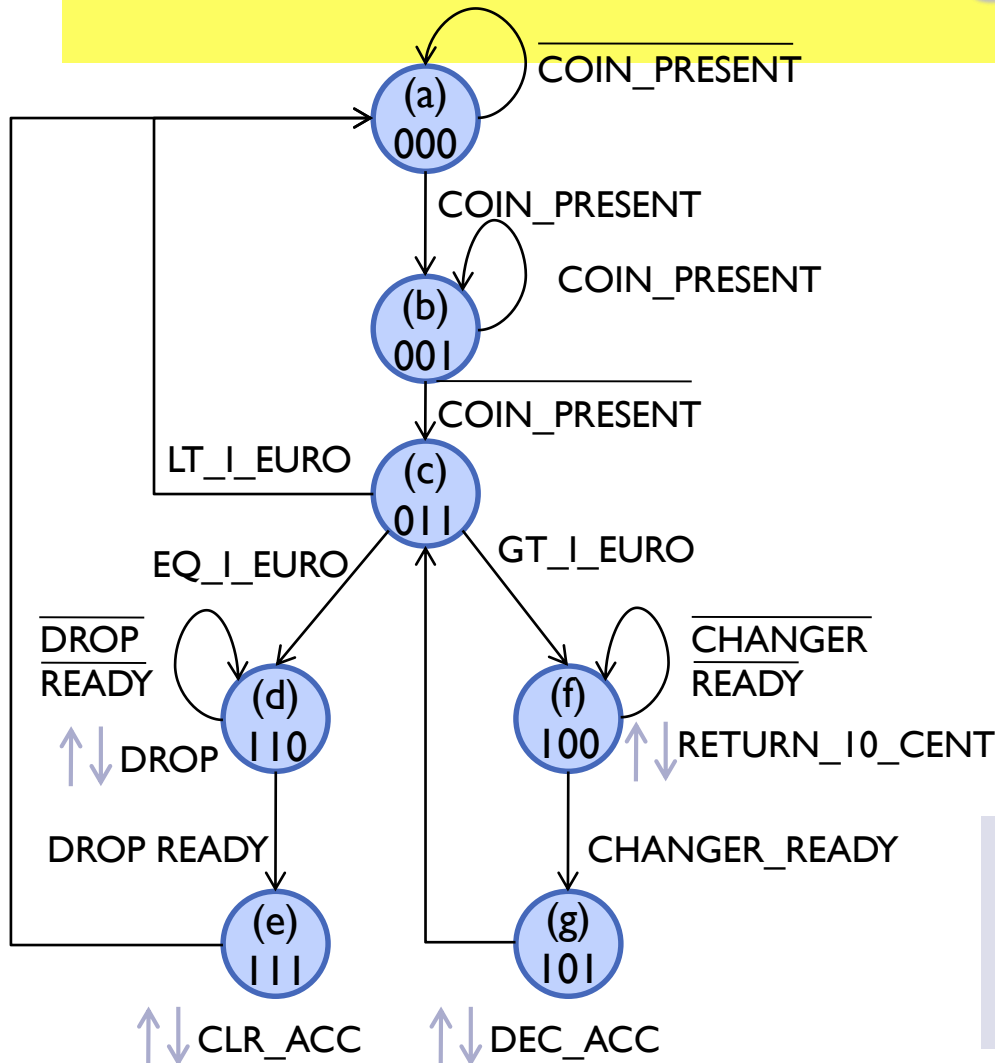

- The state diagram contains all information required to generate an implementation
- Assumption: D flip-flops are used as state register
- 7 states: 3 flip-flops are needed



The state variable order is ABC, i.e. state (c) is $A = 0, B = 1, C = 1$

Unused state?!

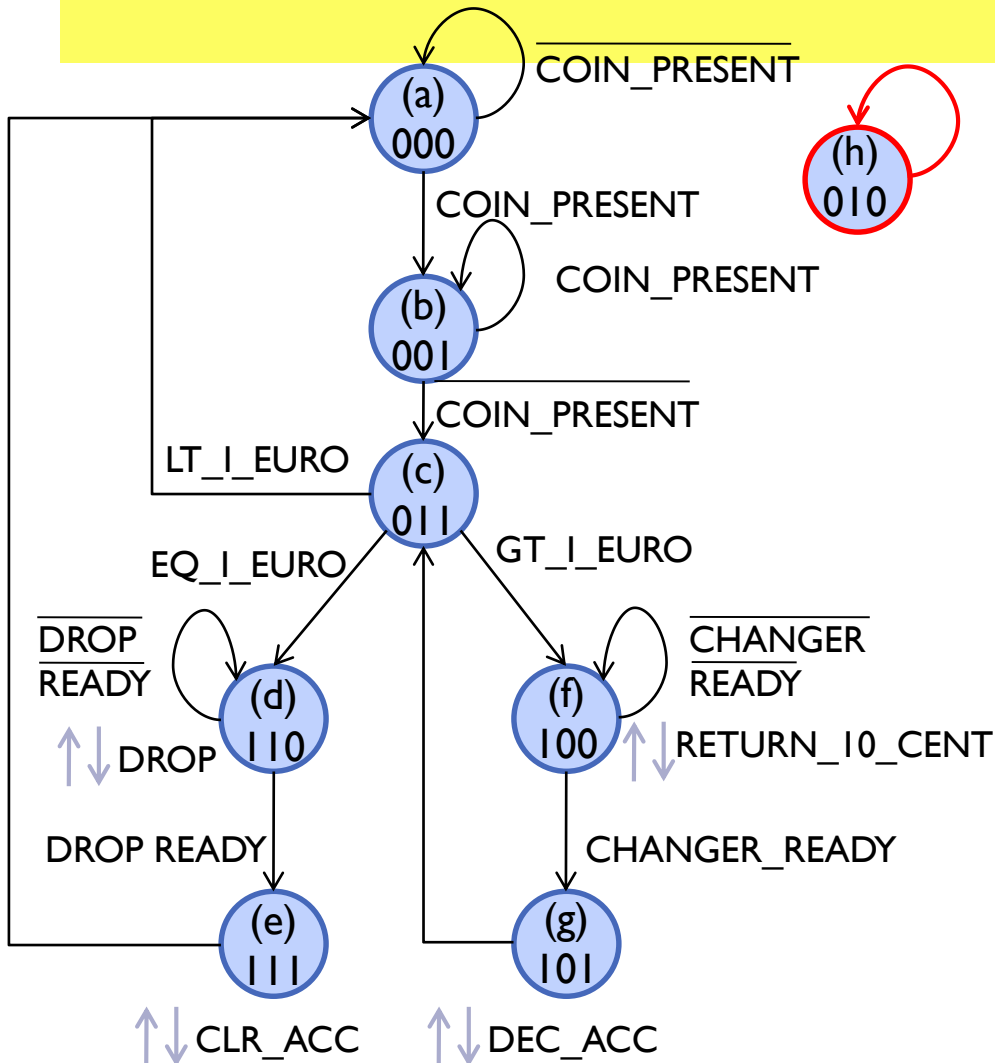


- If fall into the unused state (h) we are stuck!! Possible ways out:
 - going to (c) and continue.
 - going to (d) and offering soft drinks!!
 - going to (e) and resetting any previous payment.
- Which option do you prefer for your design?!
- Which option leads to a simpler design?

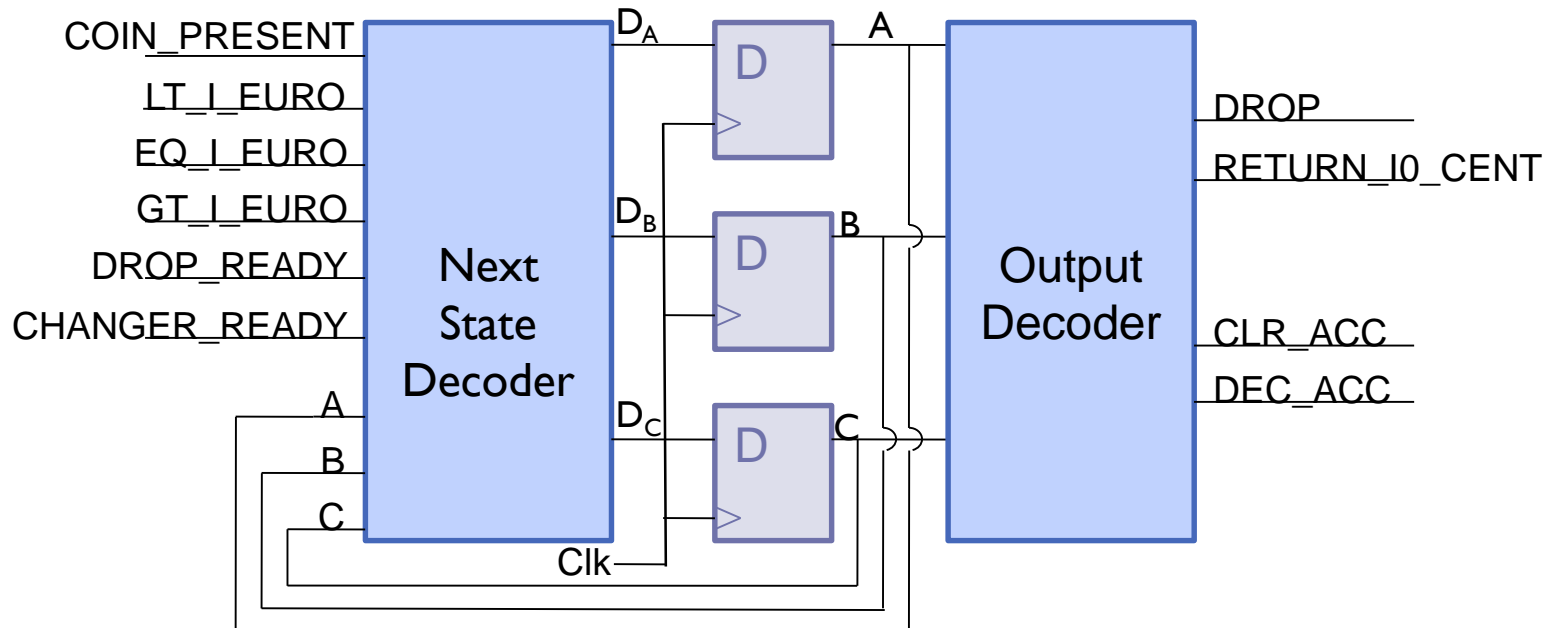 Construction of next-state and output decoders (Moore machine)




At next step, we develop the logic for the next state (D_A , D_B , D_C) and outputs

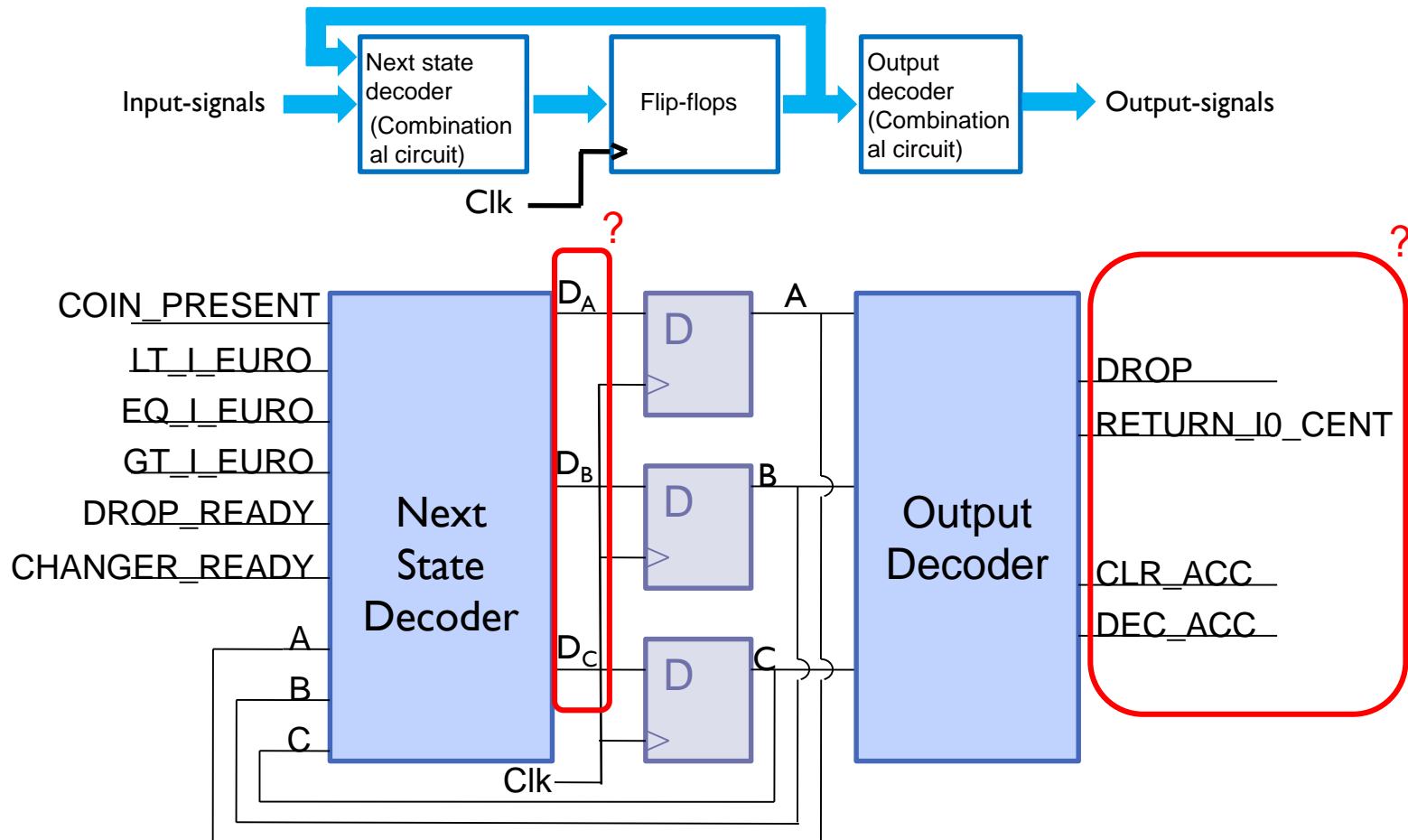Construction of next-state and output decoders





At next step, we develop the logic for the next state (D_A , D_B , D_C) and outputs


Decoder: Next state - D_A

 


D_A		AB			
		00	01	11	10
C	0	0	-	1	
	1				

  


Decoder: Next state - D_A

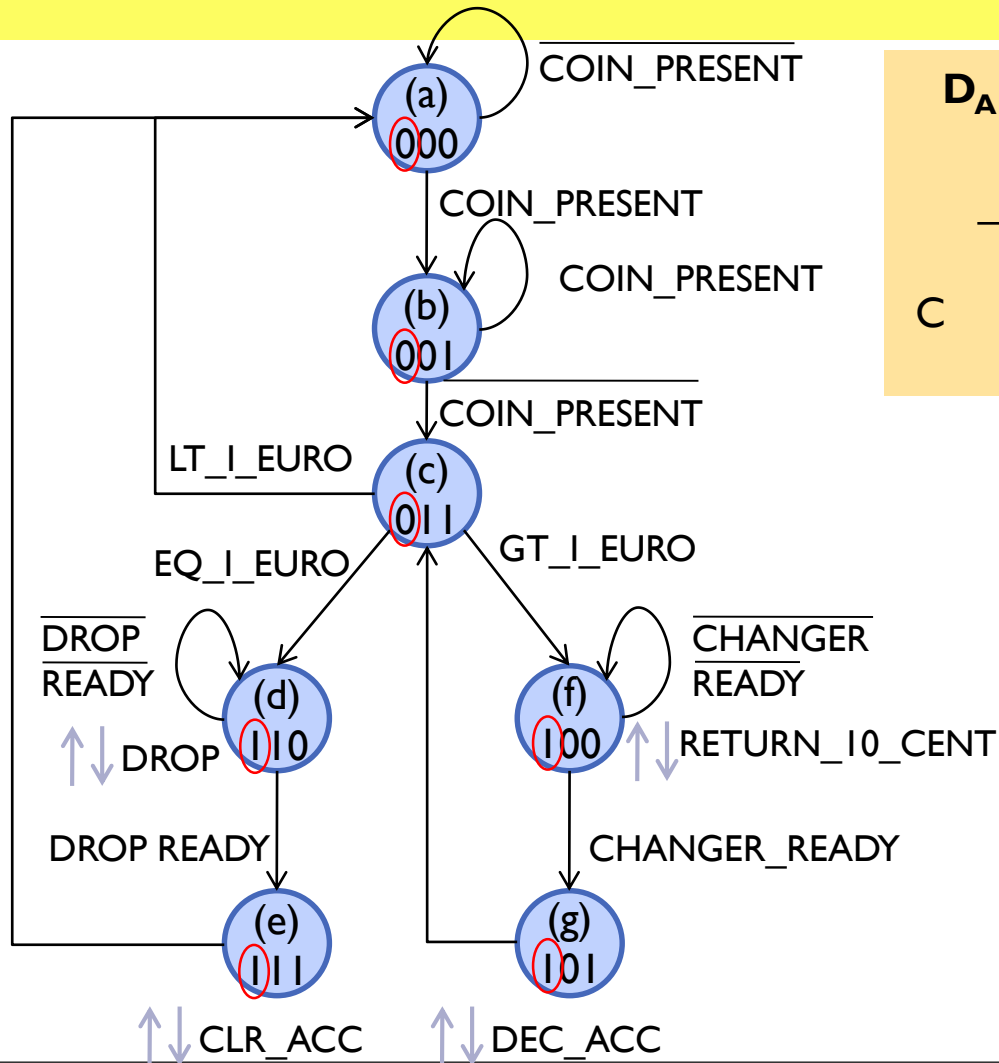

D_A	AB			
	00	01	11	10
C	0	-	1	
	1	(=) + (>)		0

 

Decoder: Next state - D_A

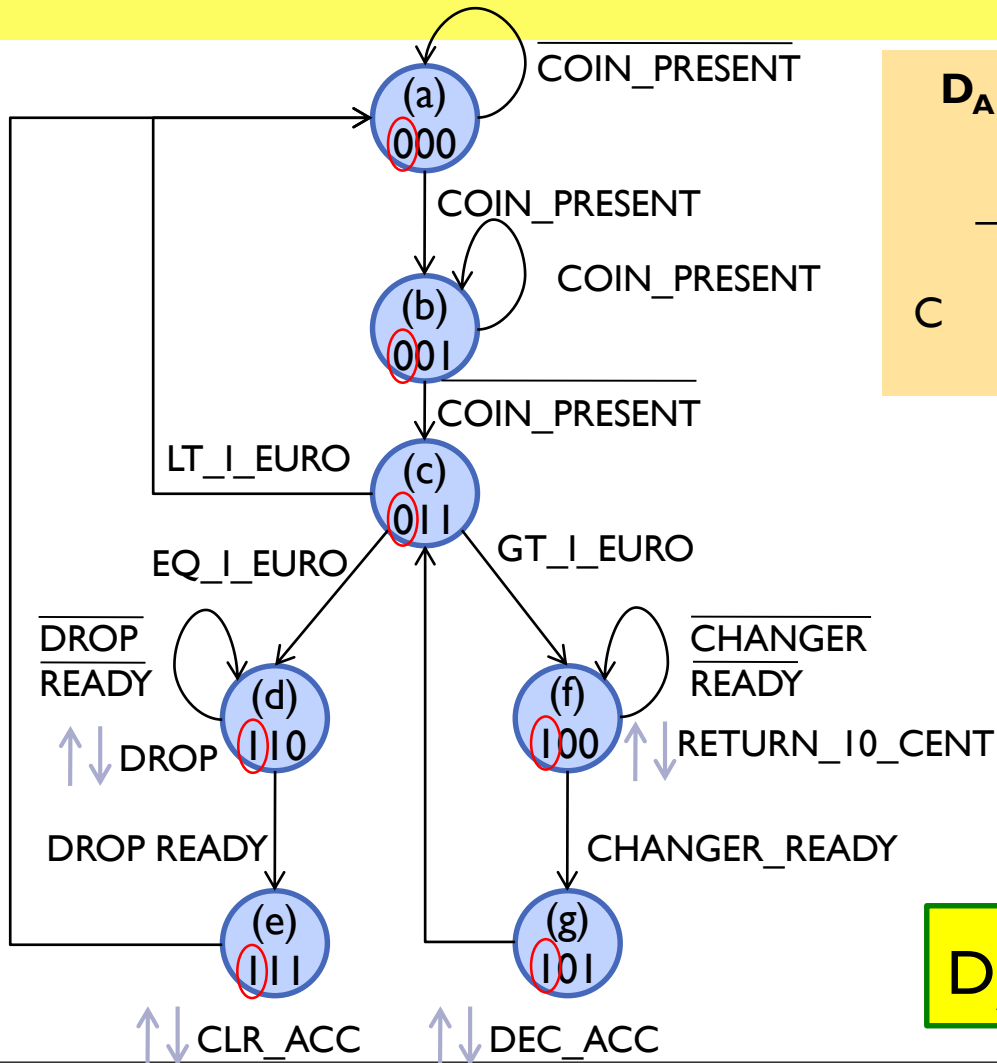

D_A		AB			
		00	01	11	10
C	0	0	-	1	1
	1	0	(=) + (>)	0	0

(=) : EQ_1_EURO
(>) : GT_1_EURO


$$D_A = \overline{A}B(=) + \overline{A}B(>) + A\overline{C}$$

Variable-Entered Mapping (VEM)

- Variable-Entered Mapping can help to draw and minimize Karnaugh diagrams with many variables.
 - In this example there are several variables as:
Coin_Present, Drop_Ready, Changer_Ready, GT, LT, EQ.
- Instead of opening an "extra dimension" we write a variable into the Karnaugh map
- You must be extra careful when drawing circuits so that you do not forget a variable combination!


D_A		AB			
		00	01	11	10
C	0	0	-	1	1
	1	0	(=) + (>)	0	0

Decoder: Next state - D_B

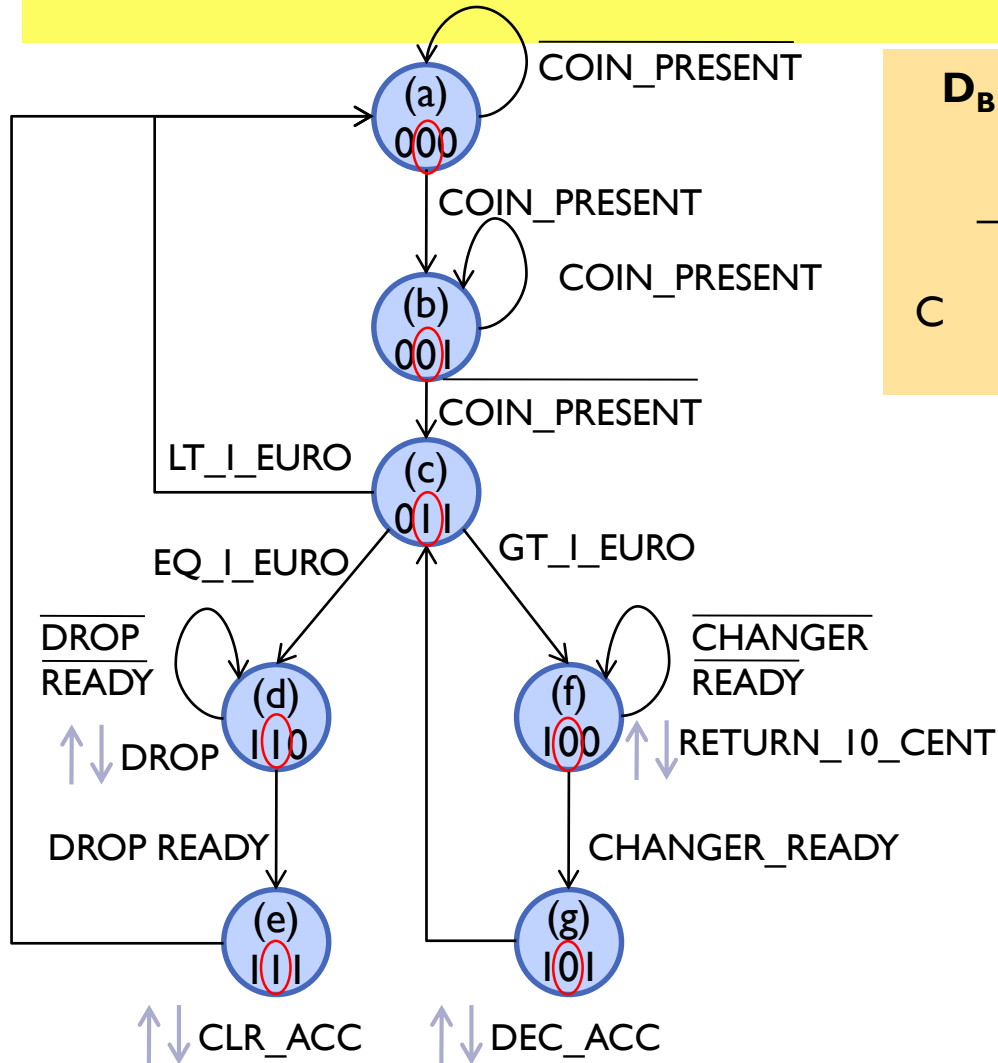

D_B		AB			
		00	01	11	10
C	0				
	1				

Decoder: Next state - D_B

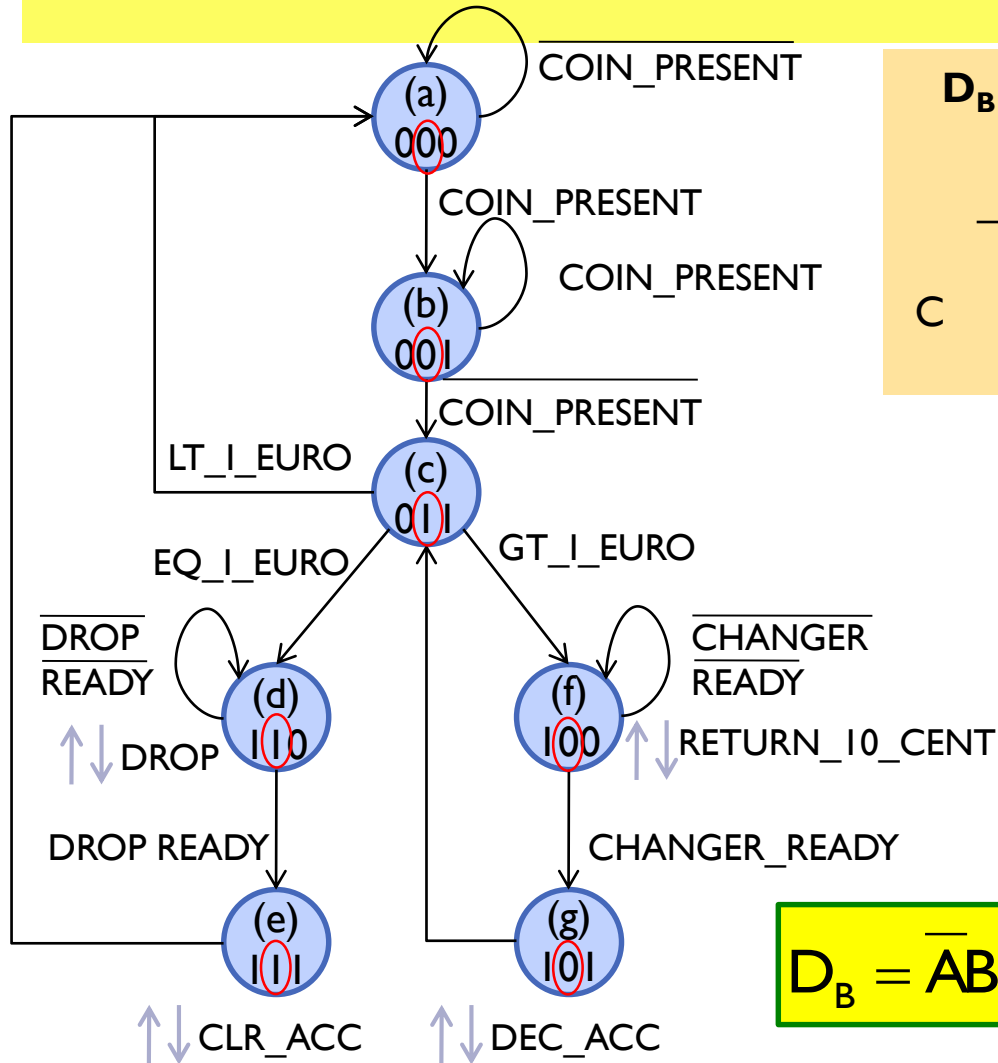


D_B		AB			
C		00	01	11	10
	0	0	-	1	0
	1	$\overline{\text{CP}}$	(=)	0	1

(=) : EQ_1_EURO
CP : COIN_PRESENT

$$D_B = \overline{A}\overline{B}(=) + \overline{B}\overline{C} + \overline{B}\overline{C}(\overline{\text{CP}}) + A\overline{B}\overline{C}$$

Decoder: Next state- D_C

 


D_C		AB			
		00	01	11	10
C	0	CP	-	DR	CR
	1	1	0	0	1

CP : COIN_PRESENT
 DR: DROP_READY
 CR: CHANGER_READY

$$D_C = \overline{A}\overline{C}(CP) + B\overline{C}(DR) + A\overline{B}(CR) + \overline{B}C$$


Decoder: Output signals

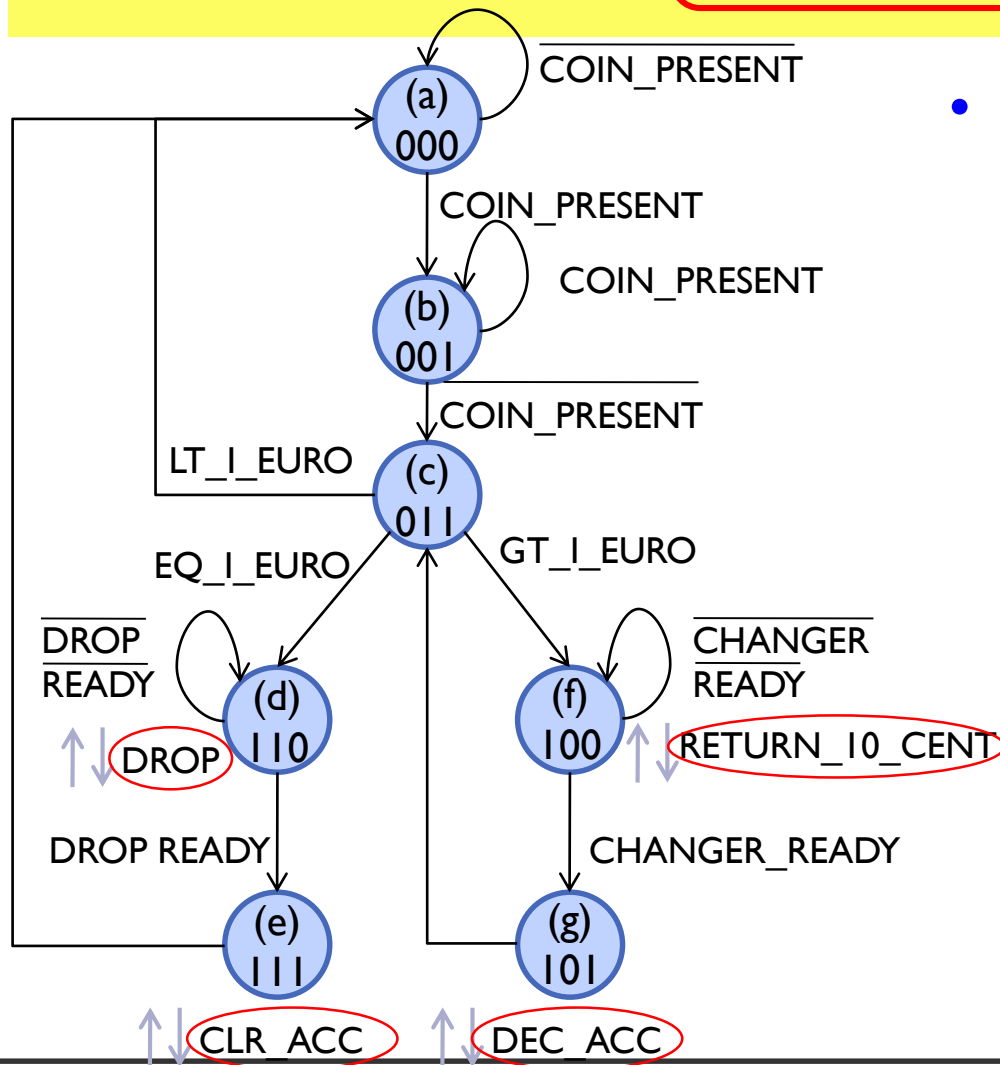- Output decoder is trivial, since its value is directly dependent on the current state




$\text{DROP} = \overline{A}B\overline{C}$
 $\text{CLR_ACC} = \overline{A}BC$
 $\text{RETURN_10_CENT} = \overline{A}\overline{B}C$
 $\text{DEC_ACC} = \overline{A}B\overline{C}$

Logic Design

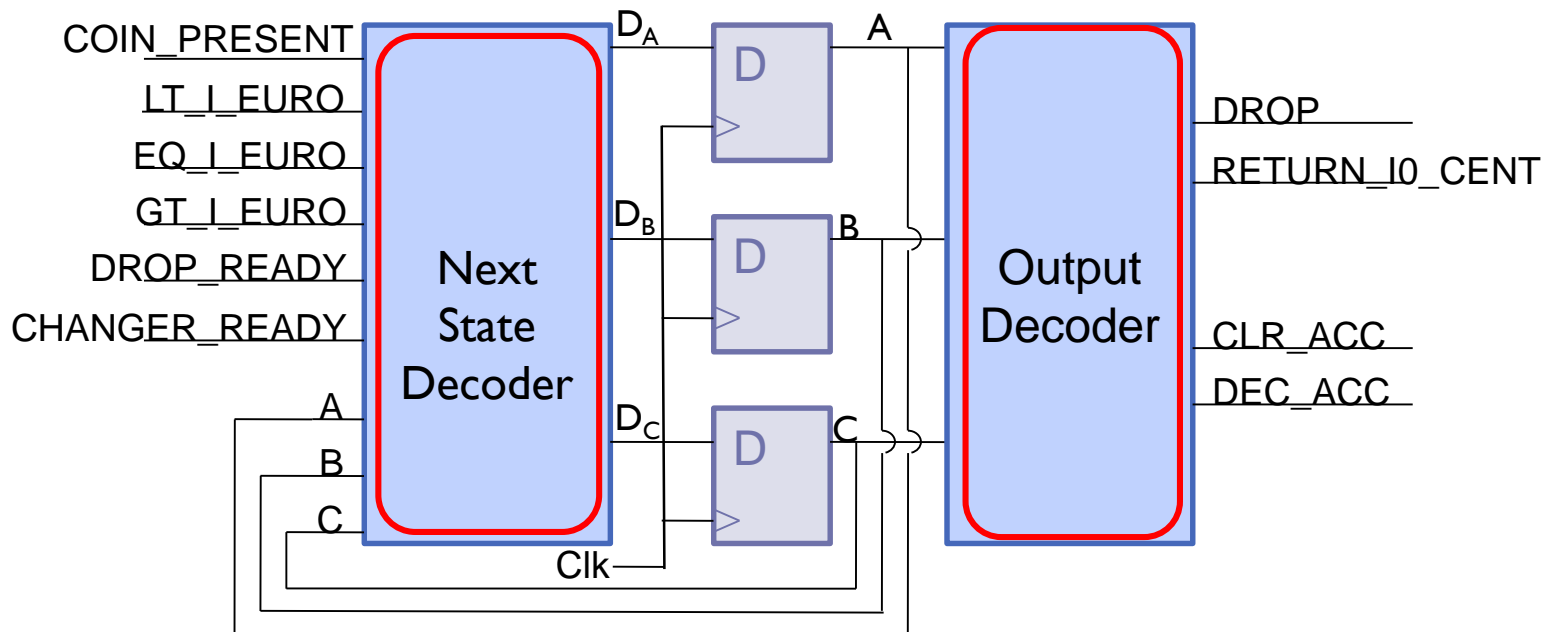

Now you can design "Next State Decoder" and "Output Decoder" by knowing the logic function of D_A , D_B , D_C , and logic function of outputs "Drop", "Return_10_Cent", "CLR_ACC", and "DEC_ACC".


Vending Machine: State diagram

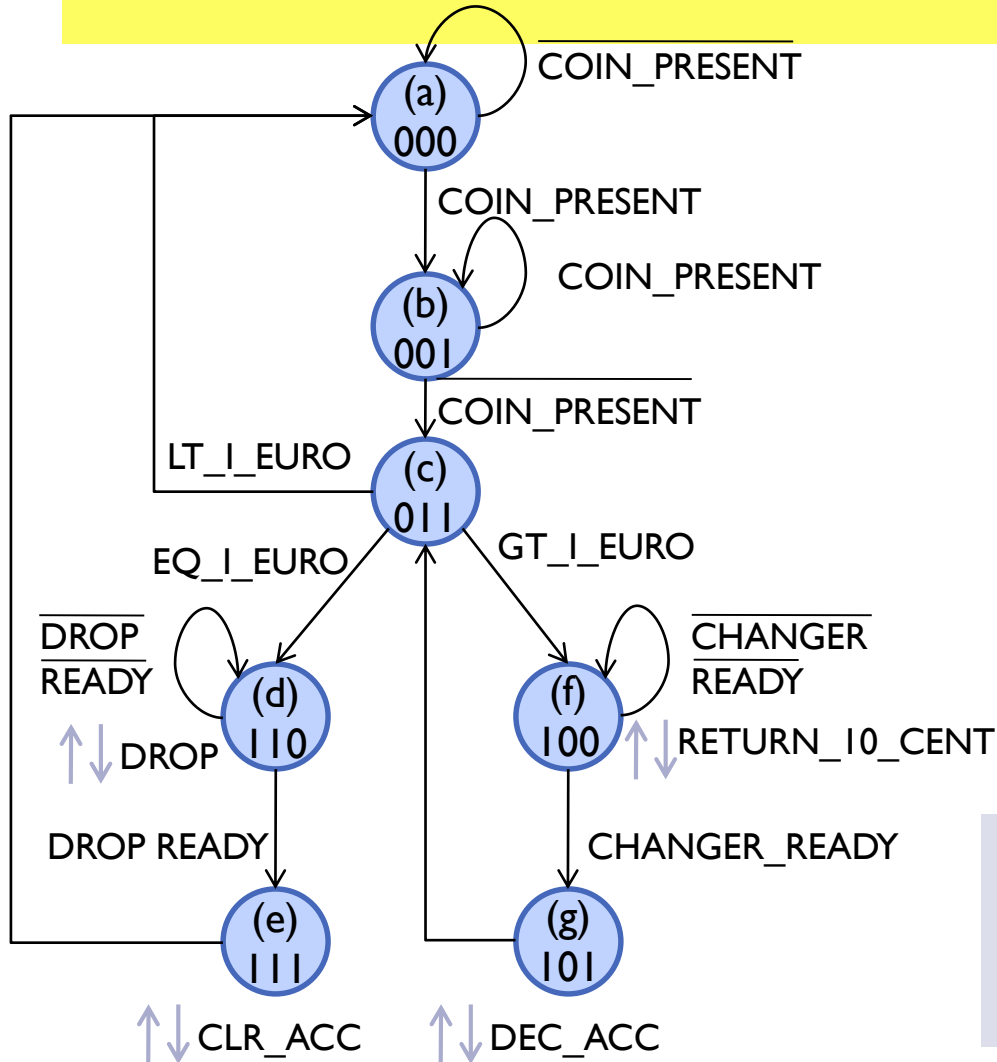

- The state diagram contains all information required to generate an implementation
- Assumption: D flip-flops are used as state register
- 7 states: 3 flip-flops are needed


The state variable order is ABC, i.e. state (c) is A = 0, B = 1, C = 1

Vending Machine: Logic design

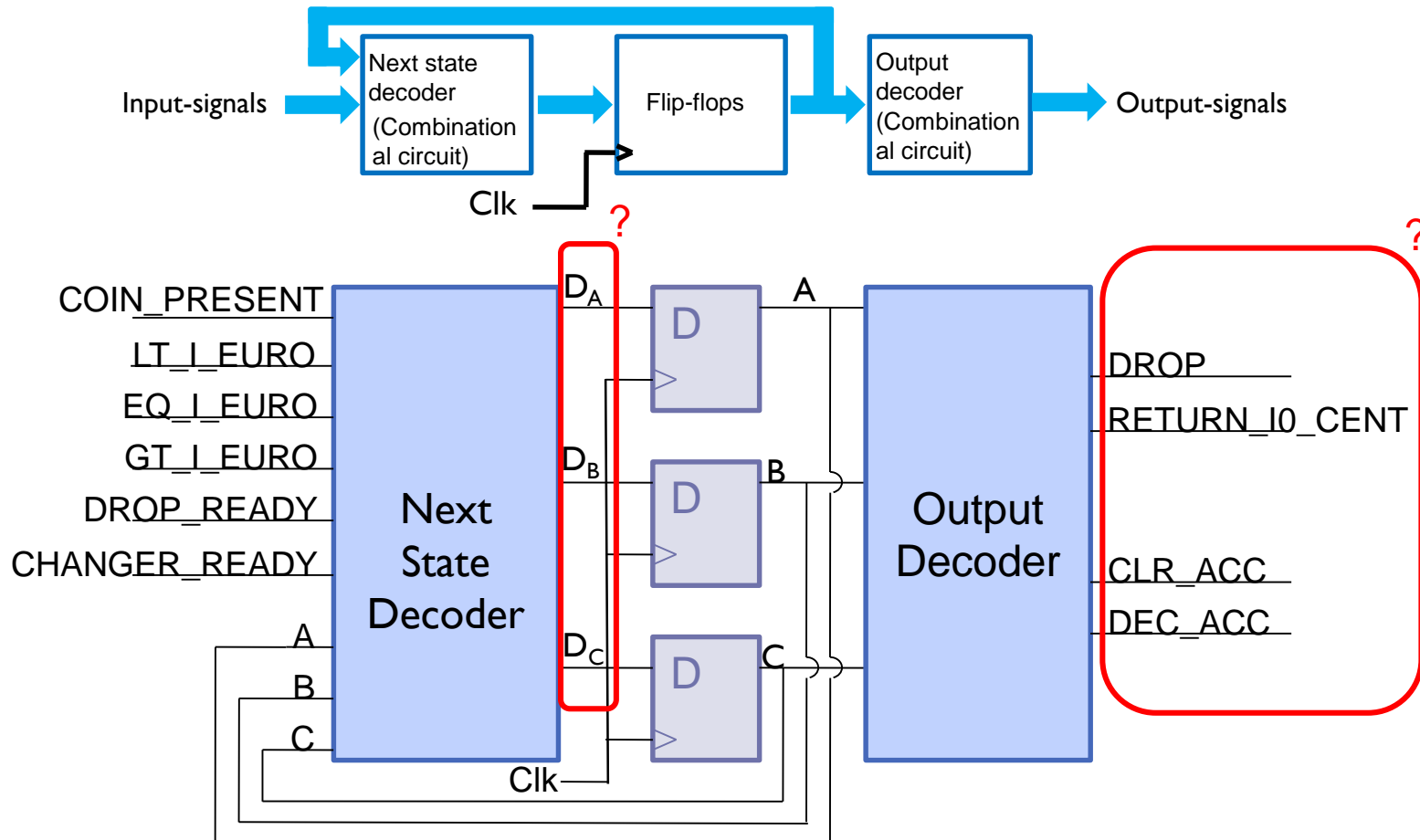

At next step, we develop the logic for the next state (D_A , D_B , D_C) and outputs

Decoder: Next state - D_A

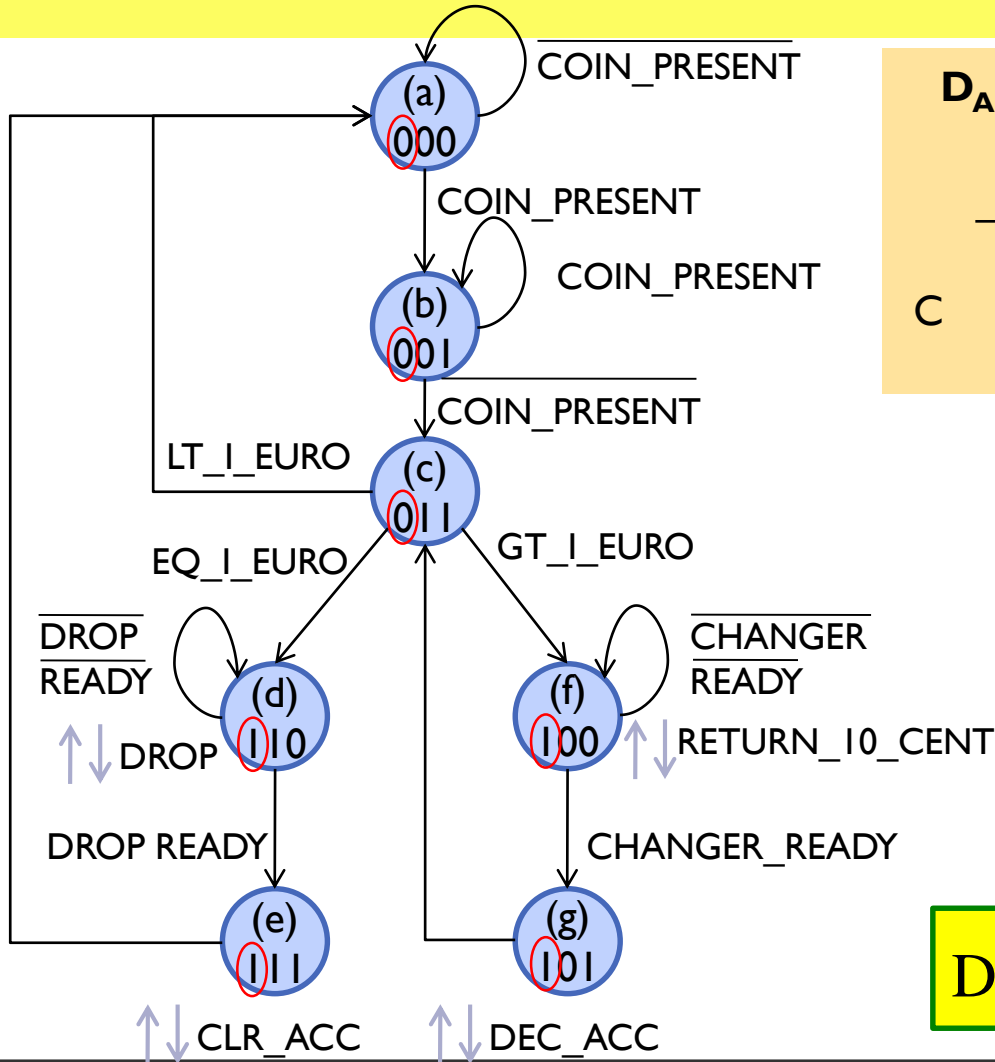


D_A		AB			
		00	01	11	10
C	0	0	-	1	1
	1	0	(=) + (>)	0	0

(=) : EQ_1_EURO
(>) : GT_1_EURO

$$D_A = \bar{A}\bar{B}(EQ) + \bar{A}\bar{B}(GT) + A\bar{C}$$

Decoder: Next state - D_B

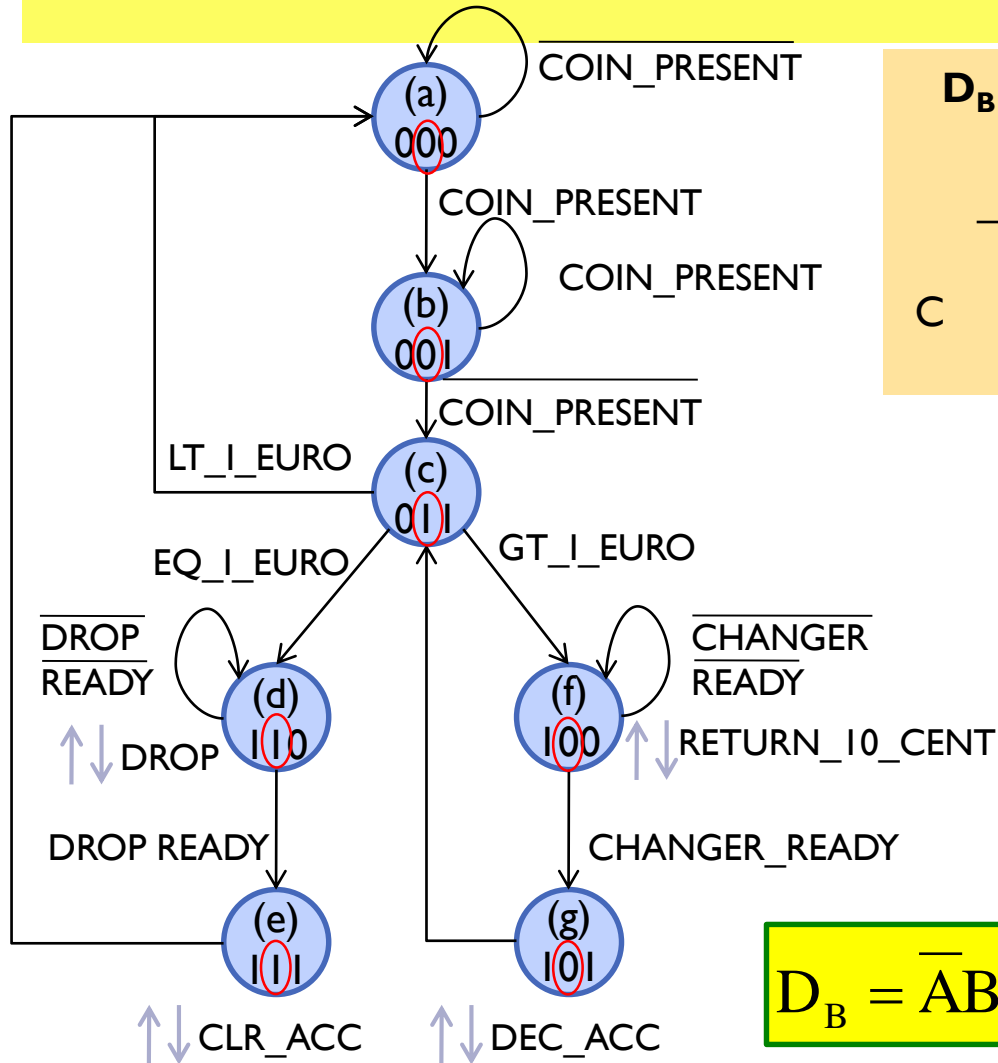


D_B		AB			
		00	01	11	10
C	0	0	-	1	0
	1	\overline{CP}	(=)	0	1

(=) : EQ_1_EURO
CP : COIN_PRESENT

$$D_B = \overline{A}B(EQ) + B\overline{C} + \overline{B}C(\overline{CP}) + A\overline{B}C$$

Decoder: Next state- D_C

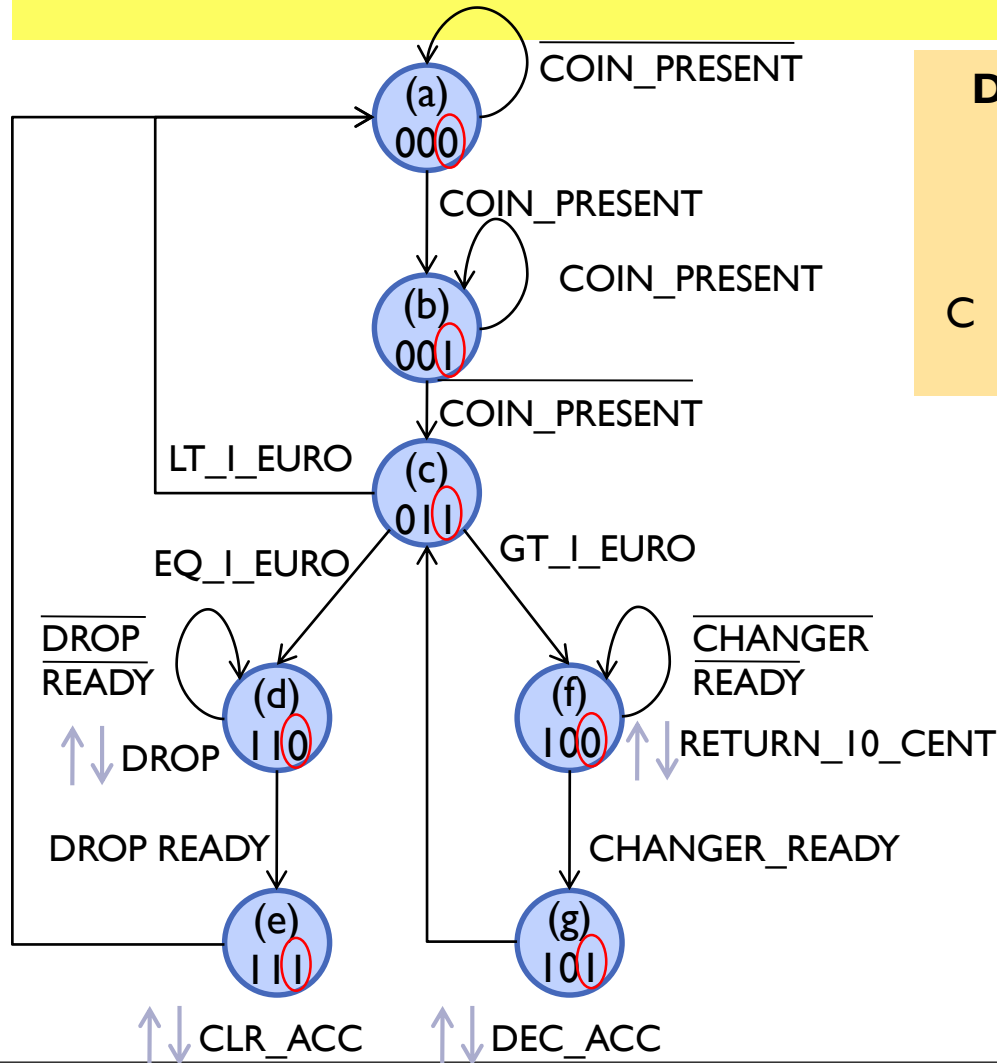


D_C		AB			
		00	01	11	10
C	0	CP	-	DR	CR
	1	1	0	0	1

CP : COIN_PRESENT
DR: DROP_READY
CR: CHANGER_READY

$$D_C = \overline{A}\overline{C}(CP) + B\overline{C}(DR) + A\overline{B}(CR) + \overline{B}C$$


Decoder: Output signals

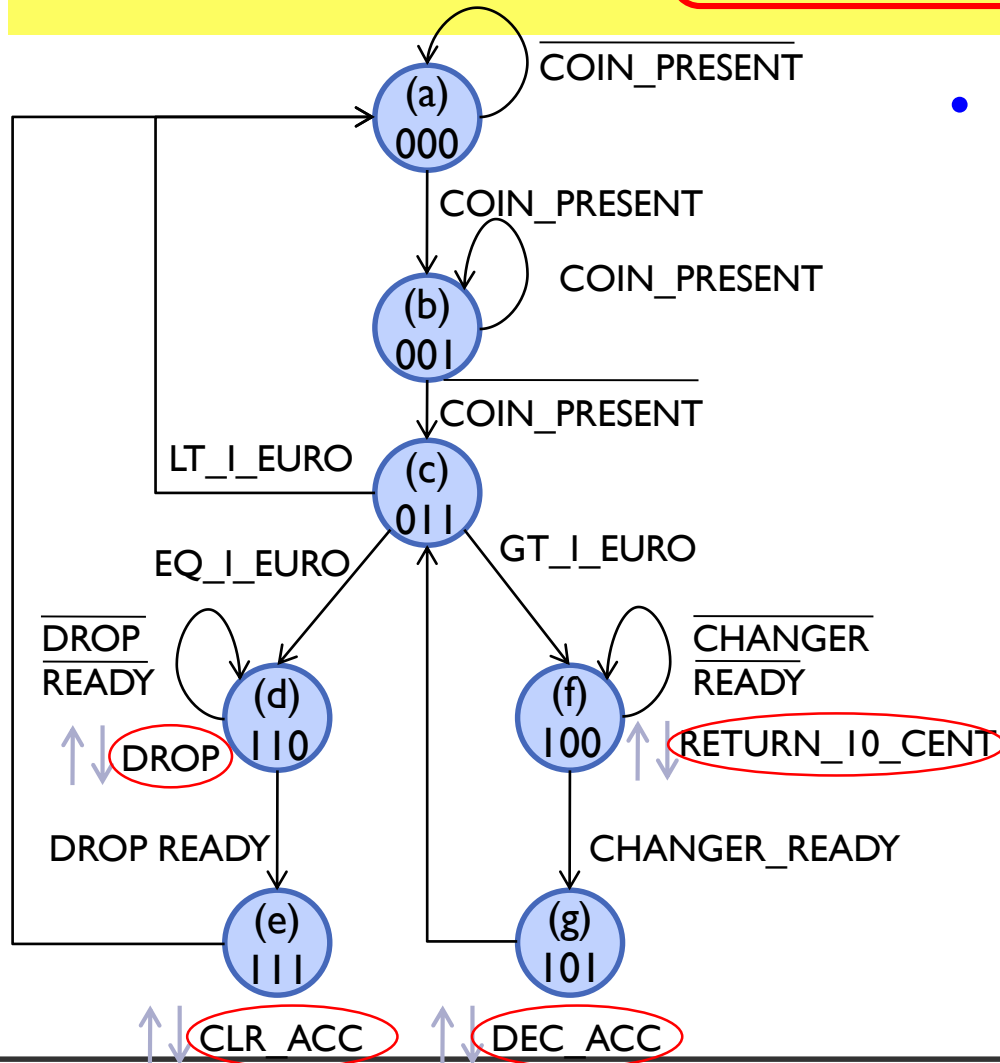- Output decoder is trivial, since its value is directly dependent on the current state



$DROP = A\bar{B}\bar{C}$
 $CLR_ACC = \bar{A}\bar{B}\bar{C}$
 $RETURN_10_CENT = A\bar{B}\bar{C}$
 $DEC_ACC = A\bar{B}\bar{C}$

Unused state?!

 

		AB			
		00	01	11	10
C	0	a	-	d	f
	1	b	c	e	g

$$\Phi = (010)_{ABC}$$

$$A^+ = \bar{A} \cdot B \cdot EQ + \bar{A} \cdot B \cdot GT + A \cdot \bar{C} \Rightarrow A^+(010)_{ABC} = 1 \cdot 1 \cdot EQ + 1 \cdot 1 \cdot GT + 0 \cdot 1 = EQ + GT$$


$$B^+ = \bar{A} \cdot B \cdot EQ + B \cdot \bar{C} + \bar{B} \cdot C \cdot \bar{C}P + A \cdot \bar{B} \cdot C \Rightarrow B^+(010)_{ABC} = 1 \cdot 1 \cdot EQ + 1 \cdot 1 + \dots = 1$$

$$C^+ = \bar{A} \cdot \bar{C} \cdot CP + B \cdot \bar{C} \cdot DR + A \cdot \bar{B} \cdot CR + \bar{B} \cdot C$$

$$\Rightarrow C^+(010)_{ABC} = 1 \cdot 1 \cdot CP + 1 \cdot 1 \cdot DR + 0 \cdot 0 \cdot CR + 0 \cdot 0 = CP + DR$$

$$A^+ B^+ C^+ = -1- = 010, 110, 011, 111 \rightarrow \Phi, d, c, e$$

Vending Machine: Logic Design

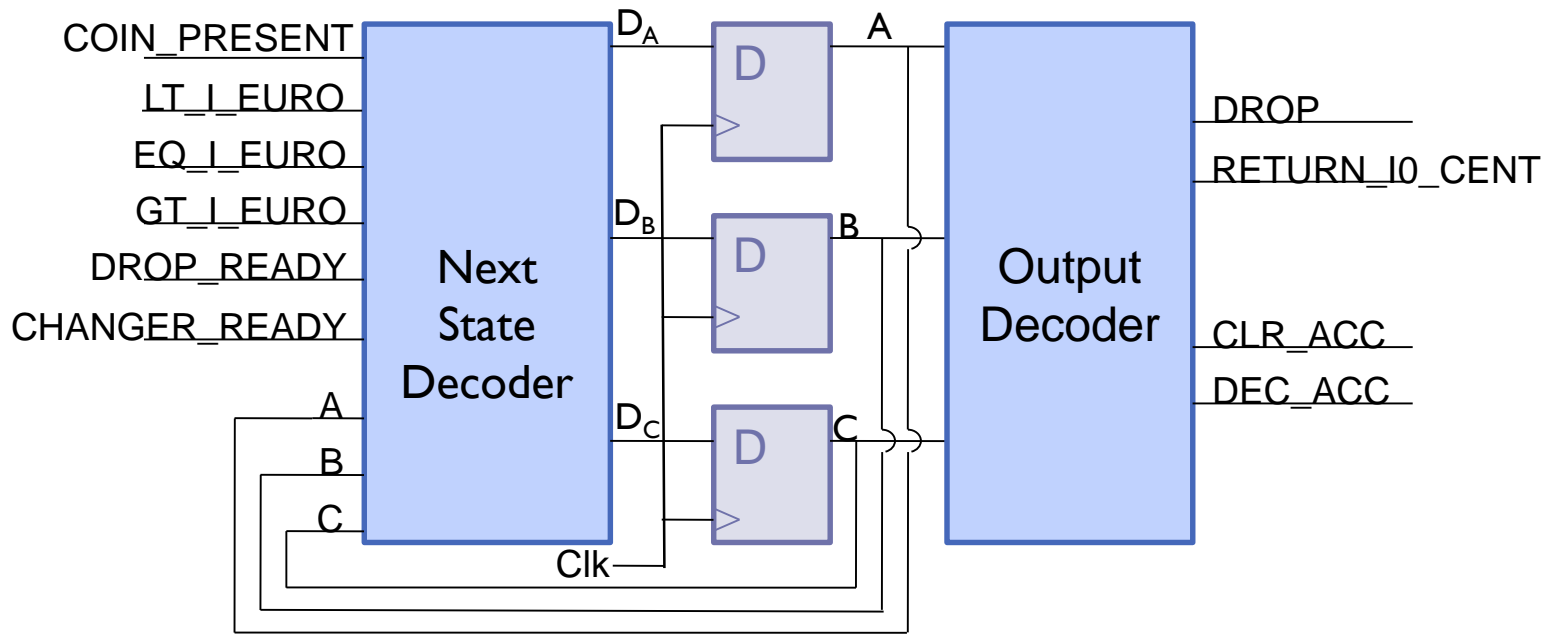

Now you can design "Next State Decoder" and "Output Decoder" by knowing the logic function of D_a , D_b , D_c , and logic function of outputs "Drop", "Return_10_Cent", "CLR_ACC", and "DEC_ACC".

Vending Machine in VHDL: Entity

- Entity describes the system as a '*black box*'
- Entity describes the interface to the outside world
- All inputs and outputs are described
- Apart from the input and output signals, block diagram needs signals for
 - Clock
 - Reset (active low)

```
ENTITY Vending_Machine IS
    PORT (
        -- Inputs
        coin_present      : IN std_logic;
        gt_1_euro         : IN std_logic;
        eq_1_euro         : IN std_logic;
        lt_1_euro         : IN std_logic;
        drop_ready        : IN std_logic;
        changer_ready     : IN std_logic;
        reset_n           : IN std_logic;
        clk               : IN std_logic;
        -- Outputs
        dec_acc           : OUT std_logic;
        clr_acc           : OUT std_logic;
        drop              : OUT std_logic;
        return_10_cent    : OUT std_logic);
END Vending_Machine;
```

Vending Machine in VHDL: Architecture

- The architecture describes the function of the machine
- We define
 - internal signals for the current and next states
 - three processes for next-state decoder, output decoder and state register

Vending Machine in VHDL: Internal Signals

- We need to create a type for internal signals
- Since we describe the states, we use an enumerated type with the values a, b, c, d, e, f, g
- We declare one variable for the current state (current_state) and one for the next state (next_state)

```
ARCHITECTURE Moore_FSM OF Vending_Machine IS
    TYPE    state_type IS (a, b, c, d, e, f, g);
    SIGNAL current_state, next_state: state_type;
BEGIN    -- Moore_FSM

...
```


Vending Machine in VHDL: Internal Signals

- If we do not specify a state assignment, synthesis tool will select it
- We can force a certain encoding using attributes (**NOTE: Attributes are dependent on synthesis tool and thus are not portable!**)

```
ARCHITECTURE Moore_FSM OF Vending_Machine IS
    TYPE    state_type IS (a, b, c, d, e, f, g);
    -- We can use state encoding according to BV 8.4.6
    -- to enforce a particular encoding (for Quartus)
    ATTRIBUTE enum_encoding : string;
    ATTRIBUTE enum_encoding OF state_type : TYPE IS "000
001 011 110 111 100 101";
    SIGNAL current_state, next_state      : state_type;
BEGIN  -- Moore_FSM
...

```

 
Vending Machine in VHDL: Process for Next-State Decoder



- Next-State-Decoder is described as a process
- Sensitivity list contains all the inputs that 'activate' the process

```
NEXTSTATE : PROCESS (current_state, coin_present,  
    gt_1_euro, eq_1_euro, lt_1_euro, drop_ready,  
    changer_ready) -- Sensitivity List  
BEGIN -- PROCESS NEXT_STATE  
  
    ...
```

 Vending Machine in VHDL: Process for Next-State-Decoder




- We now use a CASE statement to describe the transitions to the next state from each state conditions

```

CASE current_state IS
  WHEN a => IF coin_present = '1' THEN
    next_state <= b;
  ELSE
    next_state <= a;
  END IF;
  WHEN b => IF coin_present = '0' THEN
    next_state <= c;
  ELSE
    next_state <= b;
  END IF;

```

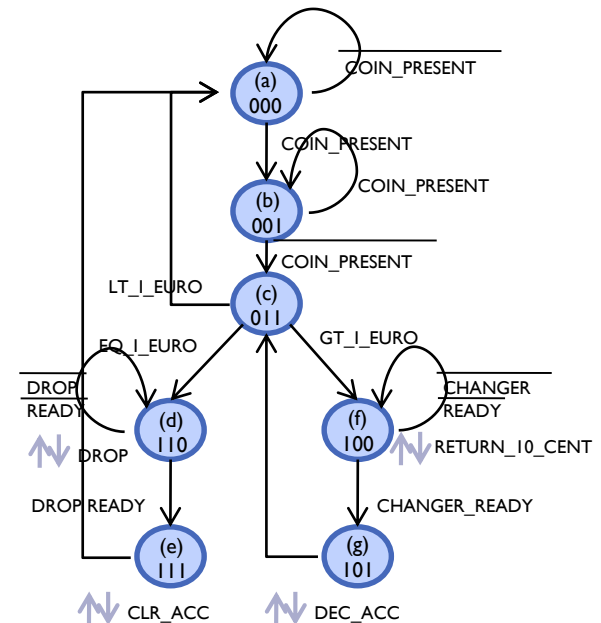

Vending Machine in VHDL: Process for Next-State-Decoder

- We can simplify the description by specifying a default value for the next state

```
...
next_state <= current_state;
CASE current_state IS
    WHEN a => IF coin_present = '1' THEN
        next_state <= b;
    END IF;
    WHEN b => IF coin_present = '0' THEN
        next_state <= c;
    END IF;
```

...


It is important to we specify all options for `next_state` signal. Otherwise we may implicitly set `next_state <= next_state` which generates a loop.

Vending Machine in VHDL: Process for Next-State-Decoder

- We terminate the CASE statement with a WHEN OTHERS statement. Here we specify that we should go to the state *a* if we end up in an unspecified state

```
...  
    WHEN g      => next_state <= c;  
    WHEN OTHERS => next_state <= a;  
END CASE;  
END PROCESS NEXTSTATE;
```

 
Vending Machine in VHDL: Process for Output-Decoder




- Output decoder is described as a separate process
- Sensitivity list contains only the current state because the outputs are directly dependent on it

Vending Machine in VHDL: Process for Output-Decoder

```
OUTPUT : PROCESS (current_state)
BEGIN  -- PROCESS OUTPUT
    drop          <= '0';
    clr_acc        <= '0';
    dec_acc        <= '0';
    return_10_cent <= '0';
    CASE current_state IS
        WHEN d      => drop          <= '1';
        WHEN e      => clr_acc        <= '1';
        WHEN f      => return_10_cent <= '1';
        WHEN g      => dec_acc        <= '1';
        WHEN OTHERS => NULL;
    END CASE;
END PROCESS OUTPUT;
```

 Vending Machine in VHDL: Process for State register




- State register is modeled as a synchronous process with asynchronous reset (active low)

```
CLOCK : PROCESS (clk, reset_n)
BEGIN  -- PROCESS CLOCK
    IF reset_n = '0' THEN -- asynchronous reset (active low)
        current_state <= a;
    ELSIF clk'EVENT AND clk = '1' THEN -- rising clock edge
        current_state <= next_state;
    END IF;
END PROCESS CLOCK;
```


Quick question

- Which state machine is represented by this VHDL code?

 
```
case state is
  when 0 =>
    if (k = '1') then
      nextstate <= 1;
    else
      nextstate <= 2;
    end if;
  when 1 => nextstate <= 2;
  when others => nextstate <= 0;
end case;
```



Alt: A

 


Alt: B

 

Alt: C



Mealy machine

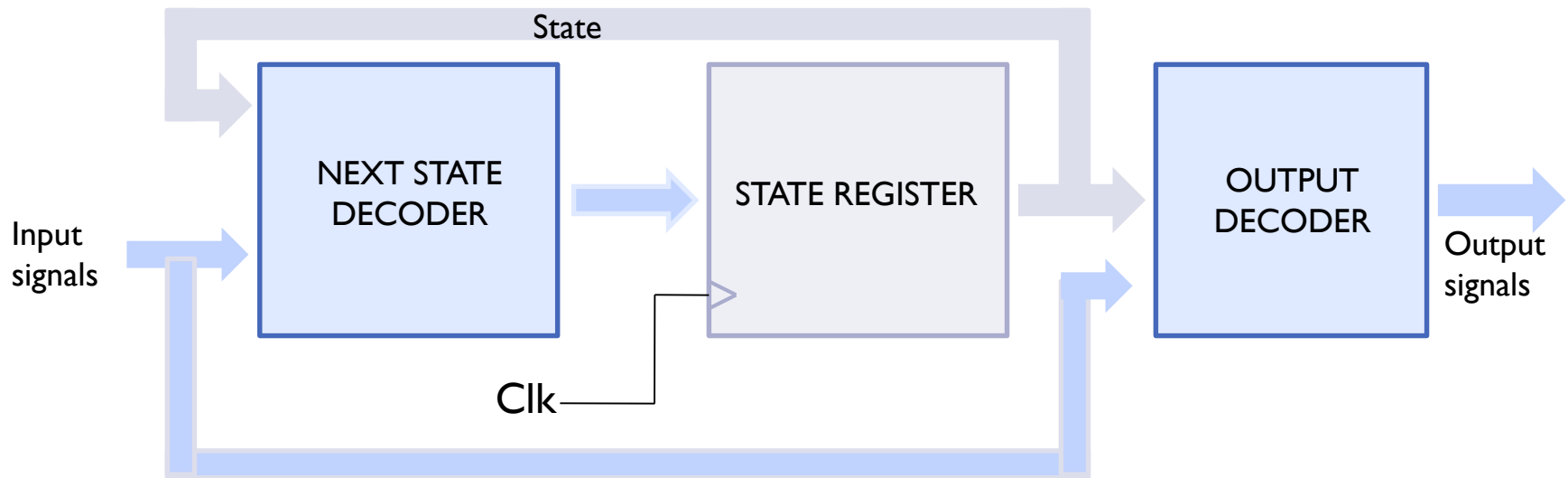

- In a Mealy machine, output signals depend on both the current state and inputs

Mealy machine in VHDL

- A Mealy machine can be modeled in the same way as the Moore machine
- The difference is that output decoder is also dependent on the input signals
- Process which models outputs needs to have input signals in the sensitivity list as well!

More on VHDL

- The sample code for bottle dispenser available on the course website
- Look at the study of "VHDL synthesis" on the course website
- Both Brown/Vranesic- and Hemert-book includes code samples

Summary

- PLD, PAL, CPLD
- FPGA
- ASIC – gate array and standard cell
- Modeling sequential circuits with VHDL
- Next lecture: BV pp. 584-640